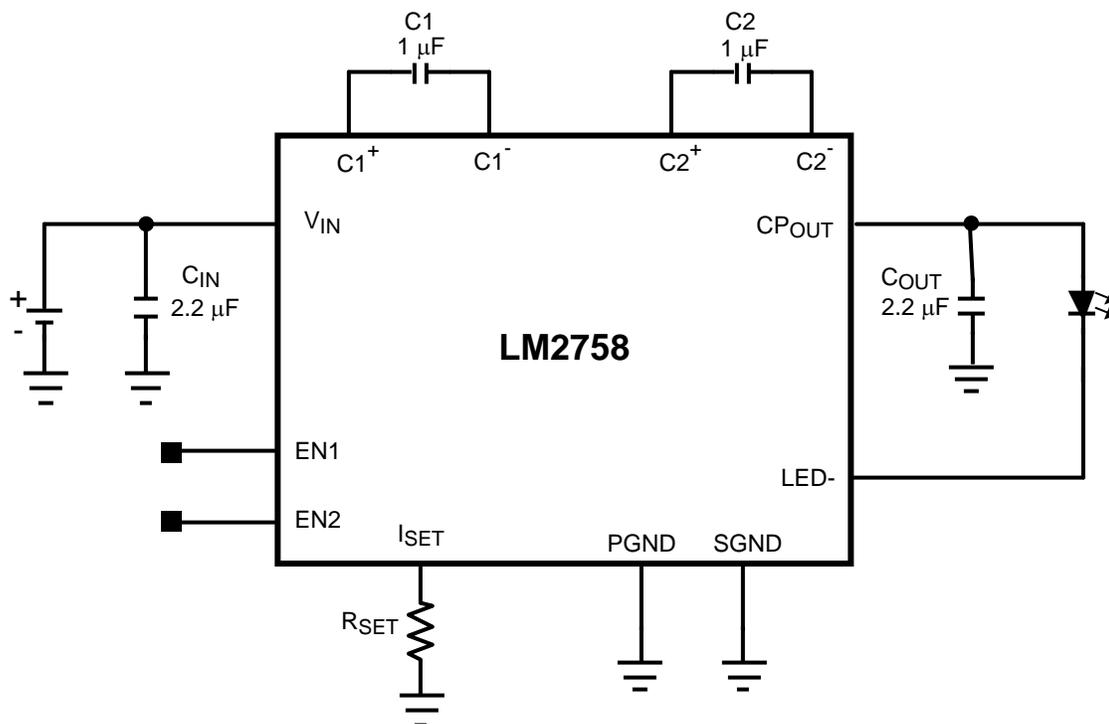


## AN-1695 LM2758 Flash LED Driver Evaluation Board

### 1 Schematic



### 2 Bill of Materials (BOM)

**Table 1. Bill of Materials (BOM)**

Manufacturer	Part No	Description	Designation	Quantity
Texas Instruments	LM2758	Flash LED Driver	U1	1
TDK	C1608X5R0J225	Ceramic cap, 2.2 μF, 6.3V, 0603	C <sub>IN</sub> , C <sub>OUT</sub>	2
TDK	C1608X5R0J105	Ceramic cap, 1.0 μF, 6.3V, 0603	C <sub>1</sub> , C <sub>2</sub>	2
Luxeon	LXCL-PWF3	Flash LED	LED	1
Vishay	CRCW06032002F	Res, 20 kΩ	R <sub>1</sub>	1
Tycol/Amp	4-103239-0-03	1 x 3, 0.1" header	EN <sub>1</sub> , EN <sub>2</sub>	2
Keystone Electronics	1573-2	Turret, DBL.0.82"L, .072 dia.	V <sub>IN</sub> GND, GND, V <sub>b</sub> , V <sub>OUT</sub> , LED-K, LED-A	7
Johnson Components	108-0902-001	Banana Jack, Insulated, Red	V <sub>IN</sub>	1
Johnson Components	108-0903-001	Banana Jack, Insulated, Black	GND	1

### 3 LM2758 Flash LED Driver Evaluation Board Layout

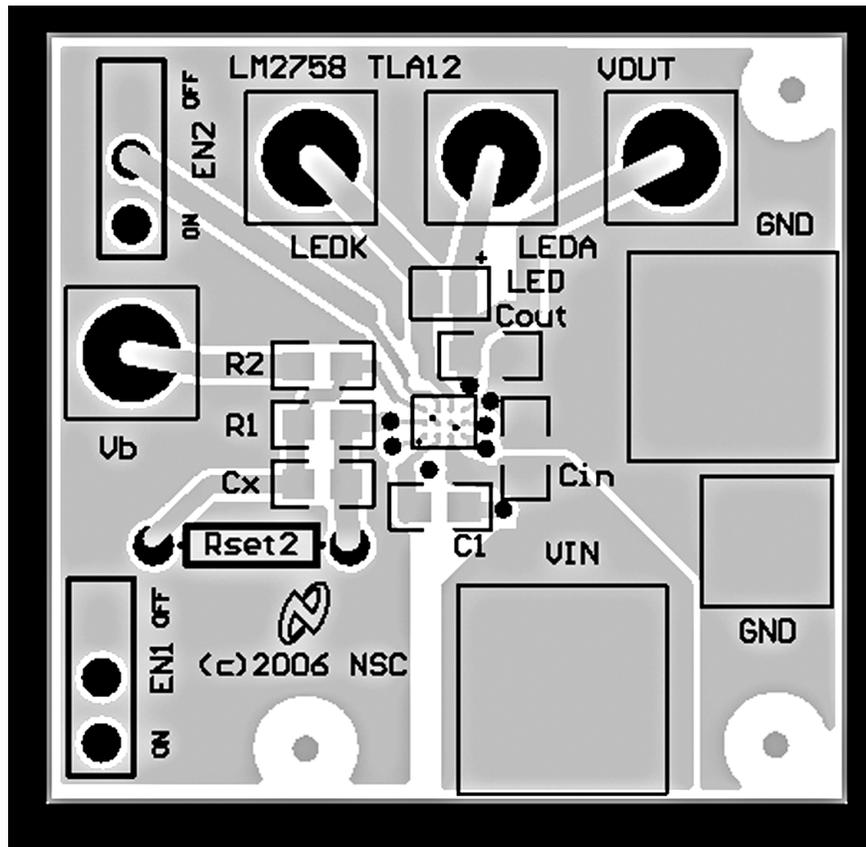


Figure 1. Top Layer

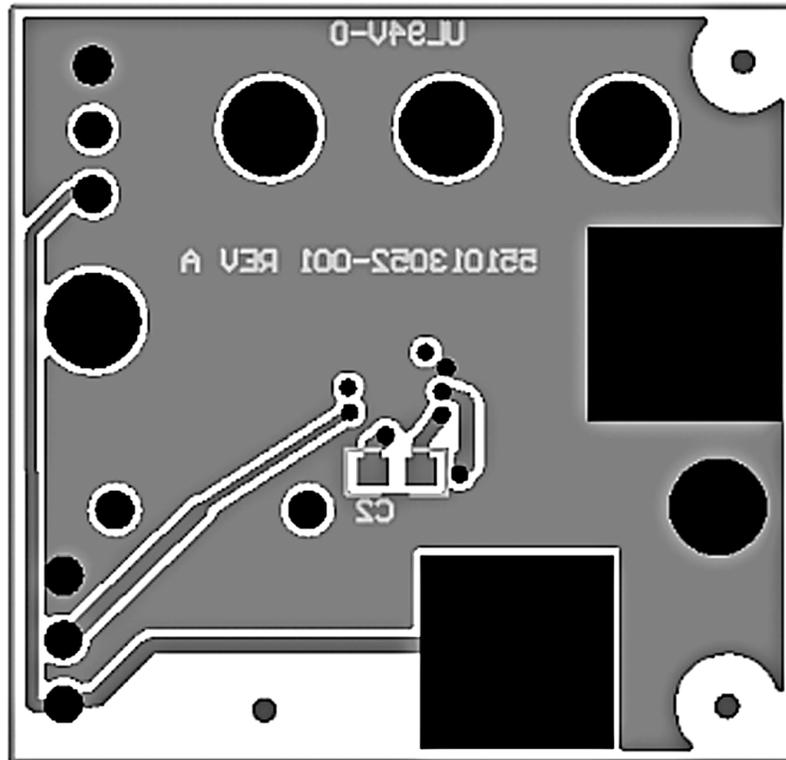


Figure 2. Bottom Layer

## 4 LM2758 Flash LED Driver Evaluation Board

### 4.1 Startup Sequence

Applying power to the  $V_{IN}$  and EN pins at the same time cause the LM2758 to start up in an unknown state. For this reason, it is not advised to apply power to the device while the EN jumper blocks is set to the “ON” position. To startup the evaluation board, set the EN1 jumper and EN2 jumper to the “OFF” position, apply power to the board, and then move the EN jumper(s) to the “ON” position. This is the expected start-up operation in the typical application where  $V_{IN}$  is tied to a voltage rail and the EN pins are controlled via logic signal.

EN1	EN2	Mode
0	0	Shutdown
1	0	Indicator
0	1	Torch
1	1	Flash

### 4.2 Gain Transition

Gain modes are designed to transition to the next higher gain when needed. The gain mode will stay in that higher gain until the Shutdown mode is cycled, resetting the gain to the lowest level. To reset the part to the minimum gain on the evaluation board, place the EN1 jumper and EN2 jumper to the “OFF” position, then to the “ON” position according to the Truth Table to the desired mode.

### 4.3 Input and Output Filters

Ferrite beads along with ceramic capacitors could be used at the input and output pin to filter out switching noise.

For detailed operating descriptions, see the *LM2758 Switched Capacitor Flash LED Driver in DSBGA Data Sheet* ([SNVS551](#)).

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)