

AN-1875 LM5073HE Evaluation Board With Active Bridge

1 Introduction

The LM5073HE (High Efficiency) evaluation board is designed as a high performance solution for both IEEE802.3af fully compliant and non-compliant High Power over Ethernet (HPoE) applications. The possible intake power of the unit is a minimum of 26.6W for a minimum input voltage of 37VDC.

To make a complete evaluation possible, the board also includes integrated Ethernet RX and TX magnetics and an RJ45 interface.

2 Features

- IEEE 802.3af fully compliant
- Programmable maximum input dc current through PD interface: 800mA
- Input voltage ranges:
 - PoE input voltage range at startup: 40 to 57V
 - PoE input voltage range with normal operation: 33 to 57V
- Efficient Mosfet Bridge polarity protection at input
- Measured Efficiency: 98% @ 37VDC, 720mA input
- Measured Efficiency: 98.5% @ 48VDC, 555mA input

3 Theory of Operation

The LM5073 is a 100V Power over Ethernet PD interface with auxiliary support. The low $R_{DS(ON)}$ PD interface hot swap MOSFET and programmable DC current limit extend the range of LM5073 applications up to twice the power level of IEEE 802.3af compliant devices. In a typical configuration, the input is polarity protected by a bridge rectifier that can cause an efficiency loss of up to 3.5%. This configuration assumes that the design requirements include maximum possible efficiency. Therefore, the polarity protection is provided by an input controlled mosfet bridge which yields a typical worst case loss of 0.44%. For a more detailed description of the various features and customizations afforded, please refer to *AN-1574 LM5073 Evaluation Board User's Guide* ([SNVA214](#)).

4 Important Information About the Maximum Power Capability, Cable Usage, and PoE Input Potentials

The LM5073HE evaluation board supports a maximum intake power of 26.6W. The user must make sure that the Power Sourcing Equipment (PSE) used can provide at least 30W, more if long cables are used.

Important: Please note that the CAT-5 cable may not support the maximum power over two pairs of twisted wires under strict safety considerations. Users shall select the proper cable wires to support the design power level without compromising the applicable safety standards. Using an improper cable at such power levels may violate various safety regulations and may cause damage.

Polarity Precaution: PoE applications are typically -48V systems, in which the notations GND and -48V normally refer to the high and low input potentials, respectively. However, for easy readability, the LM5072 datasheet was written in the positive voltage convention with positive input potentials referenced to the VEE pin of the LM5073. Therefore, when testing the evaluation board with a bench power supply, the negative terminal of the power supply is equivalent to the PoE system's -48V potential, and the positive terminal is equivalent to the PoE system ground. To prevent confusion between the datasheet and this application note, the same positive voltage convention is used.

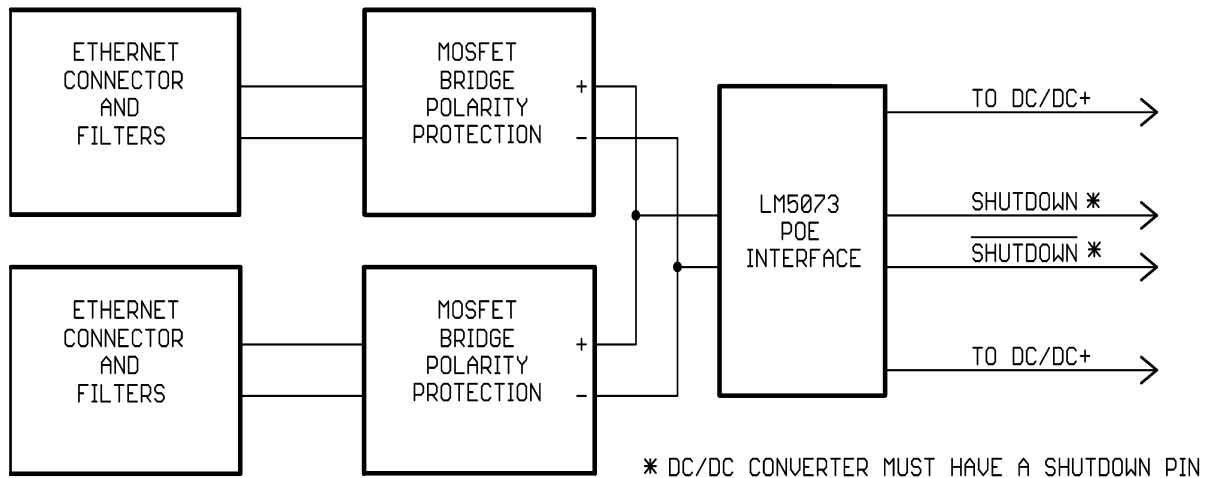


Figure 1. LM5073HE Evaluation Board Block Diagram

5 Loading


If using an electronic load, be sure that the “LOAD ON” switch does not cause a large current surge when turned on. The LM5073 cannot have a load applied until one of the shutdown outputs attempts to turn on the DC/DC converter. At this time, too much startup current may cause the LM5073 to detect an over-current condition. The typical DC/DC converter has a soft-start feature to prevent this from being a problem. If unable to monitor the shutdown outputs, simply wait a couple of seconds after applying input power before turning on the load.

If you wish to test the evaluation board with an actual DC/DC converter as a load, be sure to connect the appropriate shutdown pin (or inverted shutdown pin) of the LM5073HE board to the appropriate shutdown pin (or inverted shutdown pin) of the DC/DC converter. The dual row 6 pin socket on the LM5073HE board will mate to a standard 0.1” center dual row header. The pin out is shown below.

The typical evaluation setup shown in [Figure 2](#) uses an LM5030 evaluation board as a load. There are many other possible choices, but make sure that the electronic load at the output of the LM5030 accounts for the efficiency loss of the LM5030 board and does not exceed the limits of the LM5073HE board.

Other possible evaluation boards to consider as loads include:

- **LM5005 Evaluation Board**, a 2.5A buck regulator for low cost non-isolated PD applications
- **LM5020 Evaluation Board**, a current mode flyback converter
- **LM5025 Evaluation Board**, a voltage mode active clamp forward converter
- **LM5026 Evaluation Board**, a current mode active clamp forward converter
- **LM5032 Evaluation Board**, a current mode dual interleaved converter
- **LM5034 Evaluation Board**, a current mode dual interleaved converter with active clamp
- **LM5115 Evaluation Board**, a 5A buck regulator with synchronous rectification

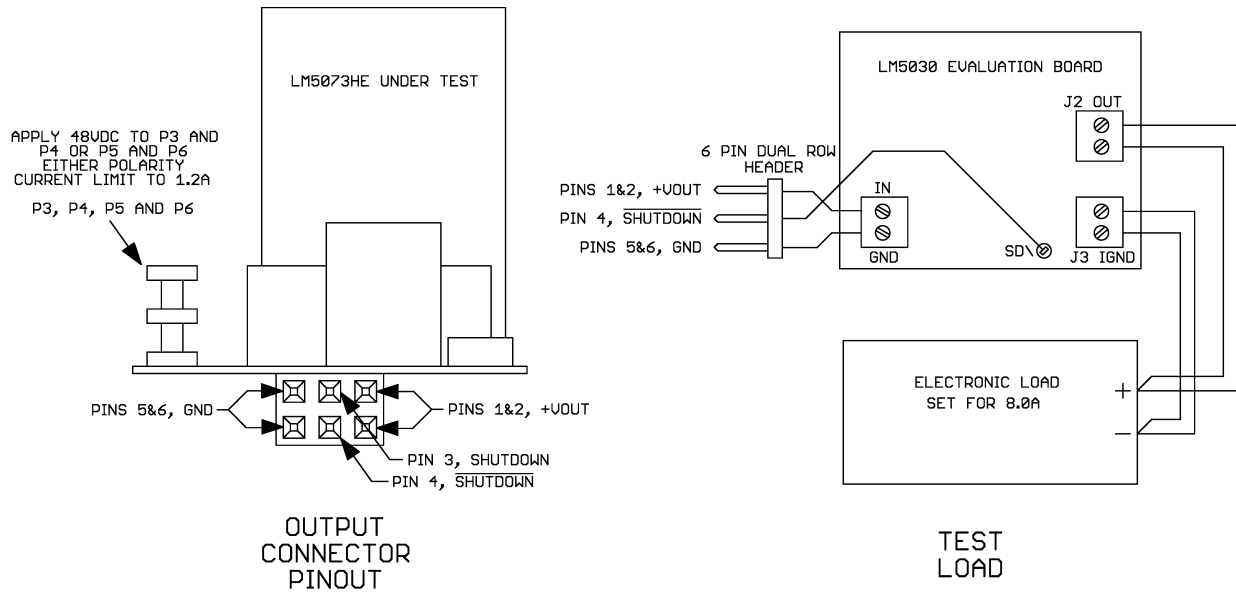

(VIEW IS THE END OPPOSITE THE DUAL RJ45 CONNECTOR)

Figure 2. Typical Evaluation Setup

6 Efficiency

Figure 3 shows the typical efficiency curve at 48VDC input verses load. Since losses are almost entirely resistive, a value of 1.05 Ohms may be used to estimate losses for other levels of current and voltage.

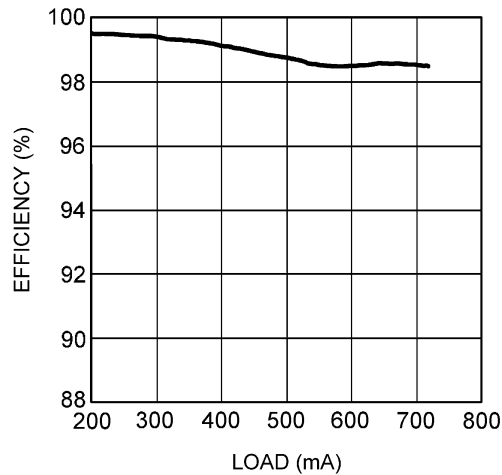


Figure 3. Efficiency at 48V Input

7 Printed Circuit Layout

The layers of the printed circuit board are shown in top down order in [Figure 4](#) to [Figure 6](#). View is from the top of the board. Scale is approximately X1.5. The printed circuit board consists of 2 layers of 2 ounce copper on FR4 material with a total thickness of 0.065 inches.

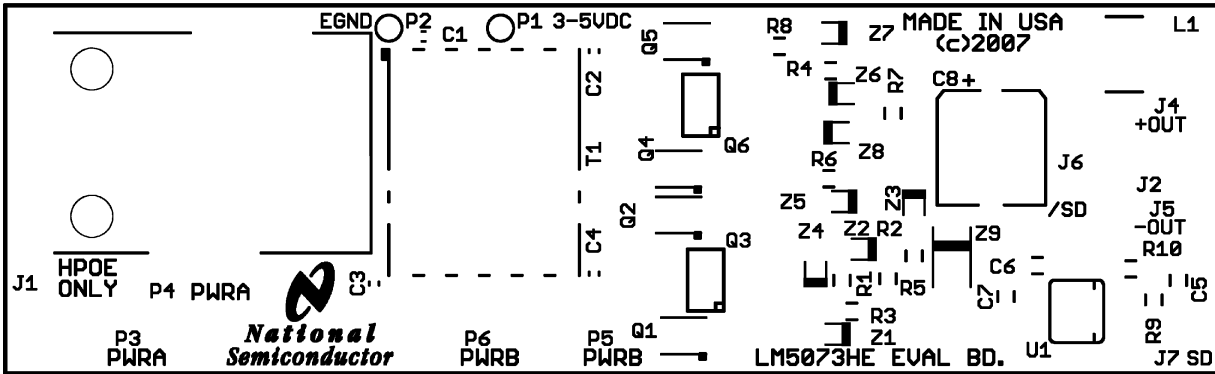


Figure 4. Top Silkscreen

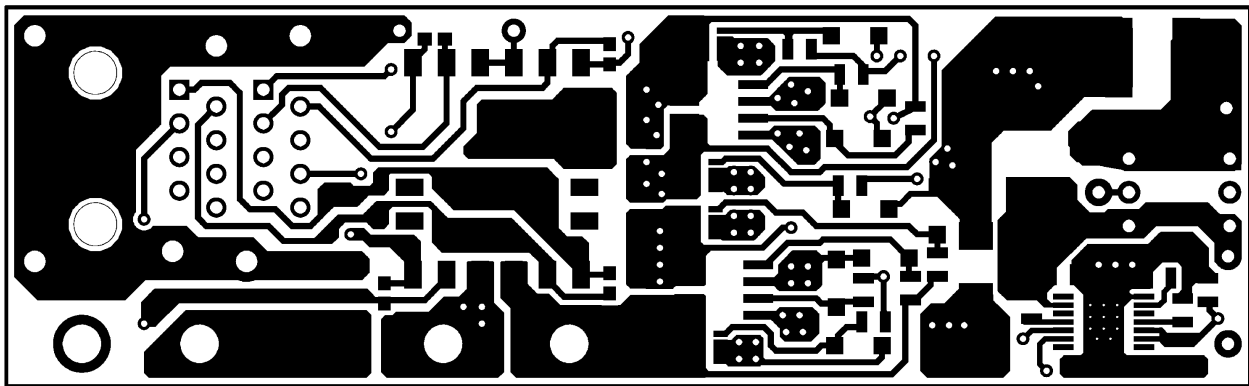


Figure 5. Top Copper

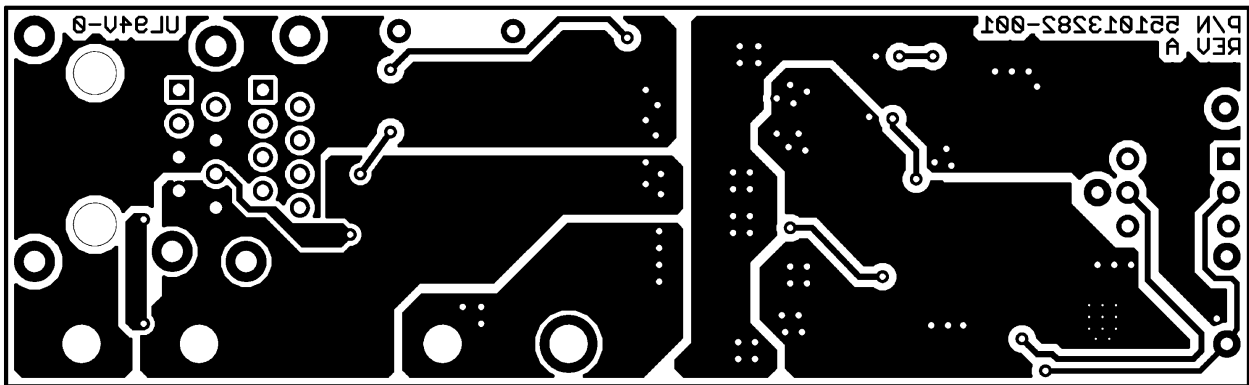


Figure 6. Bottom Copper

8 Bill of Materials

Table 1. Bill of Materials

Item	Description	Manufacturer	Part Number
C1	8.0 pF, 50V, CER, NPO, 0603	AVX	06031A8R0CAT2A
C2	8.0 pF, 50V, CER, NPO, 0603	AVX	06031A8R0CAT2A
C3	8.0 pF, 50V, CER, NPO, 0603	AVX	06031A8R0CAT2A
C4	8.0 pF, 50V, CER, NPO, 0603	AVX	06031A8R0CAT2A
C5	0.047 μ F, 100V, X7R, 0805	TDK	C2012X7R2A473K
C6	0.047 μ F, 100V, X7R, 0805	TDK	C2012X7R2A473K
C7	0.047 μ F, 100V, X7R, 0805	TDK	C2012X7R2A473K
C8	22 μ F, 100V, ALUM ELECT, LOW ESR	PANASONIC	EEV-FK2A220P
J1	JACK, MODULAR, 2 PORT RJ45	TYCO	5569381-1
J2	SOCKET, .025" SQ POST, 3 x 2, R/A	TYCO	6-535512-2
L1	INDUCTOR, 4.7 μ H, 1.8A, 56m	COILCRAFT	MSS6132-472ML
P1	TEST POINT, MINIATURE	KEYSTONE	5002
P2	TEST POINT, MINIATURE	KEYSTONE	5002
P3	TERMINAL, TURRET	KEYSTONE	1503
P4	TERMINAL, TURRET	KEYSTONE	1503
P5	TERMINAL, TURRET	KEYSTONE	1503
P6	TERMINAL, TURRET	KEYSTONE	1503
Q1	MOSFET, P-CH, 100V, 134 m Ω , 1212-8	VISHAY	SI7113DN
Q2	MOSFET, P-CH, 100V, 134 m Ω , 1212-8	VISHAY	SI7113DN
Q3	MOSFET, DUAL N-CH, 100V, 62m Ω , SO8	FAIRCHILD	FDS3992
Q4	MOSFET, P-CH, 100V, 134 m Ω , 1212-8	VISHAY	SI7113DN
Q5	MOSFET, P-CH, 100V, 134 m Ω , 1212-8	VISHAY	SI7113DN
Q6	MOSFET, DUAL N-CH, 100V, 62 m Ω , SO8	FAIRCHILD	FDS3992
R1	RESISTOR, 150K, 1%, 1/8W, 0805	VISHAY	CRCW0805150KF
R2	RESISTOR, 150K, 1%, 1/8W, 0805	VISHAY	CRCW0805150KF
R3	RESISTOR, 150K, 1%, 1/8W, 0805	VISHAY	CRCW0805150KF
R4	RESISTOR, 150K, 1%, 1/8W, 0805	VISHAY	CRCW0805150KF
R5	RESISTOR, 150K, 1%, 1/8W, 0805	VISHAY	CRCW0805150KF
R6	RESISTOR, 150K, 1%, 1/8W, 0805	VISHAY	CRCW0805150KF
R7	RESISTOR, 150K, 1%, 1/8W, 0805	VISHAY	CRCW0805150KF
R8	RESISTOR, 150K, 1%, 1/8W, 0805	VISHAY	CRCW0805150KF
R9	RESISTOR, 31.6, 1%, 1/8W, 0805	VISHAY	CRCW080531R6F
R10	RESISTOR, 15.0K, 1%, 1/8W, 0805	VISHAY	CRCW080515K0F
T1	SIGNAL PATH HPOE MAGNETICS	COILCRAFT	ETH1-230L
U1	IC, POE INTERFACE, TSSOP-14 EP	TEXAS INSTRUMENTS	LM5073
Z1	ZENER, 15V @ 50 μ A, SOD-123	CENTRAL SEMICONDUCTOR	CMHZ4702
Z2	ZENER, 15V @ 50 μ A, SOD-123	CENTRAL SEMICONDUCTOR	CMHZ4702
Z3	ZENER, 15V @ 50 μ A, SOD-123	CENTRAL SEMICONDUCTOR	CMHZ4702
Z4	ZENER, 15V @ 50 μ A, SOD-123	CENTRAL SEMICONDUCTOR	CMHZ4702
Z5	ZENER, 15V @ 50 μ A, SOD-123	CENTRAL SEMICONDUCTOR	CMHZ4702
Z6	ZENER, 15V @ 50 μ A, SOD-123	CENTRAL SEMICONDUCTOR	CMHZ4702
Z7	ZENER, 15V @ 50 μ A, SOD-123	CENTRAL SEMICONDUCTOR	CMHZ4702
Z8	ZENER, 15V @ 50 μ A, SOD-123	CENTRAL SEMICONDUCTOR	CMHZ4702
Z9	DIODE, TVS, 60V, SMA	DIODES INC.	SMAJ60A-13

9 LM5073 Evaluation Board Schematic

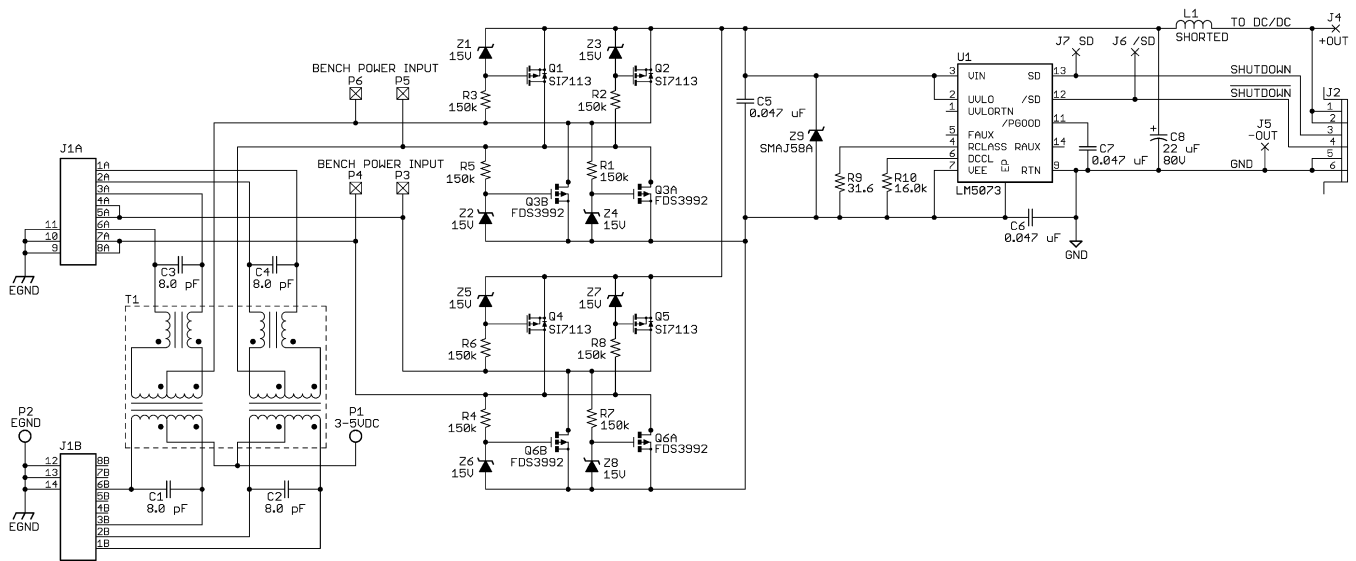


Figure 7. LM5073 Evaluation Board: Input 40-57V Startup, 720 mA

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com