

Interfacing Avago Technologies Fast Ethernet Optical Transceivers with various PHY ICs



Application Note 5582

Table of Contents

1. Introduction	2
2. AFBR-59E4APZ	2
2.1. IC+ IP101G	2
2.2. Micrel KSZ8041FTL	3
3. AFBR-5803x	4
3.1. IC+ IP101G	4
3.2. Micrel KSZ8041FTL	5
4. AFBR-5972Z	5
4.1. IC+ IP101G	6
4.2. Micrel KSZ8041FTL	6
5. AFBR-59F1Z	7
5.1. IC+ IP101G	7
5.2. Micrel KSZ8041FTL	7
6. Compatible PHY ICs	8
6.1. IC+	8

1. Introduction

This application note discusses the terminations required at both ends of the transmitter (Tx) and receiver (Rx) transmission lines for proper interconnection of different Avago Technologies Fast Ethernet Optical Transceivers with various PHY ICs from several selected manufacturers.

AC-coupling has been chosen as the general interfacing option in all cases presented in this application note due to its simplicity, compared to DC-coupling. For AC-coupling, a designer does not have to look out for common mode voltage compatibility between the output of the PHY IC and the input of the optical transceiver and vice versa, because the common mode voltage of the output signal is removed by the de-coupling capacitors and then fixed on the input side to the required level.

Avago Fast Ethernet Optical Transceivers covered in this document are:

- AFBR-59E4APZ
- AFBR-5803x
- AFBR-5972Z
- AFBR-59F1Z

The following PHY IC devices are considered:

- IC+ IP101G
- Micrel KSZ8041FTL

Some similar PHY ICs are available from IC+ that feature a Fast Ethernet Optical Transceiver interface matching with IP101G mentioned earlier. As such, the terminations described in this application note should work as well with that other PHY IC. For more details see "Compatible PHY ICs" section at the end of this document.

The interfaces (terminations) defined in this application note have been evaluated at room temperature using Spirent Fast Ethernet traffic generator and analyzer. For a PRBS7 payload of the Ethernet frames, it has been confirmed a 0% frame loss in a communication held for 30 seconds between the PHY IC and the Avago Fast Ethernet Optical Transceiver. The interfaces proposed here, however, have not been verified over voltage, temperature and other parameter shifts.

Therefore the schematics shown in this application note are recommendations and Avago cannot guarantee full function and performance. The designer should perform his own verification.

2. AFBR-59E4APZ

This optical transceiver has LVPECL input/outputs. The device already includes de-coupling capacitors for an AC-coupled interface; therefore, the only issue the circuit designer has to consider is the voltage swing of the signal supplied by the output of the PHY to the input of the optical transceiver and vice versa.

Figure 1 shows the internal configuration of AFBR-59E4APZ.

 


Figure 1. Internal structure of AFBR-59E4APZ

Table 1 shows the Signal Detect (SD) voltage levels supplied by the optical Rx of AFBR-59E4APZ.

Table 1. Signal Detect voltage levels supplied by AFBR-59E4APZ

	Min.	Max.
Invalid data signal	$V_{dd} - 1.81 \text{ V}$	$V_{dd} - 1.62 \text{ V}$
Valid data signal	$V_{dd} - 1.02 \text{ V}$	$V_{dd} - 0.88 \text{ V}$

The parameter V_{dd} shown in Table 1 has a typical value of 3.3 V.

2.1. IC+ IP101G

This PHY IC has LVPECL inputs/outputs for communication with an external 100Base-FX optical transceiver.

The output stage of LVPECL requires to source current to ground. This is usually achieved by placing two 150 Ω resistors between ground and Tx+/Tx-, respectively. For IP101G, these resistors are included in the PHY IC, and so layout of the terminations is simplified, making it easier for the circuit designer to connect IP101G to an optical transceiver. On the other hand, the resistors required for the 50 Ω impedance matching of the input stage are also built-in within the PHY IC. Therefore, the only terminations required by this PHY are the resistors that provide the correct common mode level to the input stage.

As the common mode level required by LVPECL is 2.0V, the resistors shown in Figure 2 are a good combination. The high values of these resistors ensure low current through them, which translates into low power consumption.

Table 2 shows the SD input voltage levels required by IP101G. The values shown in Table 1 and Table 2 allow setting the correct voltage divider for the connection of SD.

Table 2. Signal Detect voltage levels required by IP101G

	Min.	Max.
Invalid data signal	1.3 V	1.7 V
Valid data signal	2.0 V	3.3 V + 0.5 V

Figure 2 shows the interconnection of AFBR-59E4APZ and IP101G.

 


Figure 2. Interconnection between AFBR-59E4APZ and IP101G

2.2. Micrel KSZ8041FTL

This PHY IC has CML inputs/outputs for communication with an external 100Base-FX optical transceiver.

The output stage of CML is based on an open-drain differential pair, which sinks current that must be supplied from outside. This current is usually provided by connecting 50 Ω resistors between V_{CC} and Tx+/Tx-. At the input stage, a common mode level of around 3.3 V is required by KSZ8041FTL. This common mode level is achieved by connecting 50 Ω resistors between V_{CC} and Rx+/Rx-.

AFBR-59E4APZ has LVPECL input/outputs. The voltage swing of the signal at the outputs Tx+/Tx- of the PHY IC is compatible with the voltage swing expected by the optical module at its inputs Tx+/Tx-. Also the voltage swing of the signal at the outputs Rx+/Rx- of the optical module is compatible with the voltage swing expected by the PHY IC at its inputs Rx+/Rx-. As such, both devices — optical

module and PHY IC — can directly be connected to each other, because AFBR-59E4APZ is AC-coupled and it includes the correct terminations inside the housing (see Figure 1).

Table 3 shows the SD input voltage levels required by KSZ8041FTL. The values shown in Table 1 and Table 3 allow the correct voltage divider to be set for the connection of SD.

Table 3. Signal Detect voltage levels required by KSZ8041FTL

	Min.	Max.
Invalid data signal	1.0 V	1.8 V
Valid data signal	2.2 V	–

Figure 3 shows the schematic of the interconnection between KSZ8041FTL and AFBR-59E4APZ.

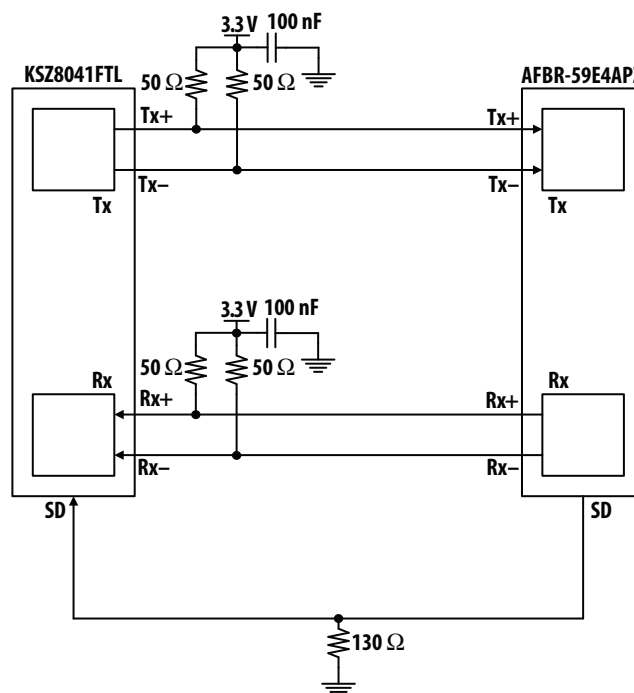


Figure 3. Interconnection between AFBR-59E4APZ and KSZ8041FTL

3. AFBR-5803x

This optical transceiver also features LVPECL inputs/outputs. In opposition to AFBR-59E4APZ, AFBR-5803Z does not include built-in de-coupling capacitors or adaptation resistors.

Figure 4 shows the internal structure of AFBR-5803x.

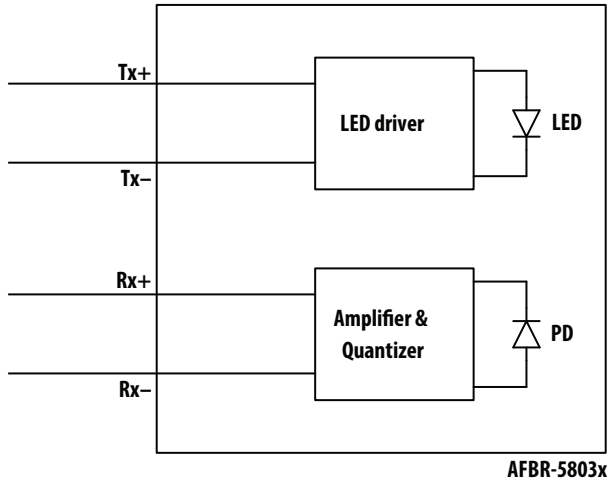


Figure 4. Internal structure of AFBR-5803x

Since AFBR-5803x does not include any built-in adaptation resistors, an 82 Ω /130 Ω voltage divider is required at the Tx+/Tx- inputs to provide 50 Ω impedance matching, as well as to fix the common mode level to 2.0 V, which is the level required by these LVPECL inputs. On the other hand, 150 Ω resistors connected to ground are required at the Rx+/Rx- outputs to provide a path to ground for the emitter current of the output stage.

Table 4 shows the SD voltage levels supplied by the optical Rx of AFBR-5803x.

Table 4. Signal Detect voltage levels supplied by AFBR-5803Z

	Min.	Max.
Invalid data signal	$V_{dd} - 1.83 \text{ V}$	$V_{dd} - 1.55 \text{ V}$
Valid data signal	$V_{dd} - 1.085 \text{ V}$	$V_{dd} - 0.88 \text{ V}$

The AFBR-5803x can be operated at a nominal voltage of either 3.3 V or 5 V. Only the 3.3 V supply option will be considered for AFBR-5803x here, as the tested PHY ICs work at this supply voltage.

3.1. IC+ IP101G

A 10 k Ω /15 k Ω voltage divider at both Rx+/Rx- is the only adaptation network required by IP101G. This voltage divider fixes the common mode level at 2.0 V and ensures a low current flow through it at the same time.

Table 2 and Table 4 show that a 10 Ω /174 Ω voltage divider is a good option to fix the proper voltage levels at the SD input of the PHY IC.

Figure 5 shows the schematic of the interconnection between IP101G and AFBR-5803x.

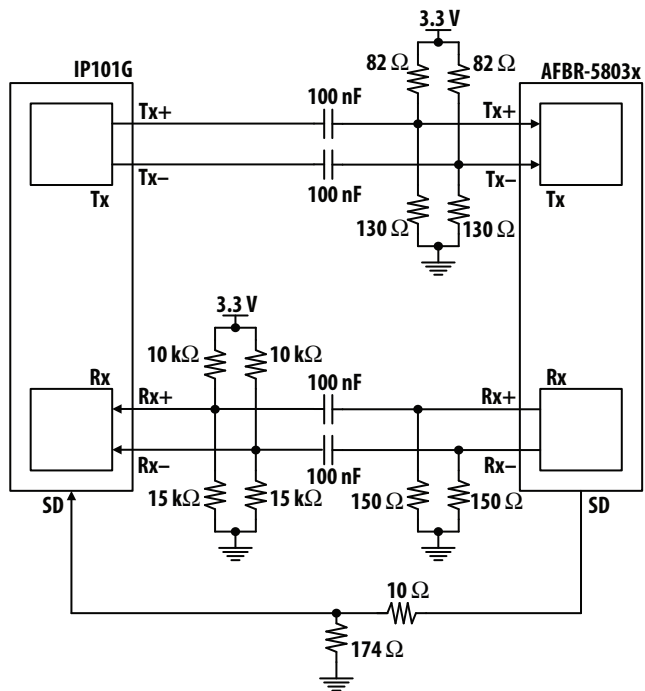


Figure 5. Interconnection between AFBR-5803x and IP101G

3.2. Micrel KSZ8041FTL

This PHY IC has CML inputs/outputs for communication with an external 100Base-FX optical transceiver.

It requires 50 Ω resistors between V_{CC} and Tx+/Tx- to source current to the open-drain output stage, and 50 Ω resistors between V_{CC} and Rx+/Rx- to fix the common mode level at the Rx+/Rx- inputs to 3.3 V as well as to provide 50 Ω impedance matching.

Table 3 and Table 4 show that a 130 Ω resistor between the SD trace and ground is enough to fix the voltage to the correct levels at the SD input of the PHY IC.

Figure 6 shows the schematic of the interconnection between KSZ8041FTL and AFBR-5803x.

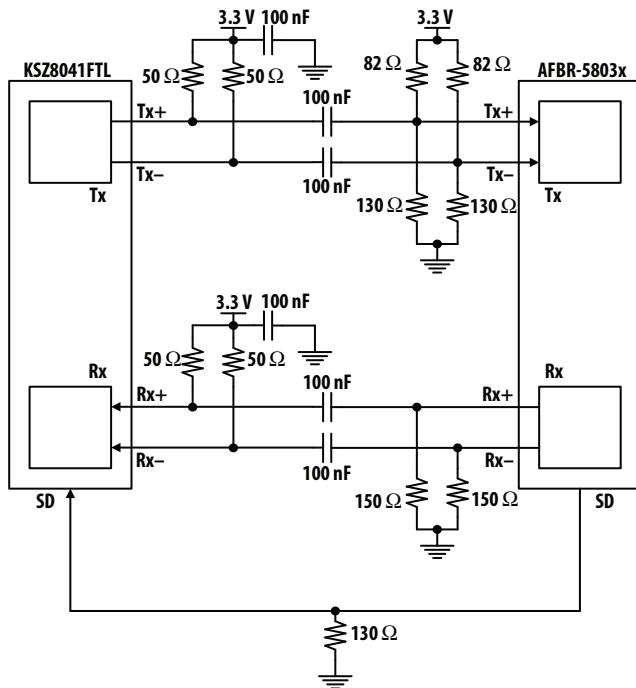


Figure 6. Interconnection between AFBR-5803x and KSZ8041FTL

4. AFBR-5972Z

This optical transceiver accepts LVDS/LVPECL signals at the Tx+/Tx- inputs and delivers LVPECL signals at the Rx+/Rx- outputs.

LVDS is the standard used in this application note for the evaluation of AFBR-5972Z.

Figure 7 shows the internal configuration of AFBR-5972Z.

 


Figure 7. Internal structure of AFBR-5972Z

As AFBR-5972Z will be AC-coupled to the PHY IC, the terminations required by the optical transceiver are the ones needed to establish the common mode level at the Tx+/Tx- inputs and to source current to ground at the Rx+/Rx- outputs. The 50 Ω impedance matching at the Tx lines is provided by the internal 100 Ω resistor between Tx+ and Tx-. The common mode level at the Tx+/Tx- inputs will be fixed at 1.65 V, which is within the range defined for an LVDS differential input. This level is achieved by connecting a 10 kΩ pull-up resistor and a 10 kΩ pull-down resistor to Tx+/Tx-.

Table 5 shows the SD voltage levels supplied by the optical Rx of AFBR-5972Z.

Table 5. Signal Detect voltage levels supplied by AFBR-5972Z

	Min.	Max.
Invalid data signal	$V_{dd} - 1.83\text{ V}$	$V_{dd} - 1.50\text{ V}$
Valid data signal	$V_{dd} - 1.16\text{ V}$	$V_{dd} - 0.88\text{ V}$

The parameter V_{dd} shown in Table 1 has a typical value of 3.3 V.

4.1. IC+ IP101G

Figure 8 shows the schematic of the interconnection between IP101G and AFBR-5972Z.

Table 2 and Table 5 show that a 10 Ω /174 Ω voltage divider is a good option to fix the proper voltage levels at the SD input of the PHY IC.

 


Figure 8. Interconnection between AFBR-5972Z and IP101G

The 10 k Ω /15 k Ω voltage divider placed at both Rx+/Rx- is the only adaptation network required by IP101G. This voltage divider fixes the common mode level at 2.0 V and ensures a low current flow through it at the same time.

4.2. Micrel KSZ8041FTL

The KSZ8041FTL PHY IC requires 50 Ω resistors between V_{cc} and Tx+/Tx- to source current to the open-drain output stage, and also 50 Ω resistors between V_{cc} and Rx+/Rx- to fix the common mode level at the Rx+/Rx- inputs at 3.3 V as well as to provide 50 Ω impedance matching.

Table 3 and Table 5 show that a 130 Ω resistor between the SD trace and ground is enough to fix the voltage at the correct levels at the SD input of the PHY IC.

Figure 9 shows the schematic of the interconnection between KSZ8041FTL and AFBR-5972Z.

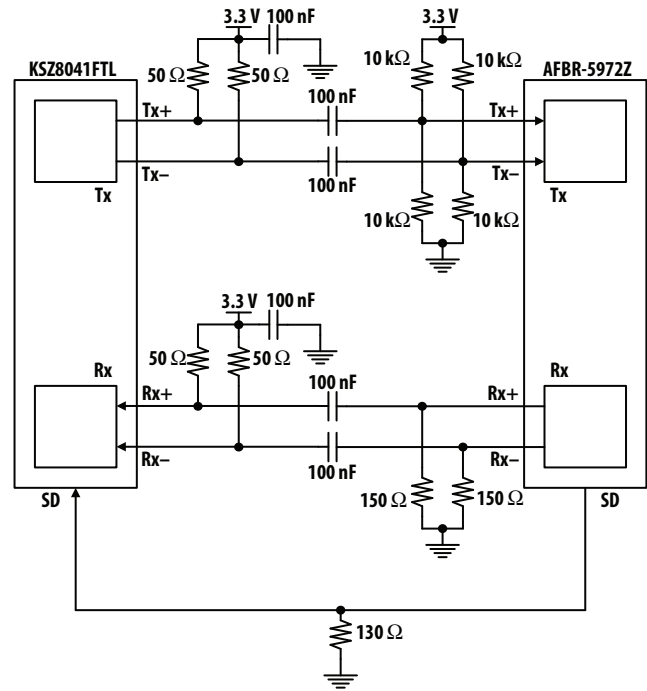


Figure 9. Interconnection between AFBR-5972Z and KSZ8041FTL

5. AFBR-59F1Z

This optical transceiver has LVPECL input/outputs. It does not include built-in de-coupling capacitors or adaptation resistors.

Figure 10 shows the internal structure of AFBR-59F1Z.

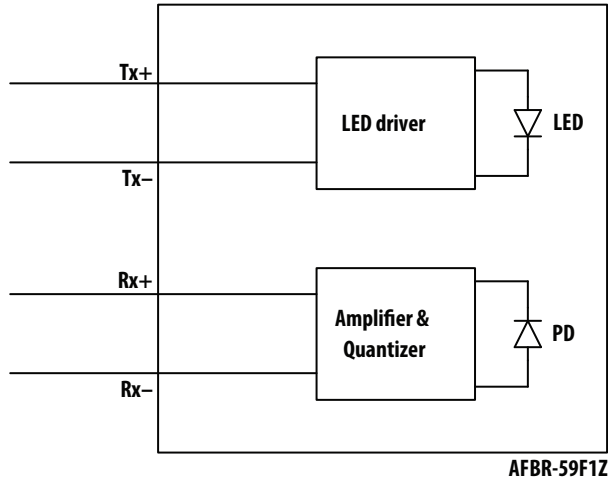


Figure 10. Internal structure of AFBR-59F1Z

As AFBR-59F1Z does not include any built-in adaptation resistors, an 82 Ω /130 Ω voltage divider is required at the Tx+/Tx- inputs to provide 50 Ω impedance matching, as well as to fix the common mode level at 2.0 V. 150 Ω resistors connected to ground are needed at the Rx+/Rx- outputs to provide a path to ground to the emitter current of the output stage.

Table 6 shows the SD voltage levels supplied by the optical Rx of AFBR-59F1Z.

Table 6. Signal Detect voltage levels supplied by AFBR-59F1Z

	Min.	Typ.	Max.
Invalid data signal	–	$V_{dd} - 1.7 \text{ V}$	–
Valid data signal	–	$V_{dd} - 0.8 \text{ V}$	–

5.1. IC+ IP101G

A 10 k Ω /15 k Ω voltage divider at both Rx+/Rx- is the only adaptation network required by IP101G. This voltage divider fixes the common mode level at 2.0 V and ensures a low current flow through it at the same time.

Table 2 and Table 6 show that a 10 Ω /174 Ω voltage divider is a valid option to fix the proper voltage levels at the SD input of the PHY IC.

Figure 11 shows the schematic of the interconnection between IP101G and AFBR-59F1Z.

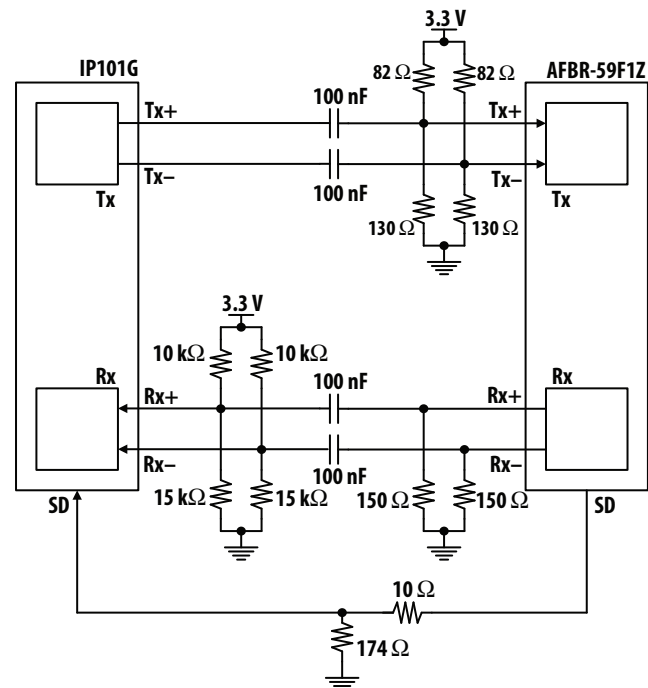


Figure 11. Interconnection between AFBR-59F1Z and IP101G

5.2. Micrel KSZ8041FTL

This PHY IC has CML inputs/outputs for communication with an external 100Base-FX optical transceiver; therefore, it requires 50 Ω resistors between V_{CC} and Tx+/Tx- to source current to its open-drain output stage and also 50 Ω resistors between V_{CC} and Rx+/Rx- to fix the common mode level at the Rx+/Rx- inputs to 3.3 V, as well as to provide 50 Ω impedance matching.

Table 3 and Table 6 show that a 130 Ω resistor between the SD trace and ground is enough to fix the voltage to the correct levels at the SD input of the PHY IC.

Figure 12 shows the schematic of the interconnection between KSZ8041FTL and AFBR-59F1Z.

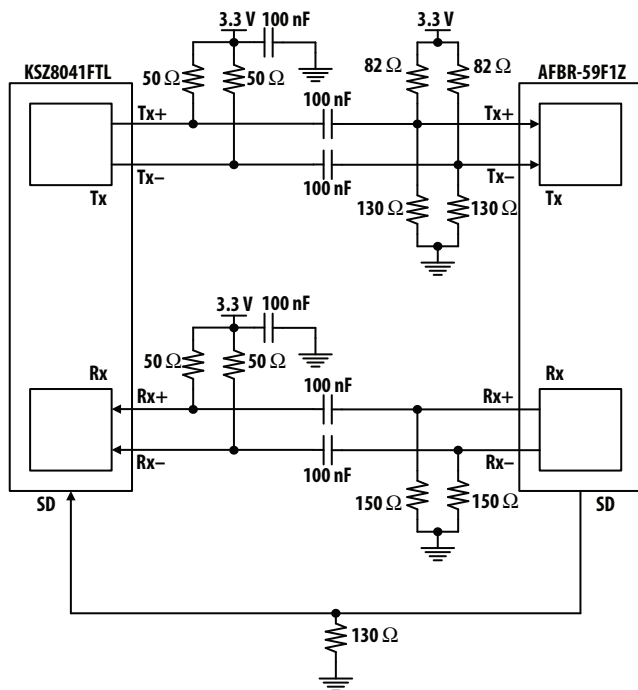


Figure 12. Interconnection between AFBR-59F1Z and KSZ8041FTL

6. Compatible PHY ICs

In addition to IC+ IP101G, there are similar PHY ICs from this manufacturer featuring the same interface for Fast Ethernet Optical Transceivers as the one included in this document.

These other PHY ICs, which are listed as follows, should work perfectly with the terminations described in this application note. They, however, have not been tested; therefore, Avago cannot guarantee full function and performance. The designer should perform his own verification.

6.1. IC+

1. IP175GH: This is a five-port embedded 10/100 PHY Switch Controller. It includes four 100Base-TX ports and one 100Base-FX port.
2. IP178G: This is an eight-port embedded 10/100 PHY Switch Controller. It includes six 100Base-TX ports and two 100Base-FX ports.

The configurations shown in Figure 2, Figure 5, Figure 8 and Figure 11 should also be valid for IP175GH and IP178G, as explained.

For product information and a complete list of distributors, please go to our web site: www.avagotech.com

Avago, Avago Technologies, and the A logo are trademarks of Avago Technologies in the United States and other countries. Data subject to change. Copyright © 2005-2014 Avago Technologies. All rights reserved. AV02-4572EN - September 24, 2014

Avago
TECHNOLOGIES