

## DN80

# Bipolar transistors for MOSFET gate driving applications

Peter Blair, Product Development Manager

---

Over the last few years MOSFETs have become the device of choice in power switching applications. Whilst on-resistances have significantly reduced, they often require a driver stage to obtain the best performance, particularly when driven from low-voltage, low-current sources. This is where the bipolar transistors inherent advantages excel, as explained below.

Power MOSFETs are often presented as voltage driven devices and as such may be mistakenly expected to be driven from any signal source, irrespective of current capability. This may be an acceptable assumption when driving in DC or very low frequency switching applications where fast edge speeds are not important, but increasingly power MOSFETs are used in switching circuits of hundreds of kHz to 10MHz and in these circumstances the gate charge requirements are a major consideration. The charge necessary to fully enhance a power MOSFET derives from its gate-source and gate-drain capacitances and is delivered via an external resistor. The gate voltage follows a characteristic RC time constant which (within EMI constraints) has to be short enough to traverse the linear region without incurring excessive switching losses in the power MOSFET.

The average gate current during the switching event can be calculated thus:

$$I_G = Q/t,$$

where:

$I_G$  is the average gate current

$Q$  is the total gate charge ( $Q_{GS} + Q_{GD}$ )

$t$  is the switching transient time ( $t_{ON}$  or  $t_{OFF}$ )


For example a typical 100V, 35m $\Omega$  DPAK MOSFET requires approximately 50nC. If it was required to switch in 20ns a gate current of 2.5 Amps is required.

There are many potential solutions to provide gate drive for power MOSFETs, including dedicated IC drivers, standard logic ICs, discrete MOSFETs and bipolar transistors. The selection criteria for gate driving usually include:

- Switching speed (hence current capability)
- Cost
- Current gain
- Size

Bipolar transistors are eminently suitable for this function as they exhibit fast switching in linear mode, have high pulse current capability, high current density, hence small size and cost.

One of the most popular and cost effective drive circuits is a bipolar, non-inverting totem-pole type driver as shown in Figure 1.

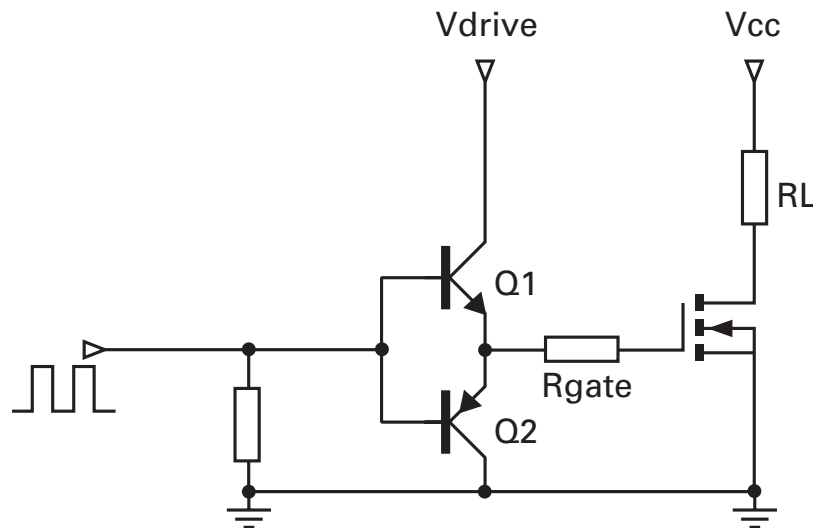

**Figure 1 Totem pole driver stage for power MOSFET**

If in the above example the power MOSFET was required to switch at a frequency of 1MHz and driven to 5Vgs the power dissipation in each driver transistor can be calculated, worst case (assuming Rg = 0), as approximately:

$$\begin{aligned}
 P_D &= ((V_{drive} * I_G * t * f) \div 2) + (V_{BE(ON)} * (I_C \div h_{FE}) * \text{Duty Cycle}) \\
 &= ((5 * 2.5 * 2E^{-8} * 1E^6) \div 2) + (0.8 * 8.3 E^{-3} * 2E^{-8} * 1E^6) \\
 &= 125.1mW
 \end{aligned}$$

where:

- P<sub>D</sub> is the power dissipation
- V<sub>drive</sub> is the drive voltage applied to the bipolar base
- I<sub>G</sub> is the average gate current
- t is the switching transient time (t<sub>ON</sub> or t<sub>OFF</sub>)
- f is the switching frequency
- V<sub>BE(ON)</sub> is the forward base-emitter voltage
- I<sub>C</sub> is the transistor collector current
- h<sub>FE</sub> is the transistor forward current gain
- Duty cycle is the proportion of each cycle in the on condition

Assuming the base current is supplied from V<sub>drive</sub> the losses per transistor are approximately

$$\begin{aligned}
 P_D &= ((V_{drive} * I * t * f) \div 2) + (V_{drive} * (I_C \div h_{FE}) * 2E^{-8} * 1E^6) * \text{Duty Cycle} \\
 &= ((5 * 2.5 * 2E^{-8} * 1E^6) \div 2) + ((5 * 8.3 E^{-3} * 2E^{-8} * 1E^6) * 0.02) \\
 &= 125.8mW
 \end{aligned}$$

With these power losses it is clear that bipolar transistors packaged in small surface mount packages are suitable, preferably co-packaged as complimentary dual devices. Some example transistors suitable for gate driving are shown in Table 1.

Device	Type	Package	$V_{CE0}$ (V)	$I_C$ (A)	$I_{CM}$ (A)	$h_{FE}$ (typ)
<b>Singles</b>						
FMMTL618	NPN	SOT23	20	1.25	4	450
FMMTL718	PNP	SOT23	20	-1.0	-2	450
FMMT617	NPN	SOT23	15	3.0	12	450
FMMT717	PNP	SOT23	-12	-2.5	-10	450
FMMT491A	NPN	SOT23	40	1.0	2	450
FMMT591A	PNP	SOT23	-40	-1.0	-2	450
ZXTN2025F	PNP	SOT23	-50	-5	-10	350
ZXTN2018F	NPN	SOT23	60	5	12	200
ZXTP2027F	PNP	SOT23	-60	-4	-10	200
ZXTN2031F	NPN	SOT23	80	5	12	350
ZXTN2020F	NPN	SOT23	100	4	12	200
ZXTP2029F	PNP	SOT23	-100	-2.5	-5	200
ZXT1M322	NPN	2x2mm MLP 3-L	15	4.5	15	450
ZXTAM322	PNP	2x2mm MLP 3-L	-12	-4.0	-12	450
ZXT3M322	NPN	2x2mm MLP 3-L	50	4.0	6	450
ZXTCM322	PNP	2x2mm MLP 3-L	-40	-3.0	-4.0	450
<b>Duals</b>						
ZXTD6717	NPN/PNP dual	SOT23-6	15 -12	1.5 -1.25	5 -3	300 300
ZXTDA1M832	NPN/PNP dual	3x2mm MLP 8-L	15 -12	4.5 -4.0	15 -12	300 300
ZXTD4591E6	NPN/PNP dual	SOT23-6	60 -60	1.0 -1.0	2 -2	200 200
ZXTDE4M832	NPN/PNP dual	3x2mm MLP 8-L	80 -70	3.5 -2.5	5 -3	450 450

**Table 1 Example transistors suitable for gate driving**

In conclusion, whilst MOSFETs have become the default choice of power switch for many designers bipolar transistors have many useful attributes which can be used beneficially in certain applications. One such application is power MOSFET gate driving, where the bipolar transistor's fast switching in linear mode, high pulse current capability, high current density, and small size and cost make them eminently suitable for this function.

Europe	Americas	Asia Pacific	Corporate Headquarters
Zetex GmbH Streitfeldstraße 19 D-81673 München Germany	Zetex Inc 700 Veterans Memorial Highway Hauppauge, NY 11788 USA	Zetex (Asia Ltd) 3701-04 Metroplaza Tower 1 Hing Fong Road, Kwai Fong Hong Kong	Zetex Semiconductors plc Zetex Technology Park, Chadderton Oldham, OL9 9LL United Kingdom
Telefon: (49) 89 45 49 49 0 Fax: (49) 89 45 49 49 49 europe.sales@zetex.com	Telephone: (1) 631 360 2222 Fax: (1) 631 360 8222 usa.sales@zetex.com	Telephone: (852) 26100 611 Fax: (852) 24250 494 asia.sales@zetex.com	Telephone (44) 161 622 4444 Fax: (44) 161 622 4446 hq@zetex.com

These offices are supported by agents and distributors in major countries world-wide.

This publication is issued to provide outline information only which (unless agreed by the company in writing) may not be used, applied or reproduced for any purpose or form part of any order or contact or be regarded as a representation relating to the products or services concerned. The company reserves the right to alter without notice the specification, design, price or conditions of supply of any product or service.