

## Boost the Run-Time of Portable Electronics with a One-Two Punch

### Introduction

A popular power source for portable devices is a single lithium-ion (Li+) cell battery (Figure 1), which provides 4.2V at full charge and 2.8V near the end of discharge. Some functions within portable electronics, such as RF amplifier circuits for wireless communication and common microcontrollers, require 2.8V and 3.3V input power rails.



Figure 1. The Battery's Ongoing Fight Against Time

These rails are normally provided by low-noise linear dropout regulators (LDOs) to ensure a quiet supply. The LDO's inputs ( $V_{CC}$  in Figure 2) must be at a slightly higher voltage than the highest LDO output. Hence,  $V_{CC}$  ends up right in the middle of the Li+ battery's range of operation. The use of a step-up/down voltage regulator, capable of operating from an input ( $V_{BATT}$ ) that can be higher or lower than the output, becomes a necessity.

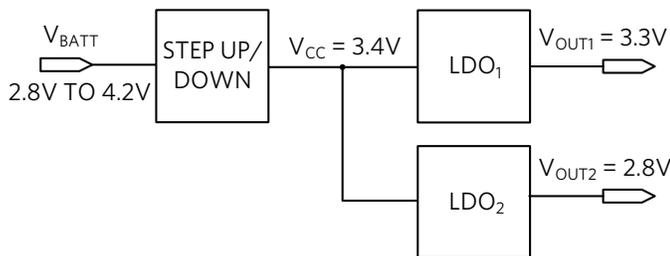


Figure 2. LDO Input Voltages Set by a Step-Up/Down Converter

In portable applications, the voltage regulator efficiency is of the utmost importance since higher efficiency translates into longer untethered operation. In this article, we will review the available options, compare their performance, and present a one-two punch approach to the most efficient solution.

### Bypass-Boost

One way to solve the battery-to-LDO voltage mismatch is to use a bypass-boost converter, namely a boost converter with an extra "pass" transistor integrated between the power source ( $V_{BATT}$ ) and the LDO input ( $V_{CC}$ ). Figure 3 shows the bypass-boost power train architecture and its operation table. Here the bypass transistor  $T_3$  accomplishes a "poor man's" step-down operation.

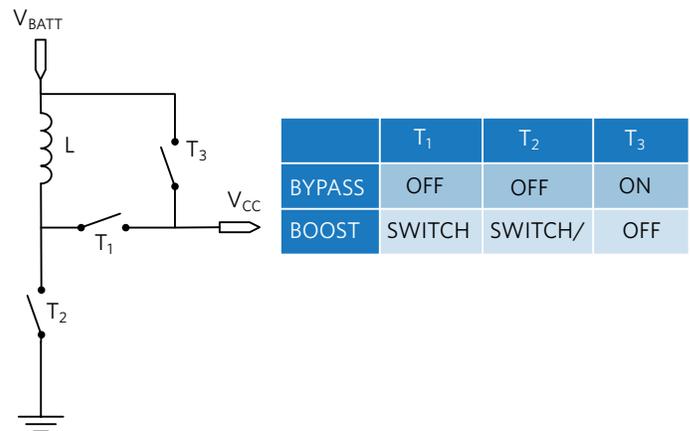


Figure 3. Bypass-Boost Power Train Schematic

This architecture can only regulate  $V_{BATT}$  voltages lower than the set  $V_{CC} = 3.4V$ . For  $V_{BATT} > 3.4V$ , the boost converter stops regulating and the pass transistor turns on, directly connecting  $V_{BATT}$  to  $V_{CC}$ . For most of the time ( $V_{BATT} > 3.4V$ ), the pass transistor in the bypass-boost architecture literally "passes the buck" to the LDOs downstream. The LDOs bear the task of regulating the high  $V_{BATT}$  value down to their output set values. Since this regulation is linear the result is high power dissipation inside the LDO. The higher heat generated becomes a burden on the PCB in terms of cost, size, and reliability.

## Buck-Boost

In contrast to the bypass-boost architecture, a buck-boost converter used in this circuit will never stop regulating its output to 3.4V. In addition, the regulation is entirely switch mode, which provides high-efficiency operation. Figure 4 shows the buck-boost power train architecture and its operation table.

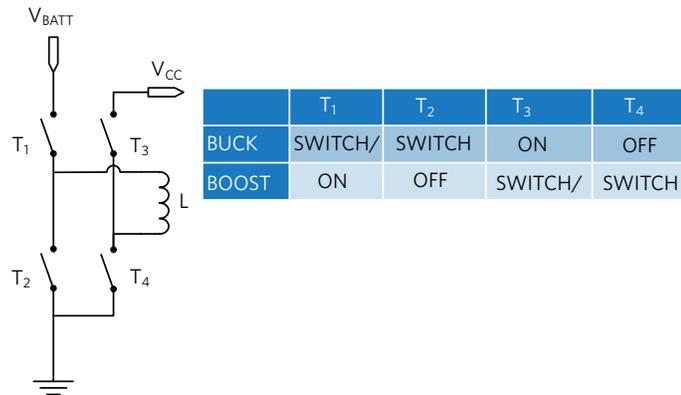


Figure 4. Buck-Boost Power Train

For  $V_{BATT} > V_{CC}$ , the IC regulates in buck (step-down) mode, while for  $V_{BATT} < V_{CC}$  it seamlessly transitions to boost (step-up) operation ensuring that the  $V_{CC}$  output remains in regulation and is glitch-free. The entire battery voltage range is covered in a switch-mode, high-efficiency fashion.

## Buck-Boost vs. Bypass-Boost

In the Figure 5 test setup, we compare the system efficiency (from  $V_{BATT}$  to  $V_{OUT}$ ) with Maxim's **MAX77816** buck-boost IC vs. a competitive bypass-boost IC. Each step-up/down converter feeds a single 3.3V LDO loaded with 500mA.

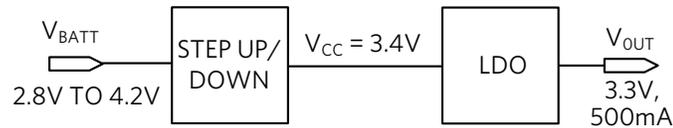


Figure 5. Efficiency Test Setup

Figure 6 shows the result of the comparison. Solid curves indicate efficiency and dashed curves show battery current consumption for each solution. The buck-boost efficiency (above 93% across the entire operation range) is far superior to that of the bypass-boost (as low as 81% with full battery). This superior performance is due to the ability of the buck-boost IC to supply power to the LDO in switch mode across the entire range of operation. The vertical dotted line highlights the transition point from step-up/down to step-down/up mode.

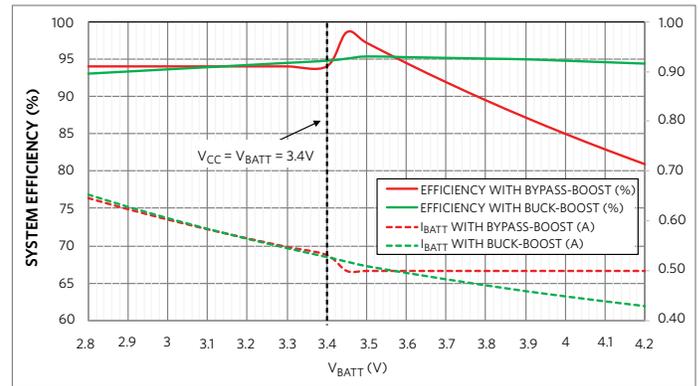


Figure 6. Buck-Boost vs. Bypass-Boost System Efficiency Comparison ( $V_{BATT}$  to  $V_{OUT}$ )

## Buck-Boost vs. Buck-Boost

In Figure 7, we compare the efficiency (from  $V_{BATT}$  to  $V_{CC}$ ) of MAX77816 to a similar buck-boost IC. The comparison in this case uses  $V_{CC} = 3.3V$  and  $V_{BATT} = 3.3V$ , since the competing data is readily available, as opposed to  $V_{CC} = 3.4V$ .

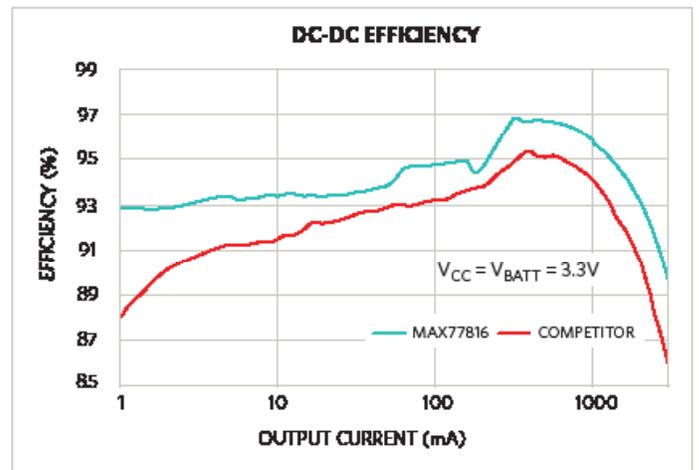


Figure 7. MAX77816 vs. Competitor Buck-Boost

The test results show that the MAX77816 outperforms the competing buck-boost over the entire current range from 1mA to 3A. The efficiency advantage is as high as 5%. This leads to the “first punch” of the solution to the efficiency problem: use the best available buck-boost converter.

## DVS for Efficiency

Dynamic voltage scaling (DVS) can further improve system efficiency. The buck-boost load is normally comprised of many LDOs, all at different  $V_{OUT}$ . These LDOs may not all be operational at the same time. When the LDO with the highest  $V_{OUT}$  is disabled, the system can lower the buck-boost output ( $V_{CC}$ ) in a manner compatible with the next highest  $V_{OUT}$ , effectively reducing the voltage dropout and thus save power.

## DVS With Direct Hardware Control

A two-level output voltage selection is easily achieved with a dedicated DVS logic-input pin when direct hardware control is desired. The MAX77816 supports a programmable general-purpose input pin that can be configured as a DVS input between two preset/programmable values. The default values are 3.4V and 5V, but can be adjusted upon request. For further power savings, a more granular selection of output voltages must be implemented, which requires a different type of output voltage control. This is discussed in the next section.

## The Advantage of an I<sup>2</sup>C-Driven DVS

The MAX77816 features an I<sup>2</sup>C-compatible serial interface, used for regulator on/off control, setting output voltage value and slew rates, and additional functions. With I<sup>2</sup>C, the regulator output voltage can be dynamically adjusted, thus enabling finer control of system power consumption without the need for a dedicated DVS input pin.

The curves in Figure 8 refer to a Li<sup>+</sup> battery-powered, step-up/down converter loaded with a 3V-output, 32mA LDO, and a second 2.85V-output, 18mA LDO. The descending, orange curve, is the discharge profile of the Li<sup>+</sup> battery with typical system shutdown at 3.4V (systems seldom deplete the battery all the way down to 2.8V). The rest of the curves profile the accumulated extended battery operating time of the MAX77816 due to voltage scaling. The light-blue curve shows the advantage of the buck-boost with 3.4V output vs. a boost-bypass architecture. The rest of the curves show the advantage of reducing the buck-boost output  $V_{CC}$  via I<sup>2</sup>C down to 3.15V for duty cycles from 25% to 75%.

The extended battery operating time varies from 45 to 82 minutes. The second punch of the solution is clear: employ DVS via an I<sup>2</sup>C bus.

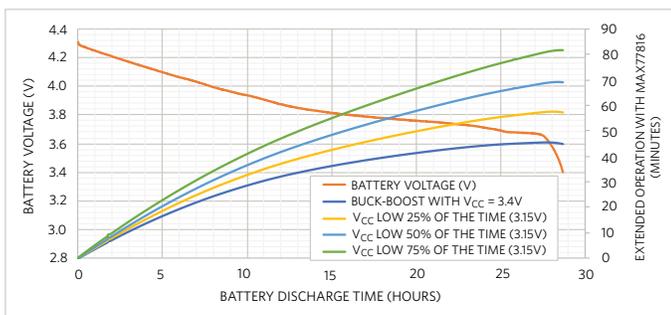


Figure 8. The MAX77816 I<sup>2</sup>C Advantage

## Conclusion

A comparison of the buck-boost architecture to the bypass-boost architecture shows that, in principle, the buck-boost is a superior architecture. A practical comparison of the MAX77816 buck-boost solution versus a competing bypass-boost solution shows that in operation, the MAX77816 has an efficiency advantage of up to 13%. When compared to a competing buck-boost solution, the MAX77816 outperforms it by as much as 6 efficiency points. These efficiencies, combined with those derived from dynamic voltage scaling via an I<sup>2</sup>C bus or via a dedicated DVS input pin, result in extended operation for a battery-powered device of up to 90 minutes. Thus, a buck-boost IC with DVS is the ideal solution for power-stingy portable applications.

## Glossary Terms

**DVS:** Dynamic voltage scaling

**I<sup>2</sup>C Bus:** Inter-integrated circuit bus

## Learn more:

[MAX77816 3A High-Efficiency Buck-Boost Regulator](#)

[Design Solution 1: Choosing the Right Step-Up/Down Voltage Regulator for Portable Applications](#)

Design Solutions No. 73

Rev 0; December 2017

[Visit the Maxim Support Center](#)

[Find More Design Solutions](#)

Maxim Integrated  
160 Rio Robles  
San Jose, CA 95134 USA  
408-601-1000

[maximintegrated.com/design-solutions](http://maximintegrated.com/design-solutions)

