

Combinational Logic Design Trainer Lab Manual

Table of Contents

Combinational Logic Design Trainer	1
1 Combinational Logic Design Trainer	4
2 Microprocessors	7
2.1 Introduction to Microprocessors.....	7
2.2 Combinational and Sequential Circuit Analogy.....	9
3 Digital Logic Circuits	10
3.1 Basic Logic Gates.....	10
3.1.1 AND, OR and NOT Gates.....	10
3.1.2 Truth Tables.....	11
3.1.3 Logic Symbols.....	11
3.1.4 NAND, NOR, XOR and XNOR Gates	11
3.2 Digital Circuits	13
3.3 Identifying Combinational Circuits.....	14
3.4 Analysis of Combinational Circuits	14
3.5 Boolean Algebra.....	16
3.5.1 Expressions and Equations	16
3.5.2 Axioms and Theorems.....	17
3.5.3 Manipulating Boolean Equations	18
3.5.4 Relationship between Boolean Equations and Combinational Circuits	18
3.6 Simplifying Combinational Circuits.....	19
3.6.1 Using Boolean Algebra	19
3.6.2 Using K-Maps	20
3.7 Synthesis of Combinational Circuits	24
4 Labs	27
4.1 Lab 1: Basic Gates, Lights, Action!	28
4.2 Lab 2: NAND, NOR, XOR and XNOR Gates	32
4.3 Lab 3: Designing Combinational Circuits	35
4.4 Lab 4: Multiplexers	38
4.5 Lab 5: Decoders.....	40
4.6 Lab 6: Comparators	42
4.7 Lab 7: Full Adder	44
4.8 Lab 8: 4-bit Adder	46
4.9 Lab 9: 4-bit Adder/Subtractor	48
4.10 Lab 10: 2-bit Arithmetic and Logic Unit (ALU).....	53
4.11 Lab 11: BCD to 7-segment LED Decoder	58