

# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter

## About this document

### Scope and purpose

This document provides a comprehensive functional description and guide for the REF\_500W\_CYCLO\_BDSGAN solar microinverter reference design based on a cycloconverter topology. The circuit functionality is discussed in detail. The system implementation including converter architecture, control algorithms, and firmware is also described. Waveforms are shown under all operating conditions, and test measurement data is presented.

### Intended audience

This application note is intended for design engineers, applications engineers, and students.

### Infineon components featured

- OptiMOS™ 6 power MOSFET 80 V [ISC014N08NM6](#), 1.45 mΩ N-channel in a 5 mm x 6 mm SuperSO8 package
- OptiMOS™ 6 power MOSFET 80 V [ISC056N08NM6](#), 5.6 mΩ N-channel in a 5 x 6 mm SuperSO8 package
- CoolGaN™ bidirectional switch 650 V G5 [IGLT65R055B2](#), 55 mΩ enhancement mode bidirectional GaN HEMT with GIT gate structure in top-side cooled PG-HDSOP-16 package
- EiceDRIVER™ 120 V [2EDL8034F5B](#), 3 A/4 A source/sink isolated high-side and low-side gate driver in SO-8 (PG-DSO-8) package
- EiceDRIVER™ [2EDR7259X](#) 5 A/9 A source/sink dual-channel gate driver for CoolMOS™ and CoolGaN™
- PSOC™ Control C3 [PSC3M5FDS2AFQ1](#), Arm® Cortex®-M33 32-bit MCU+FPU+DSP, 180 MHz, up to 256 KB flash/64 KB SRAM, real-time control

### Keypoints

- Specifications for a high-efficiency microinverter design based on cycloinverter topology employing bidirectional GaN HEMT devices at the AC switching side
- Set the control algorithms, implement the firmware for the microinverter, design the PCB layout, and test the performance

## About this product family

### Product family

Infineon's [CoolGaN™](#) solution offers unmatched quality that operates at higher switching speeds resulting in lower power losses, higher efficiency paving the way for smaller and lighter power supplies with the same power supplies with the same size but increased power capability.

### Target applications

#### [Solar microinverters](#)

## Important notice

### Important notice

**“Evaluation Boards and Reference Boards” shall mean products embedded on a printed circuit board (PCB) for demonstration and/or evaluation purposes, which include, without limitation, demonstration, reference and evaluation boards, kits and design (collectively referred to as “Reference Board”).**

**Environmental conditions have been considered in the design of the Evaluation Boards and Reference Boards provided by Infineon Technologies. The design of the Evaluation Boards and Reference Boards has been tested by Infineon Technologies only as described in this document. The design is not qualified in terms of safety requirements, manufacturing and operation over the entire operating temperature range or lifetime.**

**The Evaluation Boards and Reference Boards provided by Infineon Technologies are subject to functional testing only under typical load conditions. Evaluation Boards and Reference Boards are not subject to the same procedures as regular products regarding returned material analysis (RMA), process change notification (PCN) and product discontinuation (PD).**

**Evaluation Boards and Reference Boards are not commercialized products, and are solely intended for evaluation and testing purposes. In particular, they shall not be used for reliability testing or production. The Evaluation Boards and Reference Boards may therefore not comply with CE or similar standards (including but not limited to the EMC Directive 2004/EC/108 and the EMC Act) and may not fulfill other requirements of the country in which they are operated by the customer. The customer shall ensure that all Evaluation Boards and Reference Boards will be handled in a way which is compliant with the relevant requirements and standards of the country in which they are operated.**

**The Evaluation Boards and Reference Boards as well as the information provided in this document are addressed only to qualified and skilled technical staff, for laboratory usage, and shall be used and managed according to the terms and conditions set forth in this document and in other related documentation supplied with the respective Evaluation Board or Reference Board.**

**It is the responsibility of the customer’s technical departments to evaluate the suitability of the Evaluation Boards and Reference Boards for the intended application, and to evaluate the completeness and correctness of the information provided in this document with respect to such application.**

**The customer is obliged to ensure that the use of the Evaluation Boards and Reference Boards does not cause any harm to persons or third-party property.**

**The Evaluation Boards and Reference Boards and any information in this document is provided "AS IS" without any warranty and liability and Infineon Technologies disclaims any warranties, express or implied, including but not limited to warranties of non-infringement of third-party rights and implied warranties of fitness for any purpose, or for merchantability.**

**Infineon Technologies shall not be responsible for any damages resulting from the use of the Evaluation Boards and Reference Boards and/or from any information provided in this document. The customer is obliged to defend, indemnify and hold Infineon Technologies harmless from and against any claims or damages arising out of or resulting from any use thereof.**

**Infineon Technologies reserves the right to modify this document and/or any information provided herein at any time without further notice.**

## Safety precautions

### Safety precautions

Note: Please note the following warnings regarding the hazards associated with development systems

Table 1 Safety precautions

|                                                                                     |                                                                                                                                                                                                                                                                                                                                                                                                                                                   |
|-------------------------------------------------------------------------------------|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
|    | <b>Warning:</b> This reference design is intended for evaluation in a laboratory environment using a grid simulator and observing high voltage safety precautions. It is NOT intended for connection directly to the AC power grid and is not certified for this purpose! <b>DO NOT CONNECT DIRECTLY TO THE AC POWER GRID!</b>                                                                                                                    |
|    | <b>Warning:</b> The evaluation or reference board contains DC bus capacitors which take time to discharge after removal of the main supply. Before working on the system, wait at least ten minutes for capacitors to discharge to safe voltage levels. Failure to do so may result in personal injury or death. Darkened display LEDs are not an indication that capacitors have discharged to safe voltage levels.                              |
|    | <b>Caution:</b> The heat sink and device surfaces of the evaluation or reference board may become hot during testing. Hence, necessary precautions are required while handling the board. Failure to comply may cause injury.                                                                                                                                                                                                                     |
|   | <b>Caution:</b> Only personnel familiar with power electronics and trained in testing and evaluating such power boards should plan, install, commission and subsequently service the system. Failure to comply may result in personal injury and/or equipment damage.                                                                                                                                                                             |
|  | <b>Caution:</b> The evaluation or reference board contains parts and assemblies sensitive to electrostatic discharge (ESD). Electrostatic control precautions are required when installing, testing, servicing or repairing the assembly. Component damage may result if ESD control procedures are not followed. If you are not familiar with electrostatic control procedures, refer to the applicable ESD protection handbooks and guidelines. |
|  | <b>Caution:</b> The reference board is shipped with packing materials that need to be removed prior to installation. Failure to remove all packing materials that are unnecessary for system installation may result in overheating or abnormal operating conditions.                                                                                                                                                                             |

## Table of contents

### Table of contents

|                                                           |           |
|-----------------------------------------------------------|-----------|
| <b>About this document.....</b>                           | <b>1</b>  |
| <b>About this product family .....</b>                    | <b>1</b>  |
| <b>Important notice .....</b>                             | <b>2</b>  |
| <b>Safety precautions.....</b>                            | <b>3</b>  |
| <b>Table of contents.....</b>                             | <b>4</b>  |
| <b>1 Introduction .....</b>                               | <b>7</b>  |
| 1.1 Microinverter basics .....                            | 7         |
| 1.2 Microinverter topologies.....                         | 8         |
| 1.2.1 Traditional microinverter topologies .....          | 8         |
| 1.2.2 What is a cycloconverter? .....                     | 9         |
| 1.2.2.1 Benefits of bidirectional GaN.....                | 10        |
| <b>2 Specifications .....</b>                             | <b>11</b> |
| 2.1 Electrical characteristics.....                       | 11        |
| 2.1.1 Input DC side .....                                 | 11        |
| 2.1.2 Output AC side.....                                 | 11        |
| 2.2 Mechanical specifications.....                        | 12        |
| 2.3 Environment and cooling.....                          | 12        |
| 2.3.1 Dimensions and weight .....                         | 12        |
| 2.3.2 Input and output connectors.....                    | 12        |
| 2.4 Efficiency requirements .....                         | 13        |
| 2.5 Signal sensing and protections.....                   | 13        |
| <b>3 Control and communication .....</b>                  | <b>14</b> |
| 3.1.1 Control functionality.....                          | 14        |
| 3.1.2 Connectivity .....                                  | 14        |
| <b>4 Schematics.....</b>                                  | <b>15</b> |
| <b>5 Hardware functional description .....</b>            | <b>26</b> |
| 5.1 Control scheme .....                                  | 27        |
| 5.1.1 Switching states .....                              | 30        |
| 5.1.2 Soft switching (ZVS) .....                          | 36        |
| 5.1.3 Frequency domain analysis .....                     | 37        |
| 5.1.3.1 Transmission power and RMS resonant current ..... | 39        |
| 5.1.4 Modulation optimization .....                       | 40        |
| 5.1.4.1 Fixed-switching frequency analysis .....          | 40        |
| 5.1.4.2 Variable switching frequency analysis .....       | 41        |
| 5.1.4.3 ZVS optimization modulation .....                 | 45        |
| 5.2 Power stage and gate drivers.....                     | 50        |
| 5.2.1 Transformer turns ratio selection .....             | 51        |
| 5.2.2 Resonant inductor and capacitor selection .....     | 54        |
| 5.3 Output filter and relay.....                          | 56        |
| 5.4 On board auxiliary power.....                         | 56        |
| 5.5 Control and monitoring circuitry.....                 | 57        |
| 5.6 Control and firmware .....                            | 57        |
| 5.7 Control algorithm.....                                | 57        |
| 5.7.1 MPPT control.....                                   | 59        |
| 5.7.2 Feedforward control .....                           | 60        |
| 5.7.3 Burst mode control .....                            | 60        |

## Table of contents

|           |                                                            |            |
|-----------|------------------------------------------------------------|------------|
| 5.8       | Firmware implementation .....                              | 62         |
| 5.8.1     | Overview .....                                             | 62         |
| 5.8.2     | Main.c and background tasks .....                          | 63         |
| 5.8.3     | Control ISR.....                                           | 64         |
| 5.8.4     | MPPT .....                                                 | 70         |
| 5.8.5     | Communication and command set.....                         | 70         |
| 5.8.6     | Protection.....                                            | 71         |
| <b>6</b>  | <b>Test setup .....</b>                                    | <b>73</b>  |
| 6.1       | Connections used for all tests.....                        | 73         |
| 6.1.1     | Auxiliary supply connections .....                         | 73         |
| 6.1.2     | Connecting to the PC and GUI .....                         | 74         |
| 6.1.3     | DC input supply connections.....                           | 75         |
| 6.2       | Off-grid test setup .....                                  | 75         |
| 6.3       | On-grid test setup.....                                    | 76         |
| 6.3.1     | Grid simulator connections .....                           | 77         |
| 6.3.2     | Constant output current mode.....                          | 78         |
| 6.3.3     | MPPT mode .....                                            | 78         |
| <b>7</b>  | <b>GUI tool and operation.....</b>                         | <b>79</b>  |
| 7.1.1     | Basic functions .....                                      | 79         |
| 7.1.2     | Off-grid operation .....                                   | 80         |
| 7.1.3     | On-grid (grid-tied) constant current operation .....       | 82         |
| <b>8</b>  | <b>Bill of materials.....</b>                              | <b>85</b>  |
| 8.1       | Electrolytic capacitor board .....                         | 85         |
| 8.2       | Main power board .....                                     | 85         |
| 8.3       | Heatsink drawings.....                                     | 101        |
| <b>9</b>  | <b>Transformer and inductor specifications .....</b>       | <b>103</b> |
| 9.1       | Step-up transformer (TR1) .....                            | 103        |
| 9.2       | Filter inductors (Lf1 and Lf2) .....                       | 105        |
| 9.3       | Auxiliary power inductor (T1) .....                        | 107        |
| <b>10</b> | <b>PCB layout design .....</b>                             | <b>109</b> |
| 10.1      | Electrolytic capacitor board .....                         | 113        |
| <b>11</b> | <b>Test results.....</b>                                   | <b>114</b> |
| 11.1      | Power and efficiency measurements .....                    | 114        |
| 11.1.1    | Off-grid operation .....                                   | 114        |
| 11.1.1.1  | Voltage and current harmonics.....                         | 115        |
| 11.1.2    | On-grid operation with burst mode enabled .....            | 116        |
| 11.1.2.1  | CEC weighted efficiency measurements and calculation ..... | 117        |
| 11.1.3    | MPPT efficiency .....                                      | 118        |
| 11.2      | Thermal measurements.....                                  | 120        |
| 11.3      | Operating waveforms.....                                   | 121        |
| 11.3.1    | Off-grid operation .....                                   | 121        |
| 11.3.2    | On-grid operation.....                                     | 122        |
| 11.3.2.1  | Input 35 VDC.....                                          | 122        |
| 11.3.2.2  | Input 50 VDC.....                                          | 127        |
| 11.3.3    | On-grid operation in burst mode.....                       | 129        |
| <b>12</b> | <b>Conclusion .....</b>                                    | <b>130</b> |
| <b>13</b> | <b>Related resources .....</b>                             | <b>131</b> |
|           | <b>References.....</b>                                     | <b>132</b> |

## Table of contents

|                       |     |
|-----------------------|-----|
| Revision history..... | 133 |
| Disclaimer.....       | 134 |

## 1 Introduction

### 1 Introduction

#### 1.1 Microinverter basics


Solar microinverters along with optimizers fall into the category of module-level power electronics (MLPE). These modules are attached underneath solar panels typically installed on a roof. Microinverters convert DC current converted from sunlight by solar panels<sup>1</sup>, to AC output to be connected to the power grid. Devices that can transfer power to the grid are referred to as “grid tied”. Microinverters differ from central and string inverters because, instead of receiving power from an array of PV panels, they operate at the panel level in a modular manner with their outputs connected in paralleled.

In a typical example, the Enphase IQ8+ microinverter is rated for a continuous output power of 290 VA<sup>2</sup> and an input power of 235 W to 440 W from a voltage of 16 V to 58 V. The advantage of microinverters and other MLPE devices such as power optimizers, is that the maximum power point can be utilized for each individual PV panel. In this way, shading of one panel in the array does not limit the power conversion ability of other panels receiving more sunlight as it would with series connected PV panels. Because of this, MLPE installations produce more solar energy.

Traditional string inverters are much larger and bulkier than microinverters, which are slightly larger than the junction box on a solar panel and typically weigh 2 lbs to 4 lbs.. A solar installation with microinverters is costlier overall than one using a string inverter.

Most solar microinverters are plug-and-play devices, meaning they can be connected and operated in a few easy steps or disconnected with minimal time and tools required. They usually include built-in MC4 connectors for quick and easy connection.

Microinverters are generally supported with remote monitoring technology so that the status of each device in the installation and hence the solar energy performance of each panel can be monitored with a smartphone application.

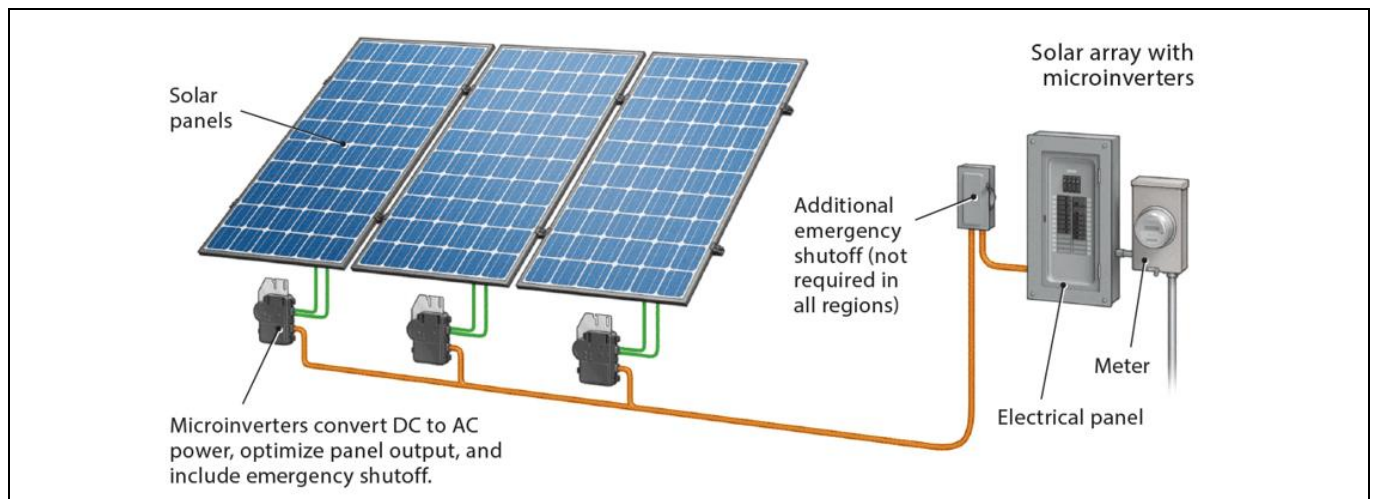

**Figure 1** Solar installation using microinverters

<sup>1</sup> Also known as PV (photovoltaic) panels.

<sup>2</sup> The AC output rating in VA indicates that the microinverter can transfer active and reactive power to the grid.


## 1 Introduction

### 1.2 Microinverter topologies

Microinverters are based on a two-stage architecture, the front-end stage is the MPPT block which converts PV panel voltage to a higher voltage- suitable for the back-end inverter stage to convert to AC to be tied to the grid.


#### 1.2.1 Traditional microinverter topologies

Microinverter designs have traditionally used a DC to DC front-end stage to produce a high voltage DC bus voltage, which is then converted to line frequency sinusoidal AC by the back-end inverter stage.

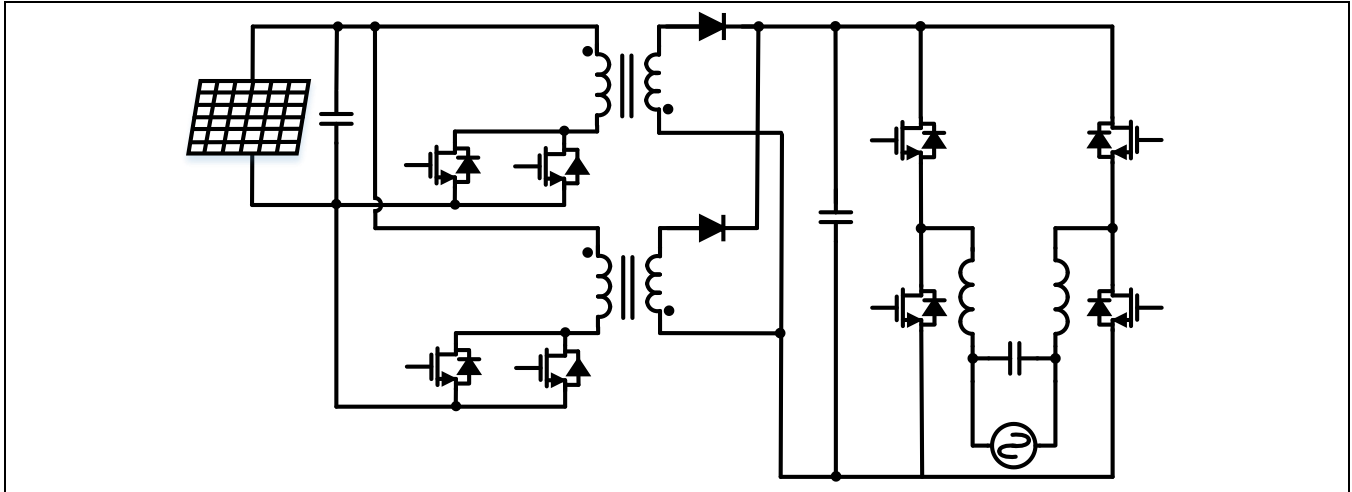

**Figure 2** Flyback + full-bridge type microinverter


The voltage source flyback based MPPT followed by a full bridge inverter is less complicated but has lower efficiency than alternative design concepts. In the above example, efficiency is improved by using parallel flyback stages. A more popular current source flyback implementation is shown in the following figure.

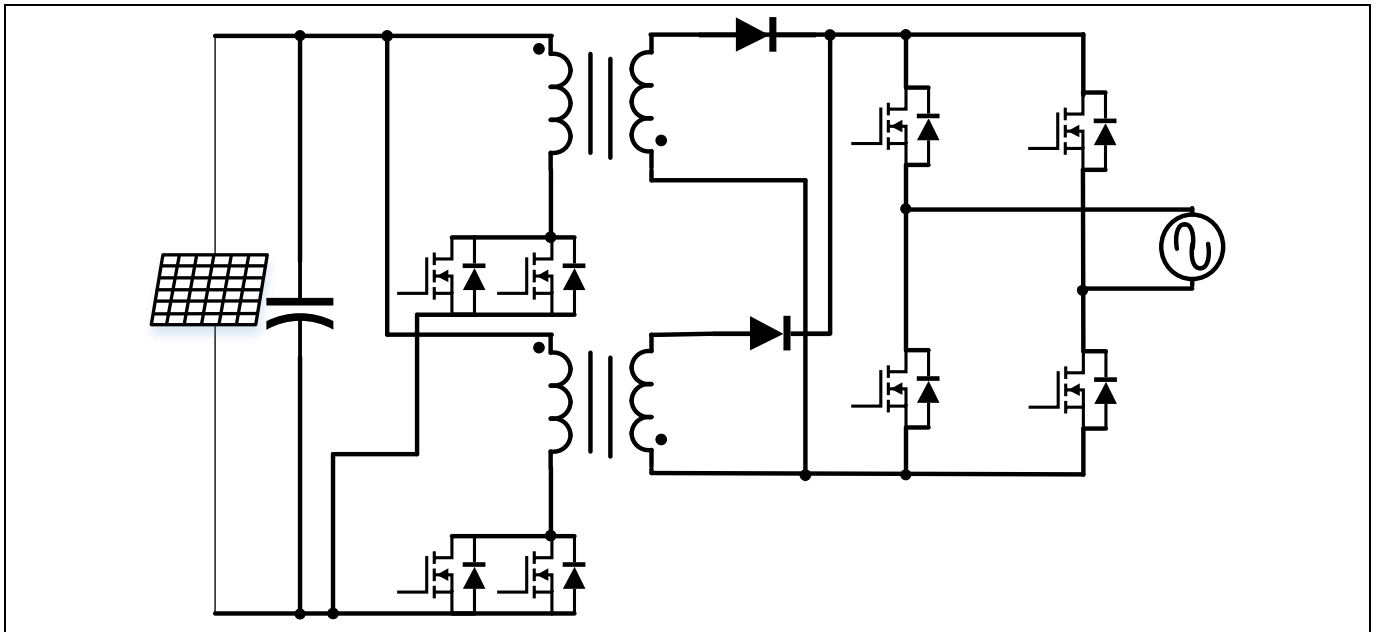

**Figure 3** Flyback + unfolding type microinverter

## 1 Introduction

The dual-active bridge offers better efficiency than the flyback by eliminating the rectifier diodes and using a direct energy transfer transformer based current source approach. The output bridge is used as a low frequency unfolding stage only. This design is more complex than the flyback but simpler than a cycloinverter.

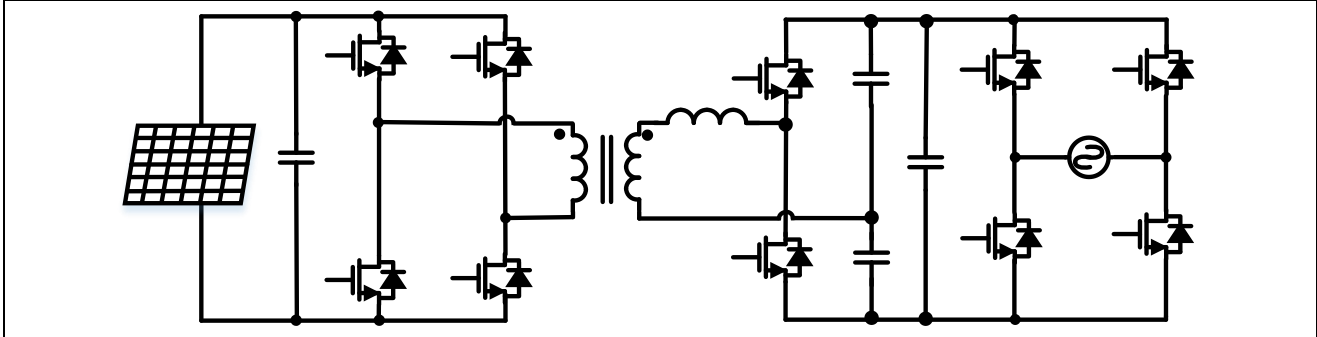

**Figure 4** Dual active bridge and unfolding type microinverter

### 1.2.2 What is a cycloinverter?

A broad definition of a cycloinverter (also known as a cycloconverter) is a power conversion system, which converts AC electrical power directly from one frequency to another without the need for an intermediate DC link, hereby eliminating conduction losses from the rectifying diodes used in other topologies to improve efficiency. The cycloinverter is a resonant design able to operate with soft-switching over a wide operating range.

Infineon's REF\_500W\_CYCLO\_BDSGAN reference design is based on a cycloinverter topology based on a full bridge primary stage, which employs a bidirectional switch. A detailed description of the topology and theory of operation is provided in Section 5.



**Figure 5** REF\_500W\_CYCLO\_BDSGAN reference design board

## 1 Introduction

### 1.2.2.1 Benefits of bidirectional GaN

CoolGaN™ BDS 650 V G5 offers a significant improvement in system efficiency and power density compared to traditional back-to-back unidirectional solutions. The cycloinverter efficiency depends on achieving zero voltage switching (ZVS) over a wide range of line and load, which is explained in more detail in this document. Since  $C_{oss}$  for GaN power switches is inherently much lower than for silicon MOSFET devices with much less variation over voltage, using GaN enables ZVS operation over a wider range with reduced dead-time, thereby enabling efficiency improvement.

GaN transistors operate laterally, which allows the monolithic integration of several devices on a single chip. Compact switches able to block high voltages in both polarities provides high-performance bidirectional switches in a single package offering significant space saving to offer an area/cost advantage over conventional realizations with vertical MOSFET switches by almost a factor of 4.

Infineon's CoolGaN™ GIT technology is based on a hybrid-drain HEMT with p-GaN gate resulting in a robust normally off power switch. To deal with the particularities of this concept, an innovative differential gate-drive concept has been implemented. The isolated gate drive circuit based on Infineon's EiceDRIVER™ 2EDR7259X provides negative  $V_{GS}$  voltage, which leads to safe off-states during switching transients. Additionally, it protects the GaN switch against spurious turn-on.

## 2 Specifications

## 2 Specifications

### 2.1 Electrical characteristics

#### 2.1.1 Input DC side

**Table 1** Input operating parameters

| Parameter                              | Value             |
|----------------------------------------|-------------------|
| PV module compatibility                | 60/66/72/78 cells |
| Minimum/Maximum input voltage          | 16/60 V           |
| Minimum/Maximum Start-up voltage       | 22/58 V           |
| Minimum/Maximum MPPT voltage           | 25/50 V           |
| Maximum short-circuit DC input current | 18 A              |

#### 2.1.2 Output AC side

**Table 2** Output operating conditions

| Condition                                       | Value                       |
|-------------------------------------------------|-----------------------------|
| Maximum continuous output power                 | 500 W                       |
| AC nominal (L-L) voltage                        | 240 VRMS                    |
| AC (L-L) voltage operating range                | 185-276 VRMS                |
| Maximum continuous output current               | 2.1 ARMS                    |
| Nominal line frequencies supported <sup>1</sup> | 50/60 Hz                    |
| Total harmonic distortion of current            | <5% for >50% load condition |
| Grid-tied power factor setting range            | -0.8 to 1, +0.8 to 1        |
| Off-grid mode minimum load                      | 50 W                        |

<sup>1</sup> The default line frequency setting is 60 Hz. A firmware parameter change is required for 50 Hz operation.

## 2 Specifications

### 2.2 Mechanical specifications

### 2.3 Environment and cooling

**Table 3** Ambient operating temperature

| Condition       | Description                                       |
|-----------------|---------------------------------------------------|
| Testing ambient | Room temperature (~25 °C)                         |
| Cooling         | Natural convection – no fans<br>Optional heatsink |

#### 2.3.1 Dimensions and weight

**Table 4** Dimension and weight limits

| Specification          | Value                   |
|------------------------|-------------------------|
| Enclosure              | No enclosure provided   |
| Dimensions (H x W x D) | 190 mm x 145 mm x 35 mm |
| Weight                 | 0.7 kg                  |

*Note:* Size includes fully populated PCB and heatsink and excludes connectors and possible housing.

#### 2.3.2 Input and output connectors

| MC4                                    |                         |
|----------------------------------------|-------------------------|
| Cable Cross-Section (mm <sup>2</sup> ) | 2.5 - 10                |
| Contact Material                       | Tin-platted copper      |
| Rated Current                          | 39 - 104A               |
| Max. Voltage                           | 1,000V                  |
| IP Index                               | IP65                    |
| Max. Temperature                       | 105°C                   |
| Safety Class                           | II                      |
| Safety Mechanism                       | Plug lock               |
| Locking/Unlocking Tool                 | Useful but not required |



**Figure 6** Connection system, DC side, MC4 connectors matching the PV panel output

These connectors are not supplied as part of the REF\_500W\_CYCLO\_BDSGAN reference design kit but if needed can be attached to the board via ring terminals with sufficient current rating.

## 2 Specifications

### 2.4 Efficiency requirements

**Table 5** Efficiency requirements

| Efficiency type         | Requirement |
|-------------------------|-------------|
| Peak efficiency         | > 97%       |
| CEC weighted efficiency | > 96%       |

CEC weighted efficiency is calculated as in the following equation:

$$(0.04 \times Eff@10\%) + (0.05 \times Eff@20\%) + (0.12 \times Eff@30\%) + (0.21 \times Eff@50\%) + (0.53 \times Eff@75\%) + (0.05 \times Eff@100\%)$$

**Equation 1**

Efficiency is measured at  $T_{amb} = 25^{\circ}\text{C}$ ,  $V_{in} = 35\text{ V}$ ,  $V_{out} = 240\text{ V}_{RMS}$  after at least 30-minutes operation.

### 2.5 Signal sensing and protections

**Table 6** Fault protections

| Signals          | Sensing method                  | Protection     |
|------------------|---------------------------------|----------------|
| DC voltage       | Resistor divider network        | OV, UV         |
| DC current       | Current shunt resistor          | OC             |
| AC voltage       | Resistor divider network        | OV, UV, OF, UF |
| AC current       | Hall current sensor             | OC             |
| Resonant current | Current transformer             | OC             |
| Temperature      | Resistance temperature detector | OTP            |

Differential amplifier circuits based on operational amplifiers are used in most of the cases listed above to scale the measured signals appropriately for the MCU ADC inputs in the zero to 3.3 V range.

## 3 Control and communication

### 3 Control and communication

The control and communication is based on the Infineon PSOC™ Control C3 MCU.

#### 3.1.1 Control functionality

The following supervision, protection, and performance measurement are implemented:


- System state machine
- MPPT incremental conductance algorithm
- Grid synchronization and grid tie operation
- Single Microinverter standalone operation
- Reactive power control
- Software protection for fault conditions detailed in the above table
- MPPT remove option to test with a regular current DC source at input
- Soft switching range > 50% @ rated power

#### 3.1.2 Connectivity


- **Programmer/debugger type:** Segger J-Link supporting SWD interface
- **Programmer/debugger interface:** Arm® Serial Wire Debug (SWD) interface (P3)
- **Control interface:** UART1 serial port (P1)
  - **Baud rate:** 115200
  - **Flow control:** None
  - **Check bit:** None
  - **Stop bits:** 1
- **Graphical User Interface (GUI) tool:** Infineon Cyclo uInverter Commander

## 4 Schematics


### 4 Schematics

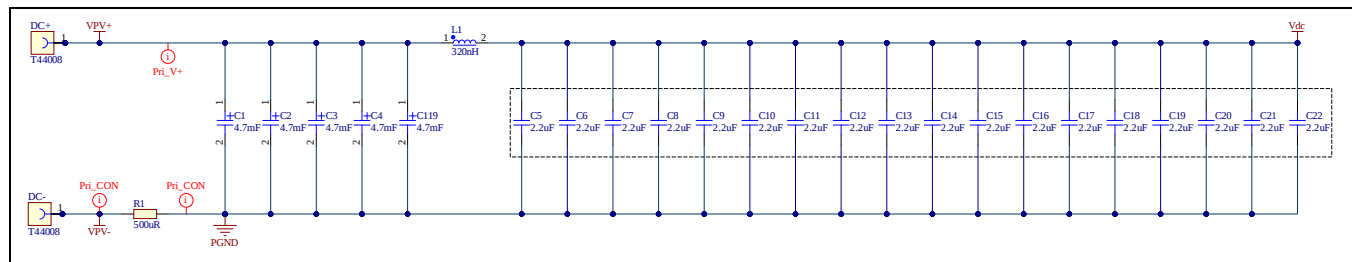

**Figure 7** PV input section

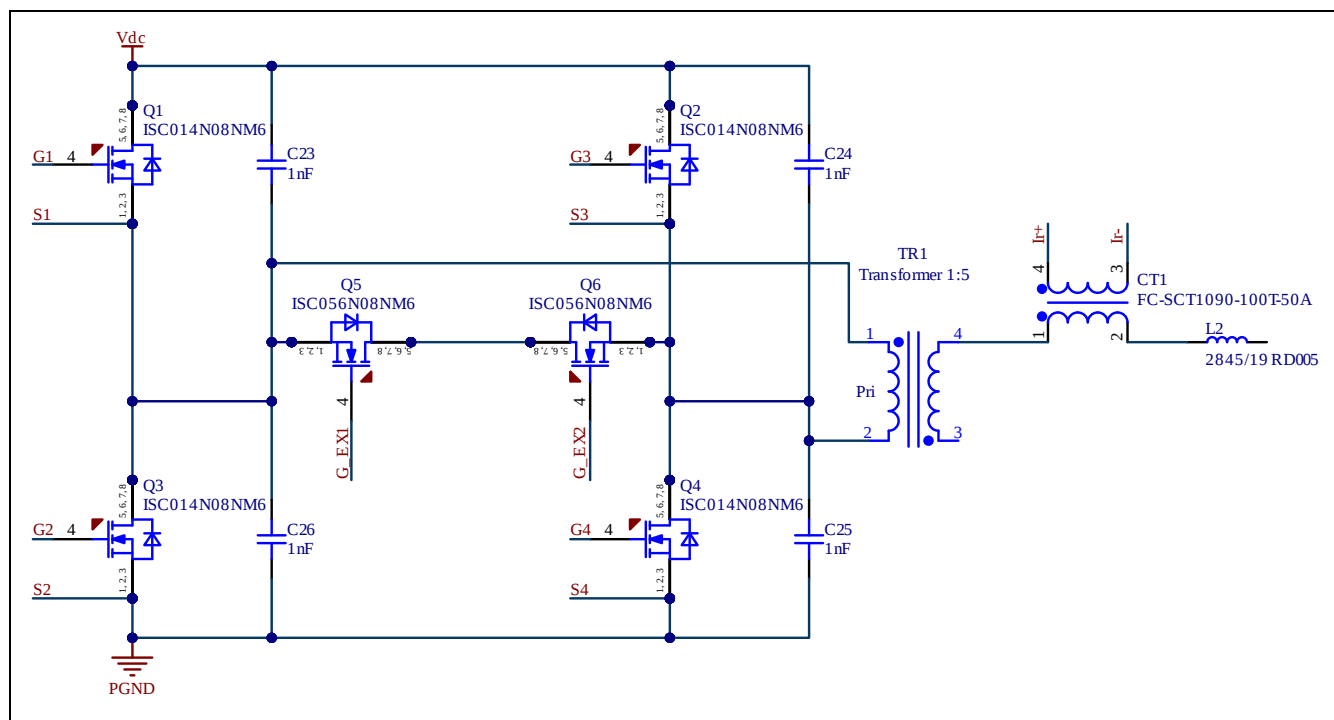

**Figure 8** Primary side and step-up transformer

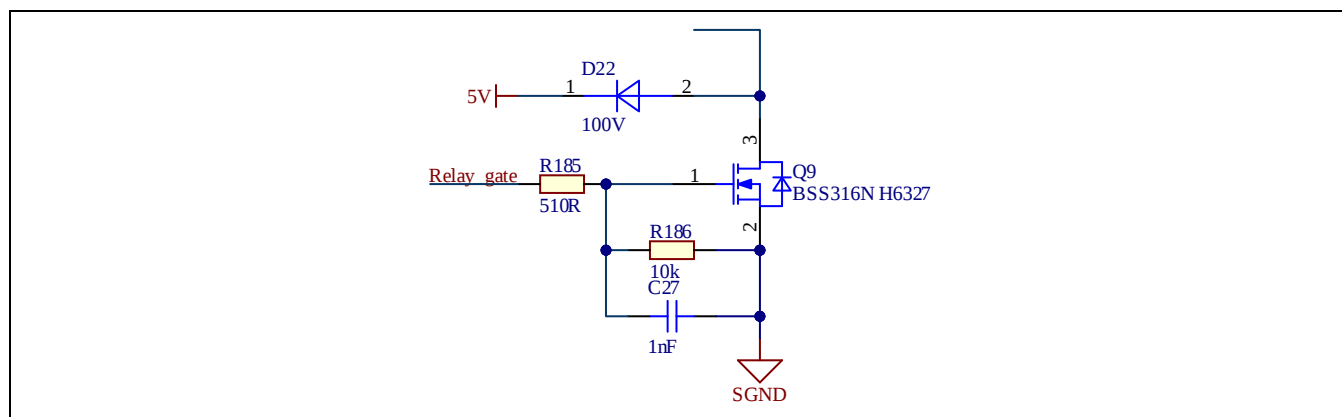

**Figure 9** Relay drive circuit

V 1.1  
2025-09-18



# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter

## 4 Schematics


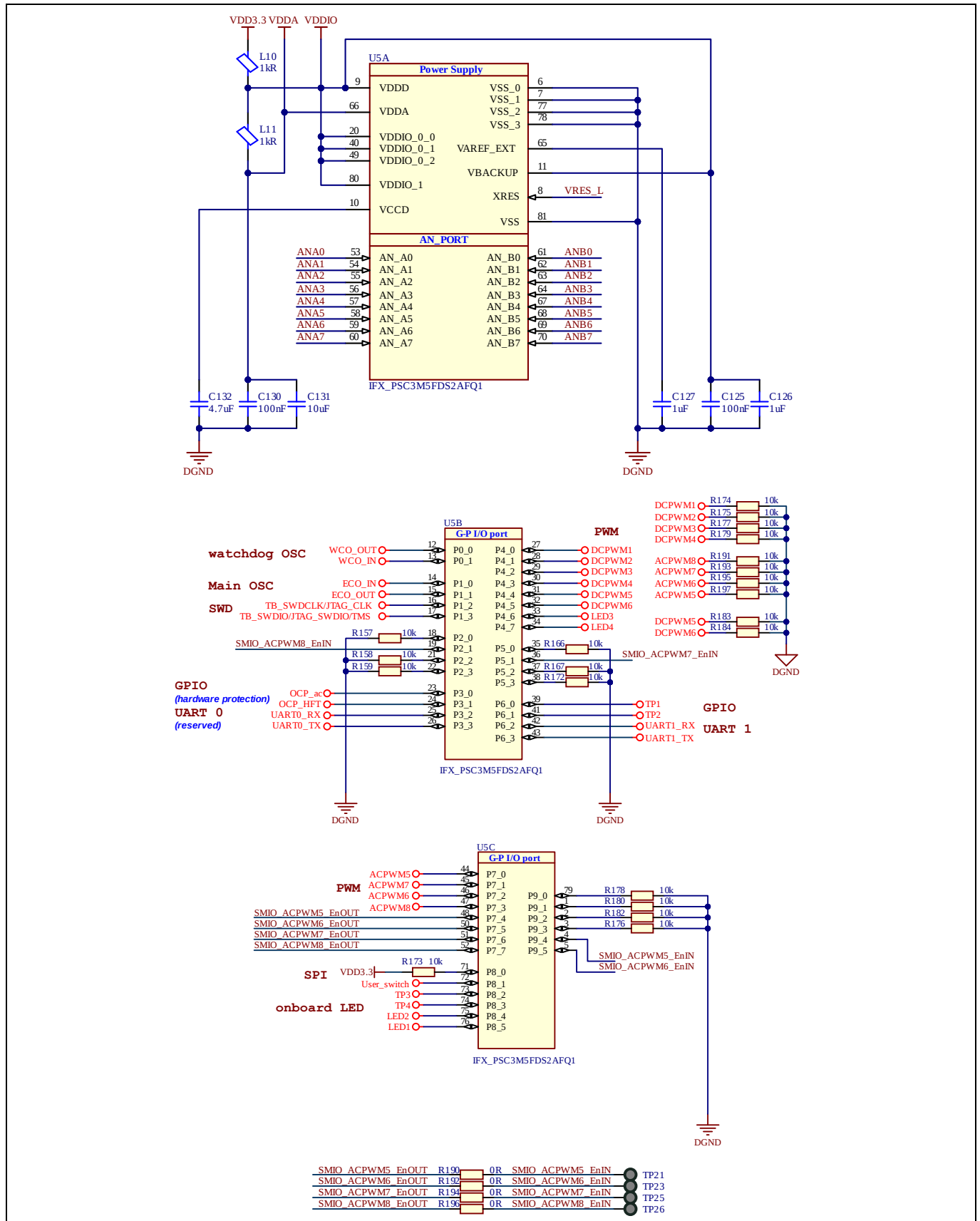


Figure 14 Microcontroller section

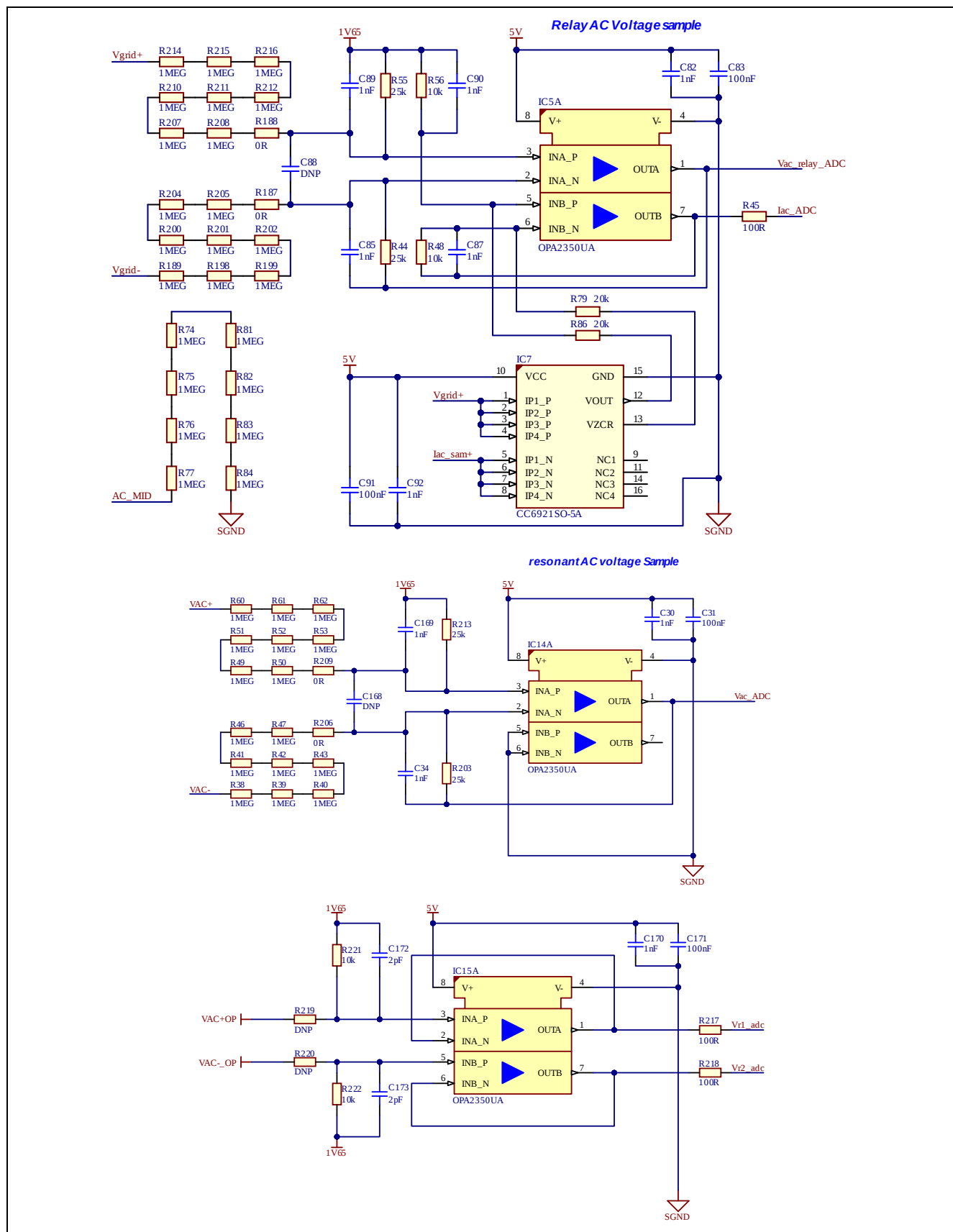


# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter
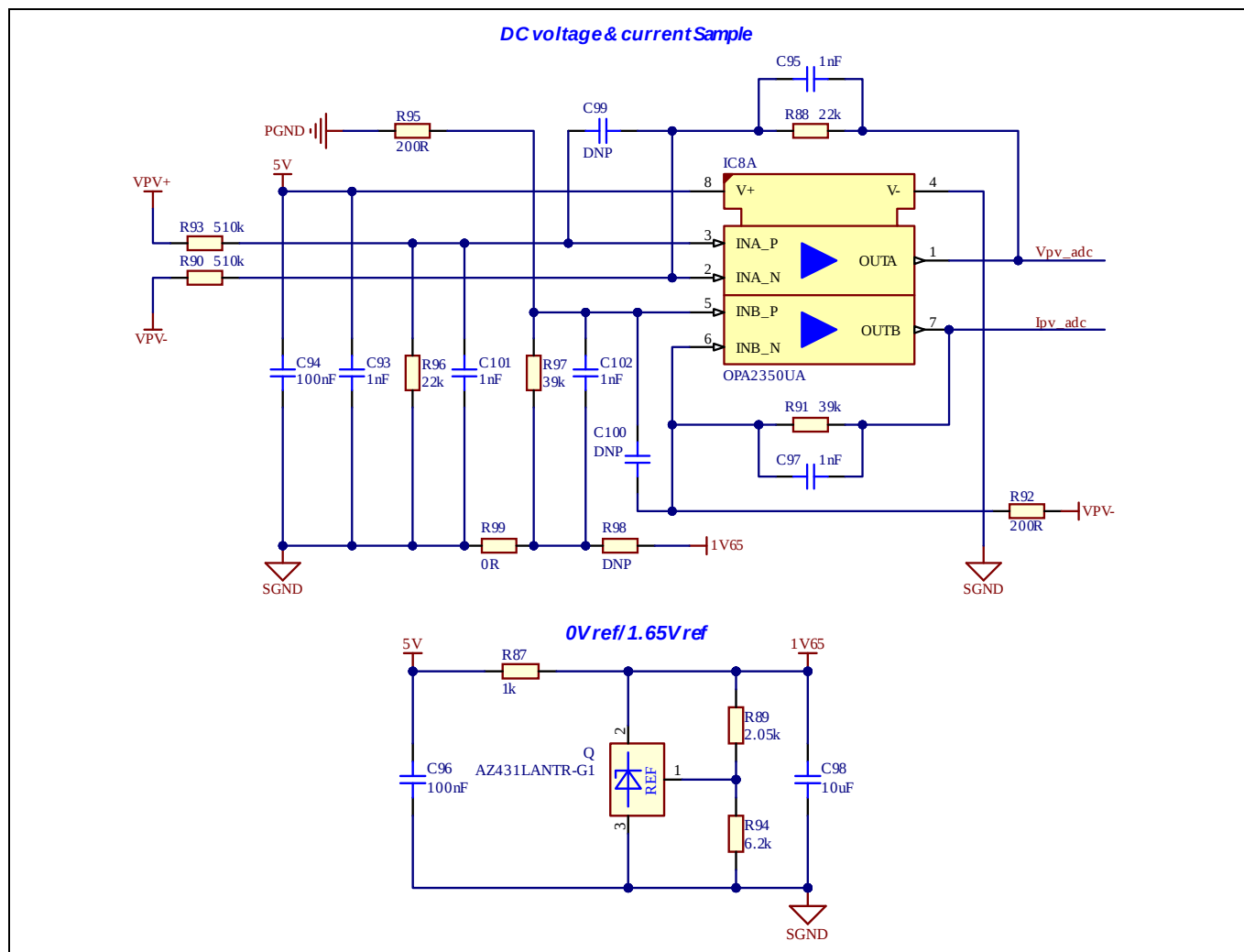
## 4 Schematics

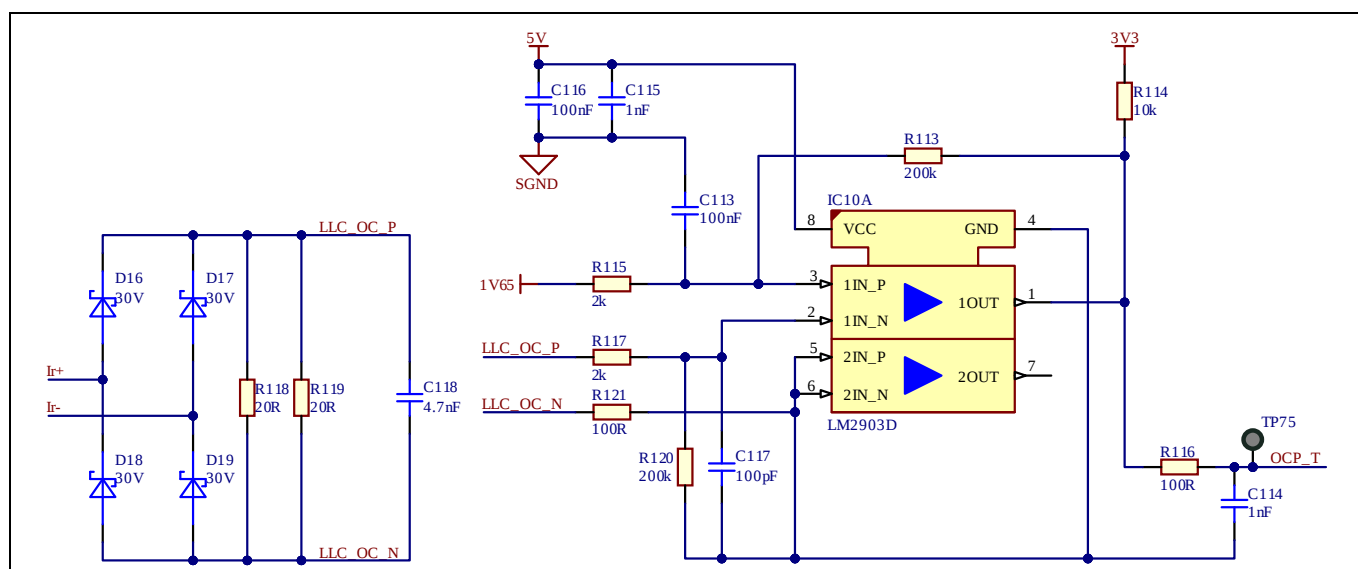


**Figure 19** AC voltage sensing

## 4 Schematics

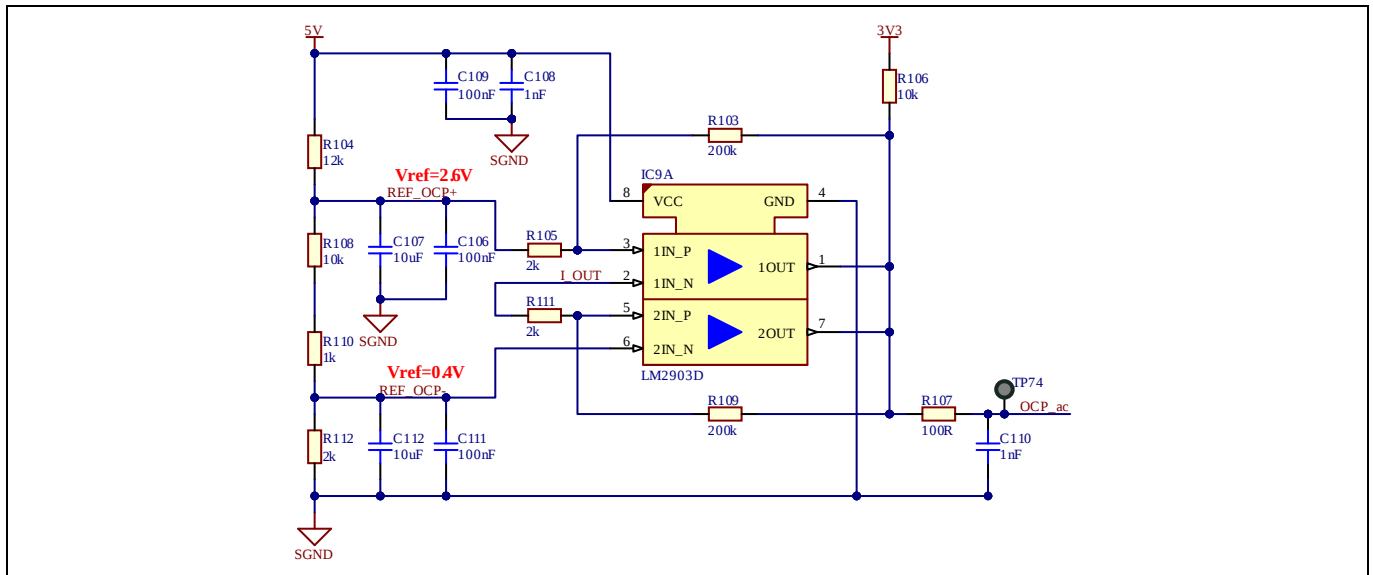


**Figure 20** PV input DC voltage sensing

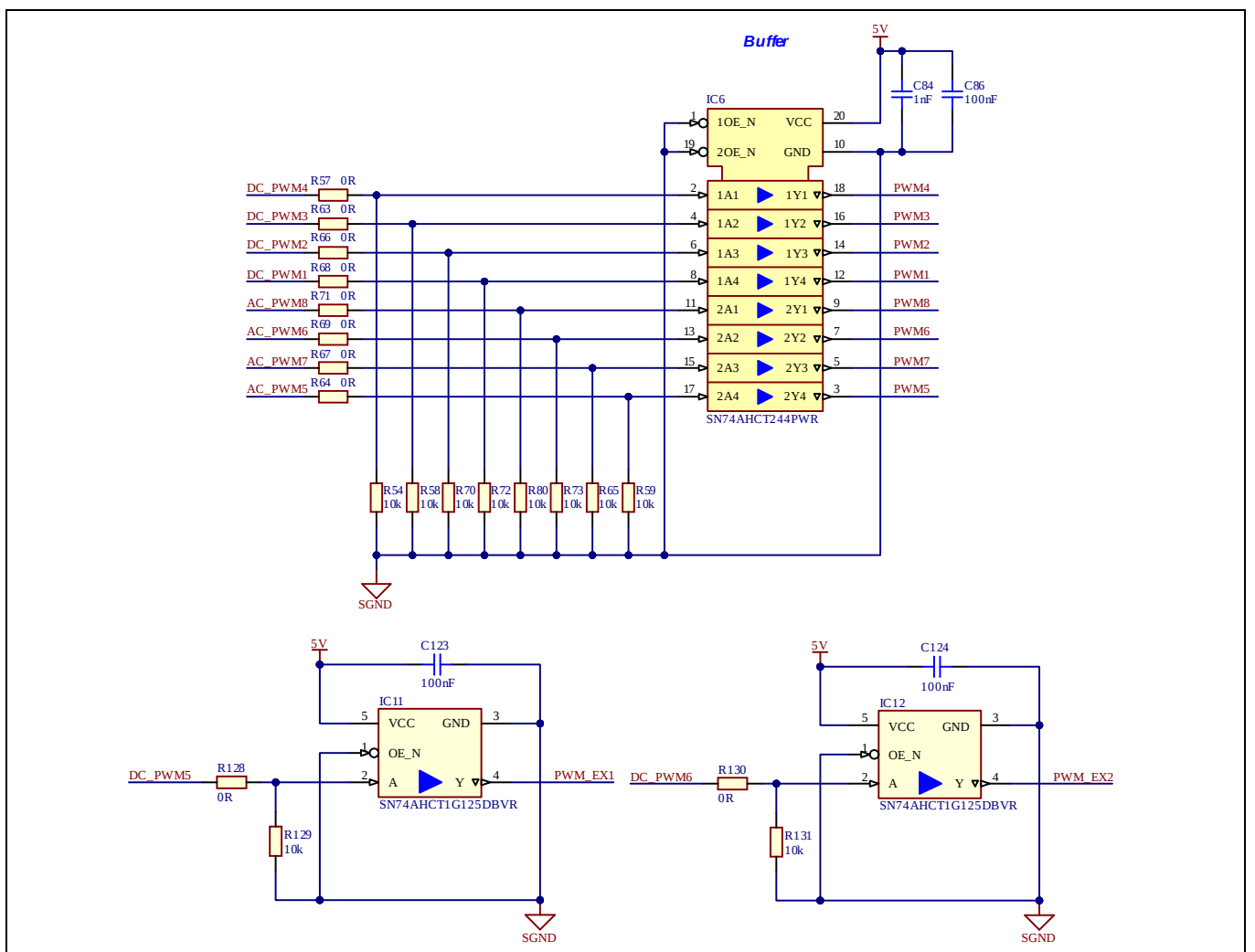


**Figure 21** AC current sensing

## 4 Schematics

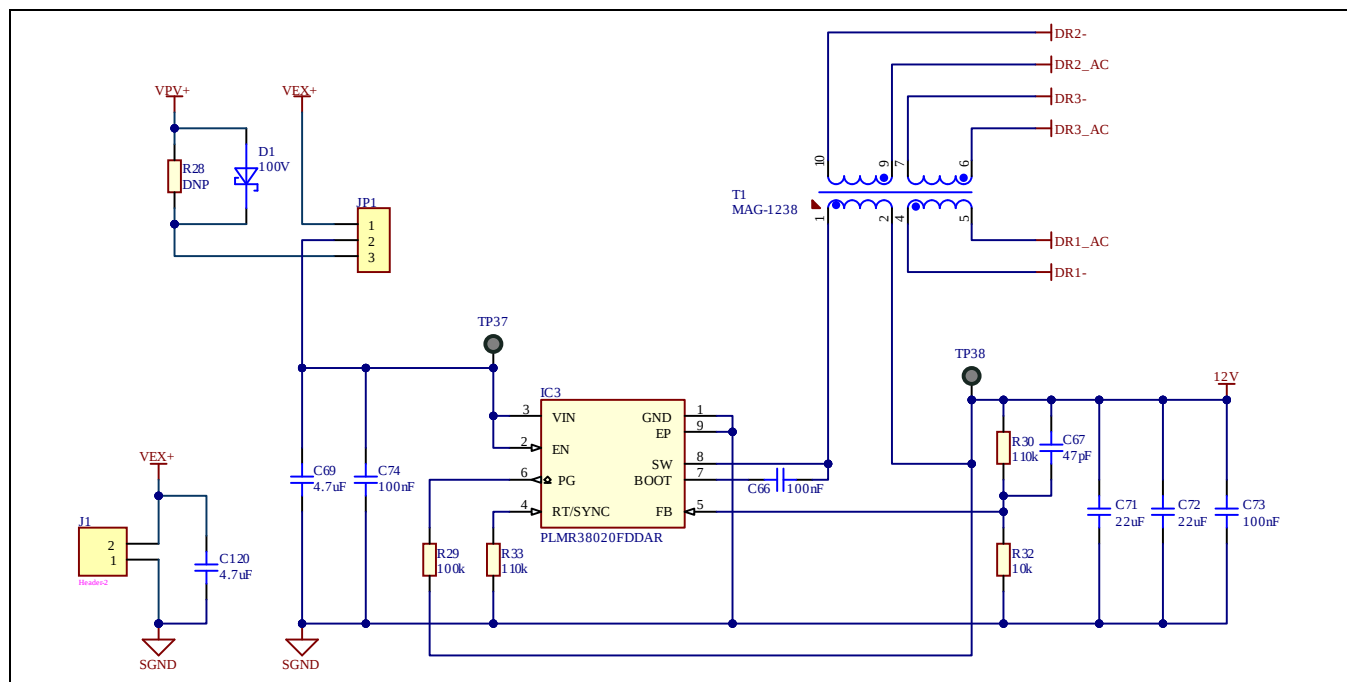


**Figure 22** Overcurrent detection

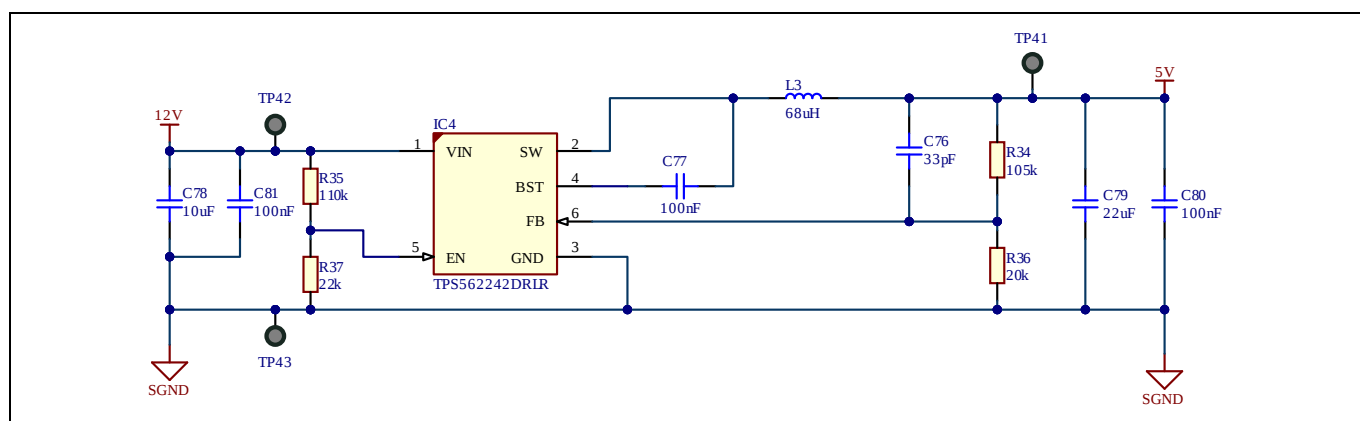


**Figure 23** PWM buffer

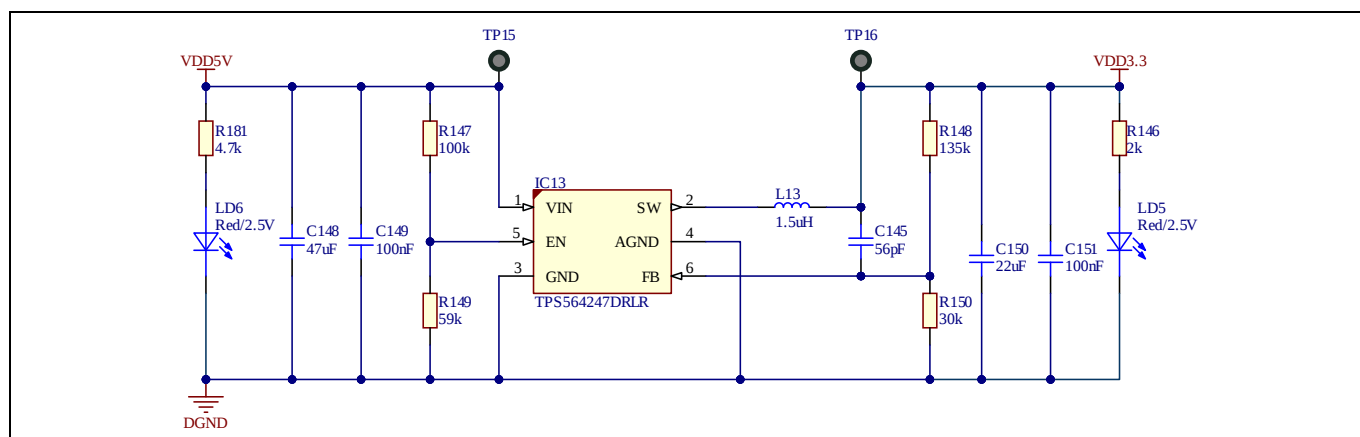
## 4 Schematics



**Figure 24** Auxiliary power supply primary side

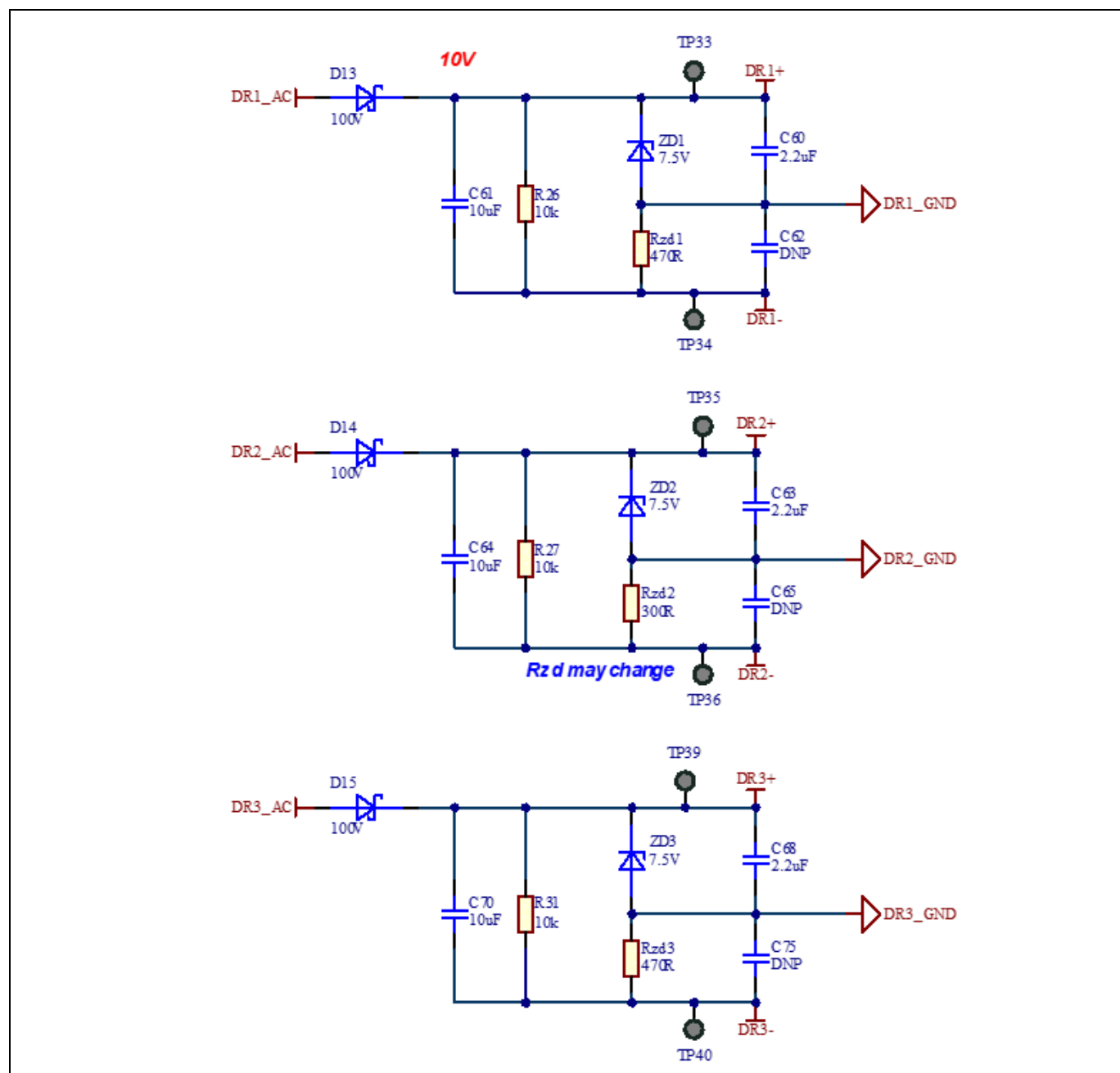


**Figure 25** 12 V to 5 V buck converter




**Figure 26** 5 V to 3.3 V buck converter
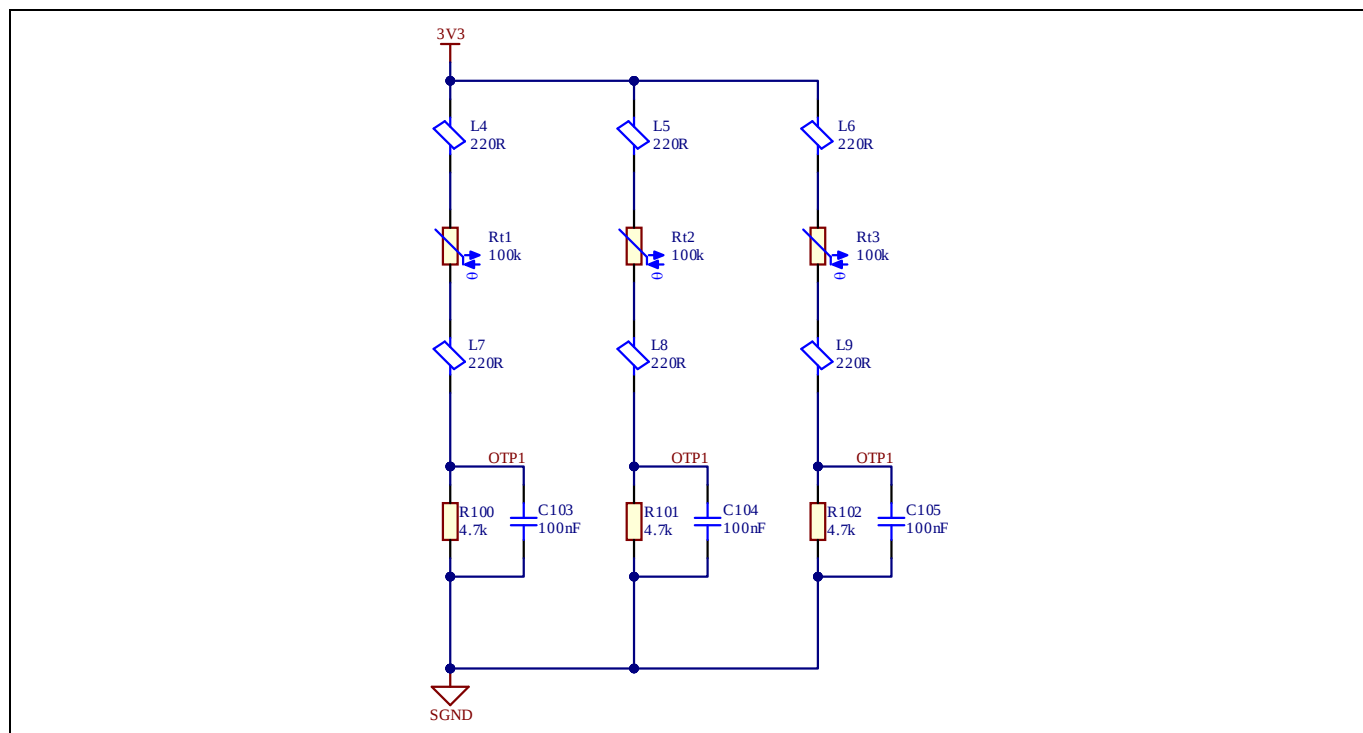
## 4 Schematics

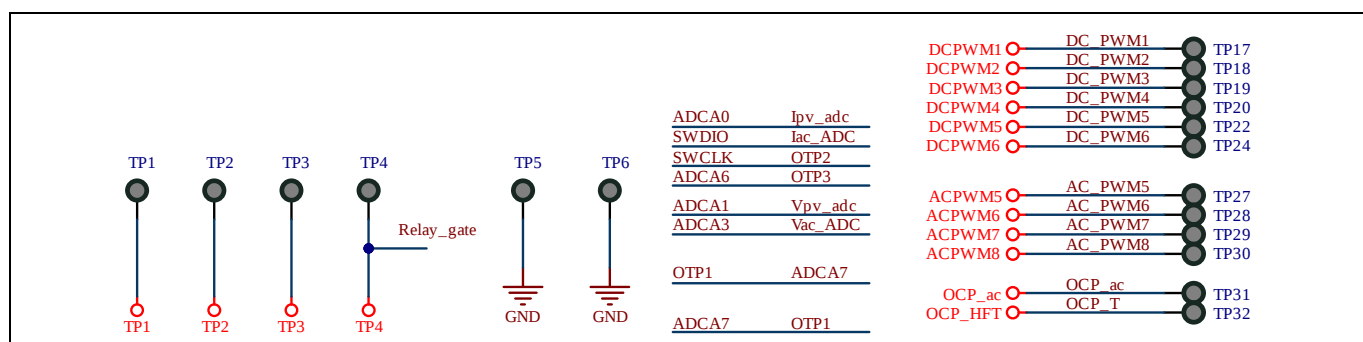


**Figure 27** Isolated power supplies

## 4 Schematics




**Figure 28** Temperature sensing



**Figure 29** Test points

### 5 Hardware functional description


The REF\_500W\_CYCLO family of microinverter reference design boards is based on Infineon's proprietary cycloinverter topology, which is different from existing topologies and does not infringe any associated patents.

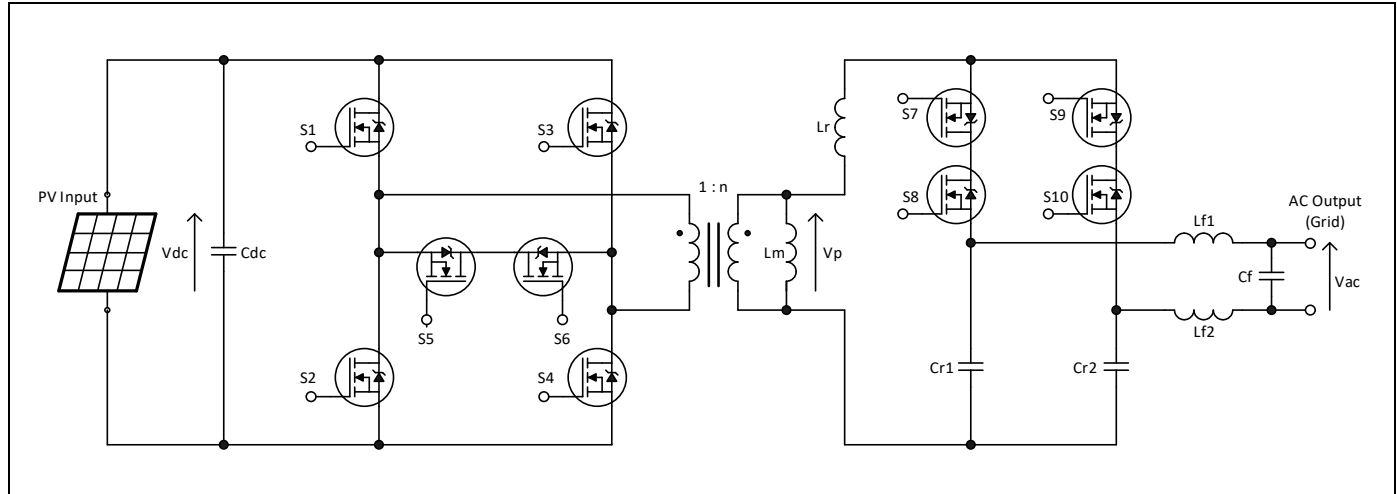

**Figure 30** Infineon cycloinverter topology

This two-stage topology primary DC to AC full-bridge consists of S1, S2, S3, and S4 with an additional bidirectional switch formed by S5 and S6 that drives a step-up transformer.  $L_m$  represents the transformer magnetizing inductance and  $L_k$  represents the leakage inductance. The AC to AC cycloconverter secondary stage consists of a half-bridge formed with bidirectional switches S7-8 and S9-10, which are implemented using common drain bidirectional GaN devices integrated into a single package on the REF\_500W\_CYCLO\_BDSGAN reference design. The transformer secondary is referenced to the mid-point of the two series capacitors Cr1 and Cr2. The output is connected to the AC grid via a filter represented by Lf1, Lf2 and Cf in the above figure. A more complex filter design is used in the REF\_500W\_CYCLO\_BDSGAN design.

The system can be modeled by the following equivalent circuit:

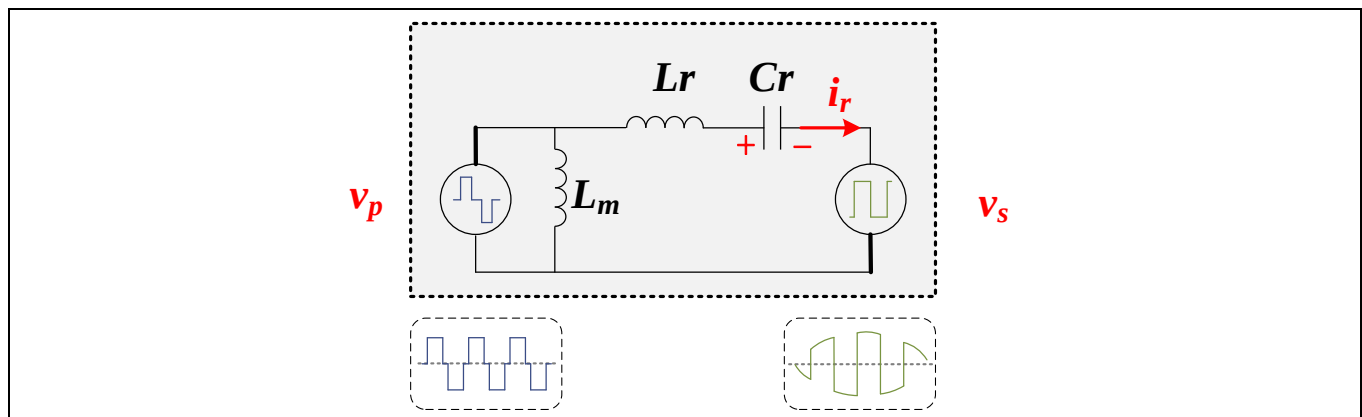

**Figure 31** Cycloinverter circuit model

The secondary winding of the transformer is represented by a modulated AC source with resonant elements  $L_r$  and  $C_r$ , where  $L_r$  is equal to  $L_k$  and  $C_r$  is equal to  $Cr1 + Cr2$ , which are of equal value.


## 5 Hardware functional description

The voltage at the transformer secondary ( $V_p$ ) is determined by the modulation of the primary stage and transformer turns ratio  $n$ .  $V_{dc}$  refers to the input voltage from the connected photovoltaic (PV) panels with DC bus capacitors  $C_{dc}$  required to absorb the low frequency ripple at twice the output grid frequency.


The secondary side of the cycloinverter can be described as a bi-polar voltage-doubler rectifier. Resonant current is transferred from the primary to the secondary with the transformer providing isolation and voltage step up. The positive portion of the current passes through one bidirectional HV switch to charge the corresponding capacitor and the negative portion passes through the other bidirectional switch to charge the other capacitor. The sum of the voltage across both of these capacitors passes to the AC grid through the filter network. The polarities alternate during the positive and negative half cycles of the AC grid.

### 5.1 Control scheme

The DC side consisting of S1 to S6 can provide three different voltage levels at the transformer primary  $v_p'$ ,  $+V_{dc}$ , 0 or  $-V_{dc}$  according to the switch states shown in the following figures:

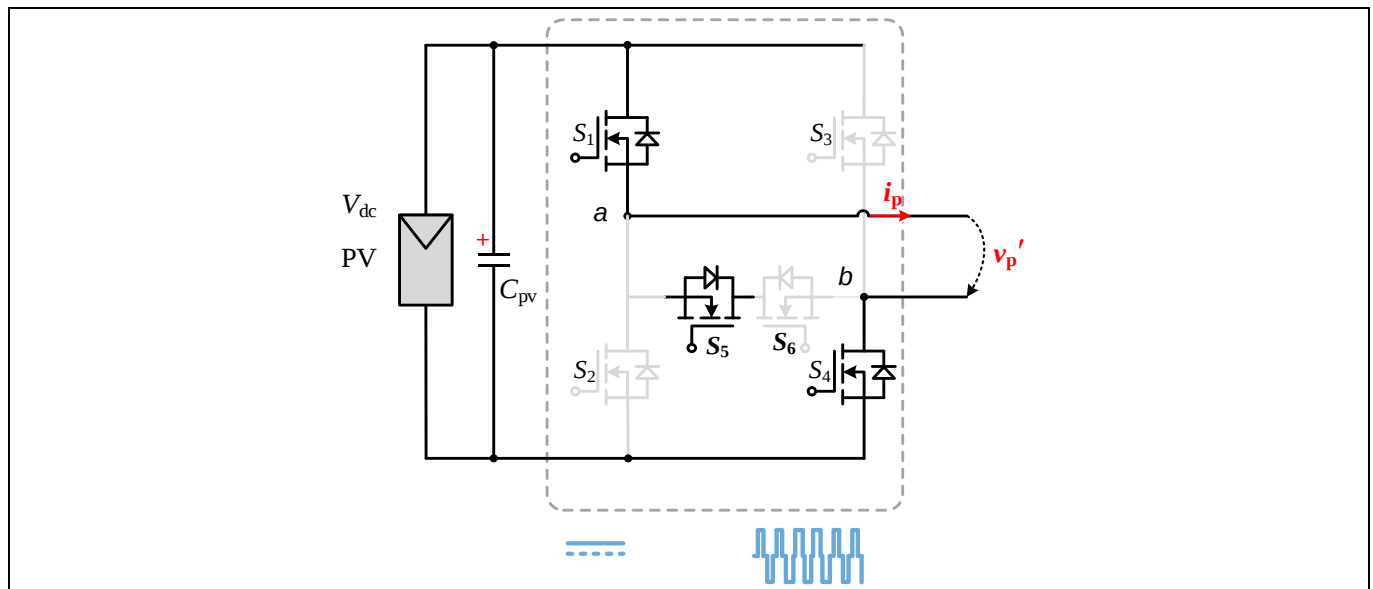


**Figure 32**  $V_p'$  equal to  $+V_{dc}$

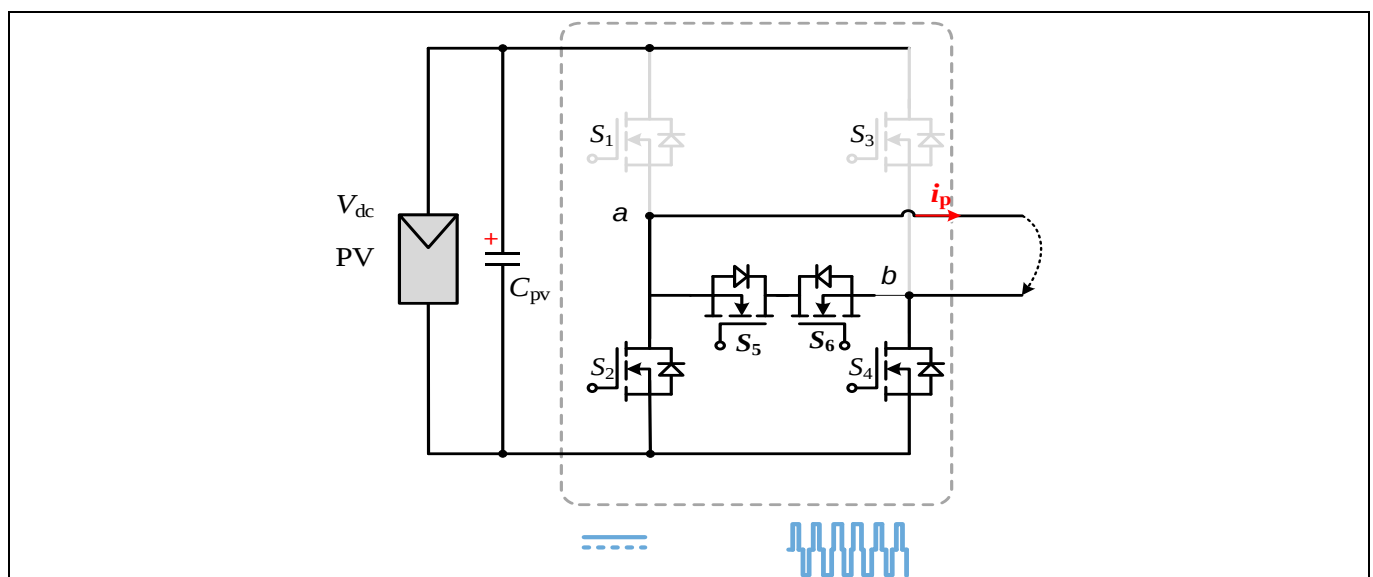

**Figure 33**  $V_p'$  equal to zero

## 5 Hardware functional description

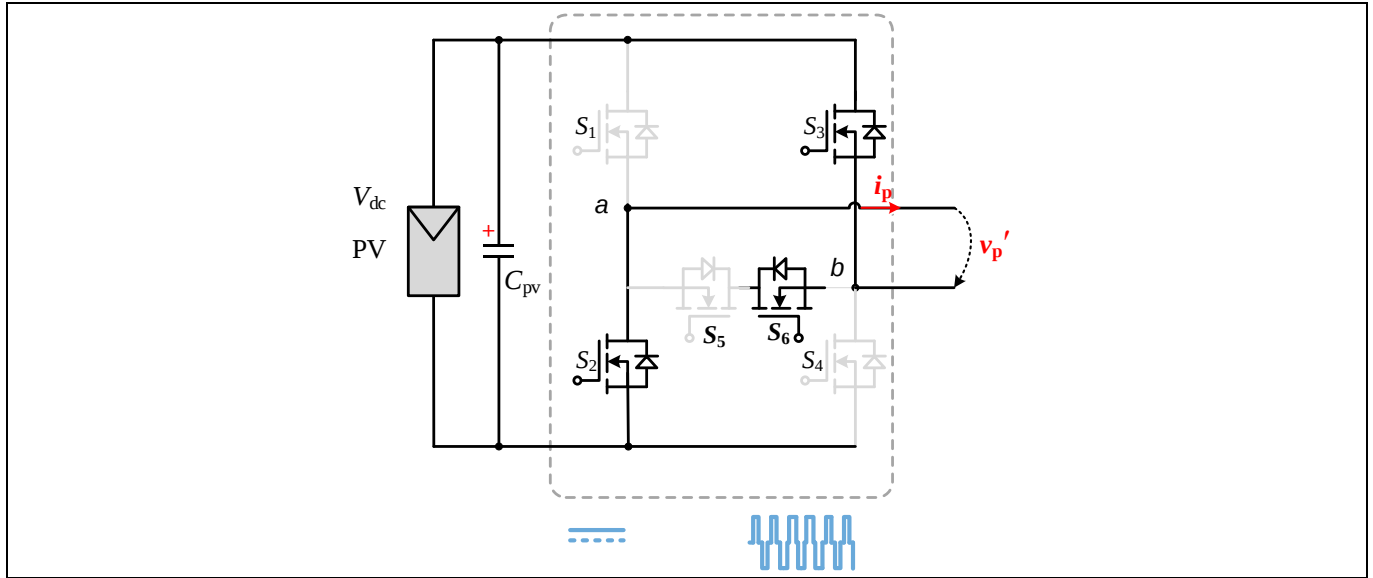

**Figure 34**  $V_p'$  equal to  $-V_{dc}$

The voltage  $V_p$  indicated in Figure 30 represents  $V_p'$  stepped up through the transformer with turns ratio  $n$ , therefore it can be equal to;  $+nV_{dc}$ , 0 or  $-nV_{dc}$ . The voltage  $V_s$  represents the secondary side resonant tank, which may be equal to  $+|V_g|/2$  or  $-|V_g|/2$  where  $V_g$  is the instantaneous voltage at the AC grid connection.

The control scheme used in the REF\_500W\_CYCLO\_BDSGAN design includes three adjustable parameters, which are as follows:


- $f_s$ : the switching frequency, for adjusting the impedance point in the resonant tank
- $D_1$ : the inner phase shift ratio
- $D_\delta$ : the outer phase shift ratio

The value of  $D_2$  is calculated with the formula:

$$D_2 = D_\delta + \frac{D_1}{2}$$

**Equation 2**

These signals are illustrated as follows:

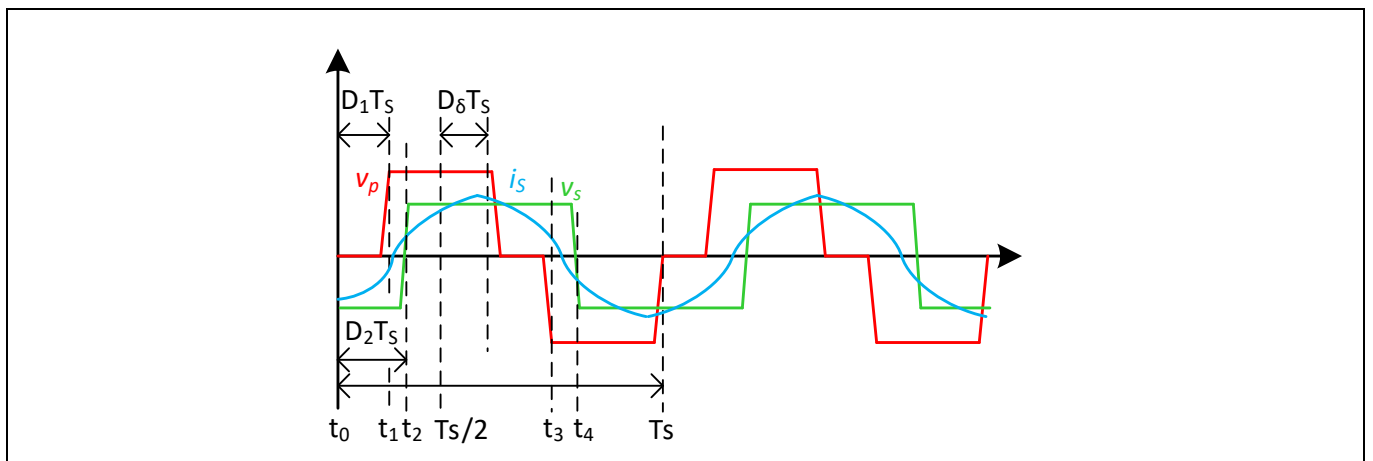

**Figure 35** Operating waveforms

## 5 Hardware functional description

The time intervals  $t_1$ ,  $t_2$ , and  $t_3$  are calculated as:


$$\begin{cases} t_1 = D_1 T_s + \frac{(0.5 - D_1)}{2} T_s = \frac{D_1}{2} T_s + \frac{0.5}{2} T_s \\ t_2 = D_2 T_s + \frac{0.5}{2} T_s \\ t_2 = t_1 + D_\delta T_s \end{cases} \Rightarrow D_2 = D_\delta + \frac{D_1}{2}$$

**Equation 3**


## 5 Hardware functional description

### 5.1.1 Switching states


The following six switching states are used in the PWM scheme of the cycloinverter during the positive AC grid half-cycle. The switching of S7+S8 and S9+S10 is swapped with S7+S8 on during the negative half-cycle:

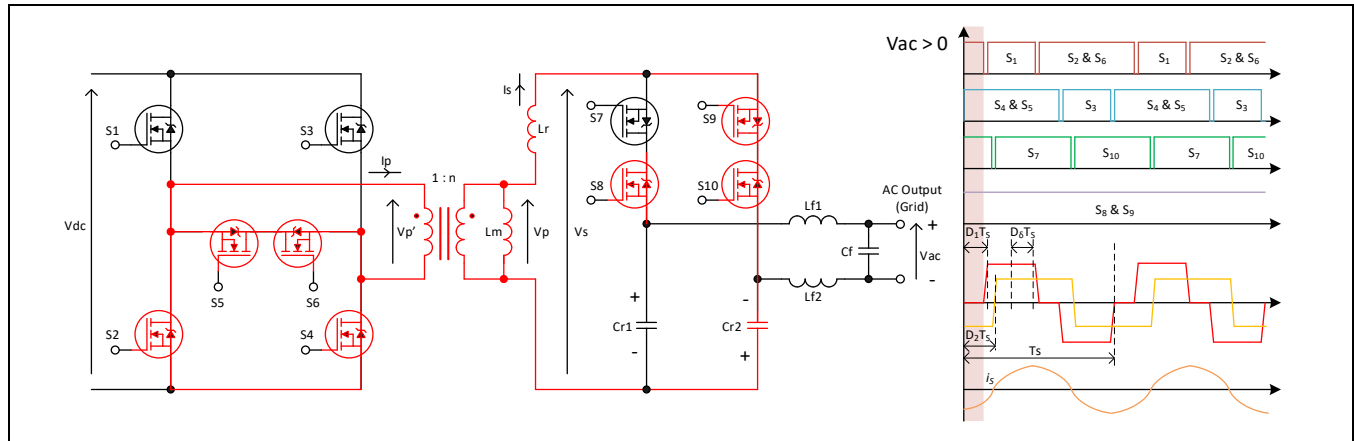

**Figure 36 State 1**

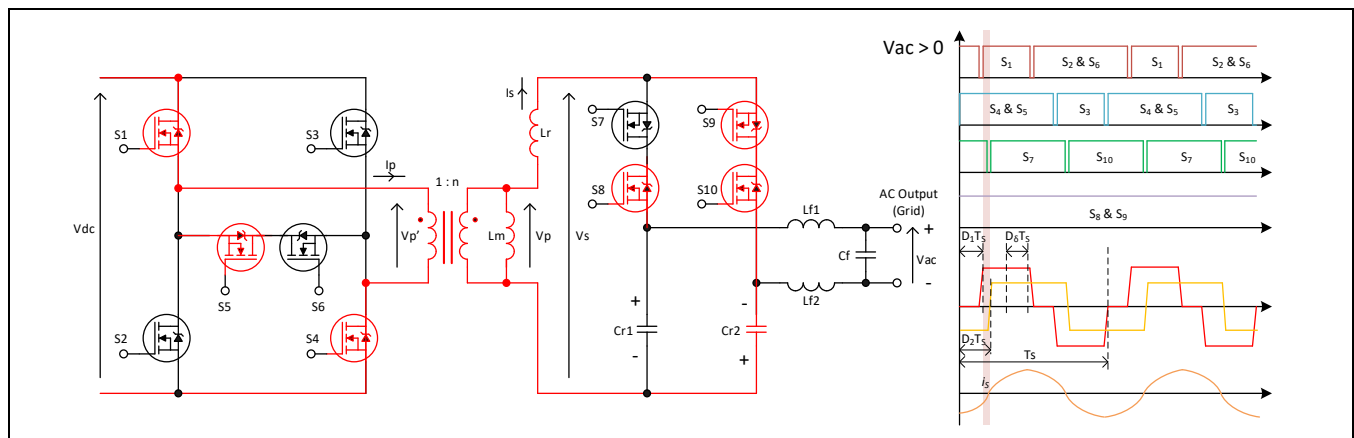


**Figure 37 State 2**

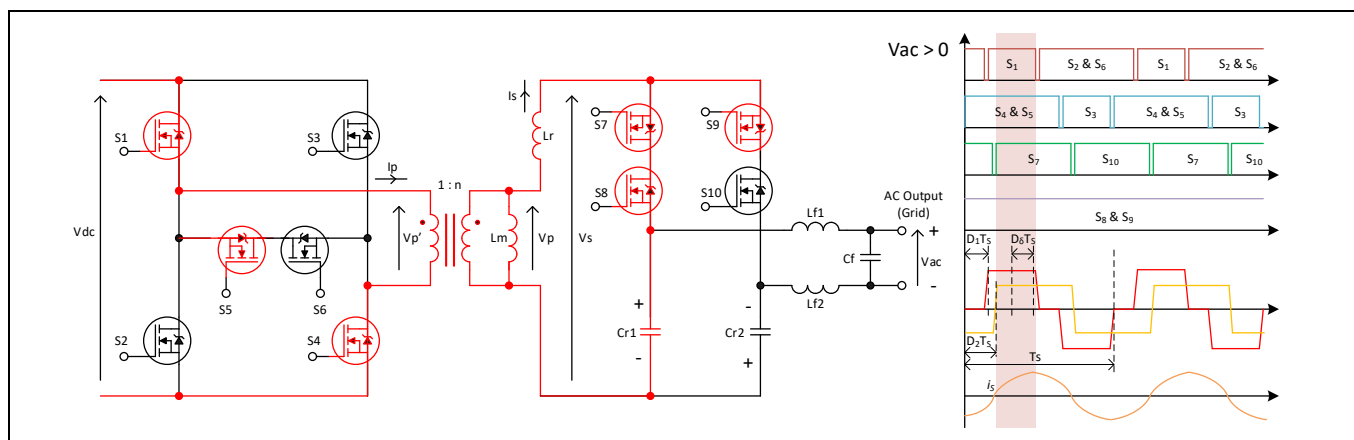


**Figure 38 State 3**

# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter


## 5 Hardware functional description

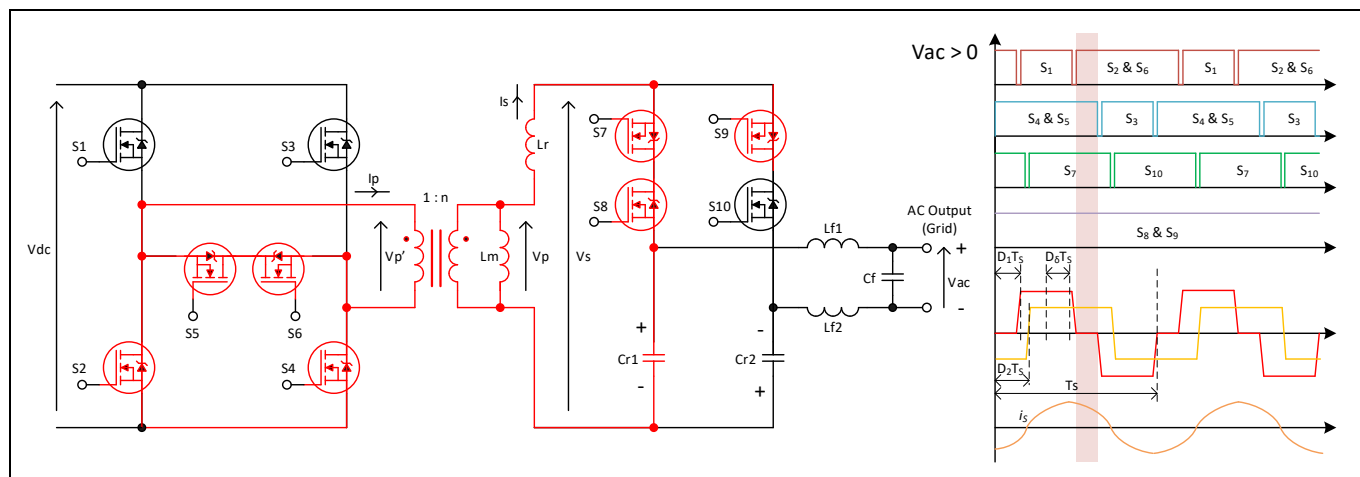

**Figure 39** State 4

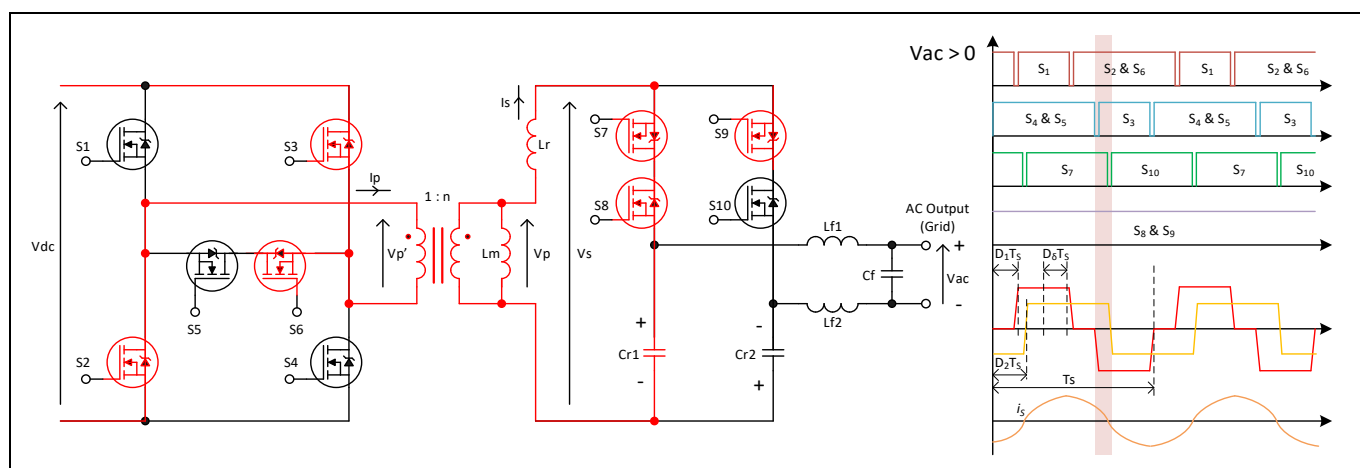

**Figure 40** State 5

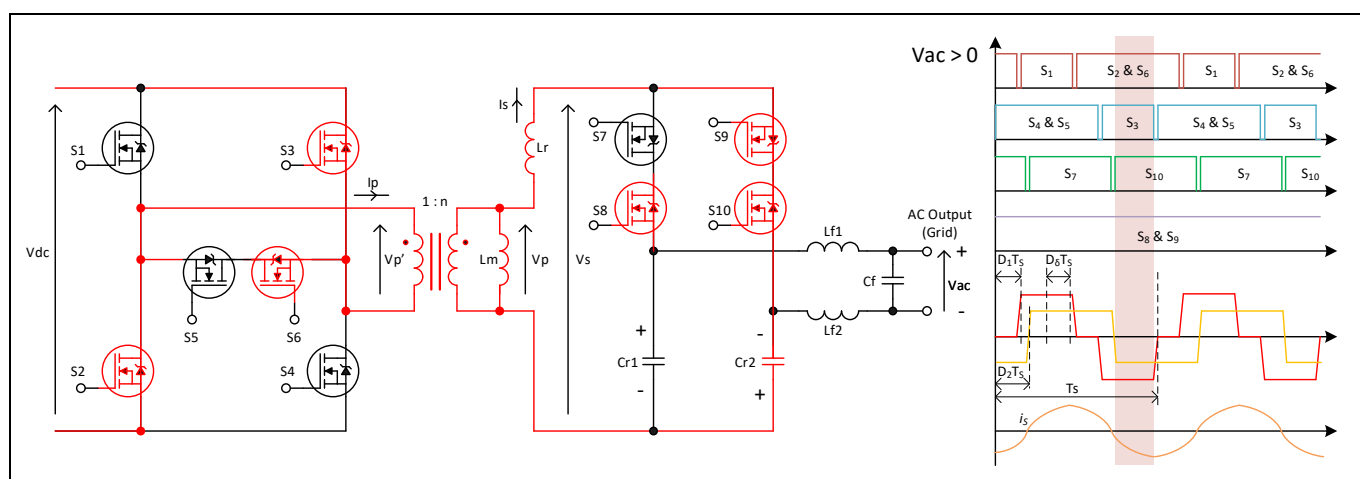

**Figure 41** State 6

## 5 Hardware functional description

The states are summarized in the following table:

**Table 7 Switching state summary Vac positive half-cycle (gate drives ON/OFF)**


| State | S1  | S2  | S3  | S4  | S5  | S6  | S7  | S8 | S9 | S10 | Vp   | Vs    | Vx       |
|-------|-----|-----|-----|-----|-----|-----|-----|----|----|-----|------|-------|----------|
| 1     | OFF | ON  | OFF | ON  | ON  | ON  | OFF | ON | ON | ON  | 0    | -VCr2 | - Vac /2 |
| 2     | ON  | OFF | OFF | ON  | ON  | OFF | OFF | ON | ON | ON  | Vdc  | -VCr2 | - Vac /2 |
| 3     | ON  | OFF | OFF | ON  | ON  | OFF | ON  | ON | ON | OFF | Vdc  | +VCr1 | + Vac /2 |
| 4     | OFF | ON  | OFF | ON  | ON  | ON  | ON  | ON | ON | OFF | 0    | +VCr1 | + Vac /2 |
| 5     | OFF | ON  | ON  | OFF | OFF | ON  | ON  | ON | ON | OFF | -Vdc | +VCr1 | + Vac /2 |
| 6     | OFF | ON  | ON  | OFF | OFF | ON  | OFF | ON | ON | ON  | -Vdc | -VCr2 | - Vac /2 |

*Note:* In the PWM scheme used here, S2 and S6 are always on and off at the same time as are S4 and S5.

S8 and S9 are on continuously during the AC grid positive half cycle while S7 and S10 are switching complementary to each other. During the negative grid half-cycle S7 and S10 are on continuously while S8 and S9 are switching.

The AC output voltage before the output filter is equal to the sum of the two capacitor voltages Vcr1 and Vcr2.


The operating conditions during different switching states are outlined in the following figures, which describe the energy transfer to the resonant capacitors C1 and C2, which supply the output to the grid. In a non-active state when all of the switches are off, the output voltage is equal to the sum of the voltages across C1 and C2 as follows:

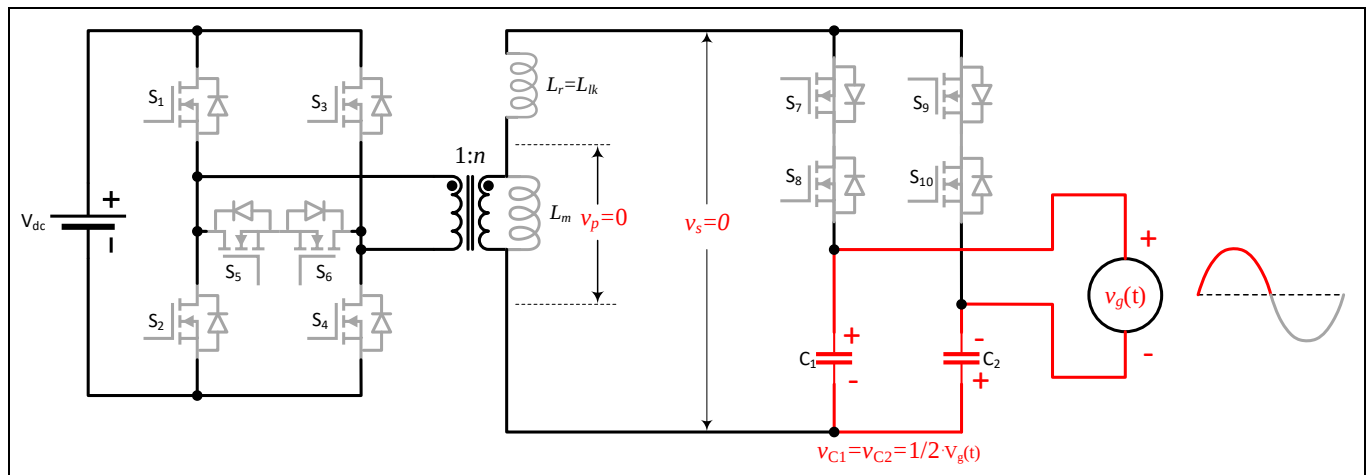


**Figure 42 All switches OFF**

## 5 Hardware functional description

The following diagrams describe the energy transfer taking place in the previously described switching states. The equations shown in each diagram describe the relationships between the voltages and currents in the capacitive and inductive elements.

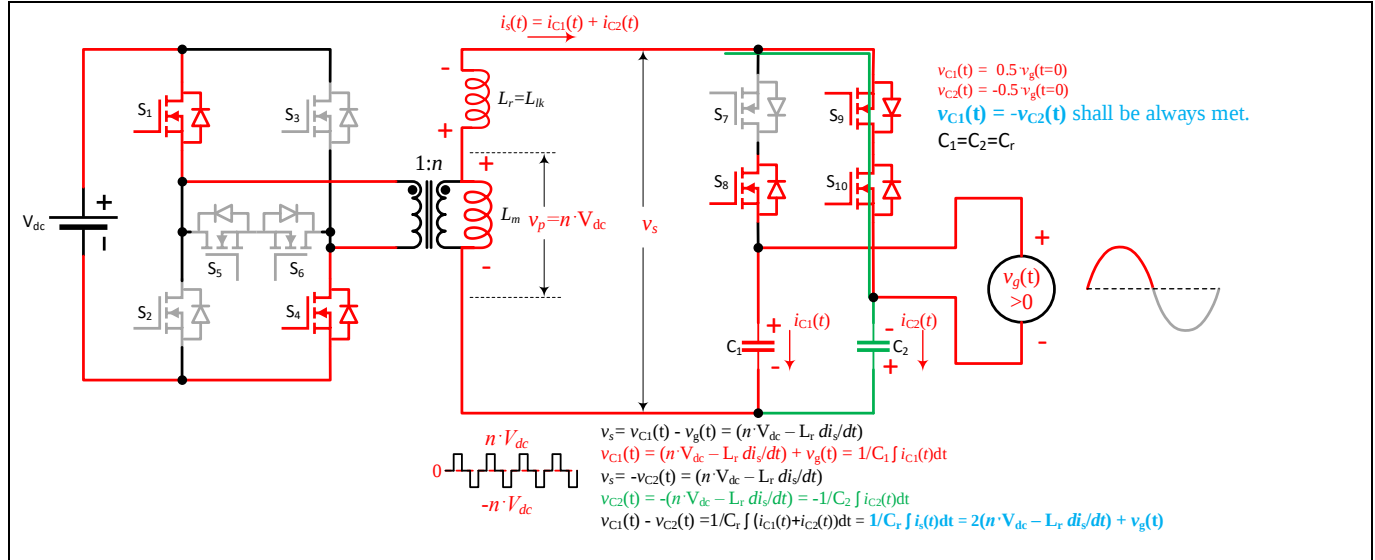


**Figure 43 State 2**

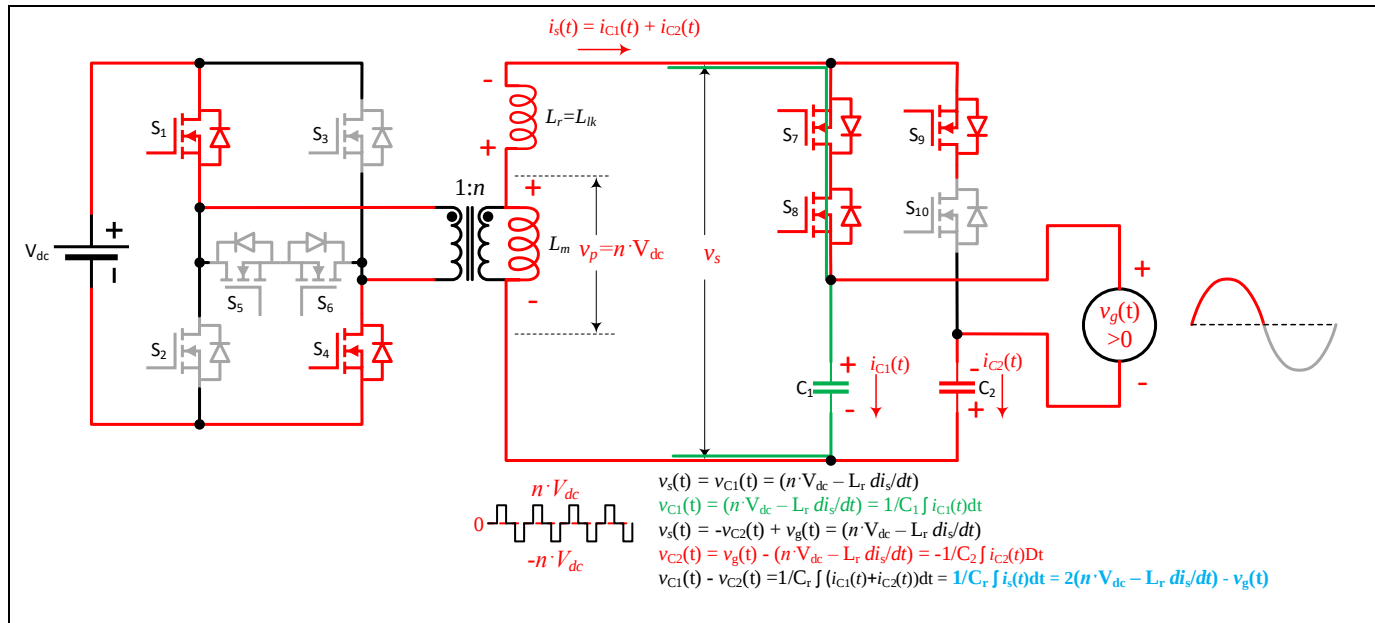


**Figure 44 State 3**

## 5 Hardware functional description

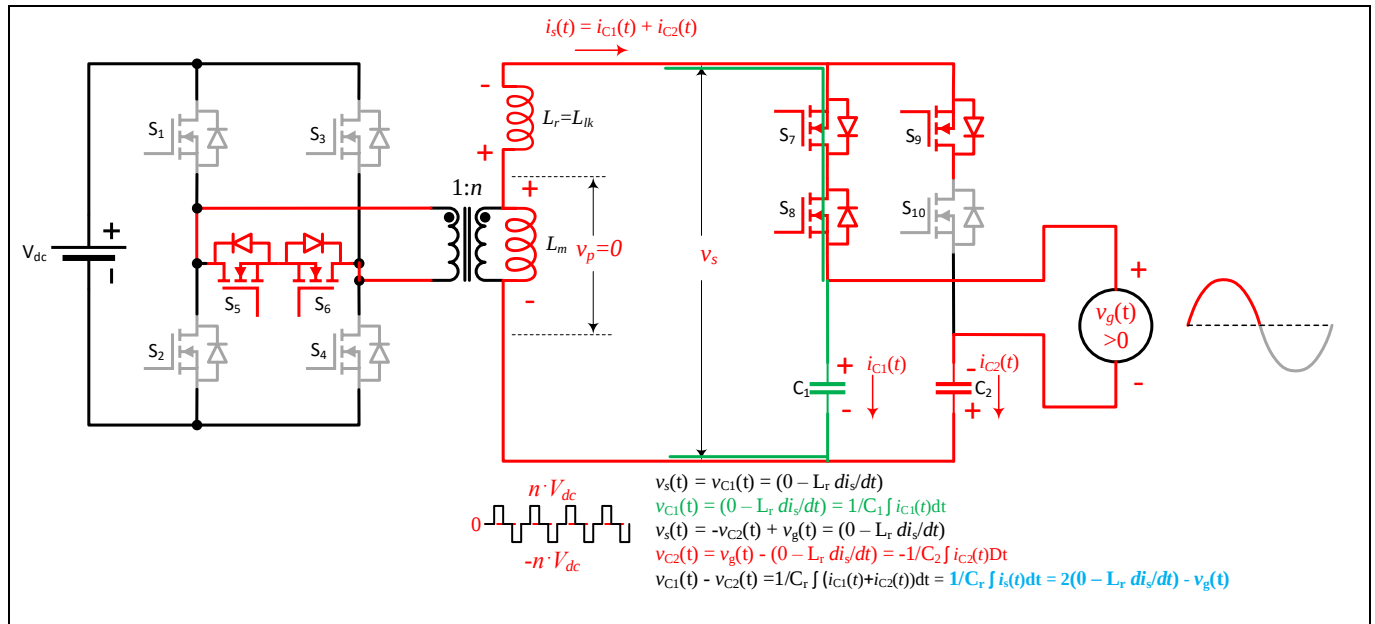

**Figure 45 State 4**

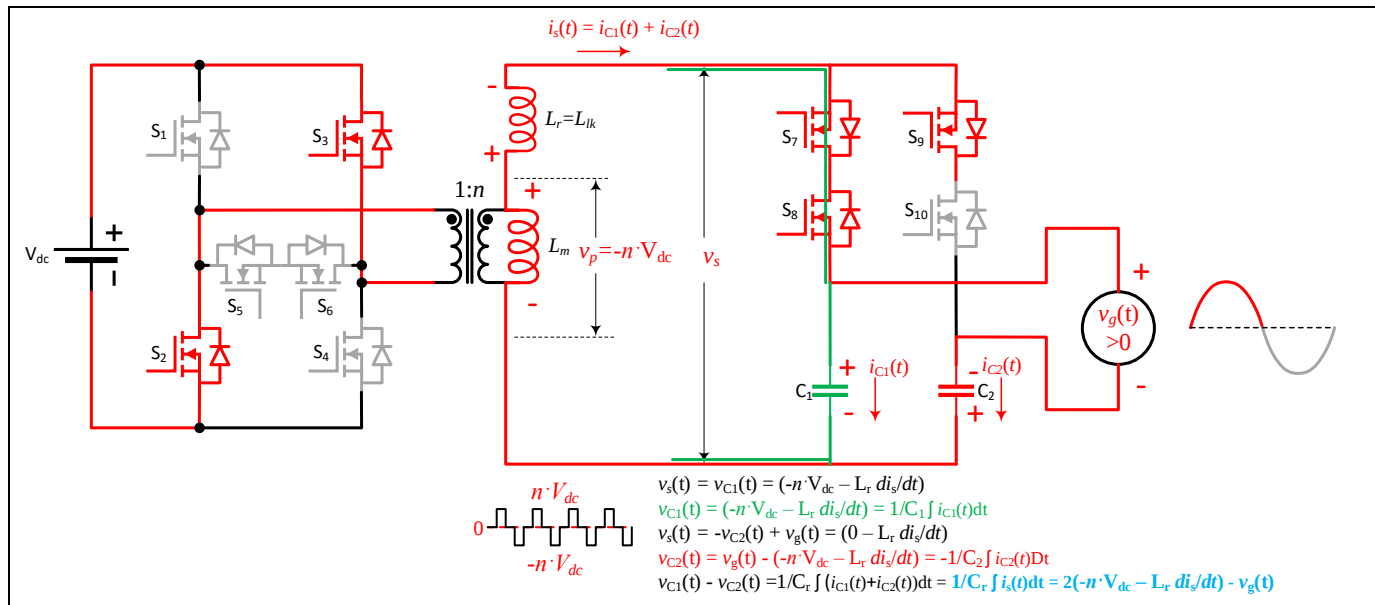

**Figure 46 State 5**

## 5 Hardware functional description

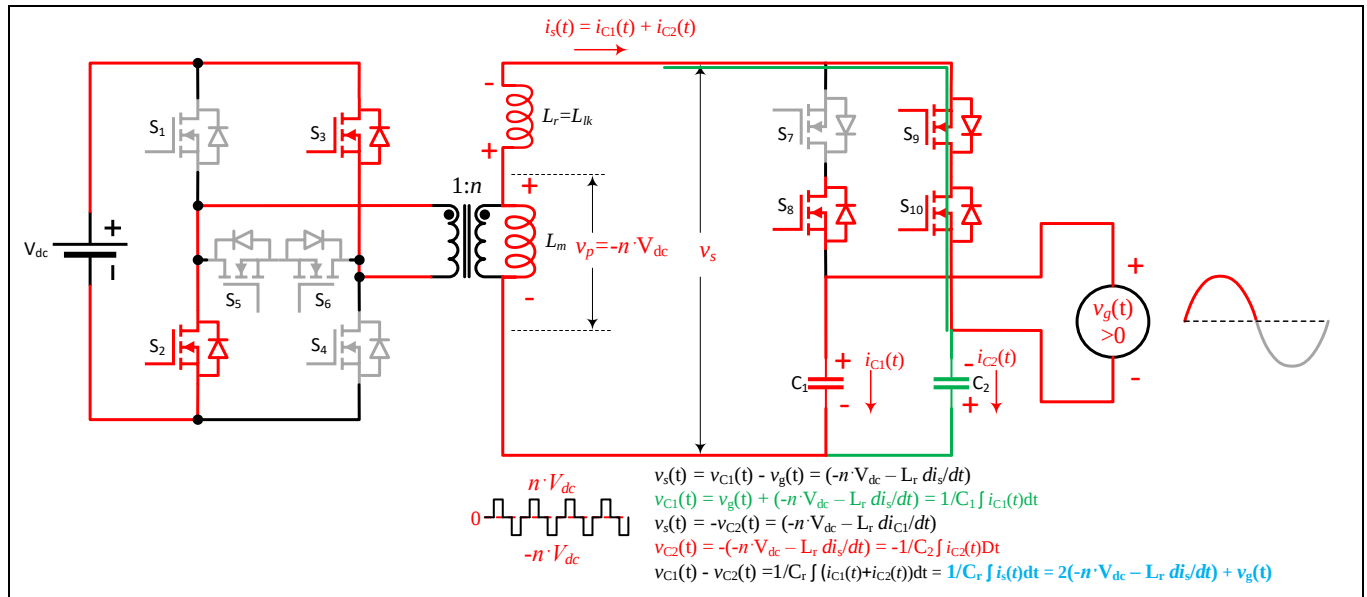


Figure 47 State 6

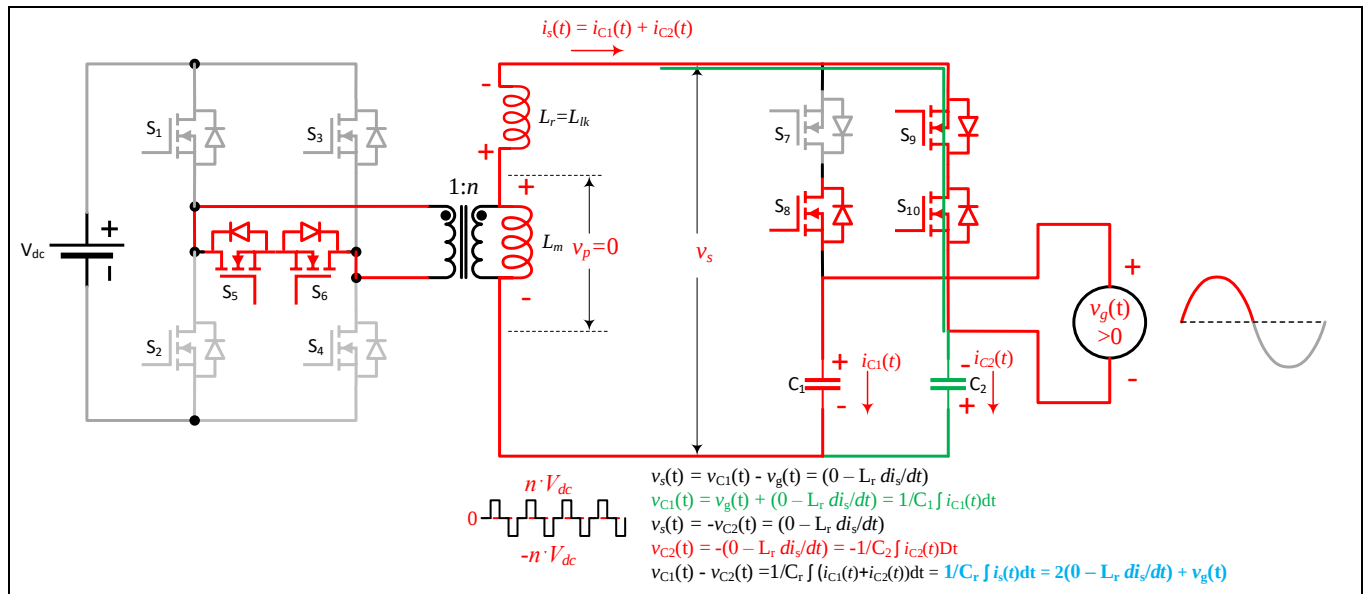



Figure 48 State 7

## 5 Hardware functional description

### 5.1.2 Soft switching (ZVS)

Zero Voltage Switching<sup>1</sup> (ZVS) is achieved to enable high efficiency in this converter. During state 1 the resonant current  $i_s$  is below zero and the  $V_{DS}$  of S1 is equal to  $V_{dc}$ . Commutation occurs during the dead-time between states 1 and 2 when the  $V_{DS}$  of S1 is discharged by the primary circulating current  $i_p$  until body diode conduction occurs, which enables ZVS of S1 to be achieved. In state 2 the resonant current transitions from negative to positive. When S10 switches off  $i_s$  charges the drain-source capacitance ( $C_{OSS}$ ) of S10 also discharging the  $C_{OSS}$  of S7 causing the  $V_{DS}$  of S10 to rise and that of S7 to fall to enable ZVS switching once the body diode is conducting. In state 3,  $i_s$  charges the  $C_{OSS}$  of S1 and discharges the  $C_{OSS}$  of S2 and S6 until the body diodes of these two devices conduct and ZVS can be realized. ZVS switching is achieved for all switches in the different switching states provided there is sufficient load to produce enough resonant current. This is not the case at light load, which is why a burst mode function has been implemented to maintain high efficiency.

The ZVS constraint can be further explained by means of a phasor diagram:

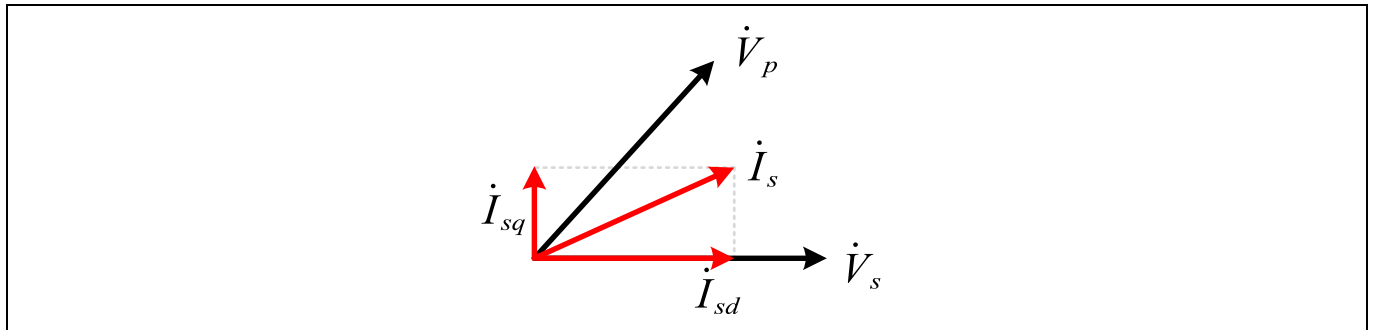

**Figure 49 Phasor diagram of the resonant voltage and current fundamental components**

The diagram shows the fundamental components of the primary voltage  $V_p'$  and secondary voltage  $V_s$ , which is the phase reference located on the real axis. The magnitude and phase angle of  $V_p'$  change with the change in inner and outer phase angles  $D_1$  and  $D_\delta$ . The resonant current  $I_s$  contains real and reactive components, which have been separated onto the real and imaginary axes. To achieve ZVS operation, a sufficiently large component of lagging reactive current  $I_{sq}$  is necessary, however this also increases the overall amplitude of  $I_s$ .

When  $I_s$  lags behind the  $V_p'$  by an angle of  $\varphi_1/2$ , the primary side lagging switches can achieve ZVS. When  $I_s$  leads  $V_s$ , the secondary side switches can realize soft switching. Therefore, when the current phase angle is in the middle of the original and secondary side voltage vectors, the soft switching of all switches can be realized, that is:

$$0 \leq \angle I_s \leq \varphi_\delta - \frac{\varphi_1}{2}$$

**Equation 4**

Where,  $\varphi_1 = 2\pi D_1$  and  $\varphi_\delta = 2\pi D_\delta$

<sup>1</sup> Also referred to as h switching.

## 5 Hardware functional description

### 5.1.3 Frequency domain analysis

The resonant tank voltages according to Figure 30 can be expressed by Fourier transform for the harmonic components  $k$  are as:

$$v_p(t) = \sum_{k=1,3,\dots}^N \frac{4V_p}{k\pi} \cos\left(k \frac{\varphi_1}{2}\right) \sin(k\omega_s t + k\varphi_\delta)$$

$$v_s(t) = \sum_{k=1,3,\dots}^N \frac{2|v_g|}{k\pi} \sin(k\omega_s t) = \sum_{k=1,3,\dots}^N \frac{4mV_p}{k\pi} \sin(k\omega_s t)$$

$$m = \frac{|v_g|/2}{V_p}, \varphi_1 = 2\pi D_1, \varphi_\delta = 2\pi D_\delta, \omega_s = 2\pi f_s$$


**Equation 5**

Where  $\omega_s = 2\pi f_s$  is the switching frequency,  $v_g$  is the instantaneous grid voltage, and  $V_p = nV_{dc}$ , 4 therefore:

$$m = \frac{|v_g|}{2nV_{dc}}$$

**Equation 6**

For the period of the AC grid half cycle where  $m > 1$ , the converter is said to be working in *boost* mode and when  $m \leq 1$ , it is said to be working in *buck* mode. The transformer turns ratio  $n$  therefore determines how much of each line half cycle is spent operating in each mode, which strongly influences the overall converter efficiency.

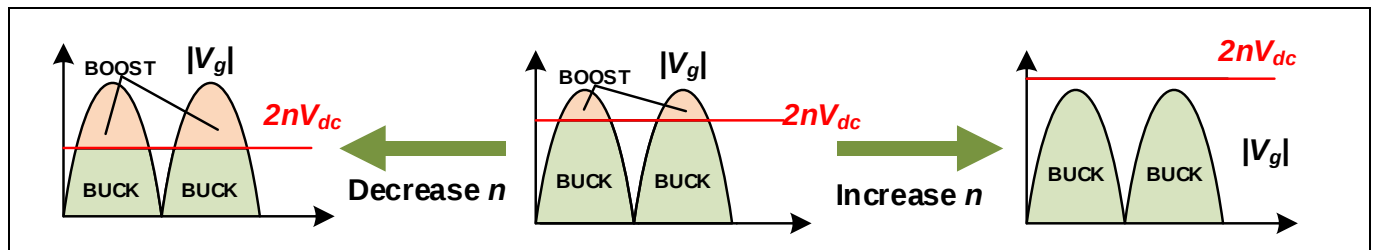

**Figure 50 Buck and boost mode periods of operation according to transformer turns ratio**

The resonant current is expressed as:

$$i_r(t) = \sum_{k=1,3,\dots}^N \frac{4V_p}{k\pi Z_r} \frac{\sqrt{A^2 + B^2}}{\left(\frac{k\omega_s}{\omega_r} - \frac{\omega_r}{k\omega_s}\right)} \sin\left[k\omega_s t + \theta_v - \frac{\pi}{2}\right]$$

**Equation 7**

## 5 Hardware functional description

Where

$$Z_r = \sqrt{\frac{L_r}{C_r}}$$

**Equation 8**

$$A = \cos\left(\frac{\varphi_1}{2}\right) \sin(\varphi_\delta) \text{ and } B = \cos\left(\frac{\varphi_1}{2}\right) \cos(\varphi_\delta) - m$$

**Equation 9**

$$\theta_V = \arctan2\left(\frac{A}{B}\right)$$

**Equation 10**

## 5 Hardware functional description

### 5.1.3.1 Transmission power and RMS resonant current

The power transmitted by the converter in one switching cycle can be calculated as:

$$P_{trans} = \frac{1}{T_s} \int_0^{T_s} v_s(t) i_r(t) dt = \sum_{k=1,3,\dots}^N \frac{8mV_p^2}{k^2 \pi^2 Z_r} \frac{\sqrt{A^2 + B^2}}{\left(\frac{k\omega_s}{\omega_r} - \frac{\omega_r}{k\omega_s}\right)} \sin(\theta_v)$$

$$= \sum_{k=1,3,\dots}^N \frac{8mV_p^2}{k^2 \pi^2 Z_r \left(\frac{k\omega_s}{\omega_r} - \frac{\omega_r}{k\omega_s}\right)} \cos\left(\frac{\varphi_1}{2}\right) \sin(\varphi_\delta)$$

**Equation 11**

Where  $\omega_r = 2\pi f_r$  is the resonant frequency.

Considering the fundamental component only, the power transmitted by the transformer during one switching cycle is simplified to:

$$P_{trans}^1 = \frac{8mV_p^2}{\pi^2 Z_r \left(\frac{\omega_s}{\omega_r} - \frac{\omega_r}{\omega_s}\right)} \cos\left(\frac{\varphi_1}{2}\right) \sin(\varphi_\delta) = \frac{4nV_{dc}|v_g|}{\pi^2 Z_r \left(\frac{\omega_s}{\omega_r} - \frac{\omega_r}{\omega_s}\right)} \cos\left(\frac{\varphi_1}{2}\right) \sin(\varphi_\delta)$$

**Equation 12**

According to the expression for resonant current, the effective value of resonant current can be calculated as:

$$i_{r,rms} = \sqrt{\frac{1}{T_s} \int_0^{T_s} [i_r(t)]^2 dt} = \sqrt{\sum_{k=1,3,\dots}^N \left[ \frac{2\sqrt{2}V_p}{k\pi Z_r} \frac{\sqrt{A^2 + B^2}}{\left(\frac{k\omega_s}{\omega_r} - \frac{\omega_r}{k\omega_s}\right)} \right]^2}$$

**Equation 13**

For the fundamental component, the effective value of the transformer secondary current is simplified to:

$$i_{r,rms}^1 = \frac{2\sqrt{2}V_p}{\pi Z_r \left(\frac{\omega_s}{\omega_r} - \frac{\omega_r}{\omega_s}\right)} \sqrt{\left[ \cos\left(\frac{\varphi_1}{2}\right) \sin(\varphi_\delta) \right]^2 + \left[ \cos\left(\frac{\varphi_1}{2}\right) \cos(\varphi_\delta) - m \right]^2}$$

**Equation 14**

## 5 Hardware functional description

### 5.1.4 Modulation optimization

In the REF\_500W\_CYCLO\_BDSGAN cyclo-microinverter, the resonant current magnitude is one of the key factors affecting the overall converter efficiency. An increase in the resonant current increases the conduction losses of the switching devices and the copper losses of the magnetic components leading to an efficiency reduction. Optimization of the resonant current is therefore an essential part of the control strategy.

#### 5.1.4.1 Fixed-switching frequency analysis

Considering fixed-frequency operation, the  $P_{trans}$  and  $i_{s,rms}$  calculations can be simplified to:

$$P_{trans} = \frac{4nV_{dc}|v_g|}{\pi^2 Z_r \left( \frac{f_s}{f_r} - \frac{f_r}{f_s} \right)} \cos\left(\frac{\varphi_1}{2}\right) \sin(\varphi_\delta)$$

$$i_{r,rms}^1 = \frac{2\sqrt{2}nV_{dc}}{\pi Z_r \left( \frac{f_s}{f_r} - \frac{f_r}{f_s} \right)} \sqrt{A^2 + B^2}$$

$$= \frac{2\sqrt{2}nV_{dc}}{\pi Z_r \left( \frac{f_s}{f_r} - \frac{f_r}{f_s} \right)} \sqrt{\left[ \cos\left(\frac{\varphi_1}{2}\right) \sin(\varphi_\delta) \right]^2 + \left[ \cos\left(\frac{\varphi_1}{2}\right) \cos(\varphi_\delta) - m \right]^2}$$

**Equation 15**

The transmission power reference is defined as:

$$P_N(V_{dc}, v_g, f_s) = \frac{4nV_{dc}|v_g|}{\pi^2 Z_r \left( \frac{f_s}{f_r} - \frac{f_r}{f_s} \right)}$$

**Equation 16**

When the inner phase shift angle is determined, the outer phase shift angle can be calculated from the above equation:

$$\varphi_\delta = \arcsin \left[ \frac{P_{trans}}{P_N(V_{dc}, v_g, f_s)} \cdot \frac{1}{\cos(\varphi_1/2)} \right] = \arcsin \left[ \frac{M_f(V_{dc}, v_g, P_g, f_s)}{\cos(\varphi_1/2)} \right]$$

**Equation 17**

$$M_f(V_{dc}, v_g, P_g, f_s) = \frac{P_{trans}}{P_N(V_{dc}, v_g, f_s)}$$

**Equation 18**

## 5 Hardware functional description

The intermediate variable  $x = \cos(\phi_1/2)$ , therefore the following optimization problem can be solved:

$$\begin{aligned}\min(A^2 + B^2) &= \min \left\{ \left[ \cos\left(\frac{\phi_1}{2}\right) \sin(\phi_\delta) \right]^2 + \left[ \cos\left(\frac{\phi_1}{2}\right) \cos(\phi_\delta) - m \right]^2 \right\} \\ &= \min \left\{ M_f^2 + \left[ x \cos\left(\arcsin\left[\frac{M_f}{x}\right]\right) - m \right]^2 \right\} \\ &= \min \left\{ M_f^2 + \left[ \sqrt{x^2 - M_f^2} - m \right]^2 \right\} \\ &= \min \left\{ x^2 + m^2 - 2m\sqrt{x^2 - M_f^2} \right\} \\ &= \min \left\{ f(x) \right\}\end{aligned}$$

**Equation 19**

Deriving  $f(x)$  and setting the derivative to zero gives:

$$\frac{\partial f(x)}{\partial x} = 2x \left( 1 - \frac{m}{\sqrt{x^2 - M_f^2}} \right) = 0 \Rightarrow x = \sqrt{M_f^2 + m^2}$$

**Equation 20**

$$\cos\left(\frac{\phi_1}{2}\right) = x = \sqrt{M_f^2 + m^2} \Rightarrow \phi_1 = 2 \cdot \arccos\left(\min\left\{\sqrt{M_f^2 + m^2}, 1\right\}\right)$$

**Equation 21**

The inner and outer phase shift angle trajectories for the minimum RMS value of the resonant current can be obtained from these equations.

### 5.1.4.2 Variable switching frequency analysis


If switching frequency is variable over the working condition, it can be used to control the power transferred to the grid. The RMS value of resonant current is given by:

$$\left| \frac{i_{r,rms}}{i_g} \right| = \frac{\pi}{\sqrt{2}} \sqrt{\frac{A^2 + B^2}{A^2}} = \frac{\pi}{\sqrt{2}} \sqrt{1 + \frac{B^2}{A^2}} \Rightarrow |i_{r,rms}| = \frac{\pi |i_g|}{\sqrt{2}} \sqrt{1 + \frac{B^2}{A^2}} \geq \frac{\pi |i_g|}{\sqrt{2}}$$

**Equation 22**


$|i_g|$  is the current passing between the microinverter and the grid, which is directly related to the transmitted power. When  $B = 0$ , the RMS value of the resonant current reaches a minimum value of  $\pi |i_g| / 2$ . However, the condition  $B = 0$  is only possible during buck mode. In Buck mode,  $B = 0$  when the phase angle of resonant current  $\theta_i$  is zero when the vector of resonant current is exactly parallel to the vector of the secondary voltage  $V_s$ . The phasor diagram is as follows:

## 5 Hardware functional description

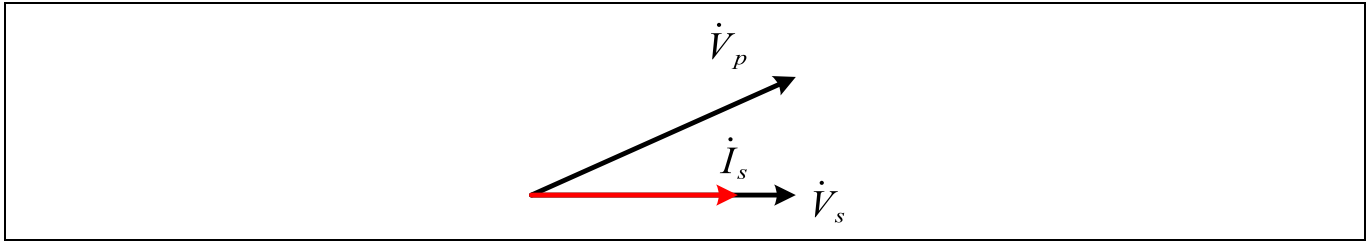

**Figure 51** Phasor diagram when  $\theta_i = 0$

The vector diagram shows that when the phase of the resonant current and the phase of the secondary voltage are equal. The corresponding RMS value of the resonant current is at its minimum so the secondary switch can achieve zero current switching. However, this condition alone does not determine the value of the inner and outer phase shift angles. On this basis, if  $\phi_\delta = \phi_1 / 2$  is specified, the zero-current switching of the primary-side switches can also be achieved. The corresponding inner and outer phase shift angle trajectory in buck mode is shown as follows:

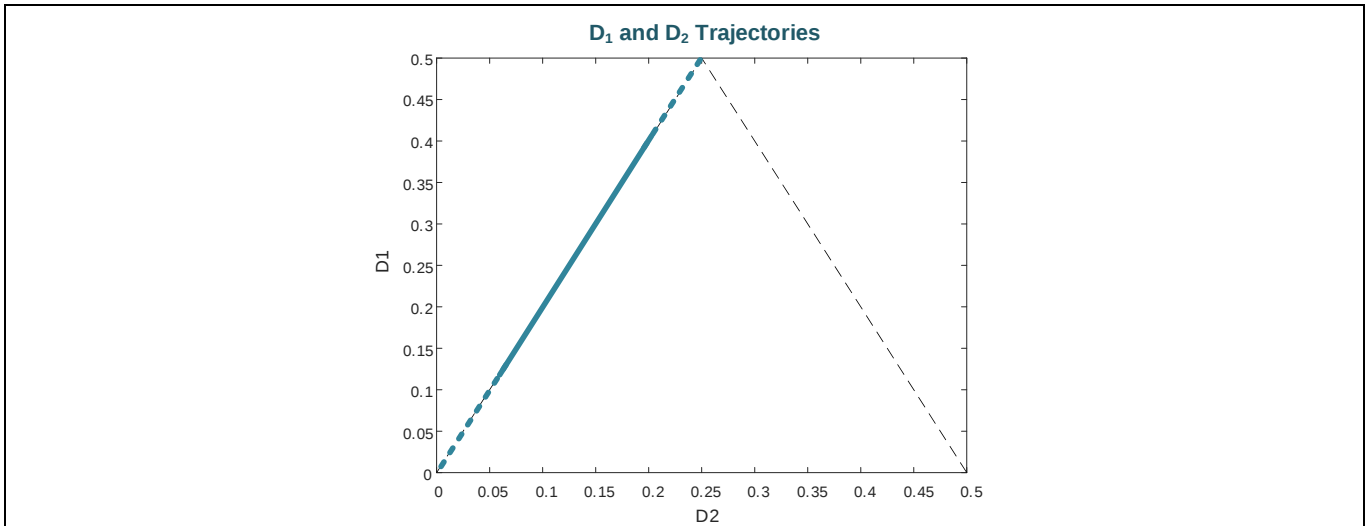

**Figure 52** D1 and D2 trajectories in buck mode

In boost mode, the inner phase shift angle remains at zero. Defining the intermediate variable  $x = \cos(\phi_\delta)$ , the expressions of resonant current can be transformed to:

$$|i_{r,rms}| = \frac{\pi |i_g|}{\sqrt{2}} \sqrt{1 + \frac{B^2}{A^2}} = \frac{\pi |i_g|}{\sqrt{2}} \sqrt{1 + \frac{(\cos \phi_\delta - m)^2}{1 - \cos^2 \phi_\delta}} = \frac{\pi |i_g|}{\sqrt{2}} \sqrt{1 + \frac{(x - m)^2}{1 - x^2}} = \frac{\pi |i_g|}{\sqrt{2}} \sqrt{g(x)}$$

**Equation 23**

Where,

$$g(x) = 1 + \frac{(x - m)^2}{1 - x^2}$$

**Equation 24**

## 5 Hardware functional description

Solving the derivative of  $g(x)$  at zero yields the maximum value:

$$\frac{\partial g(x)}{\partial x} = \frac{-2m(1-x^2)+2x(1-2mx+m^2)}{(1-x^2)^2} = \frac{-2(x-m)(mx-1)}{(1-x^2)^2} = 0 \Rightarrow x = \frac{1}{m}$$

Equation 25

$$\cos\varphi_\delta = \frac{1}{m} \Rightarrow \varphi_\delta = \arccos\left(\frac{1}{m}\right)$$


Equation 26

$$\cos\varphi_\delta = \frac{1}{m} \Rightarrow |i_{r,rms}| = \frac{\pi|i_g|}{\sqrt{2}} \sqrt{1 + \frac{\left(\frac{1}{m}-m\right)^2}{1-\frac{1}{m^2}}} = \frac{\pi m|i_g|}{\sqrt{2}}$$

Equation 27


## 5 Hardware functional description

The inner and outer phase shift angle trajectory in boost mode is shown here:

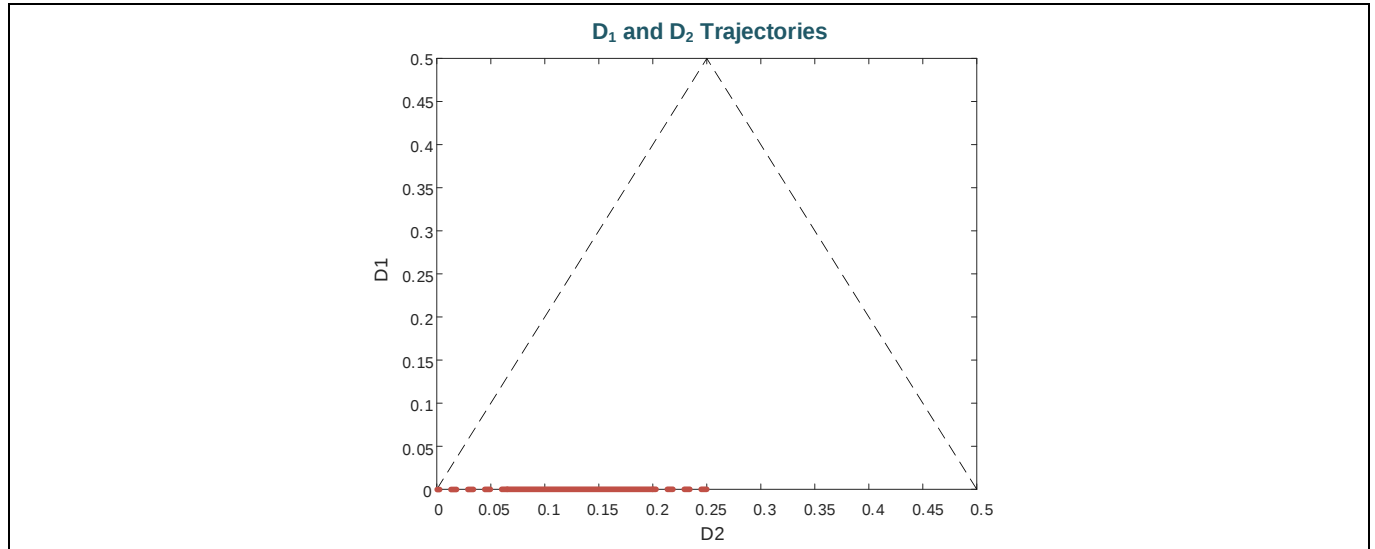

**Figure 53**  $D_1$  and  $D_2$  trajectories in boost mode

It should be noted that when the voltage gain  $m = 1$ , the corresponding inner and outer phase shift angles  $D_1$  and  $D_2$  are both equal to 0. At this point, the switching frequency is equal to the resonant frequency, which is a non-permitted condition. In order to ensure the normal operation of the circuit, it is possible to limit the minimum switching frequency of the inverter operation so that the total internal and external phase shift angle trajectories are:

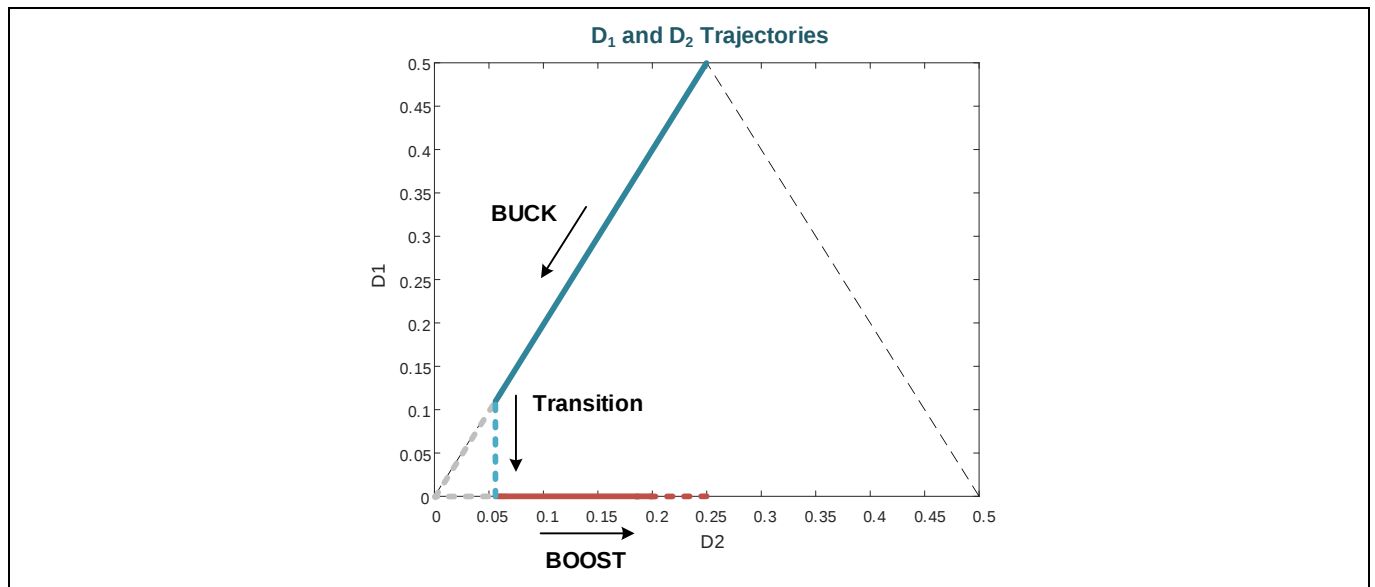


**Figure 54** Overall  $D_1$  and  $D_2$  trajectories

## 5 Hardware functional description

### 5.1.4.3 ZVS optimization modulation

With the above modulation strategy, the switches of the primary-side leading-bridge arm can achieve ZVS zero voltage switch-on, and the primary-side lagging switches and the secondary-side switches can achieve ZCS zero current switch-on. The corresponding typical waveforms are shown in [Figure 55](#):

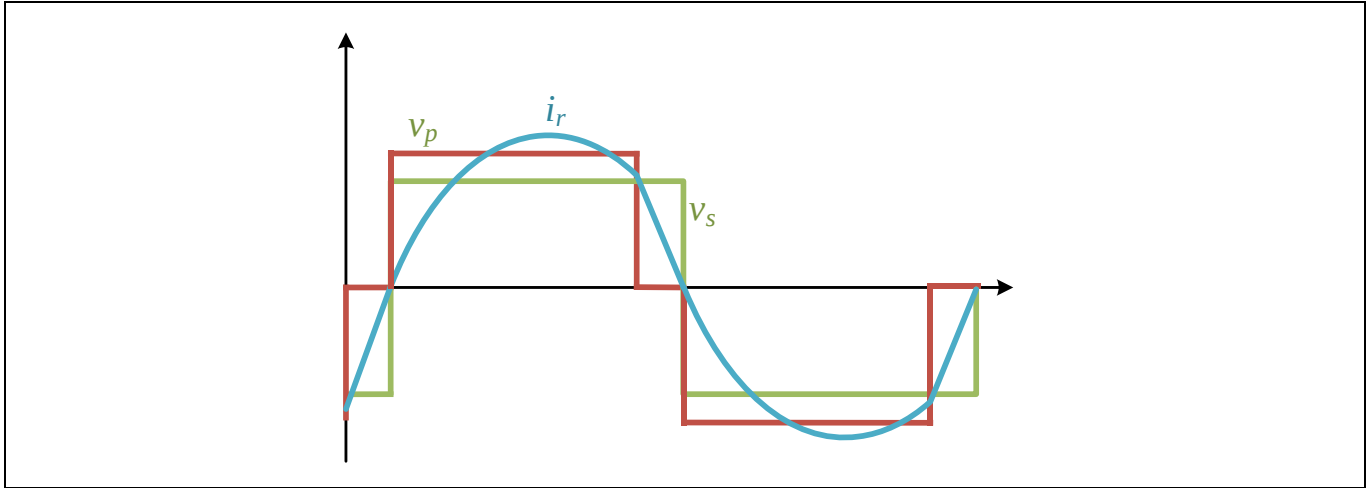


**Figure 55** Waveforms under minimum RMS current modulation

To fully realize ZVS soft switching with lag switching on the primary side and over-switching on the secondary side, a small displacement  $\Delta\phi$  can be added to the outer phase shift angle  $D_\delta$  so that the modified voltage-current waveforms are of the following form. The relationship between turn-on currents  $i_{lag}$  and  $i_{sec}$  with displacement  $\Delta\phi$  are:

$$i_{lag} + i_{sec} \approx \sqrt{2}i_{r,rms} \sin(\Delta\phi) = \frac{4nV_{dc} \sin(\Delta\phi)}{\pi Z_r \left( \frac{f_s}{f_r} - \frac{f_r}{f_s} \right)} \sqrt{\left[ \cos\left(\frac{\phi_1}{2}\right) \sin(\phi_\delta) \right]^2 + \left[ \cos\left(\frac{\phi_1}{2}\right) \cos(\phi_\delta) - m \right]^2}$$

**Equation 28**

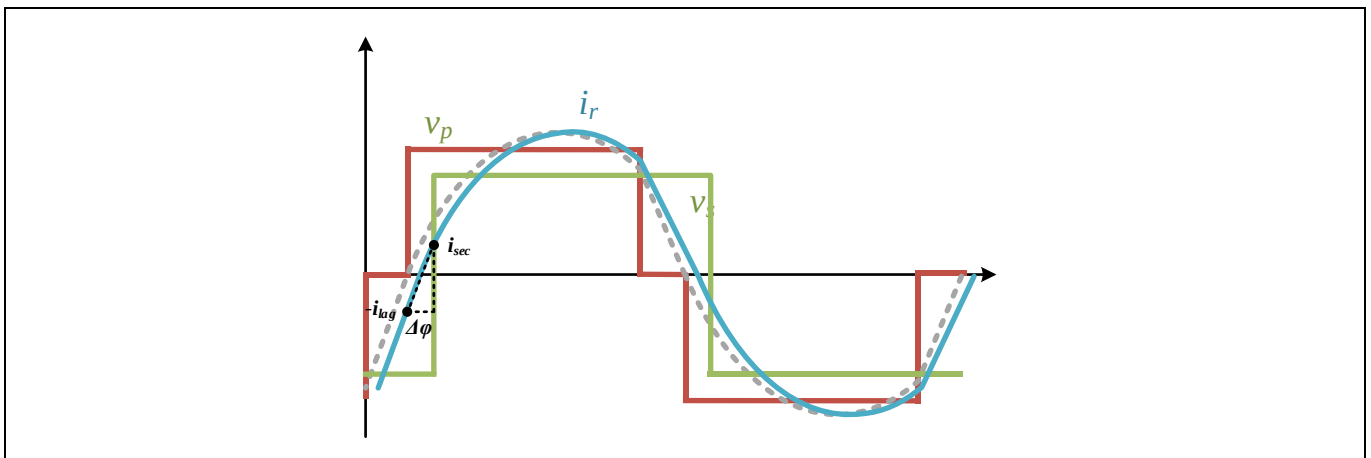

**Figure 56** Waveforms with a small displacement added to  $D_\delta$

## 5 Hardware functional description

The displacement  $\Delta\phi$  is small, therefore, assume that the amount of change in the RMS value of the resonant current after the introduction of the displacement can be neglected and thus the above equation can be simplified as:

$$I_{zvs} \approx \sqrt{2} i_{r,rms} \sin(\Delta\phi) \approx \sqrt{2} \cdot \sin(\Delta\phi) \cdot \frac{\pi |i_g|}{\sqrt{2}} \cdot \max\{1, m\} \approx \pi |i_g| \tan(\Delta\phi) \times \max\{1, m\}$$


**Equation 29**

$$I_{zvs} = i_{lag} + i_{sec}$$

**Equation 30**


By setting  $I_{zvs}$  to an appropriate value the displacement  $\Delta\phi$  can be calculated and all switches can realize ZVS, while maintaining a low RMS value of the resonant current.

In boost mode the phasor diagram of minimum RMS current modulation is:

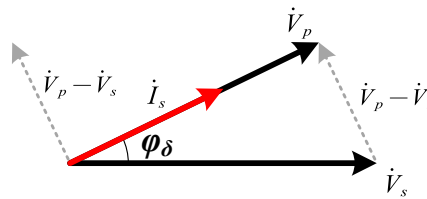

**Figure 57 Phasor diagram in boost mode**

This is because  $\cos(\phi_\delta) = 1/m = V_p/V_s$  and the vector  $\dot{V}_p - \dot{V}_s$  is perpendicular to vector  $\dot{V}_p$ . Therefore, the vector of resonant current  $i_s$  is exactly parallel to the vector of the primary voltage  $V_p$ . The corresponding typical waveforms are shown below. In boost mode, the switches of the secondary-side switches can easily achieve ZVS, while all switches on the primary side are switching at zero current.

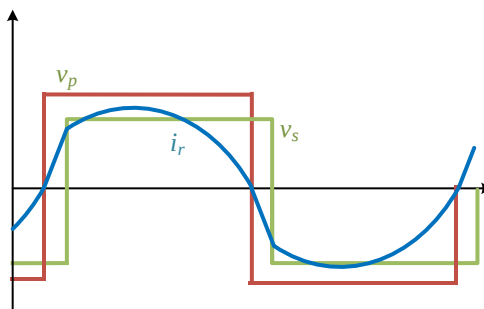


**Figure 58 Waveforms of minimum RMS current modulation under boost mode**

Similarly, a small displacement  $\Delta\phi$  can be added to the outer phase shift angle  $D_\delta$  to help achieve full ZVS of all primary switches, so same modulation strategy as in buck mode can be used in boost mode.


## 5 Hardware functional description

The PWM control scheme driving the switches is shown below of a period of several AC line cycles:

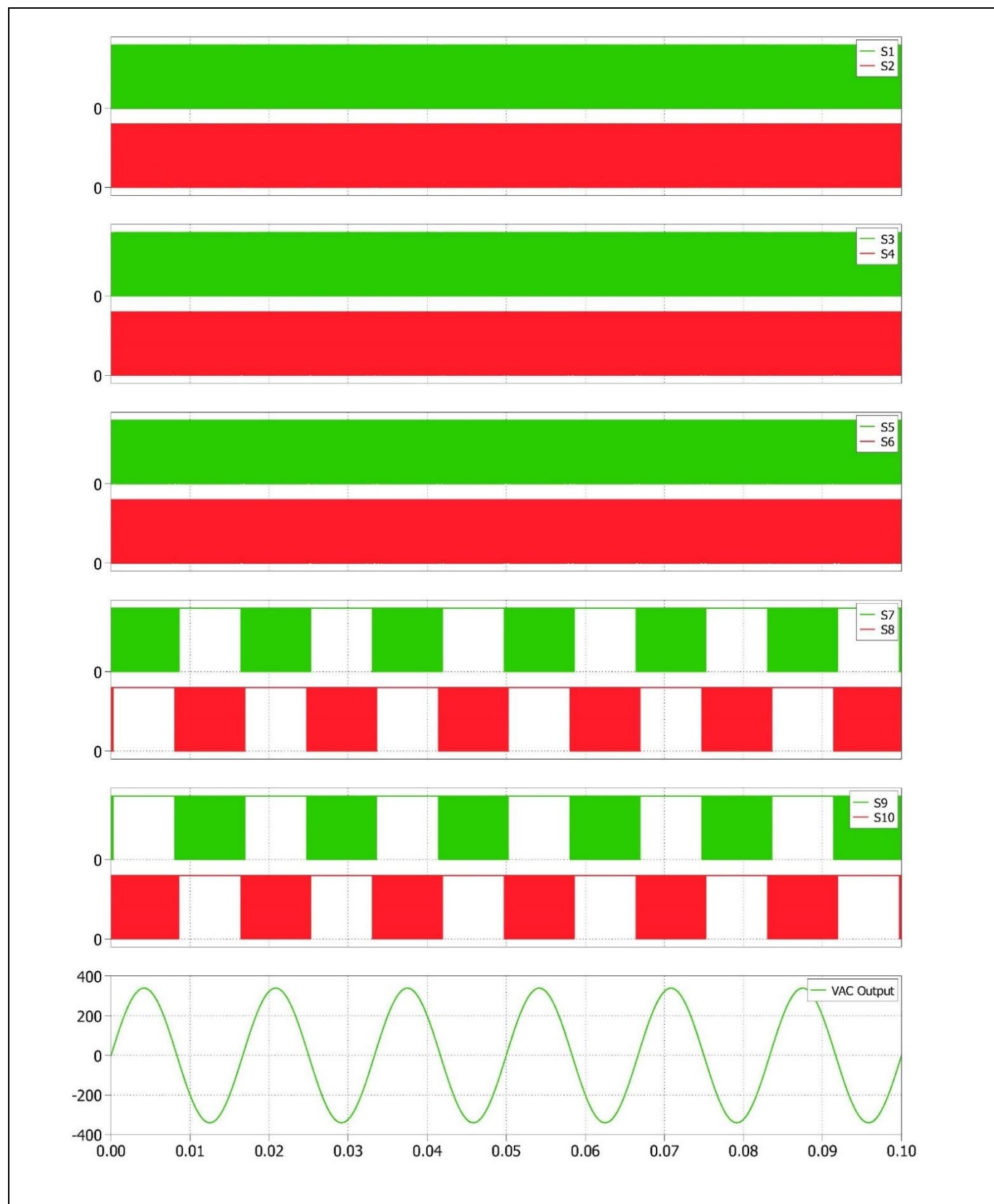


**Figure 59** Cycloinverter PWM scheme over several line cycles

## 5 Hardware functional description

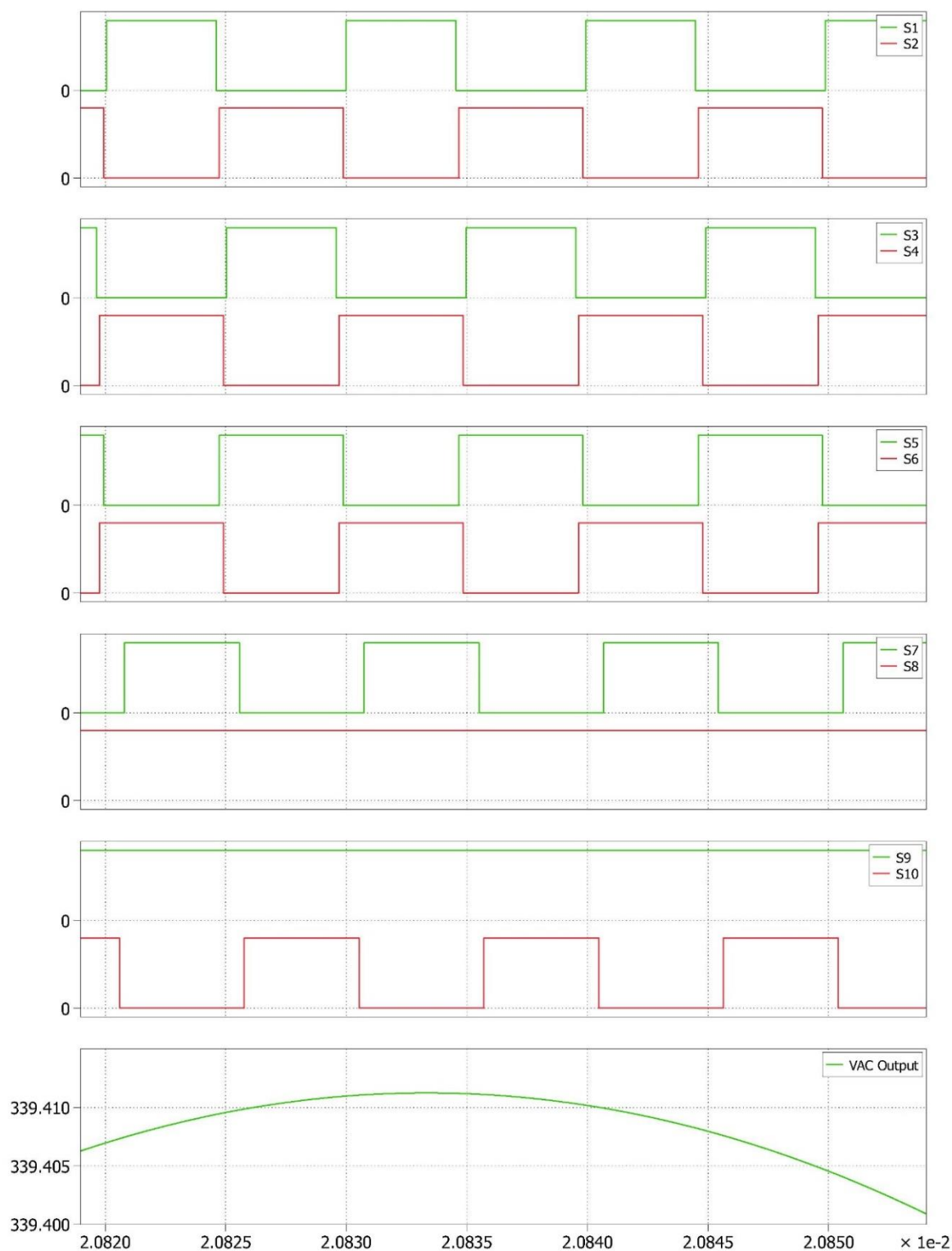


**Figure 60** Cycloinverter PWM scheme at the switching frequency (at the positive AC output peak)

## 5 Hardware functional description

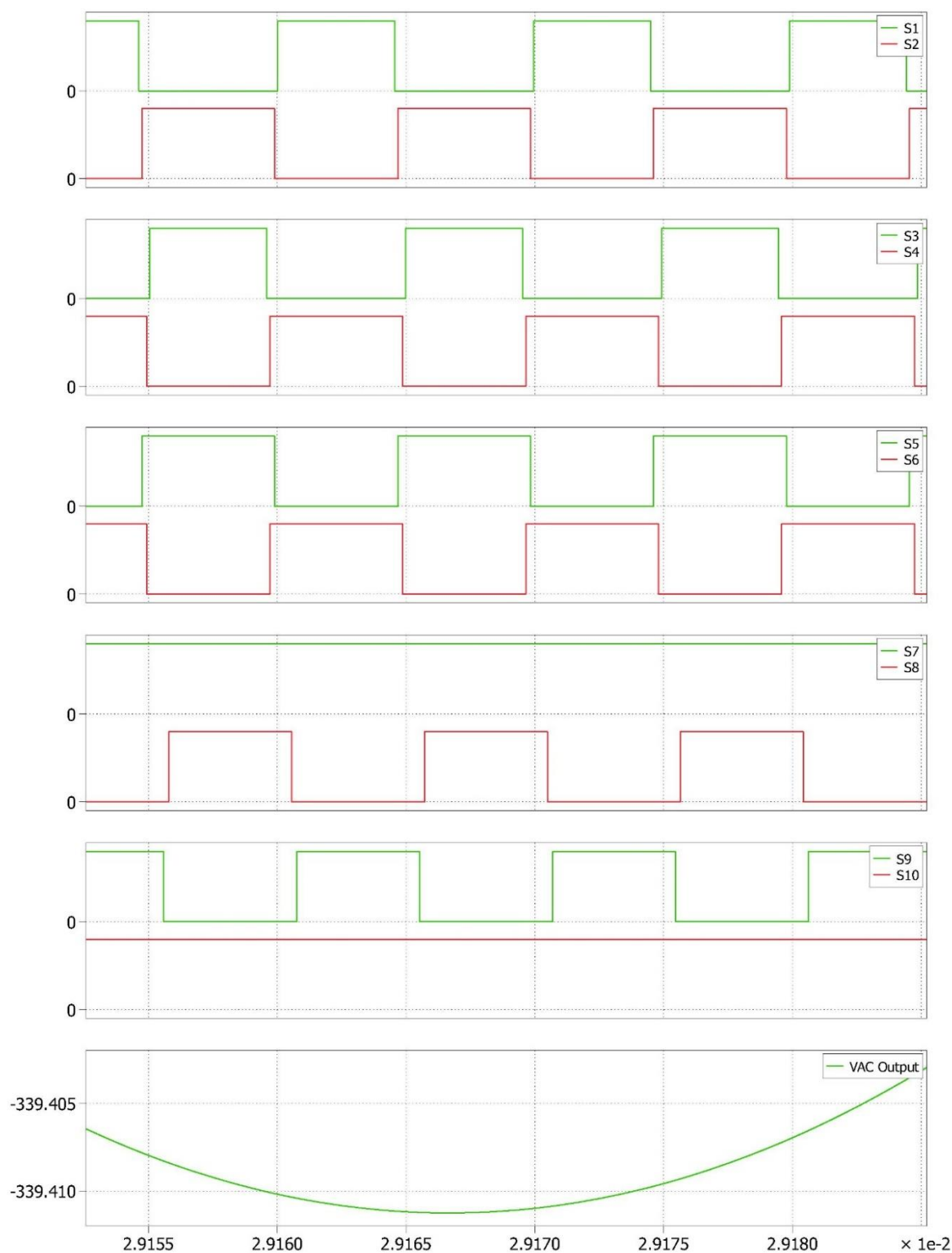

**Figure 61** Cycloinverter PWM scheme at the switching frequency (at the negative AC output peak)

## 5 Hardware functional description

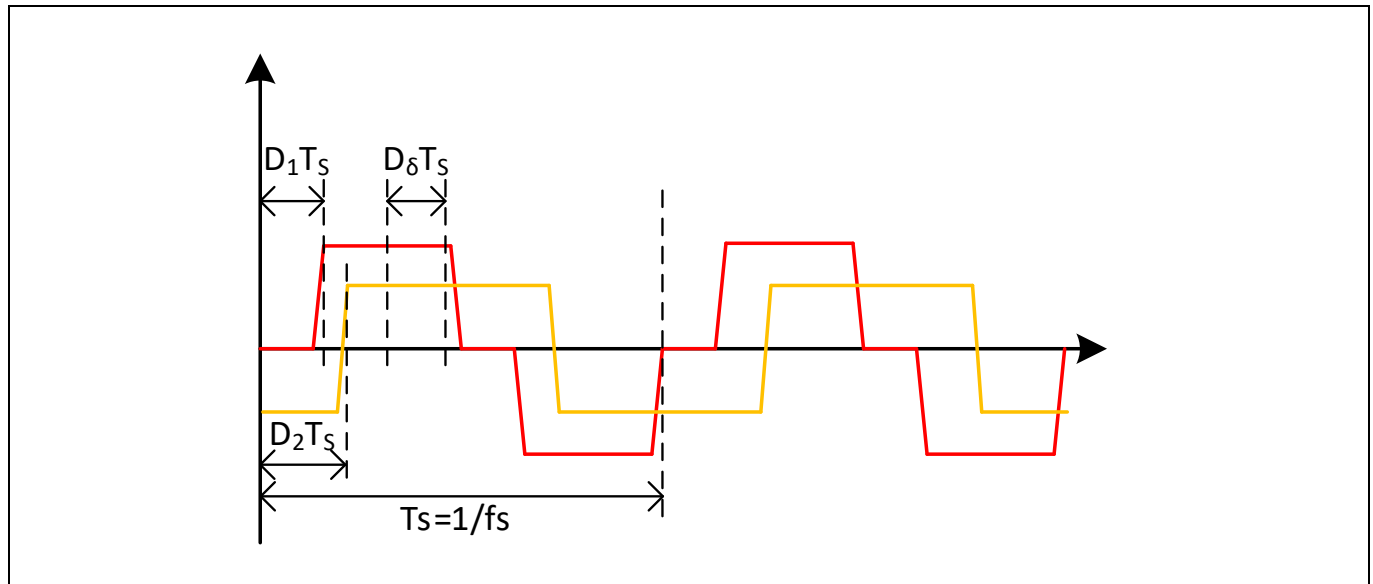

**Figure 62** Modulation scheme

The switching frequency and duty cycles are varied over the period of the grid voltage half cycle to create a frequency and phase-locked sinusoidal current source at the grid connection whose amplitude and phase shift relative to the grid may be adjusted to transfer a defined AC power, which may include real and reactive components.

The reference designators in the following sections refer to the schematics (refer to Section 4), which differ from those used in the sections above.

### 5.2 Power stage and gate drivers

The DC input includes a bank of electrolytic capacitors C1, C2, C3, C4, and C119, required to absorb low frequency ripple at twice the AC grid frequency. This is necessary to achieve accurate and stable AC power and MPPT control. Capacitor sizing is based on the following calculation where a maximum allowable input voltage ripple of +/-5 percent is assumed, which is approximately +/-1.2 V under the worst-case minimum input voltage of 25 V.

$$C_{dc} = \frac{P_{PV}}{2\pi f_{ripple} V_{MPP} v_{ripple}} = \begin{cases} \frac{500W}{2\pi \cdot 120Hz \cdot 25V \cdot 1.2V} = 22.1mF (f_{AC} = 60Hz) \\ \frac{500W}{2\pi \cdot 100Hz \cdot 25V \cdot 1.2V} = 26.5mF (f_{AC} = 50Hz) \end{cases}$$

**Equation 31**

Since we have chosen to use five parallel capacitors, the value of each one should be 26.5 mF divided by 5, which equals 5300 µF. For convenience we have used the next lowest available value of 4700 µF.

The DC input also includes a high frequency EMI filter including eighteen parallel ceramic capacitors C5 to C22.

The primary side power stage consists of a full bridge with an additional bidirectional switch as shown in Figure 29. These switches are implemented with OptiMOS™ 6 power MOSFET 80 V parts in a 5 x 6 mm QFN package with a maximum  $R_{DS(on)}$  of 1.45 mΩ. A heatsink is mounted to provide top-side cooling through a 1 mm thick thermal insulation material. The full bridge switches Q1, Q2, Q3, and Q4 are driven by non-isolated

## 5 Hardware functional description

half-bridge gate drivers IC1 and IC2 referenced to the signal ground (SGND), which is connected at a single point to the power ground (PGND) connected to the DC input negative. The microcontroller U5 ground (DGND) is also referenced to the same primary side ground with proper separation of signal, digital, and power grounds implemented in the board layout.

The primary bidirectional switch comprising Q5 and Q6 uses OptiMOS™ 6 power MOSFET 80 V parts in 5 mm x 6 mm QFN package with a maximum  $R_{DS(on)}$  of 5.6 mΩ with two single gate driver ICs with true differential inputs, U3 and U4, which are supplied from separate bootstrap circuits derived from the 12 V auxiliary supply.

The secondary side power stage consists of the two common-drain CoolGaN™ bidirectional switch 600 V Q7 and Q8 in TOLL packages with 55 mΩ typical  $R_{SS(on)}$ . Each of these devices is controlled by two separate gate drive circuits with different source potentials requiring two isolated gate drive circuits for each bidirectional switch. These are implemented by means of dual channel-isolated gate drivers U1 and U2 for which the input sides, which receive the PWM drive pulses from the microcontroller, are referenced to SGND. The outputs are all referenced to different potentials except for two that share the same ground, therefore requiring three separate floating voltage supplies.

The primary and secondary stages are linked through the transformer TR1, which provides a 1 to 5 step-up ratio. The secondary current passes through a current transformer CT1 to enable the current to be read by the microcontroller.

### 5.2.1 Transformer turns ratio selection

As discussed earlier, the turns ratio  $n$  of the main transformer is one of the most important parameters for design optimization in this topology because it affects the proportion of time in buck and boost mode operation during the AC line half cycle. Referring back to [Figure 49](#), when the turns ratio is high, the circuit will operate in buck mode for a longer period or even continuously if the turns ratio is very high. Optimized modulation in buck mode allows the RMS secondary resonant current of the transformer to reach a theoretical minimum, however the corresponding large turns-ratio results in increased RMS primary current. Conversely, when the turns ratio is small the circuit operates in boost mode for longer. In this case, the current reflected from the secondary to the primary will be relatively small but the RMS value of the secondary resonant current will be higher compared to the buck mode.

Considering the difference in the RMS values of the current, the weighted sum of the RMS values of the primary and secondary currents is taken as the optimization objective, and the modulation strategy described earlier is selected, ignoring the transition phase when switching between buck and boost modes.


## 5 Hardware functional description

An optimization function  $W$  is used, which represents the conduction loss of the primary and secondary switches and is defined as:

$$\begin{aligned}
 W &= i_{p,rms}^2 R_{on,pri} + i_{s,rms}^2 R_{on,sec} = i_{s,rms}^2 (n^2 R_{on,pri} + R_{on,sec}) \\
 &= i_{s,rms}^2 (0.00145n^2 + 0.0042) \\
 i_{s,rms} &= \sqrt{\frac{1}{T_{ac}} \int_0^{T_{ac}} i_r^2(t) dt} \\
 i_r(t) &= \begin{cases} \frac{\pi |i_g(t)|}{\sqrt{2}}, m(t) < 1 \\ \frac{\pi m |i_g(t)|}{\sqrt{2}}, m(t) \geq 1 \end{cases}
 \end{aligned}$$

**Equation 32**


At rated operating conditions  $V_{DC} = 35$  V,  $V_{AC} = 240$  V<sub>RMS</sub>,  $P = 500$  W, the optimization function  $W$  varies with turns ratio as shown:

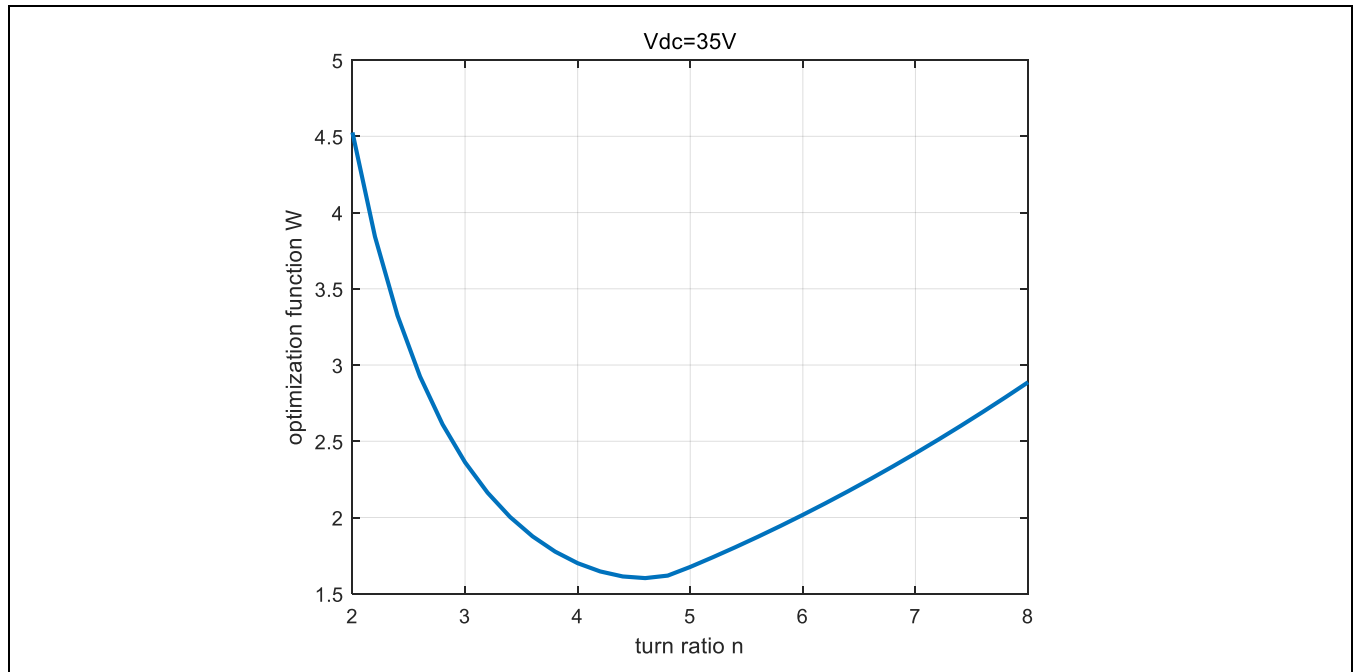

**Figure 63 Optimization function used for selection of the turns-ratio  $n$**

## 5 Hardware functional description

Curves are plotted for different operating points, which are then averaged to find the optimum turns-ratio for the design:

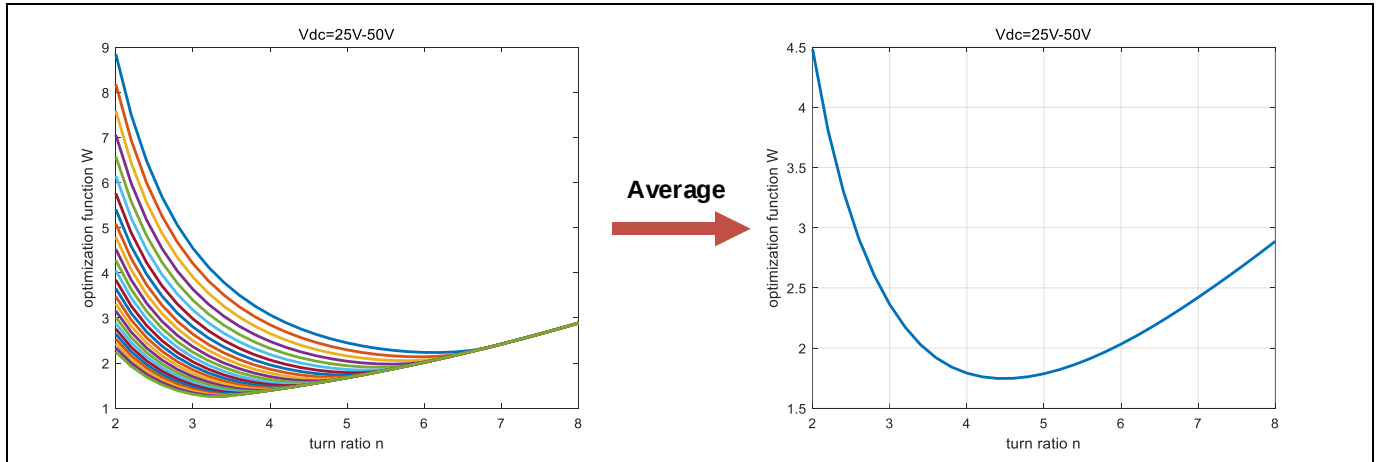

**Figure 64 Optimization function averaged for multiple operating points**

Based on the above analysis to achieve the lowest RMS resonant current, the selected transformer turns ratio is 1 to 5.

## 5 Hardware functional description

### 5.2.2 Resonant inductor and capacitor selection

The selection of resonant inductor and capacitor values is mainly related to the resonant frequency, resonant current and resonant voltage. The resonant parameters can be designed based on the current-voltage stress and transmitted power constraints. The expressions for the resonant current and resonant voltage of the microinverter are:

$$i_{r,rms}^1 = \frac{2\sqrt{2}V_p}{\pi Z_r \left( \frac{\omega_s}{\omega_r} - \frac{\omega_r}{\omega_s} \right)} \sqrt{\left[ \cos\left(\frac{\varphi_1}{2}\right) \sin(\varphi_\delta) \right]^2 + \left[ \cos\left(\frac{\varphi_1}{2}\right) \cos(\varphi_\delta) - m \right]^2}$$

$$v_{r,rms}^1 = \frac{i_{r,rms}^1}{\omega_s C_r} = \frac{\omega_r Z_r}{\omega_s} i_{r,rms}^1$$

**Equation 33**

These should satisfy the following conditions:

$$i_{r,rms} \geq \frac{\pi |i_g|}{\sqrt{2}} \cdot \max\{1, m\}$$

$$v_{r,rms} = \frac{i_{r,rms}}{\omega_s C_r} \geq \frac{\omega_r Z_r}{\omega_s} \cdot \frac{\pi |i_g|}{\sqrt{2}} \cdot \max\{1, m\}$$

**Equation 34**

The true voltage-current value ratio is always larger than the estimated value, which adds some margin for design. The voltages of capacitors C1 and C2 each need to carry half of the grid voltage thus the capacitor voltage is expressed as:

$$V_{C1} = \frac{v_g(t)}{2} + v_r(t) \Rightarrow V_{C1,max} = \frac{V_{g,max}}{2} + \sqrt{2}v_{r,rms,max}$$

**Equation 35**

The peak AC voltage should never exceed the rated DC voltage of the MLCCs and the RMS voltage of the AC grid voltage should be limited to the rated DC voltage of the MLCC divided by two-root-two, as seen below:

$$V_{ac,peak} + V_{dc,bias} < V_{rated\ DC}$$

**Equation 36**

$$V_{ac,peak} < \frac{V_{rated\ DC}}{2} \Rightarrow V_{ac,rms} < \frac{V_{rated\ DC}}{2\sqrt{2}}$$

**Equation 37**

## 5 Hardware functional description

At 500 W at 240 V<sub>RMS</sub> the peak grid current is close to 3 A. Considering a high AC line condition, the resonant current and voltage magnitudes are:

$$i_{r,rms,max} \approx \frac{\pi |i_{g,max}|}{\sqrt{2}} \cdot \frac{276 \cdot \sqrt{2}}{2 \cdot 25 \cdot 5} = 10.4A, \quad v_{r,rms} = \frac{\omega_r Z_r}{\omega_s} \cdot i_{r,rms,max} \approx 10.4Z_r$$

$$v_{ac,rms} = v_{r,rms} = 10.4Z_r, \quad v_{ac,peak} + V_{dc,bias} = \sqrt{2}v_{r,rms} + \frac{V_{g,max}}{2} = 14.7Z_r + 195$$

**Equation 38**

The MLCC with a rated voltage of 1000 V is selected as the resonant capacitor and the calculation gives the constraint relationship of the resonant impedance as follows:

$$10.4Z_r \leq \frac{1000}{2\sqrt{2}} \Rightarrow Z_r \leq 34$$

$$14.7Z_r + 195 \leq 1000 \Rightarrow Z_r \leq 54.76$$

**Equation 39**

On the other hand, the microinverter also needs to satisfy power constraints and should have the ability to transmit sufficiently high power with the stable operating point should be in a reasonable interval. In the analysis, the operating point switching frequency range for maximum instantaneous power as  $[1.1f_r, 1.4f_r]$  at the above conditions.

$$P_{trans} = \frac{4nV_{dc}V_g}{\pi^2 Z_r \left( \frac{\omega_s}{\omega_r} - \frac{\omega_r}{\omega_s} \right)} \cos\left(\frac{\varphi_1}{2}\right) \sin(\varphi_\delta) \Rightarrow P_{max} = \frac{4nV_{dc}V_g}{\pi^2 Z_r \left( \frac{\omega_s}{\omega_r} - \frac{\omega_r}{\omega_s} \right)} \Rightarrow i_{max} = \frac{4nV_{dc}}{\pi^2 Z_r \left( \frac{\omega_s}{\omega_r} - \frac{\omega_r}{\omega_s} \right)}$$

$$i_{max}(f_s = 1.1f_r) = \frac{4nV_{dc}}{\pi^2 Z_r \left( 1.1 - \frac{1}{1.1} \right)}, \quad i_{max}(f_s = 1.4f_r) = \frac{4nV_{dc}}{\pi^2 Z_r \left( 1.4 - \frac{1}{1.4} \right)}$$

$$\Rightarrow 24.6 < Z_r < 88.5$$

**Equation 40**

The resonant inductor inductance is designed to be 60 μH integrated into the transformer, with the half-bridge capacitance at 30 nF. The resonant parameters of the circuit are as follows:

$$L_r = 60\mu H, C_r = 2C_1 = 60nF$$

$$f_r = \frac{1}{2\pi\sqrt{L_r C_r}} = 83.9kHz, Z_r = \sqrt{\frac{L_r}{C_r}} = 31.6$$

**Equation 41**

## 5 Hardware functional description

### 5.3 Output filter and relay

The output from the secondary side is connected to the AC grid through the output filter and relay K1. The grid voltage is sensed directly at the output terminals and sampled by the microcontroller whether the relay is open or closed. This ensures that the system will be physically disconnected from the grid until the inverter has successfully synchronized to the voltage, frequency, and phase. The relay will be disengaged when a fault condition is detected.

High frequency components are removed by the two-stage output filter network, which consists of two common-mode inductors Lf1 and Lf2 with low DC resistance. These also include sufficient leakage inductance to filter out common and series mode noise. Filter capacitors C35, C36, and C37 are X2 safety rated metallized polypropylene film EMI suppression capacitors.

### 5.4 On board auxiliary power

The DC input feeds a fly-buck regulator based on IC3 that can operate from up to 80 V. This provides a non-isolated stable 12 V DC rail referenced to SGND as well as three floating 10 V outputs used to supply the secondary side switch gate drive circuits.

The 12 V rail supplies a second buck regulator based on IC4 to provide a stable 5 V rail, which in-turn feeds another buck stage based on IC13 to provide a stable 3.3 V rail.

These provide all of the voltage supplies needed to supply the control and gate drive circuitry.

## 5 Hardware functional description

### 5.5 Control and monitoring circuitry

The microcontroller U5 is a main line PSOC™ Control C3 MCU developed specifically for power conversion applications. It is based on real-time control Arm® Cortex® - M33 based core with 180 MHz clock frequency, 64 kB SRAM and 256 kB flash. Peripherals include 12-bit, 12-MSPS SAR ADC and 16 x 16-bit and 4 x 32-bit TCPWMs, 4-channel HRPWM with <100 ps resolution as well as UART interfaces for communication and an SPI programming/debugging interface. U5 is supplied from the 3.3 V rail.

PWM gate drive signals generated by U5 are converted from 3.3 V to 5 V via a digital buffers IC6, IC11, and IC12.

For analog AC measurements a stable 1.65 V offset is required, which is provided by Q. The output is buffered through IC15.

AC output voltage is sensed before the output filter through a differential amplifier based on IC14 and also at the grid connections through another differential amplifier based on IC5. A Hall effect current sensor IC7 is used to measure the AC output current. Amplification and offset is added through IC5.

DC input voltage is sensed via a differential amplifier based on IC3, which also provides another differential amplifier for sensing and amplifying the input current from the input shunt R1. All of the voltage and current signals are amplified or attenuated to the correct range required for the ADC inputs of U5. The resonant current measurement from the current transformer CT1 is used for over current protection. This is rectified through Schottky diodes D16-19 and amplified through IC10 to provide input to U5. An additional over current protection circuit monitors the AC grid output current from IC5 and triggers a shutdown through a dual comparator circuit IC9 if the amplitude exceeds upper and lower limits.

The system also includes three temperature sensors: Rt1, Rt2, and Rt3 placed at different points on the board to enable the firmware to monitor component temperature and shutdown in the event of overheating.

### 5.6 Control and firmware

### 5.7 Control algorithm

The control functionality of a microinverter combines MPPT for optimal harvesting of solar energy from connected PV panels, combined with AC power flow control for transferring power onto the AC grid. The REF\_500W\_CYCLO\_BDSGAN reference design board can be operated in grid-tied mode to enable AC power transfer to a grid simulator or simple inverter mode driving a passive or AC electronic load. The unit operates with a PC-based GUI via a serial interface, which enables different operating modes and operating parameters to be selected.

During off-grid mode, the user sets the output voltage through the GUI. The unit will not operate with the relay disconnected if an AC voltage is present at the output terminals during this mode.

During grid-tied mode a grid simulator should be connected to the output terminals and set to the desired voltage and line frequency. The user set the target output current through the REF\_500W\_CYCLO\_BDSGAN Cyclo microinverter commander GUI with the MPPT function turned OFF by default. MPPT will operate correctly only if the board is connected to a PV source or power supply which includes a PV emulation mode such as the Chroma 62150H-1000S used to perform the tests documented here.


*Note: The unit will shut down if no grid voltage is detected at the output during this mode.*

The individual control variables are derived mathematically by calculating the specific values of the internal and external phase shift angles and the switching frequency, given the amount of power the converter needs to transmit at that moment. In grid-tied operation, the output current can differ from the actual current due to the

## 5 Hardware functional description

presence of dead zones, and errors in the resonance parameters can lead to inaccurate calculated control quantities. These practical factors affect the magnitude and THD of the output current and influence the quality of the waveform, hence the need for closed-loop control of the microinverter.

The closed-loop block diagram of the microinverter is shown in [Figure 65](#), comprising a current closed-loop control and an optimized modulation algorithm. In the current closed-loop, the error value of the AC current is obtained by taking the difference between the measured AC current and the reference AC current. This error is then passed through a quasi-proportional resonant (QPR) controller to obtain the error  $\Delta i_{ac}$ , which also represents the difference between the commanded power and the actual power being transferred.  $\Delta i_{ac}$  and the reference current  $i_{ref}$  are added together to generate the corrected reference current value,  $i'_{ac,ref}$ . This correction is required to reduce iTHD in the output. In the optimized modulation block, the system samples the instantaneous input and output voltages. These values are used with the corrected reference current  $i'_{ac,ref}$  to determine the required switching frequency  $f_{sw}$  with the inner phase shift angle  $D_1$  and the outer phase shift angle  $D_2$ . These parameters are fed to the PWM generator to produce the gate drive pulses.

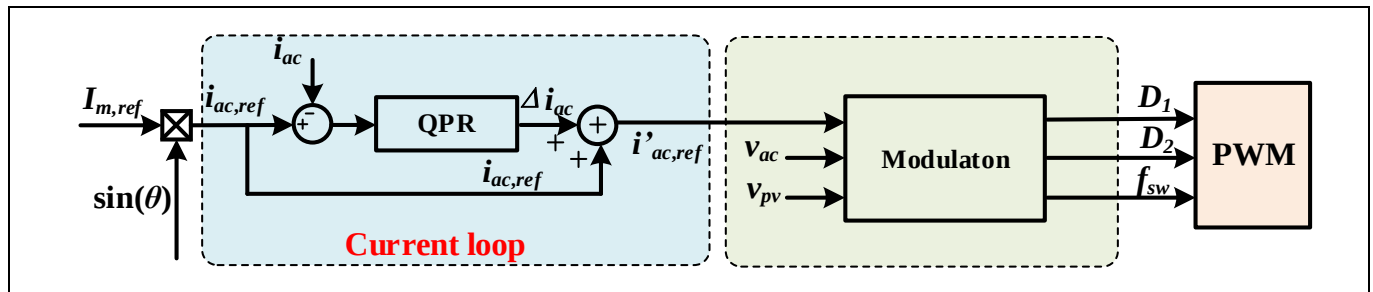


**Figure 65** Control loop block diagram

# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter

## 5 Hardware functional description

The overall control framework consists of five components:


- MPPT controller
- Voltage loop controller
- SOGI-PLL phase-locked loop
- Feedforward controller
- Current loop controller

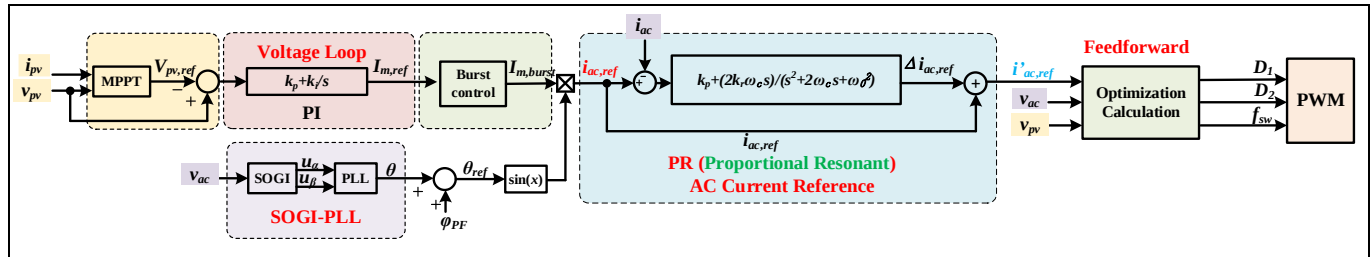

**Figure 66 Overall control framework**

The current control loop is based on a proportional resonant (PR) controller, which has a particular type of transfer function often used for the closed-loop control of systems with a sinusoidal behavior that includes both a proportional and a resonant term, which can be tuned independently.

Second-order Generalized Integrators (SOGI) for line frequency and phase synchronization in grid-tied inverters. The control structure of the SOGI-PLL is as follows:

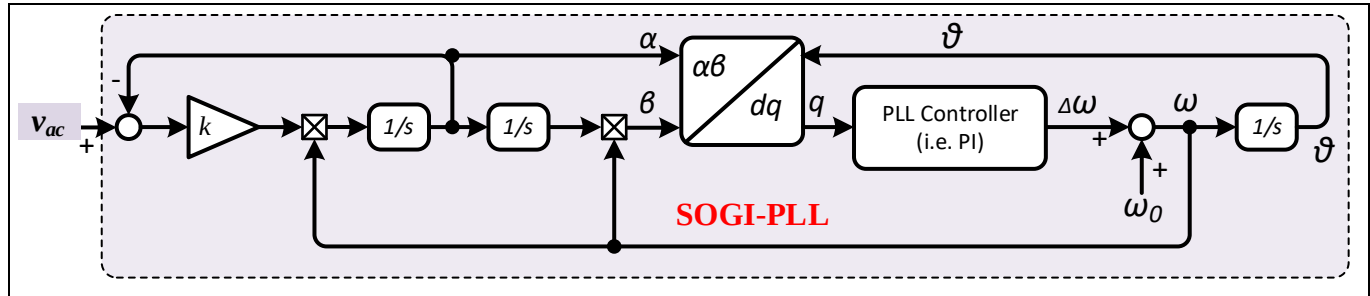

**Figure 67 SOGI-PLL block diagram**

The SOGI structure is composed of two filter types; first, a band-pass filter with zero-phase delay at the fundamental frequency for estimation of the AC grid voltage  $v_\alpha$  and secondly, a low pass filter with  $90^\circ$  phase delay to create a quadrature-shifted signal  $v_\beta$ . This enables the dq voltage signals to be calculated using the Park transform to provide inputs to a PI loop for PLL implementation.

### 5.7.1 MPPT control

The MPPT controller samples the PV terminal voltage  $v_{PV}$  and the PV output current  $i_{PV}$  at a sampling rate of 10 Hz, to provide average values with the ripple components averaged out. An incremental conductance algorithm is then used to generate the MPP reference voltage  $V_{pv,ref}$ . The difference between  $V_{pv}$  and  $V_{pv,ref}$  is adjusted by the voltage loop controller to obtain the ac current magnitude reference value  $I_{m,ref}$ . The SOGI-PLL samples the AC voltage  $V_{ac}$  and generates the AC voltage phase angle  $\theta$ . The combination of  $I_{m,ref}$ ,  $\theta$  and the given power factor angle  $\phi_{PF}$  gives the AC current reference  $i_{g,ref}$ .

## 5 Hardware functional description

### 5.7.2 Feedforward control

The feedforward controller is used to improve the response speed of the microinverter, to extend the ZVS soft-switching range and to reduce the RMS resonant current. The switching frequency  $f_{sw}$ , inner phase shift angle  $D_1$  and outer phase shift angle  $D_2$  can then be calculated by the feedforward controller and current close-loop controller.

### 5.7.3 Burst mode control

To achieve ZVS variable switching frequency modulation is adopted. Generally, the switching frequency increases at lighter loads, which leads to higher turn-off losses. Moreover, considering the maximum frequency boundary, a hard switching condition is also possible resulting in efficiency reduction under light load conditions. To mitigate this, burst mode operation is introduced.

When burst mode is enabled, it operates when the power transfer is below a defined threshold of around 200 W and the power factor is unity. In burst mode, the inverter is periodically enabled and disabled at the grid AC voltage zero crossing point. When the inverter is disabled, there is no output current and energy is stored in the electrolytic capacitors. The inverter remains in an energy storage period for a number of AC grid voltage cycles,  $N_{off}$ . During the burst period, a burst current  $I_B$  is transferred to the grid in accordance with the energy stored in the input capacitors during the previous energy storage period. The inverter operates in the burst period for a number of AC grid voltage cycles,  $N_{on}$ . To transfer the same power the output current  $I_B$  must be greater than the output current during continuous mode  $I_{ref}$ .

Usually, the relationship of  $I_B$  and  $I_{ref}$  is:

$$I_B = \frac{N_{on} + N_{off}}{N_{on}} I_{ref}$$

$$I_{ref} = \frac{P_o}{V_{ac,rms}}$$

**Equation 42**

$N_{on}$  is set to 1 (representing one complete AC grid cycle, i.e., two half cycles).

The burst mode current threshold  $I_{th}$  is defined as:

$$I_{th} = \frac{P_{th}}{V_{ac,rms}}$$

**Equation 43**


$N_{off}$  can be any integer value; 1, 2, 3, etc. As the output power drops,  $N_{off}$  increases to maintain  $I_B > I_{th}$ .

$$I_B = (1 + N_{off}) I_{ref} > I_{th} \rightarrow 1 + N_{off} = \left\lceil \frac{I_{th}}{I_{ref}} \right\rceil (\text{Round up}) = \left\lceil \frac{I_{th}}{I_{ref}} \right\rceil + 1$$

**Equation 44**

## 5 Hardware functional description

The following diagram provides an illustration of equal power transfer in normal (continuous) operation where  $I_B = I_{ref}$  and burst mode where  $I_B = 2 \times I_{ref}$  and  $N_{off} = 1$ .

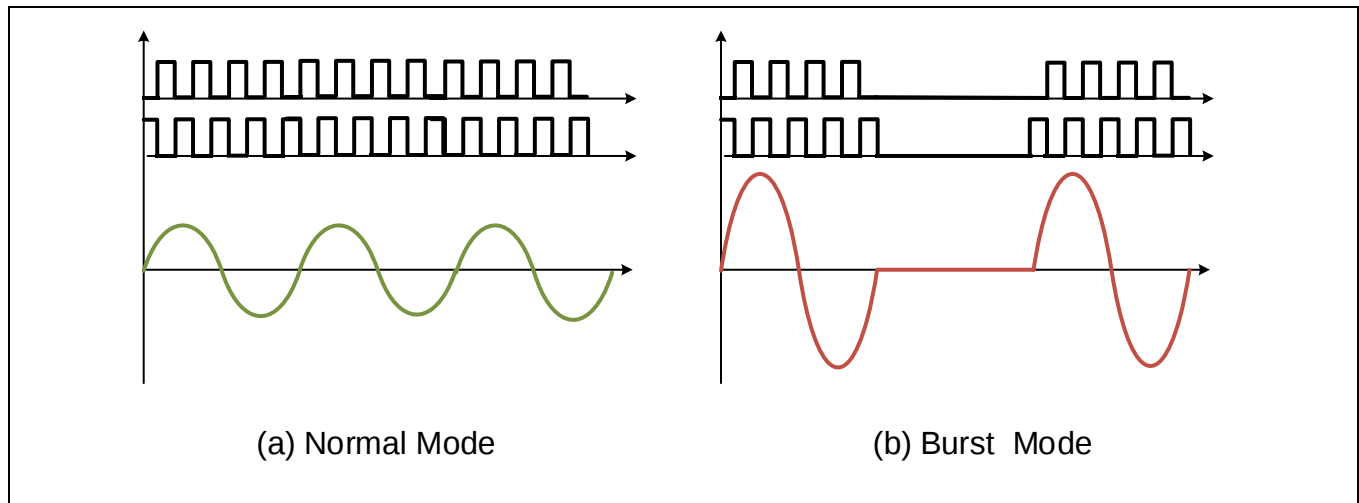

**Figure 68** Normal (continuous current) mode and burst mode operation


Note that the efficiency measurement during burst mode is more challenging since the RMS current is not so easy to measure. A normal measurement even where the current is averaged over many samples may not provide an accurate result. This can be done only by determining the RMS current in a continuous state where the peak is equal to the peak in burst mode and then multiplying this current by  $N_{on}/(N_{on}+N_{off})$  to obtain a true average RMS. For example, in the case shown in the above figure, the current would need to be set to twice the value in continuous mode to reach the same peak value as in burst mode. The RMS value could then be measured and divided by 2 to provide a result to use in calculating the true output power.

## 5 Hardware functional description

### 5.8 Firmware implementation

#### 5.8.1 Overview

The firmware is built on the Eclipse IDE for ModusToolbox™. The *main.c* file is located in the project root directory with the header and other source files in the Source folder. The main function includes calls to the board and solution files that implement the system framework along with slow background tasks. The firmware structure uses multiple events triggered interrupts to execute control algorithms, communication, input sampling, status checks, fault protection, and other functions. A high-level flow chart is shown here:

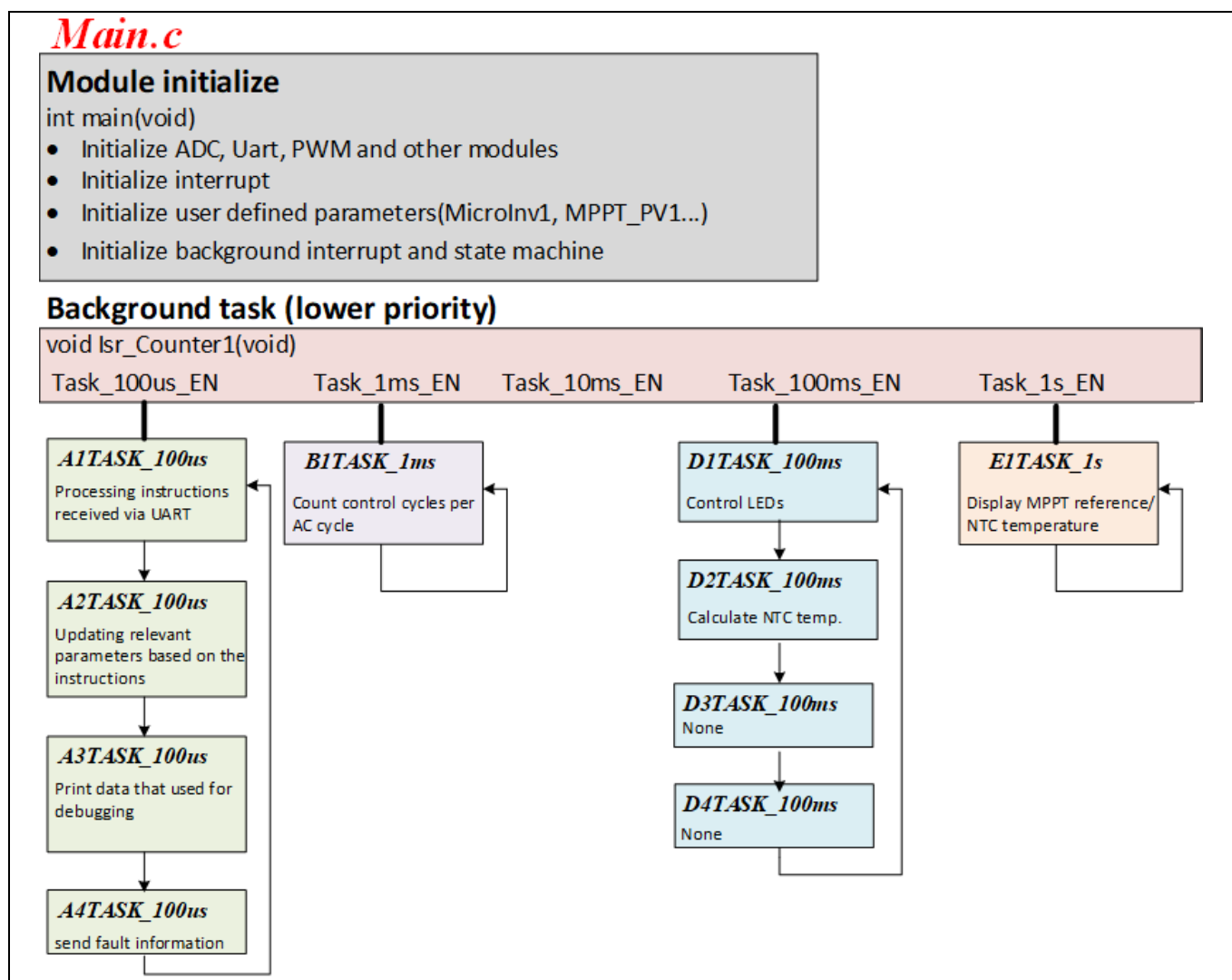

**Figure 69 Main functions**

The following table details the source and header files related to the different functions and peripherals.

**Table 8 Source and header files**


| Source file | Header file | Functions supported                                                             |
|-------------|-------------|---------------------------------------------------------------------------------|
| GlobalDef.c | GlobalDef.h | Macro and structure definitions                                                 |
| adc.c       | adc.h       | Initialization and data processing functions related to the ADC sampling module |

## 5 Hardware functional description

| Source file       | Header file       | Functions supported                                                                                                                                                            |
|-------------------|-------------------|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| User_gpio.c       | User_gpio.h       | I/O related initialization functions                                                                                                                                           |
| User_pwm.c        | User_pwm.h        | PWM module initialization                                                                                                                                                      |
| User_uart.c       | User_uart.h       | UART communication-related initialization functions                                                                                                                            |
| User_closetloop.c | User_closetloop.h | Control algorithms used in closed-loop operations                                                                                                                              |
| User_init.c       | User_init.h       | Main control variable initialization                                                                                                                                           |
| User_ISR.c        | User_ISR.h        | Interrupt service routines (ISRs) for ADC, PWM, GPIO, UART etc.                                                                                                                |
| User_MPPT.c       | User_PV.h         | Maximum Power Point Tracking (MPPT) functions                                                                                                                                  |
| User_sogi.c       | User_sogi.h       | SOGI-PLL phase-locked loop control                                                                                                                                             |
| User_control.c    | User_control.h    | Main control code for the microinverter, including state machines for various operational modes, phase angle and frequency calculations, PWM control, fault handling, and more |

### 5.8.2 Main.c and background tasks

The int main(void) function calls initialization functions such as cybsp\_init(), User\_uart\_init(), and variable initialization functions such as Inverter\_Init(). It enables the main loop and continuously calls (\*Task\_State\_Ptr()) in the for(;;) infinite loop to poll five classes of time-multiplexed background functions from A0 to E0:

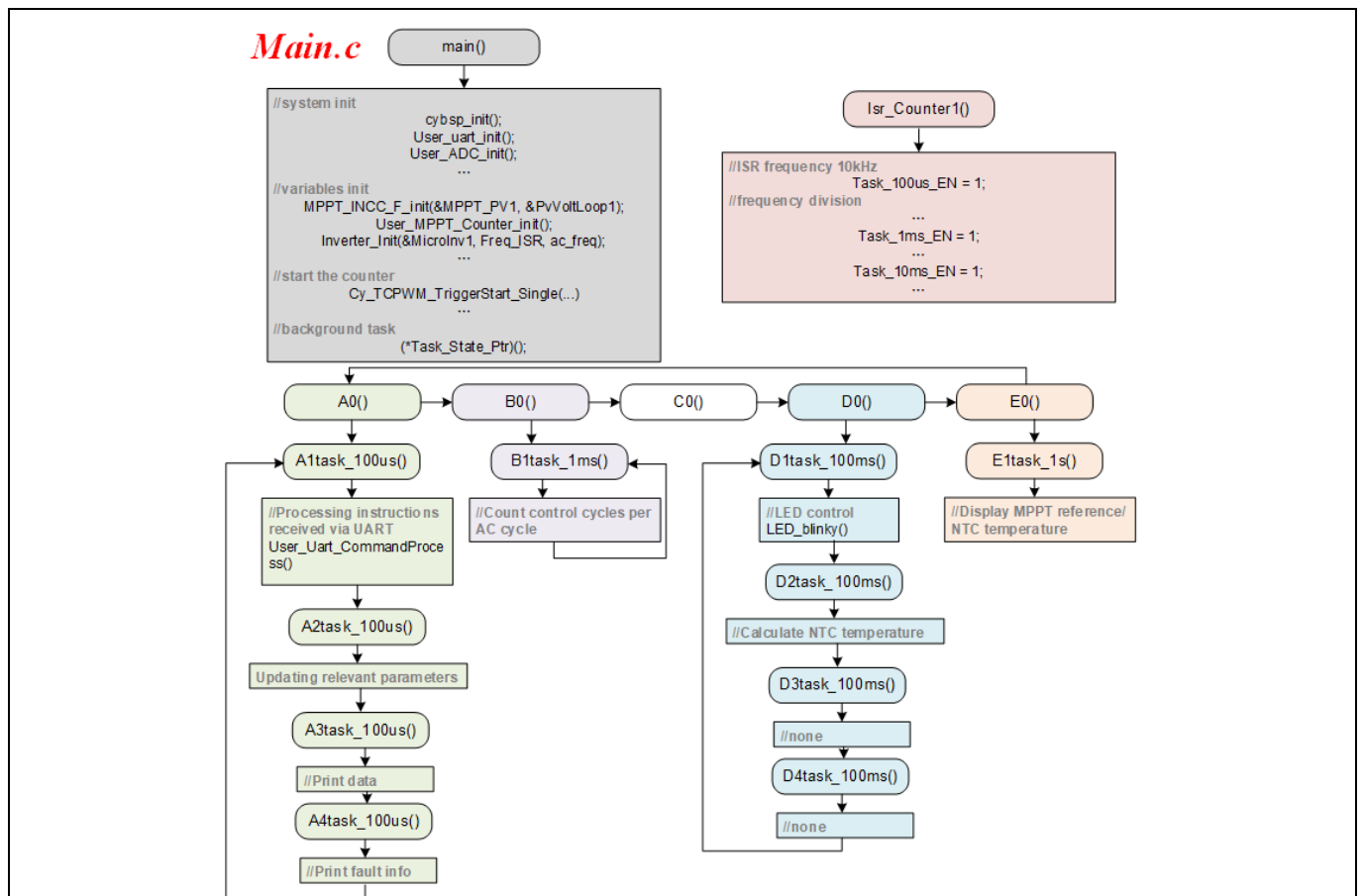

**Figure 70** Main loop and timer driven processes


## 5 Hardware functional description

Additionally, there are five flags used to determine whether the background functions are executed: Task\_100us\_EN, Task\_1ms\_EN, etc. These flags are modified by the 10 kHz always-on interrupt program ISR\_Counter. When a flag is activated, the corresponding background task is executed, such as A1task\_100us(), A2task\_100us(), etc., up to E1task\_1s(). For example, the ISR\_Counter interrupt function sets Task\_100us\_EN to 1, and (\*Task\_State\_Ptr)() checks Task\_100us\_EN in A0(void) before executing (\*A\_Task\_Ptr)(). Initially, A\_Task\_Ptr points to A1TASK\_100us, and after executing this task, it points to A2TASK\_100us, and so on in a loop.

Background tasks are executed in the for(;;) infinite loop in main(), and these tasks can be interrupted by other interrupt handling functions, having the lowest priority, making them suitable for handling tasks with lower real-time requirements. In this project, Atask is used to respond to communication commands; Btask calculates how many control cycles are contained in a single AC cycle based on the phase-locked loop frequency; Dtask controls the LED and calculates NTC temperature; and Etask is responsible for sending MPPT reference voltage and temperature.

### 5.8.3 Control ISR


The REF\_500W\_CYCLO\_BDSGAN system has three control variables: inner and outer phase angles, and switching frequency, which are related to input and output voltage, power, grid phase, and other parameters. The Control ISR function is responsible for controlling the microinverter's operating state, calculating each control variable, and generating the appropriate PWM signals as illustrated below. The Control ISR has the highest control priority in the program.

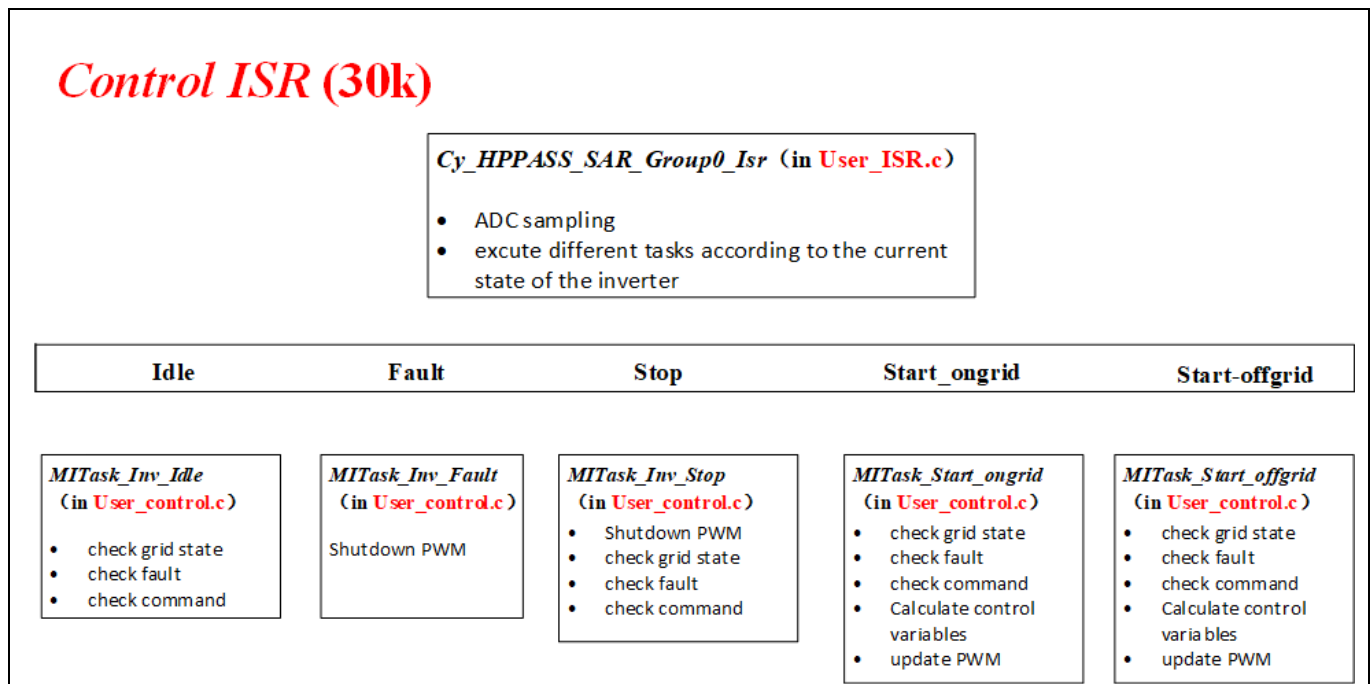

**Figure 71 Control ISR operations**

## 5 Hardware functional description

In this program, the entry point for the Control ISR is the ADC interrupt handling function `Cy_HPPASS_SAR_Group0_Isr`, located in `User_ISR.c`. The ADC is triggered by a 30kHz frequency `PWM_Tri_ADC`, and when sampling is complete, it triggers an interrupt then jumps to `Cy_HPPASS_SAR_Group0_Isr`. The flowchart for this process is as follows:

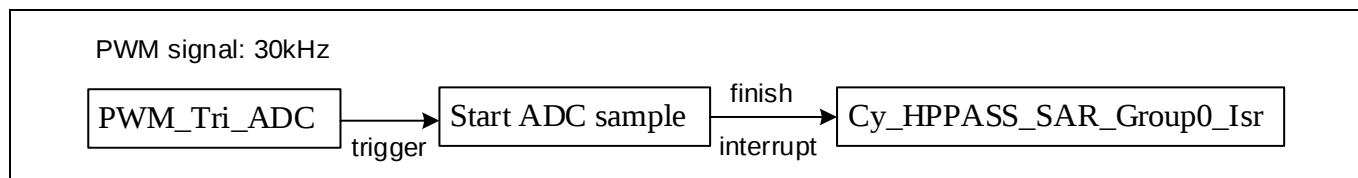

**Figure 72 30 kHz process flow**

`Cy_HPPASS_SAR_Group0_Isr()` first processes the ADC sampling data, converting the register values into actual sampled values. The system operates in the following states:


**Table 9 System states**

| State                      | Description                                                                    |
|----------------------------|--------------------------------------------------------------------------------|
| <code>Inv_Idle</code>      | Idle state, waiting for user commands                                          |
| <code>Inv_Fault</code>     | The unit has detected a fault and shut down, waiting for clear and reset       |
| <code>User_stop</code>     | The inverter is stopped by user command, waiting for re-start or reset command |
| <code>Start_ongrid</code>  | Grid tied operation, the inverter is running                                   |
| <code>Start_offgrid</code> | Off-grid operation, the inverter is running                                    |

After obtaining the corresponding sampled data, the control program jumps to execute different tasks based on the current inverter state. The functions for this part of the task are located in `User_control.c`.

`Inv_Idle` is the initial state after the processor powers on, during which all PWM signals are locked, and the converter stops running. The function executed in the `Inv_Idle` state is `MITask_Inv_Idle()`. In the idle state, it checks the grid status, fault status, and user commands. The grid status can be `Grid_Undefined`, `Grid_Ongrid`, or `Grid_Offgrid`. In the grid-connected operating state, the program detects the AC voltage at the port and closes the relay at the appropriate time; in the off-grid state, the relay only closes when there is no voltage at the port. The flow diagram for `MITask_Inv_Idle()` is shown in the following figure. In the idle state, the program may enter the `Start_ongrid` or `Start_offgrid` state based on control commands. If a fault is confirmed, it will also enter the `Inv_Fault` state.

## 5 Hardware functional description

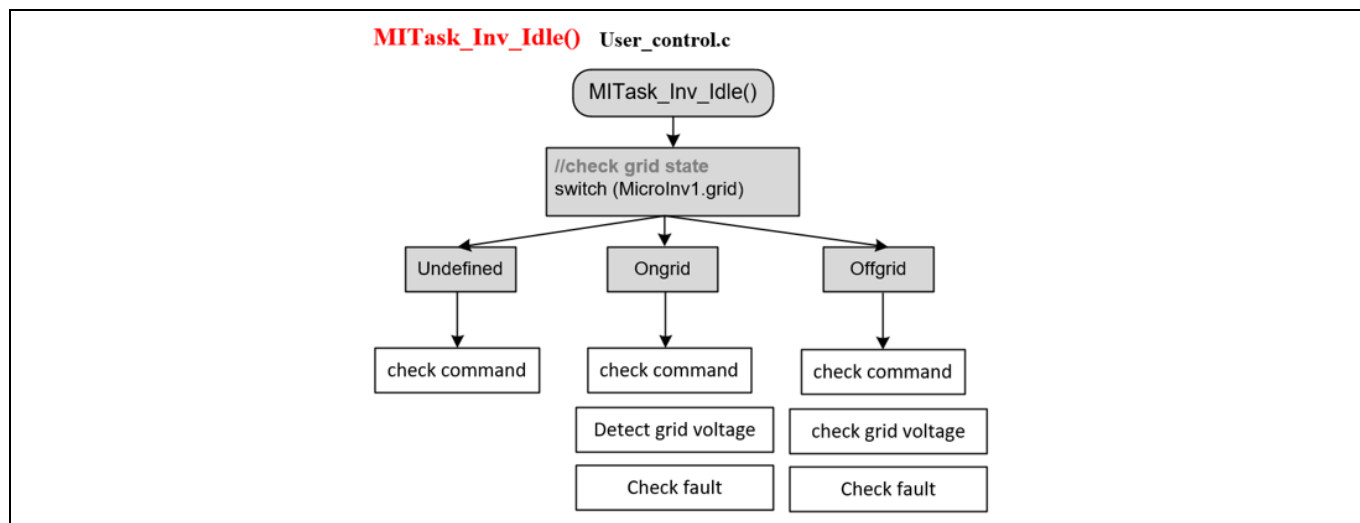


**Figure 73 Initial idle state**

When the program receives a power-on command, it can enter the Start\_ongrid or Start\_offgrid state based on the grid status control command, executing MITask\_Start\_ongrid() and MITask\_Start\_offgrid(), respectively, and the inverter begins to operate.

In the Start\_ongrid state, the function executed is MITask\_Start\_ongrid(), corresponding to the flow diagram shown in the following figure.


First, the program executes the SOGI PLL phase-locked loop to synchronize with the grid voltage. It then checks for faults or whether a shutdown command has been received; if so, it executes specific procedures to shut down; otherwise, it continues to execute Control\_OpenloopCalc\_Ongrid() to calculate the inner and outer phase angles and switching frequency.

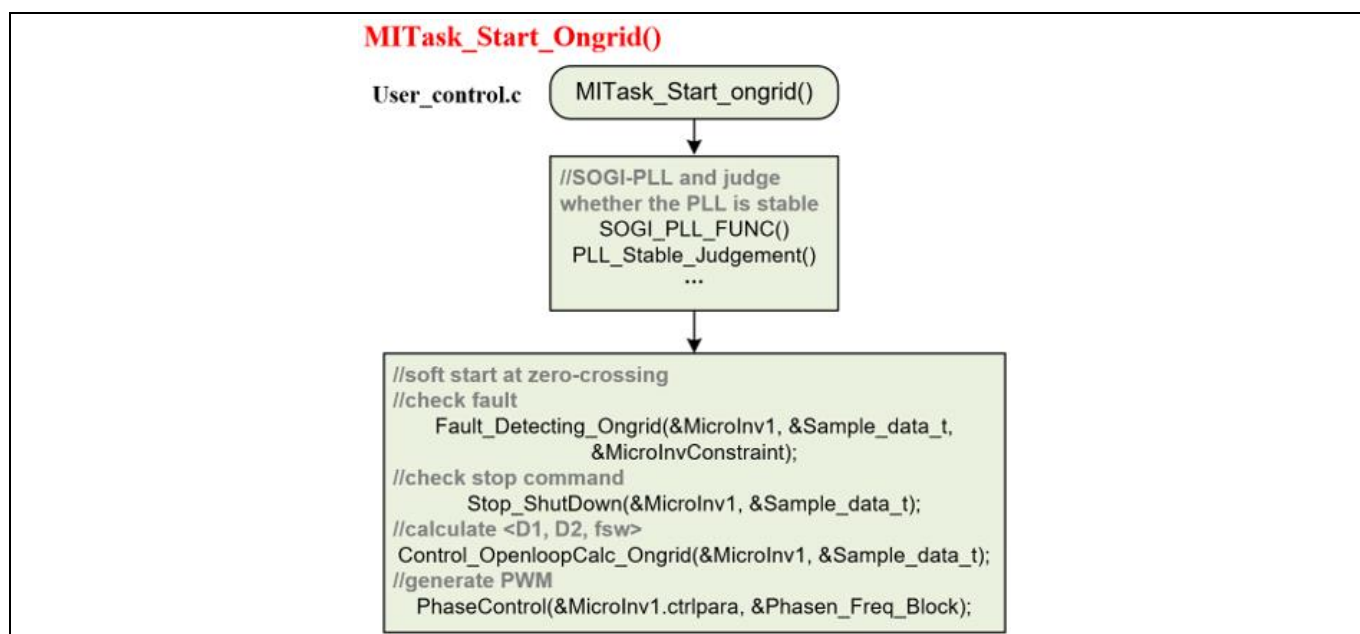

**Figure 74 Connect to the grid**

## 5 Hardware functional description

Control\_OpenloopCalc\_Ongrid() is used to calculate the inner and outer phase angles, as shown in the following flow diagram.

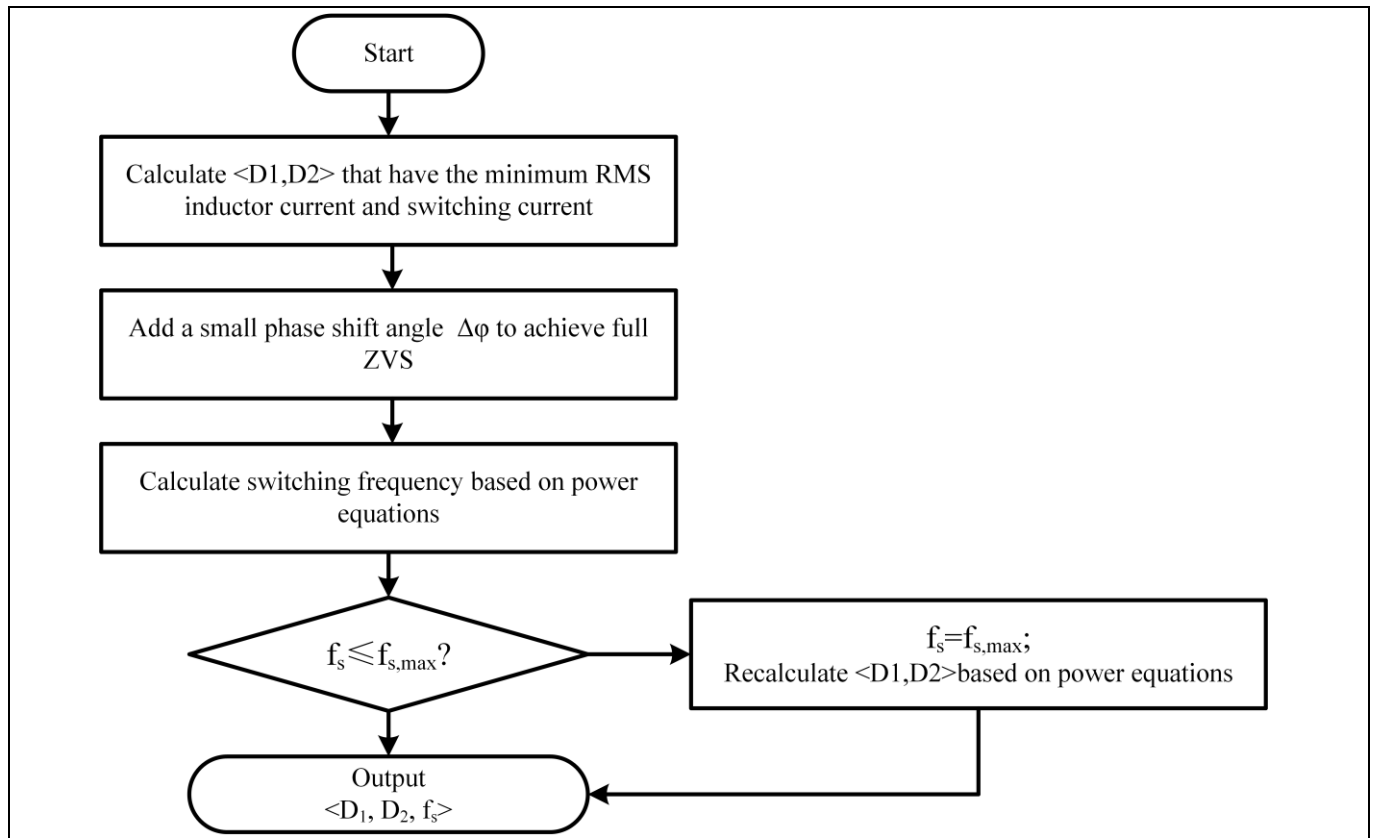

**Figure 75** Calculating the inner and outer phase angles

PhaseControl() is responsible for generating PWM control signals. To generate the PWM signals for each switch, the comparison values 1 and 2 of the PWM module must be correctly configured, as shown in the following figure. For example, the comparison values 1 and 2 for the driving signal S1 should be:

$$0.5D\_1 \times PRD^1$$

**Equation 45**

and


$$(0.5 - 0.5D\_1) \times PRD$$

**Equation 46**

respectively.


<sup>1</sup> PRD refers to the PWM cycle period, which defines the switching frequency.

## 5 Hardware functional description

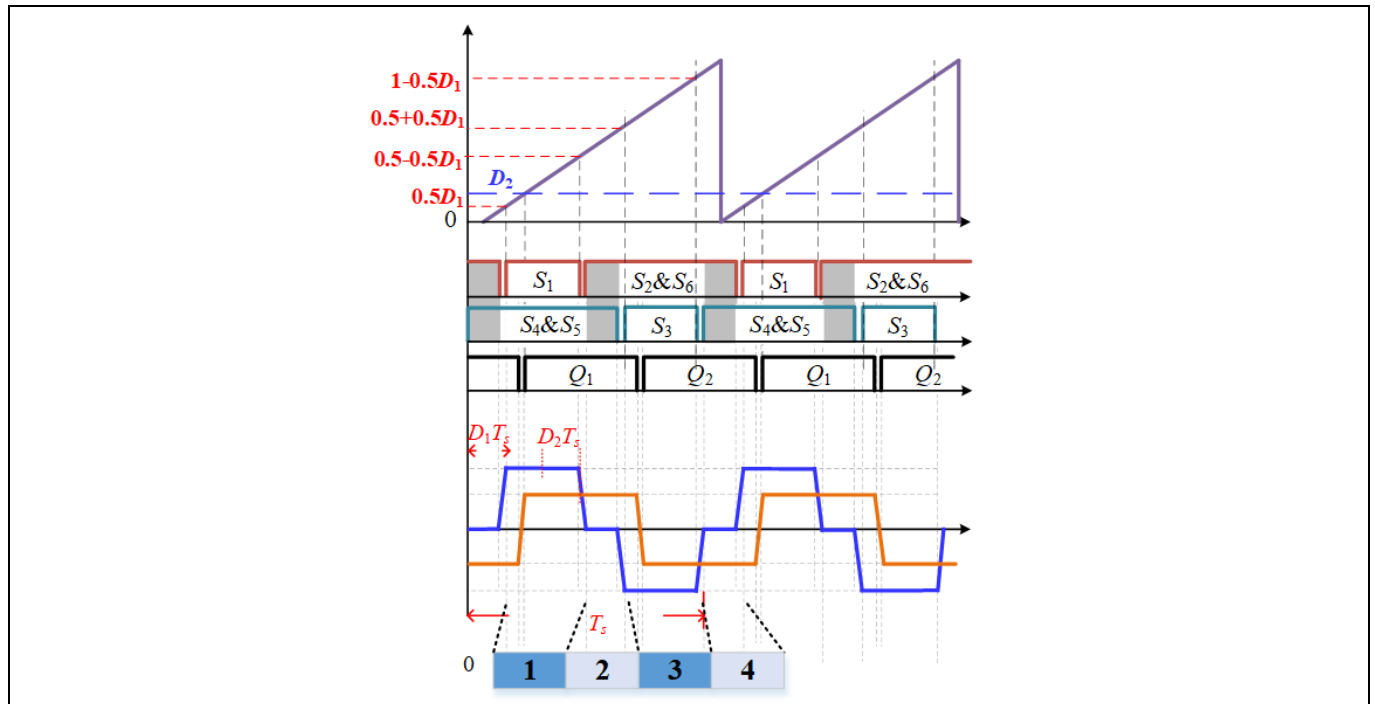

**Figure 76** PWM encoding scheme

In the Start\_offgrid state, the function executed is MITask\_Start\_offgrid(). In off-grid mode, there is no phase-locked loop; the grid phase is generated directly by the program, and the grid voltage is derived through PR closed-loop calculations. The system control flowchart under both grid-connected and off-grid conditions is shown in the following figure. The closed-loop programs for grid-connected and off-grid conditions are GridON\_CurrentCloseLoop() and GridOFF\_VoltageCloseLoop().

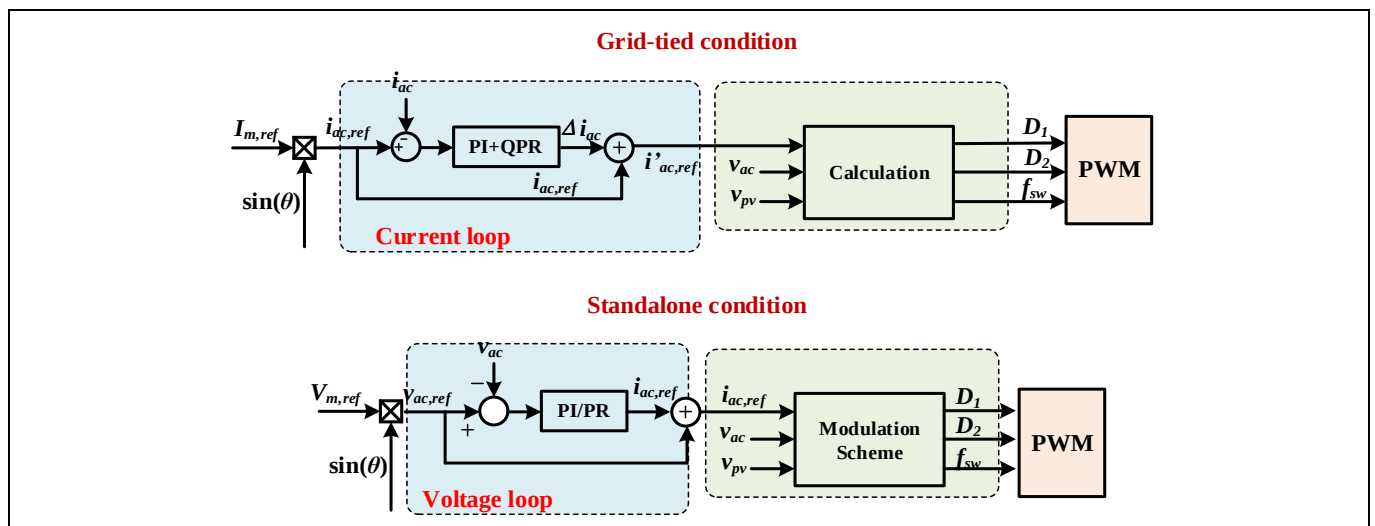

**Figure 77** Control loop structures for grid tied and standalone operating modes

During the inverter's operation, when the processor receives a STOP command, it will execute Stop\_ShutDown() to shut down the inverter. Although all switches in the primary side full-bridge circuit can be directly locked, due to the microinverter's secondary side having two sets of bidirectional switches, all switches cannot be locked directly; otherwise, the transformer current will lose its freewheeling path, resulting in high voltage across the switches, potentially damaging them.


## 5 Hardware functional description

Following the fault isolation method of a half-bridge DAB, the difference is that the common and cutoff switches on the secondary side need to switch logic based on the polarity of the grid voltage.

When the grid voltage is positive, lock the primary switches S1-S4, lock the secondary switches S6 and S8, and keep S5 and S7 conducting. After two control cycles, lock S5 and S7.

When the grid voltage is negative, lock the primary switches S1-S4, lock the secondary switches S5 and S7, and keep S6 and S8 conducting. After two control cycles, lock S6 and S8.

The flowchart for Stop\_ShutDown() is shown in the following figure. After executing the shutdown command, the converter state will switch to User\_stop.

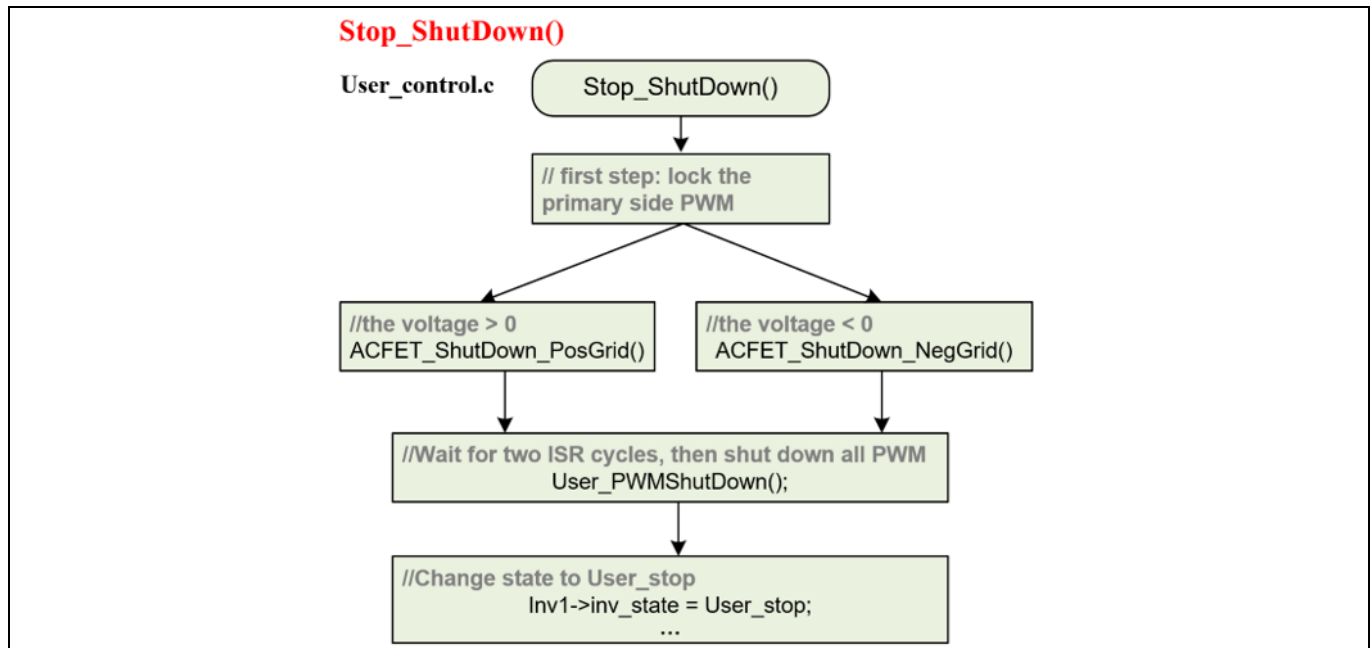

**Figure 78 Inverter stop and shutdown functions**

During the inverter's operation, when a fault is detected, the program will execute **Fault\_ShutDown()** to shut down the inverter, and the locking process is consistent with the method described above. After executing the shutdown command, the converter state will switch to **Inv\_Fault**.

In the **User\_stop** state, the function executed is **MITask\_User\_stop()**. In this state, the inverter stops running, but upon receiving a **Start** command, it will re-enter the **Start\_ongrid** or **Start\_offgrid** state based on the grid status and execute the relevant commands.


In the **Inv\_Fault** state, the function executed is **MITask\_Inv\_Fault()**. In this state, the inverter stops running, and upon receiving a **Start** command, it will not restart the inverter. The user must send the fault clearance command **FaultClear@** before the controller allows the inverter to restart.

## 5 Hardware functional description

### 5.8.4 MPPT

The inverter has MPPT functionality based on an incremental conductance algorithm, which detects the slope of the P–V curve. The maximum power point is tracked using the instantaneous conductance  $I/V$  and the incremental conductance  $dI/dV$ . Depending on the relationship between the two values, the location of the operating point of the PV module in the P–V curve can be determined. The MPPT function is disabled by default and can be enabled by the user by sending the appropriate command through the serial interface. This is most easily done via the GUI tool.

The flow diagram for the MPPT function is shown in the following figure. In the program, the clock interrupt frequency of Timer\_MPPT is configured to 480 Hz, with the interrupt handling function being ISR\_MPPT\_Task(). In ISR\_MPPT\_Task(), the program calls MPPT\_PVVolCheck() to check if the photovoltaic voltage is within the normal range and gradually updates the MPPT voltage setpoint through MPPT\_SoftStart(). Every 60 Hz, the MPPT\_PowerAvgCalc() function is executed to calculate the average voltage and current values. The MPPT algorithm MPPT\_INCC\_F\_FUNC() is executed at a frequency of 2 Hz, and the voltage reference value modified by MPPT\_SoftStart() is passed to the control program Control\_OpenloopCalc\_Ongrid() located in *User\_control.c*, which updates the current reference value through Control\_PvVoltLoop().

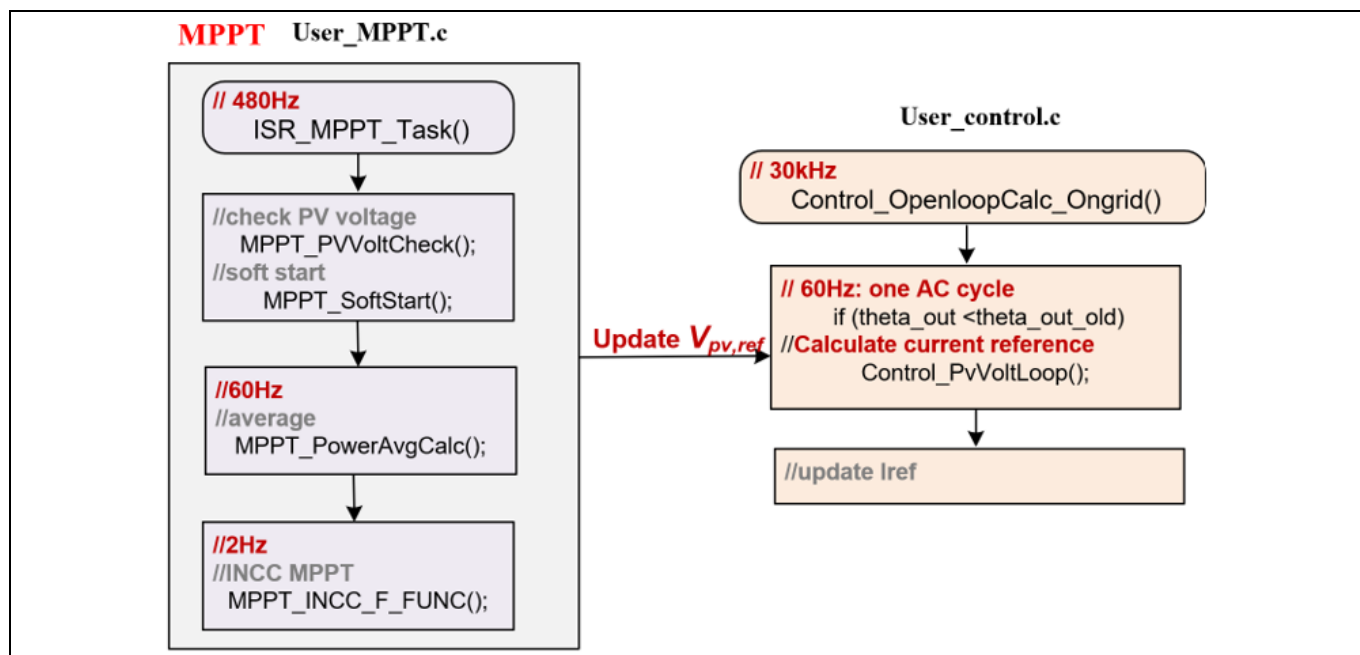


**Figure 79** MPPT functions

### 5.8.5 Communication and command set

The UART function is configured in the program to realize the communication between the host computer and the converter. The flow diagram of the UART-related function and the program related to receiving commands is shown in the following figure. After receiving the command, UART\_Interrupt\_Callback() will take out the characters from the buffer, where @ is the command end identifier. After receiving a command, the function User\_Uart\_CommandProcess will be called in A1TASK\_us() in the background function to process the received command.

The main command instructions and their related functions are shown in [Table 10](#).

## 5 Hardware functional description

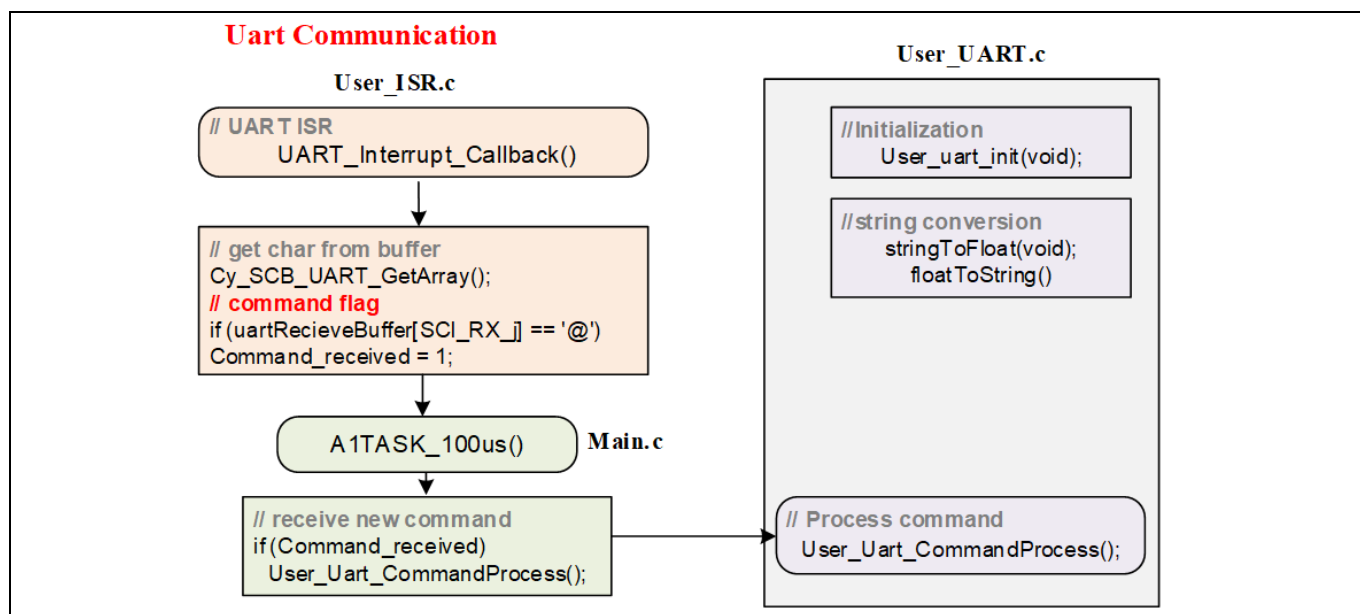

**Figure 80** Communication functions

**Table 10** System command set

| No. | Command           | Description                                                                                                          |
|-----|-------------------|----------------------------------------------------------------------------------------------------------------------|
| 1   | Grid_On@          | Set the converter to grid-connected mode                                                                             |
| 2   | Grid_Off@         | Set the converter to off-grid mode                                                                                   |
| 3   | Start@            | Start the converter                                                                                                  |
| 4   | Stop@             | Stop the converter                                                                                                   |
| 5   | Reset@            | Reset converter parameters                                                                                           |
| 6   | FaultClear@       | Clear fault flag                                                                                                     |
| 7   | VmoffX@           | Set the off-grid output voltage amplitude to X. For example, Vmoff340@: Set the grid voltage amplitude to 340 V      |
| 8   | ImonX@            | Set the grid-connected output current amplitude to X. For example, Imon2.5@: Set the grid current amplitude to 2.5 A |
| 9   | PFonY@            | Set the grid-connected power factor to Y. For example, PFon0.8@: Set the grid power factor to 0.8                    |
| 10  | BMEN@/ BMDS@      | Enable/Disable Burst mode                                                                                            |
| 11  | MPPTEN@/ MPPTDIS@ | Enable/Disable MPPT function                                                                                         |

### 5.8.6 Protection

The protection logic framework in the program is shown in the following figure. The output current and transformer current are integrated with hardware detection protection circuits, and if their values exceed the normal range, they will trigger IO interrupts to set the corresponding fault flags high. The program also includes software protection, which evaluates ADC sampling values; if they exceed the normal range, the relevant fault flags will also be set high. Upon detecting hardware or software faults, the program will execute `Fault_ShutDown()` to shut down the inverter.

## 5 Hardware functional description

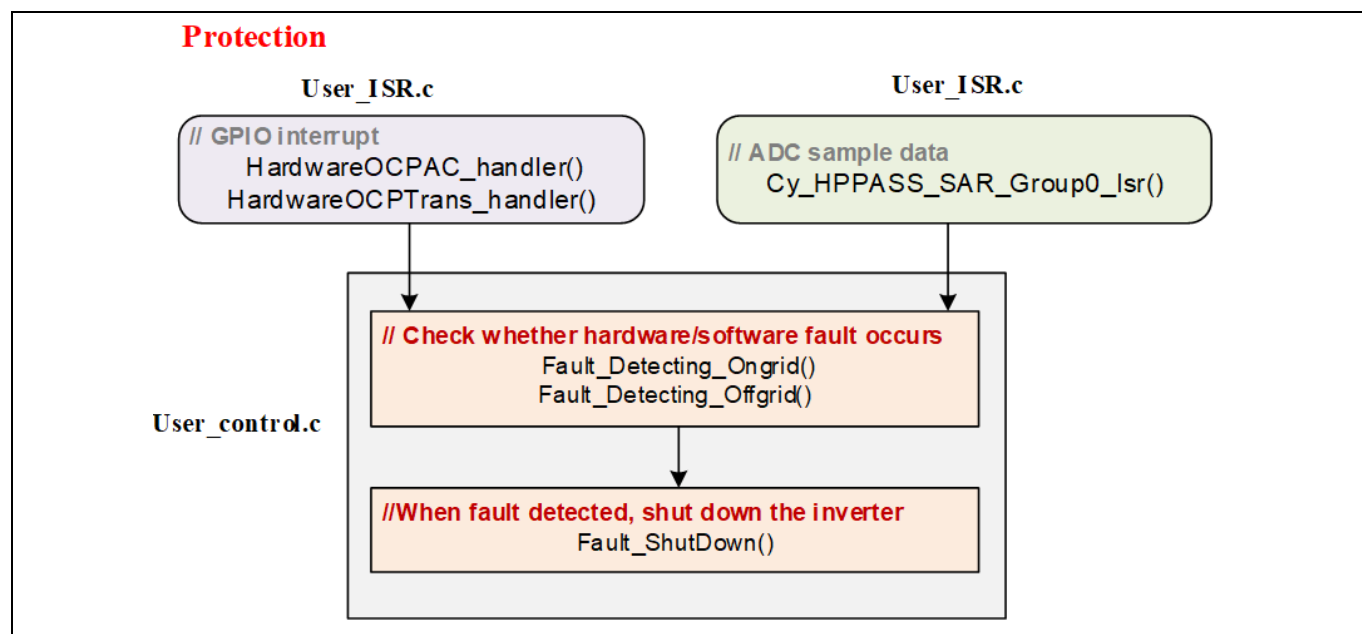


Figure 81 Protection functions


## 6 Test setup

## 6 Test setup

### 6.1 Connections used for all tests

The REF\_500W\_CYCLO\_BDSGAN board can be operated with a 24 V auxiliary power supply. This is recommended for initial tests and functionality checking where the unit may be operated from a very low DC input voltage (e.g., 5 V input with 30 V<sub>RMS</sub> output setting).

For operation within the normal input range defined in Table 1, the 24 V supply is derived from the input via an on-board DC-DC converter. In this case the jumper JP1 should be connected between pins 2 and 3.

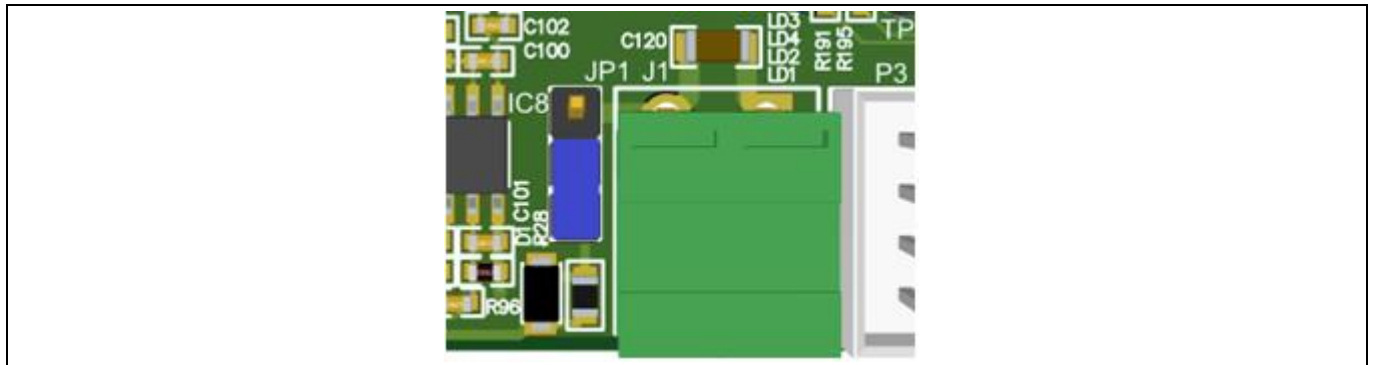


**Figure 82** Operation with on-board 24 V auxiliary power

**Attention:** *When carrying out efficiency measurements, the unit should be operated as described above and not with an external 24 V auxiliary supply.*

A power analyzer with a 64-sample averaging function was used for all efficiency measurements.

#### 6.1.1 Auxiliary supply connections

A 24 V auxiliary power supply may be connected to J1 as shown in the following figure with positive at pin 2 and negative/GND at pin 1. Connection is made via a plug-in terminal block J1a. The jumper JP1 should be connected between pins 1 and 2 for auxiliary power operation and between pins 2 and 3 to operate directly from the main DC input.

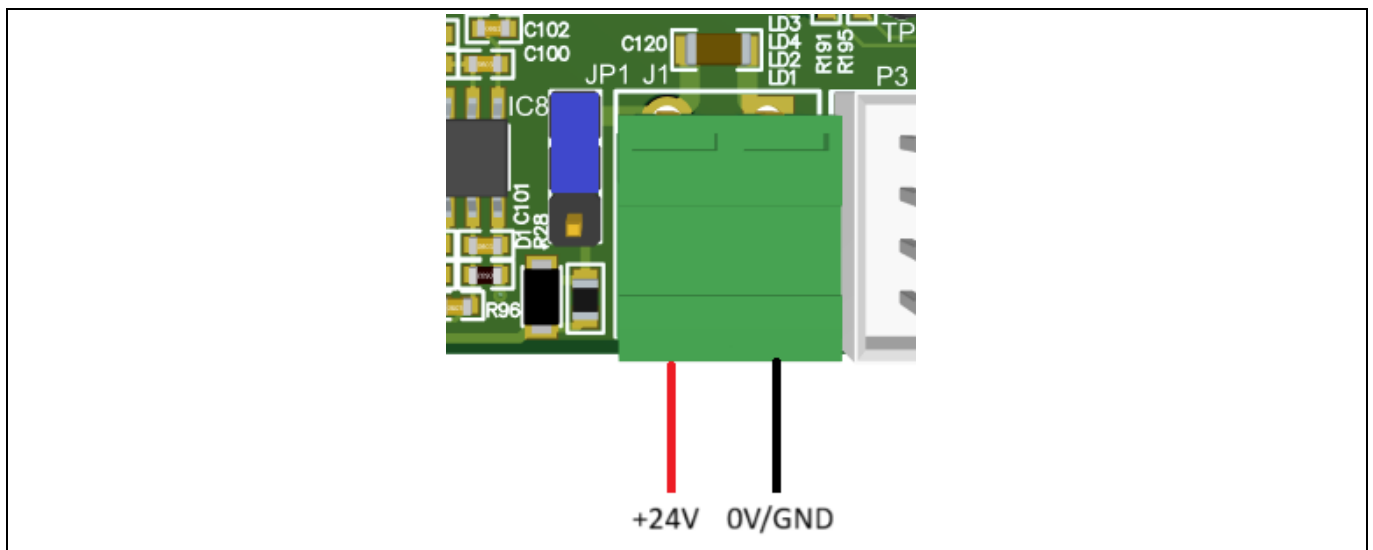

**Figure 83** 24 V auxiliary power connections and jumper setting

## 6 Test setup


### 6.1.2 Connecting to the PC and GUI

The REF\_500W\_CYCLO\_BDSGAN board requires the PC-based GUI for operation. This is connected via the UART1 port, which is connected to a PC via a serial interface. The serial interface may be tested with the auxiliary power supply connected before applying main DC (PV) input power or connecting to the AC outputs to the grid simulator. It is recommended to use an isolated USB/serial port adapter such as the Waveshare USB to RS485/RS232/TTL Converter shown here or a similar type.



**Figure 84** Isolated USB serial interface

The TTL outputs RXD, TDX, and GND can be used to connect to P1 of the board via a suitable cable. The three required connections are; transmit data (TXD), receive date (RXD) and ground.

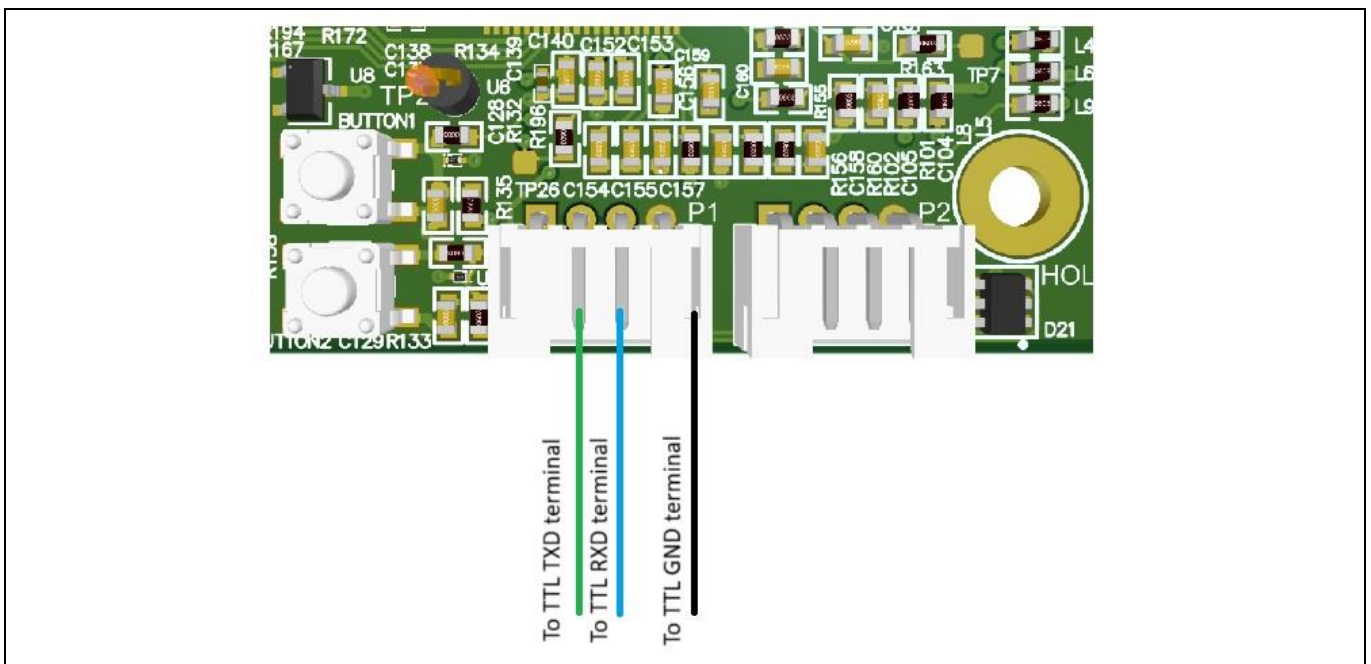

**Figure 85** Serial port connections to the REF\_500W\_CYCLO\_BDSGAN board

## 6 Test setup

*Note:* It is recommended to test the serial interface with the GUI to verify correct operation, before proceeding further.

### 6.1.3 DC input supply connections

DC input power is connected to the terminals DC+ and DC-. For correct operation it is necessary to use a cable rated to carry 20 A or more with suitable ring or U terminals.




**Figure 86** DC power connections

Additional sense leads are also attached to the terminals for voltage measurement.

### 6.2 Off-grid test setup

In off-grid mode, the cycloconverter produces a commanded constant voltage output. The output is connected to an AC electronic load, which is set to be purely resistive for testing at 100 W intervals from 100 to 500 W. Kelvin connections are required at the board terminals for accurate voltage measurement to allow accurate input and output power measurements required for efficiency calculations.

## 6 Test setup

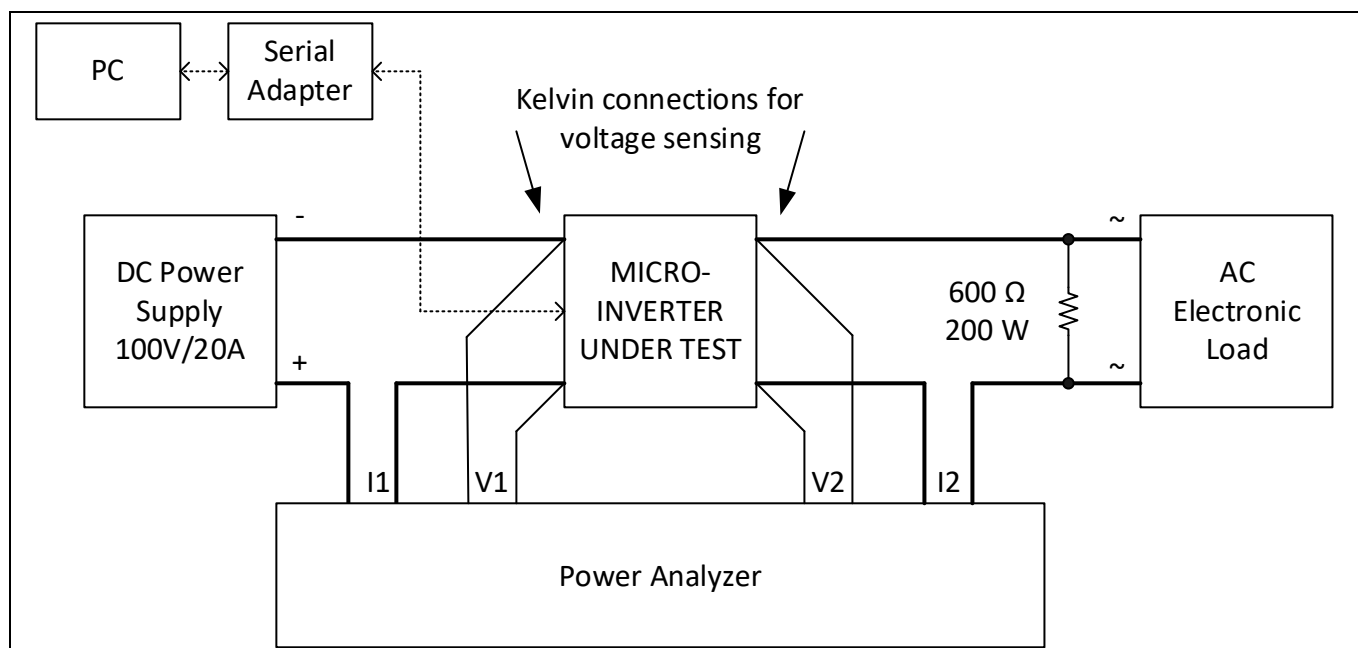

**Figure 87** Off-grid test setup

A load 600  $\Omega$  resistor is used to provide a fixed load of approximately 100 W for a 240 V<sub>RMS</sub> output. This resistor is rated at 200 W or more and is mounted to a heatsink. This resistor is necessary because the REF\_500W\_CYCLO\_BDSGAN board requires a minimum load to operate and will shut down if operated with insufficient load. Additionally, the AC electronic load requires an AC voltage to be present before it is able to apply load. It may be necessary to disable the AC electronic load's automatic bandwidth adjustment (ABA) function in order to prevent it from shutting down when load is applied. The load is set to constant resistance mode with the following resistance settings used to provide power measurements at 100 W intervals:

**Table 11** AC electronic load settings for 240 V<sub>RMS</sub> constant resistance mode with 600  $\Omega$  external pre-loading resistor

| Target power (W) | Resistance setting ( $\Omega$ ) |
|------------------|---------------------------------|
| 100              | Load OFF                        |
| 200              | 554                             |
| 300              | 282                             |
| 400              | 189                             |
| 500              | 143                             |


### 6.3 On-grid test setup

For on-grid operation, the AC outputs from the board are connected to a grid simulator able to process AC power and transfer it safely back to the actual grid while enabling the voltage to be set to a defined level and frequency. On-grid operation can be in constant current or MPPT operating modes.

## 6 Test setup

### 6.3.1 Grid simulator connections


The grid simulator is connected to the AC power terminals as follows:

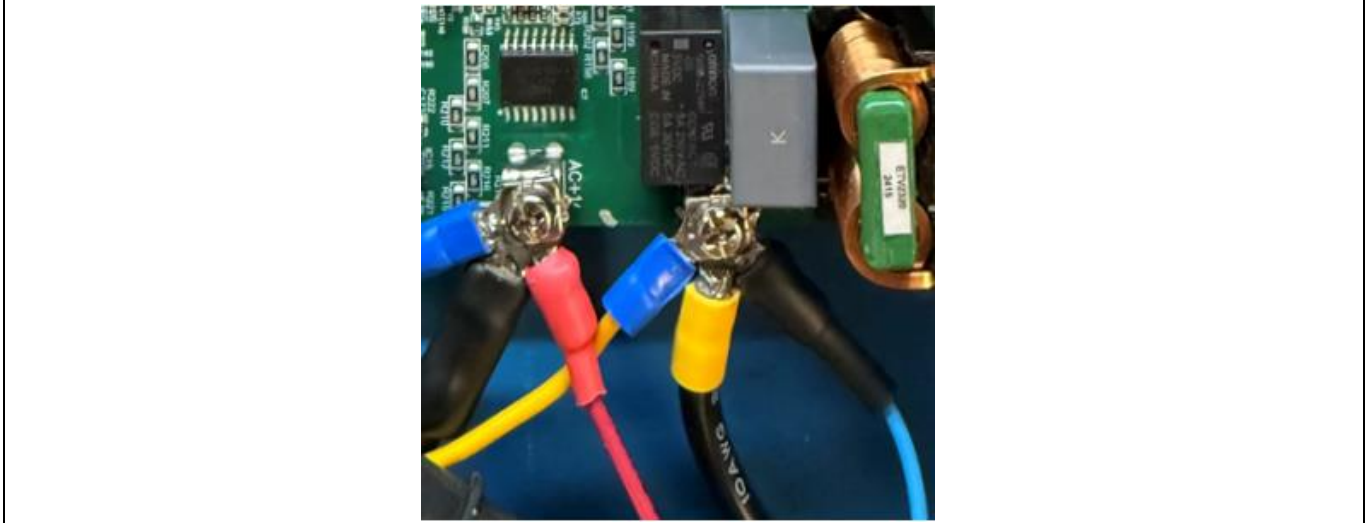

**Figure 88** AC power connections to the grid simulator

The AC cables should be rated for  $300 V_{RMS}$  and at least  $3 A_{RMS}$ . In [Figure 88](#), two additional pairs of sensing cables have been added, one is for connection to the power analyzer and the other to connect to an HV differential oscilloscope probe.

The board with all connections is shown in the following figure with a current probe connected to measure the secondary side AC current coming from the transformer. A cable loop has been added to enable connection of the current probe, which may be replaced with a jumper between the two terminals of L2 if not required.

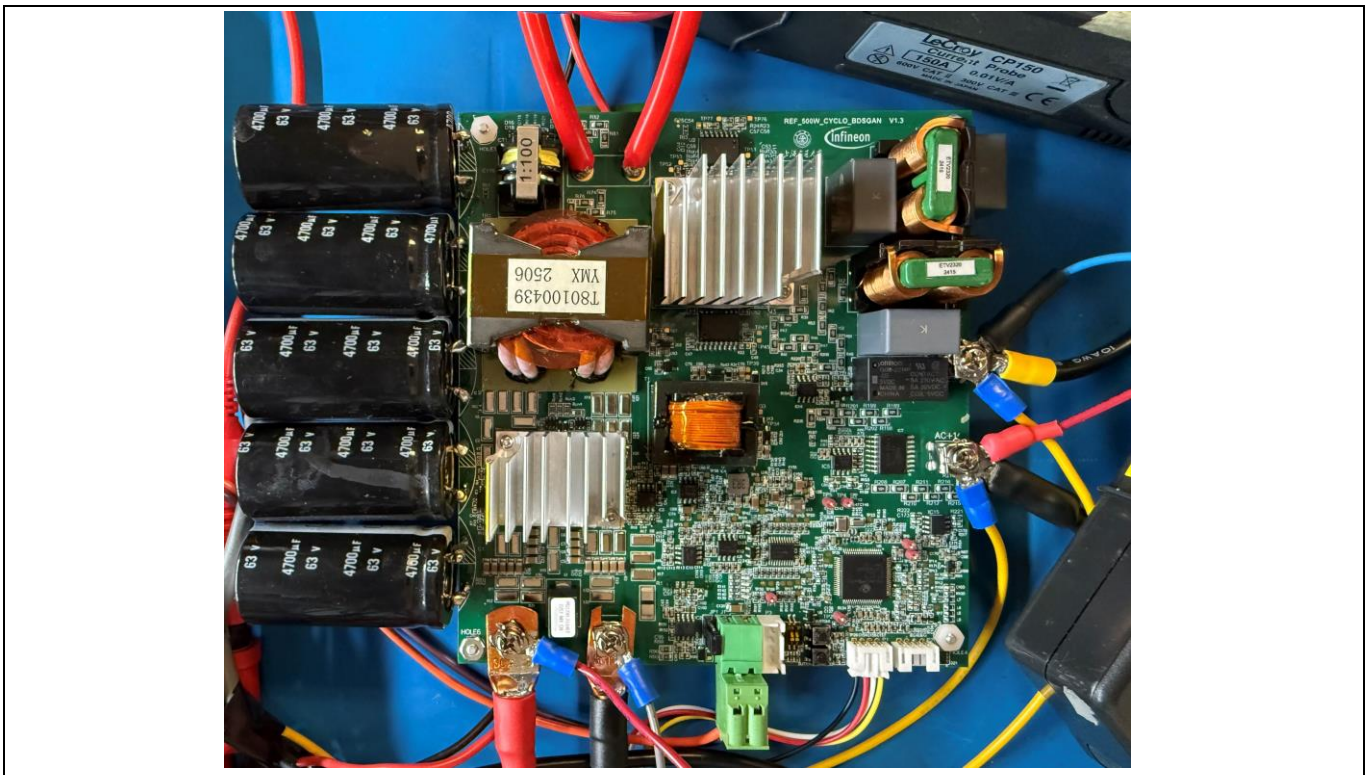


**Figure 89** REF\_500W\_CYCLO\_BDSGAN board with power and sensing connections

## 6 Test setup

### 6.3.2 Constant output current mode


The default operating mode is a constant output current mode in which the AC RMS is set to a defined level via the PC-based GUI tool. The procedure is described in Section 7. The output voltage is determined by the grid voltage and the REF\_500W\_CYCLO\_BDSGAN board operates as an AC current source to transfer the specified current onto the grid in a safe and stable manner. You can set the grid voltage and frequency via the grid simulator.

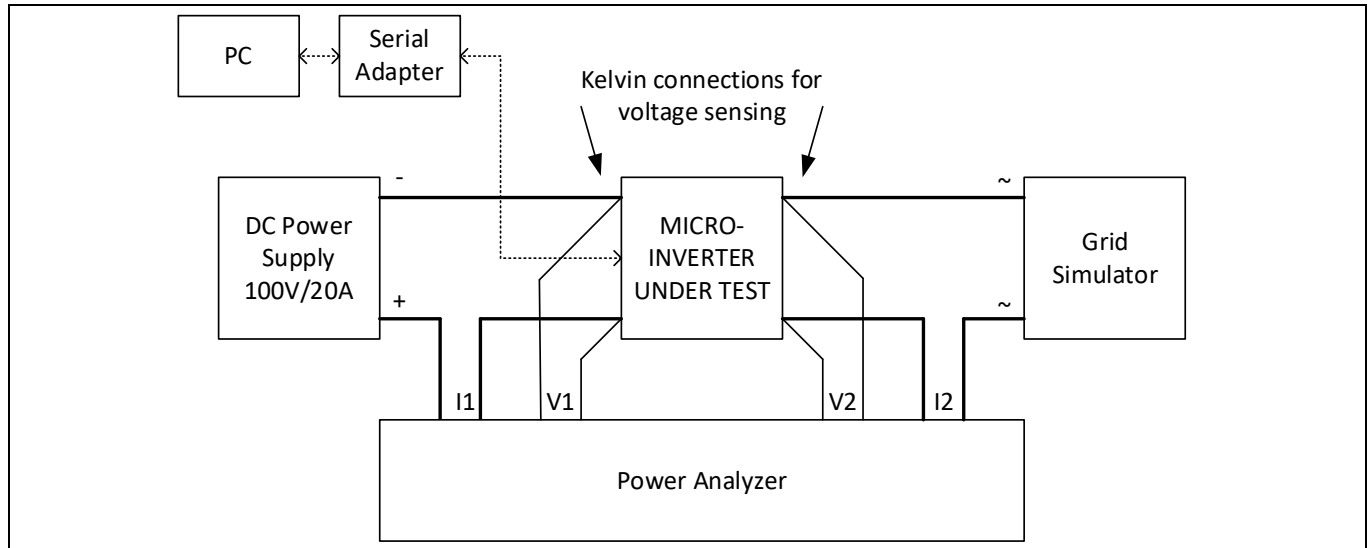

**Figure 90** On-grid constant current mode test setup

### 6.3.3 MPPT mode

A PV emulator DC power source is required for operation in MPPT mode. These are typically operated with PC-based software that allows the user to set the desired maximum power point, which must be done in order for the REF\_500W\_CYCLO\_BDSGAN board to operate correctly in MPPT mode.

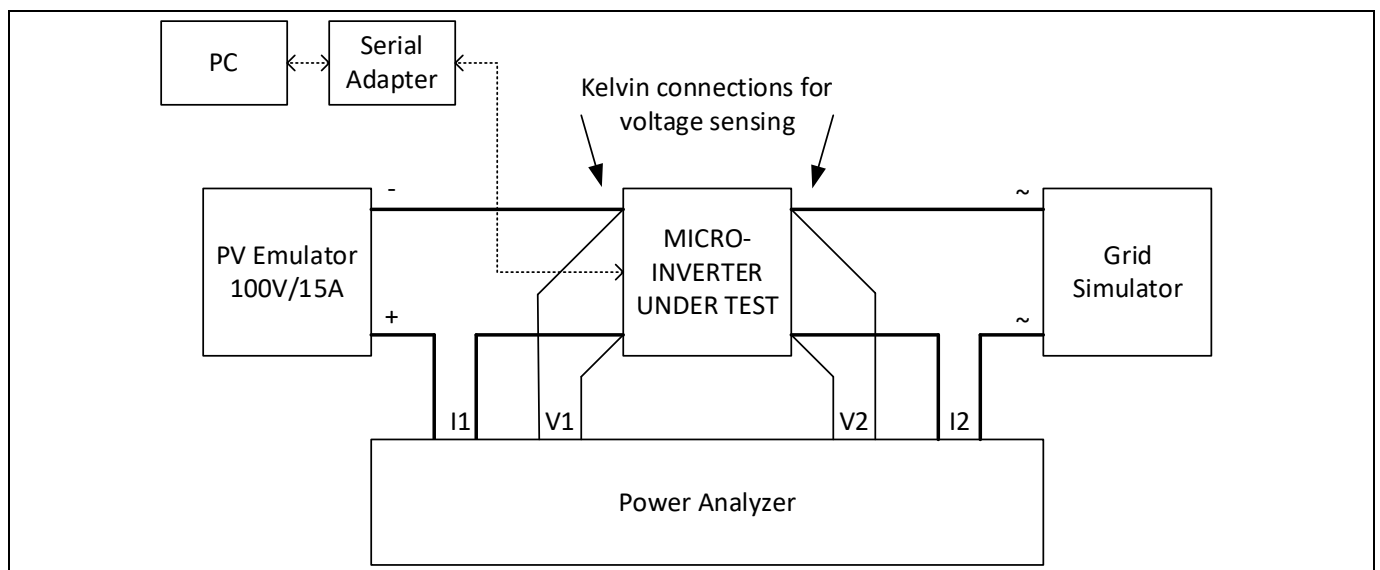

**Figure 91** On grid MPPT mode test setup

The procedure will be explained in the following sections.


## 7 GUI tool and operation

### 7 GUI tool and operation

The REF\_500W\_CYCLO\_BDSGAN reference design board is operated via an ASCII-based operating system with a defined command set defined in Table 10. A PC-based tool is available from Infineon, which provides a user-friendly GUI for easy operation (refer to Section 3.1.2). Usage of the GUI is described in this section.

#### 7.1.1 Basic functions

First install the GUI tool onto a PC and connect the PC to an isolated USB to serial port adapter as described in Section 6.1. Ensure the serial port adapter is shown in the Windows device drivers and note operating correctly, note the COM port. Select the COM port in the GUI tool and click the **CONNECT/DISCONNECT** button and check the “Port Connected” status is indicated:

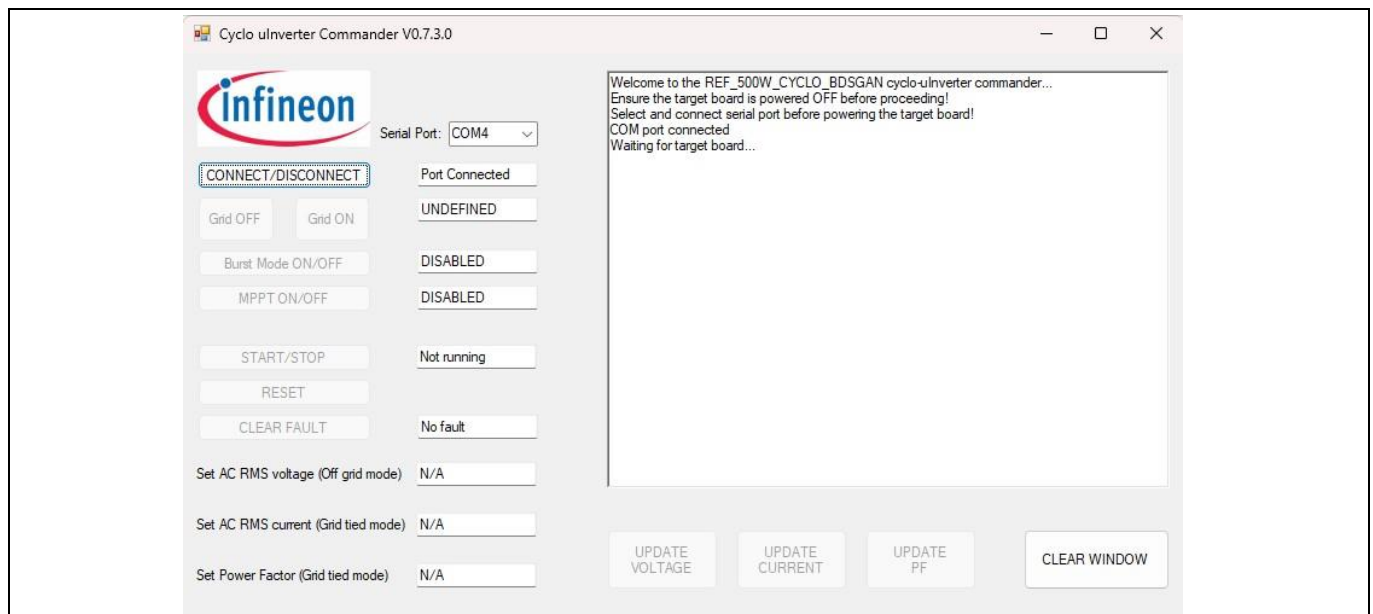

**Figure 92** Setting the COM port


Connect the serial port adapter to the target board with the auxiliary power supply as shown in Section 6.1. Then switch on the auxiliary power supply and observe the GUI detection of the target board as shown in the following figure. The grid OFF and grid ON buttons will become enabled once the target board has been detected.

Observe that all ASCII messages transmitted from the GUI to the target board are displayed in the main GUI text window preceded by “TX:” and all text received from the target board is also displayed, which is preceded by “RX:” except for the start message shown below. The target board startup message contains three lines of text followed by “Target board detected!”, which is indicated by the GUI when the preceding three lines have been received.

**Attention:** *The REF\_500W\_CYCLO\_BDSGAN board will not operate in off-grid mode and the relay will remain open if the unit is connected to an AC source such as a grid simulator if AC voltage is detected at the output terminals. Any attempt to apply AC voltage to the output terminals while operating on off-grid mode could damage the unit.*

The board will shut down immediately in startup in off-grid mode unless a passive load of at least 50 W is present at the output terminals.

## 7 GUI tool and operation

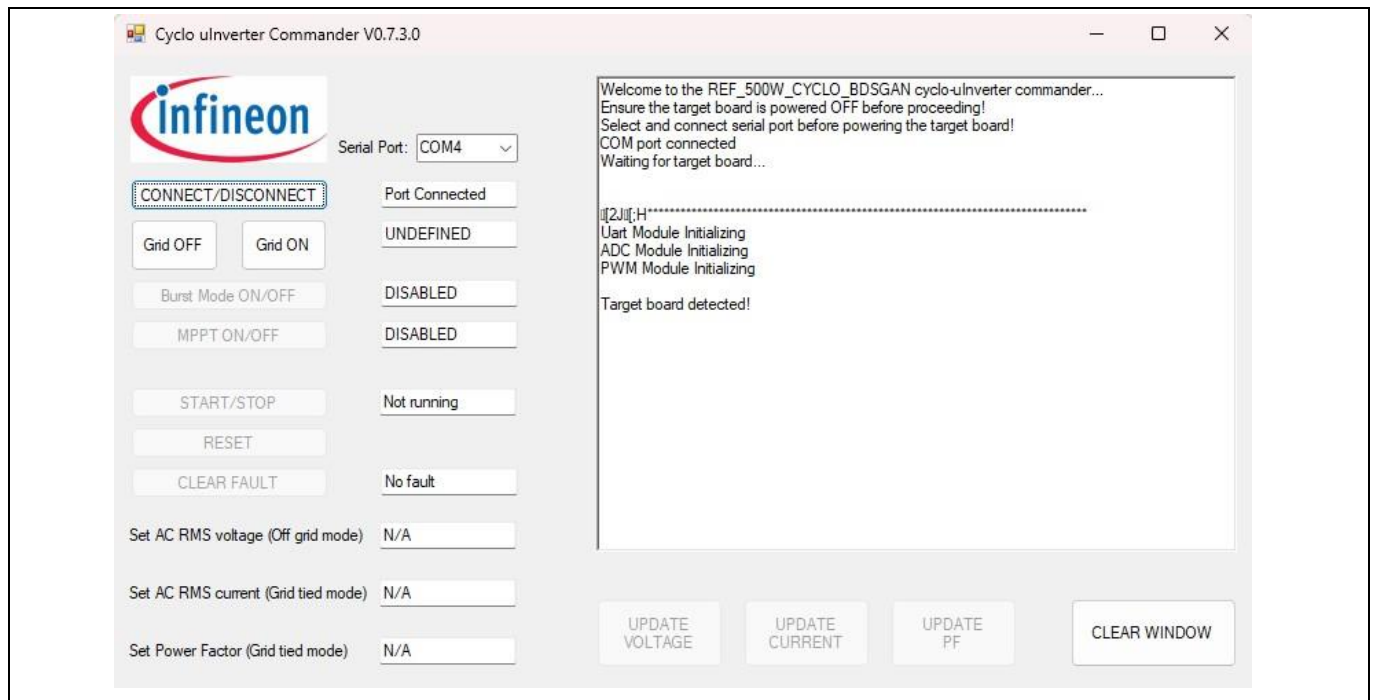

**Figure 93** Target board detection

### 7.1.2 Off-grid operation


1. To operate the system in off-grid mode, click on the **Grid OFF** button and observe the grid mode status  
The grid **OFF** and **ON** buttons become disabled and the **UPDATE VOLTAGE** button becomes active
2. Ensure the main DC power is connected to the board with the appropriate voltage and current settings
3. Enter the required RMS output voltage in the **Set AC RMS voltage** box and then click on **UPDATE VOLTAGE** to send the voltage command to the target board
4. Click the **START/STOP** button to start the cycloinverter

*Note:* A 50 W minimum load must be connected to operate in off-grid mode otherwise the unit will shut down.

# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter




## 7 GUI tool and operation

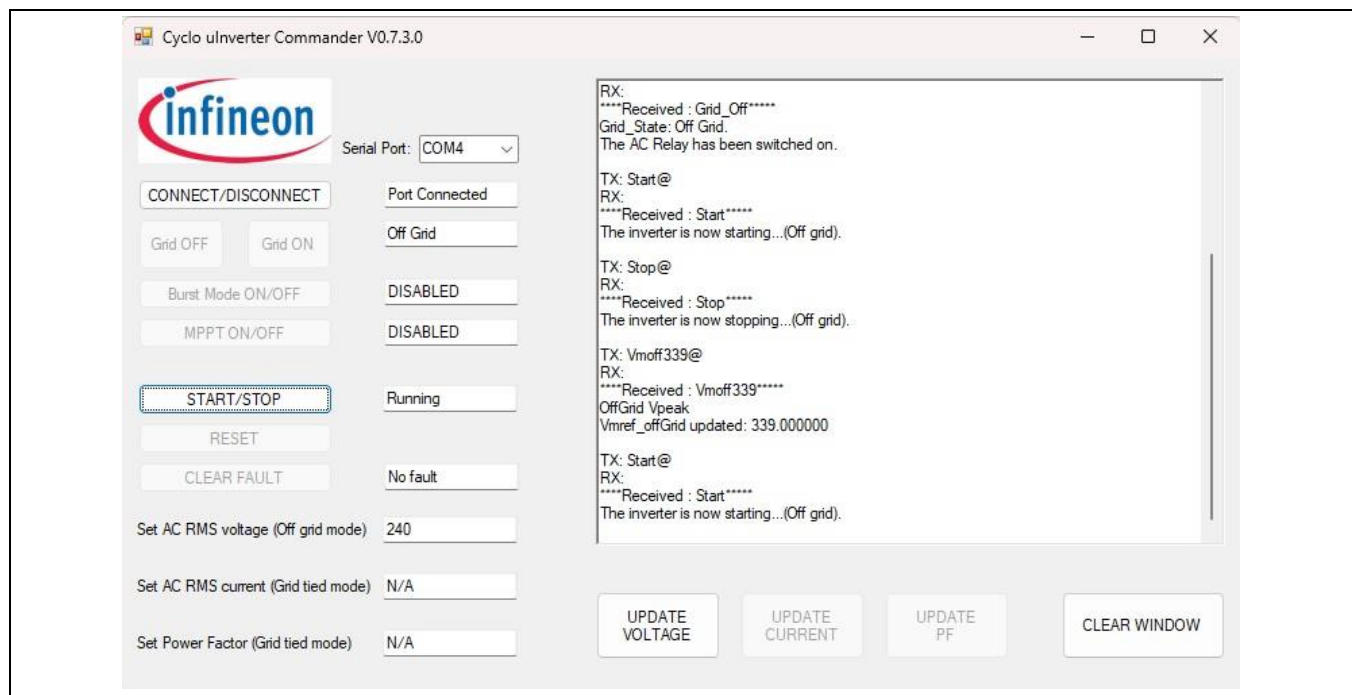

**Figure 94 Off-grid operation**

*Note: The GUI converts the RMS voltage to a peak voltage before sending the command as required by the target board firmware.*

5. To stop the inverter, click on the **START/STOP** button again.

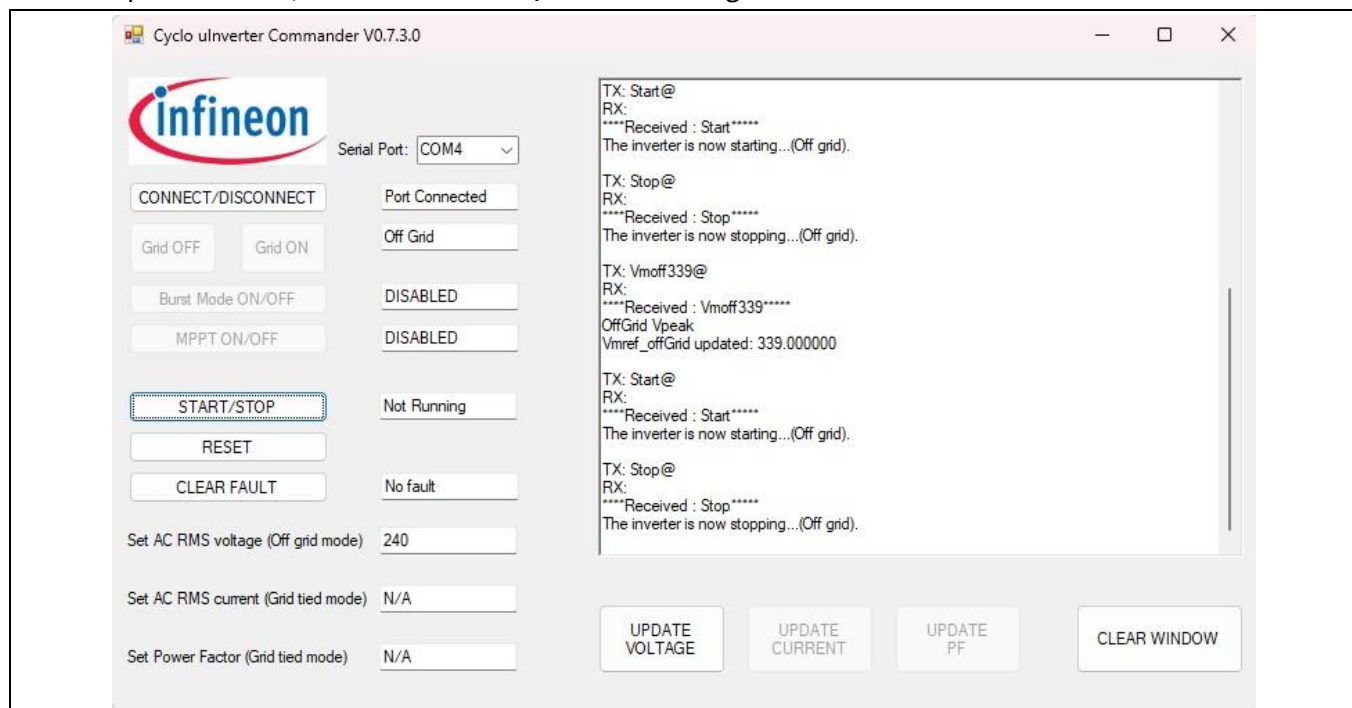

**Figure 95 Inverter stopped operation in off-grid mode**

In the event of an error causing the target board to stop running, an error message will appear in the main window and a fault status will be indicated. Click **FAULT CLEAR** button followed by the **RESET** button to return

## 7 GUI tool and operation


the target board to initial grid selection mode. In some cases, it may be necessary to power down and restart the target board.

### 7.1.3 On-grid (grid-tied) constant current operation

To operate in grid-tied mode, select the **Grid ON** button and observe the grid mode status. The grid **OFF** and **ON** buttons should then become disabled and the **UPDATE CURRENT** and **UPDATE PF** buttons become active. The REF\_500W\_CYCLO\_BDSGAN board will attempt frequency and phase lock to the AC grid voltage. If this is not successfully completed within 10 seconds, the unit will reset to the mode selection state. For this reason, the grid simulator output should be enabled before selecting grid **ON** mode.

Ensure the main DC power is connected to the board with the appropriate voltage and current settings. The next step is to enter the required RMS output current in the **Set AC RMS current** box and then click on **UPDATE CURRENT** to send the current command to the target board. Click the **START/STOP** button to start the cycloconverter.

Note that the GUI converts the RMS current to a peak current before sending the command as required by the target board firmware.

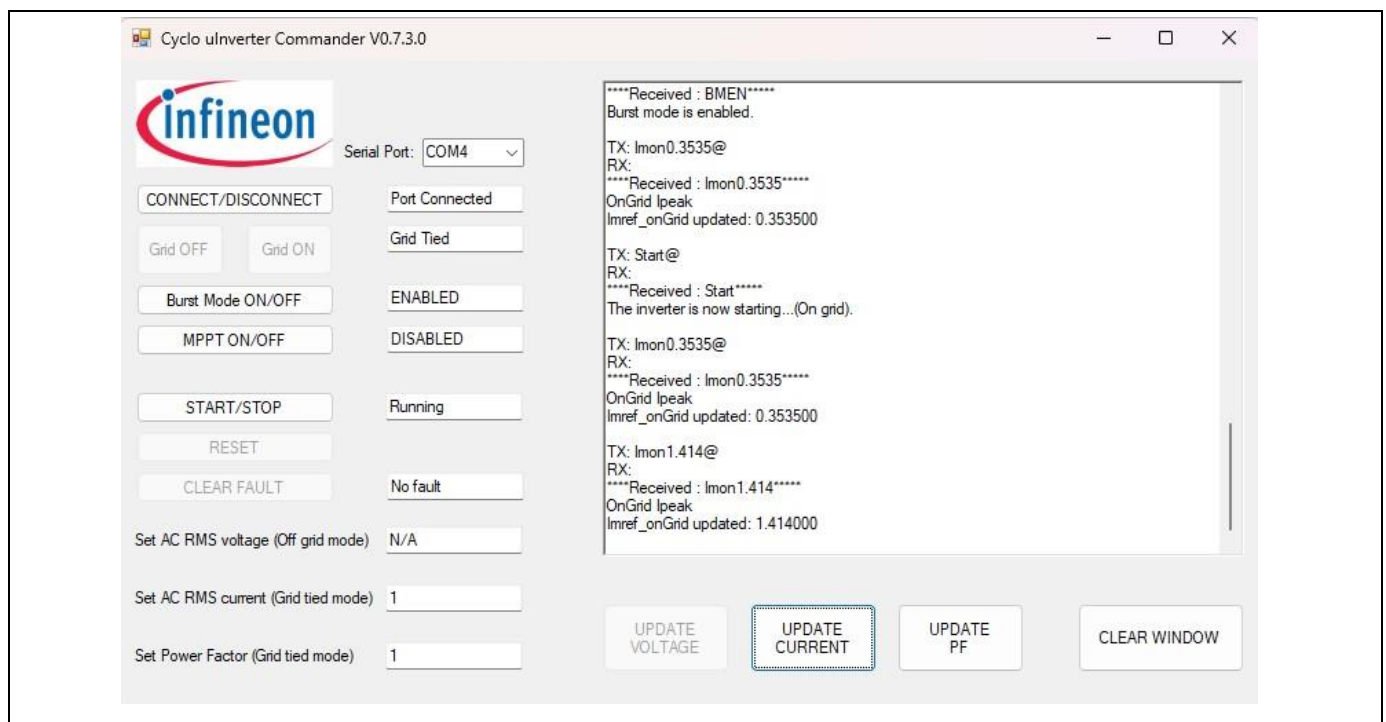


**Figure 96** Setting the output current for grid-tied operation

The power factor may also be changed while operating in this mode. This is done by entering a power factor between in the range -0.8 to 1.0 to 0.8 in the set power factor box and click on **UPDATE PF**.

# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter




## 7 GUI tool and operation

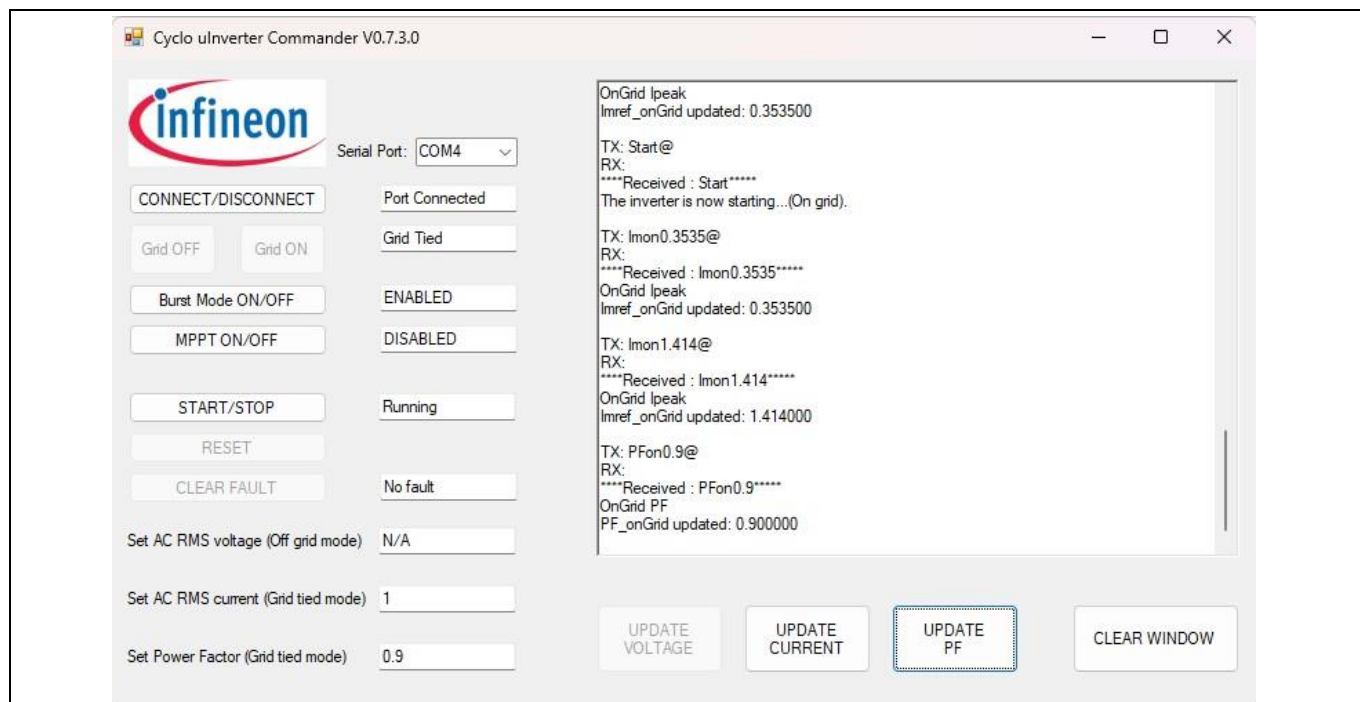

**Figure 97** Changing the power factor

Burst mode, required to achieve light load efficiency, is inactive by default and can be enabled only when the power factor is set to unity (1.0). This is done by clicking the Burst Mode **ON/OFF** button and observing the burst mode status box. Burst mode may be enabled and disabled during operation.

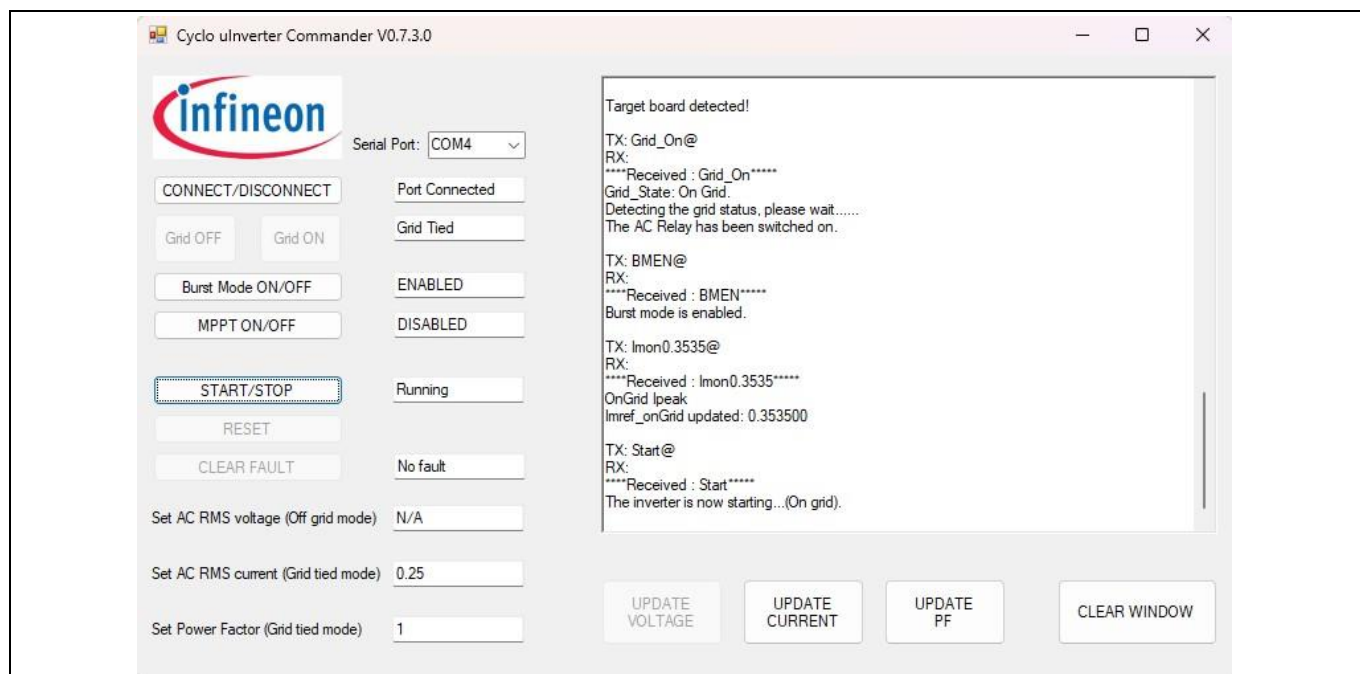


**Figure 98** Burst mode operation in on-grid mode

The inverter is stopped by clicking the **START/STOP** button.

# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter



## 7 GUI tool and operation

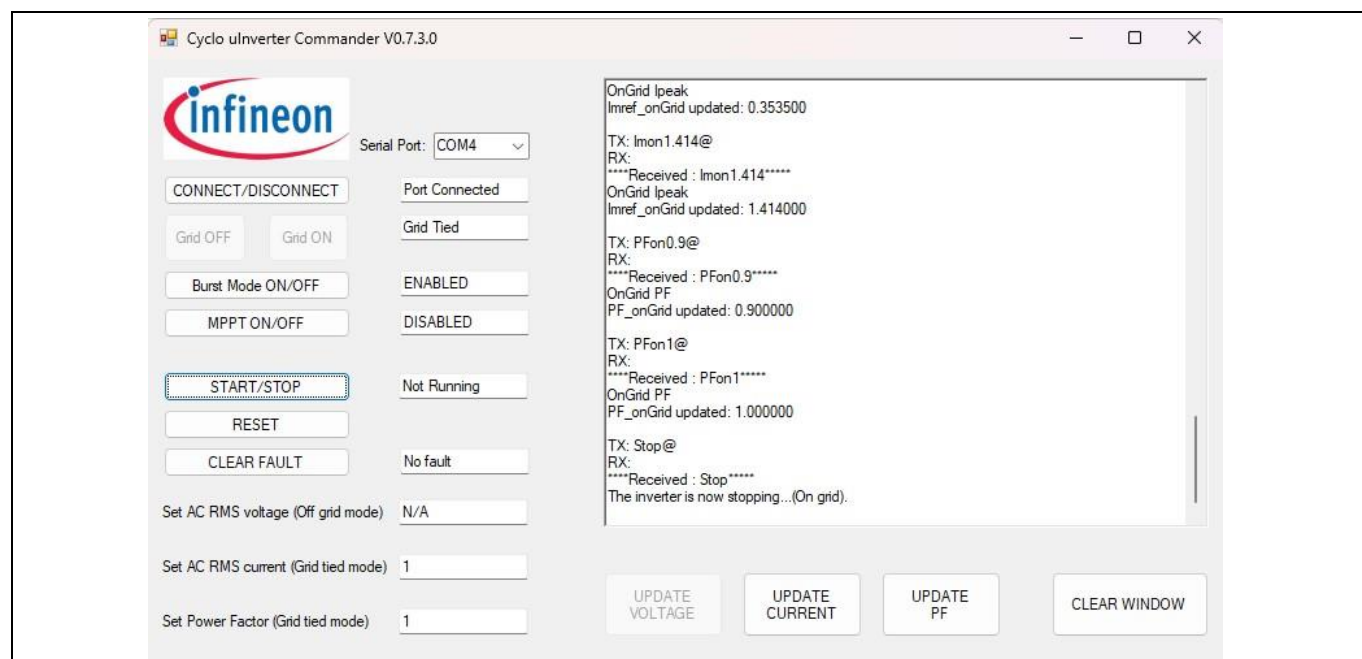

**Figure 99 Inverter stopped operation in on-grid mode**

MPPT operation is described in Section [11.1.3](#).

## 8 Bill of materials

### 8 Bill of materials

#### 8.1 Electrolytic capacitor board

| Reference            | Qty | Type      | Value/rating                                                                   | Manufacturer | Part number    |
|----------------------|-----|-----------|--------------------------------------------------------------------------------|--------------|----------------|
| C1, C2, C3, C4, C119 | 5   | Capacitor | 4.7 mF / 63 V / 20% / Aluminum electrolytic / D25 mm / L52 mm / P10mm / Radial | Nichicon     | LGY1J472MELA50 |
| PCB                  | 1   | PCB       | E-Caps / V1.0/ FR4 / 2 layers of 2oz. Cu / Green                               |              |                |

#### 8.2 Main power board

| Reference                                                                                                  | Qty | Type             | Value/rating                                      | Manufacturer | Part number         |
|------------------------------------------------------------------------------------------------------------|-----|------------------|---------------------------------------------------|--------------|---------------------|
| AC-1, AC+1, DC-, DC+                                                                                       | 4   | Connector        | 0° (vertical) / Board-to-Cable                    | XFCN         | T44008              |
| BUTTON1, BUTTON2                                                                                           | 2   | Electro Mechanic | SWITCH TACTILE / SPST-NO / 0.05A / 12V            | C&K          | PTS647SM38SMTR 2LFS |
| C5, C6, C7, C8, C9, C10, C11, C12, C13, C14, C15, C16, C17, C18, C19, C20, C21, C22                        | 18  | Capacitor        | 2.2 uF / 100 V / 10% / X7R (EIA) / 1206 (3216)    | Kyocera      | 12061C225KAT2A      |
| C23, C24, C25, C26                                                                                         | 4   | Capacitor        | 1 nF / 100 V / 5% / COG-NPO / 0603 (1608)         | MuRata       | GRM1885C2A102JA 01D |
| C27                                                                                                        | 0   | Capacitor        | DO NOT POPULATE                                   |              |                     |
| C88, C99, C100, C168                                                                                       | 0   | Capacitor        | DO NOT POPULATE                                   |              |                     |
| C30, C34, C82, C84, C85, C87, C89, C90, C92, C93, C95, C97, C101, C102, C108, C110, C114, C115, C169, C170 | 20  | Capacitor        | 1 nF / 25 V / 5% / X7R (EIA) / 0603 (1608)        | Yageo        | CC0603JRX7R8BB1 02  |
| C28, C29, C32, C33                                                                                         | 4   | Capacitor        | 15 nF / 1 kV / 5% / C0G (EIA) / NP0 / 1812 (4532) | Kemet        | CKC18X153JDGACA UTO |
| C31, C49, C54, C66, C73, C77, C80, C81, C83, C86, C91, C94, C96, C103, C104, C105, C106, C109, C111,       | 40  | Capacitor        | 100 nF / 25 V / 5% / X7R (EIA) / 0603 (1608)      | Yageo        | CC0603JRX7R8BB1 04  |

# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter



## 8 Bill of materials

| Reference                                                                                                                                                  | Qty | Type      | Value/rating                                                             | Manufacturer        | Part number              |
|------------------------------------------------------------------------------------------------------------------------------------------------------------|-----|-----------|--------------------------------------------------------------------------|---------------------|--------------------------|
| C113, C116,<br>C123, C124,<br>C149, C151,<br>C152, C153,<br>C154, C155,<br>C156, C157,<br>C158, C159,<br>C162, C163,<br>C164, C165,<br>C166, C167,<br>C171 |     |           |                                                                          |                     |                          |
| C125, C130,<br>C133, C135,<br>C137, C139,<br>C141                                                                                                          | 7   | Capacitor | 100 nF / 25 V / 10% / X7R<br>(EIA) / 0402 (1005)                         | Samsung             | CL05B104KA5NNN<br>C      |
| C35, C36, C37                                                                                                                                              | 3   | Capacitor | 470 nF / 630 V / 10% / MKP<br>(Metallized Polypropylene) /<br>THT/Radial | Kemet               | F862BY474K310ZV<br>054   |
| C38, C42, C132                                                                                                                                             | 3   | Capacitor | 4.7 uF / 25 V / 10% / X6S<br>(EIA) / 0603 (1608)                         | MuRata              | GRT188C81E475KE<br>13D   |
| C39, C43, C48,<br>C50, C51, C52,<br>C53, C55, C56,<br>C59, C121, C122,<br>C126, C127                                                                       | 14  | Capacitor | 1 uF / 25 V / 20% / X7R (EIA) /<br>0603 (1608)                           | TDK<br>Corporation  | C1608X7R1E105M0<br>80AB  |
| C40, C41, C44,<br>C45, C46, C47,<br>C57, C58, C117,<br>C160, C161                                                                                          | 11  | Capacitor | 100pF / 25 V / 5% / C0G (EIA)<br>/ NP0 / 0603 (1608)                     | AVX                 | 06033A101JAT2A           |
| C60, C62, C63,<br>C65, C68, C75                                                                                                                            | 6   | Capacitor | 2.2 uF / 25 V / 20% / X7R<br>(EIA) / 0805 (2012)                         | Kemet               | C0805C225M3RACT<br>U     |
| C61, C64, C70,<br>C78                                                                                                                                      | 4   | Capacitor | 10 uF / 25 V / 10% / X7S (EIA)<br>/ 0805 (2012)                          | MuRata              | GRM21BC71E106K<br>E11L   |
| C67                                                                                                                                                        | 1   | Capacitor | 47 pF / 100 V / 5% / C0G (EIA)<br>/ NP0 / 0603 (1608)                    | Kemet               | C0603C470J1GACT<br>U     |
| C69, C120                                                                                                                                                  | 2   | Capacitor | 4.7 uF / 100 V / 20% / X7R<br>(EIA) / 1206 (3216)                        | MuRata              | GRM31CZ72A475M<br>E11K   |
| C71, C72, C79                                                                                                                                              | 3   | Capacitor | 22 uF / 25 V / 20% / X5R (EIA)<br>/ 1206 (3216)                          | MuRata              | GRM31CR61E226M<br>E15    |
| C74                                                                                                                                                        | 1   | Capacitor | 100 nF / 100 V / 10% / X7R<br>(EIA) / 0603 (1608)                        | Wurth<br>Elektronik | 885012206120             |
| C76                                                                                                                                                        | 1   | Capacitor | 33 pF / 50 V / 5% / C0G (EIA)<br>/ NP0 / 0603 (1608)                     | TDK<br>Corporation  | CGA3E2NP01H330J<br>080AA |
| C98, C107, C112,<br>C131, C134,                                                                                                                            | 9   | Capacitor | 10 uF / 25 V / 20% / X5R (EIA)<br>/ 0603 (1608)                          | TDK<br>Corporation  | C1608X5R1E106M0<br>80AC  |

# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter



## 8 Bill of materials

| Reference                                             | Qty | Type        | Value/rating                                      | Manufacturer          | Part number         |
|-------------------------------------------------------|-----|-------------|---------------------------------------------------|-----------------------|---------------------|
| C136, C138, C140, C142                                |     |             |                                                   |                       |                     |
| C118                                                  | 1   | Capacitor   | 4.7 nF / 25 V / 5% / X7R (EIA) / 0603 (1608)      | Yageo                 | CC0603JRX7R8BB472   |
| C128, C129                                            | 2   | Capacitor   | 10 nF / 50 V / 10% / X7R (EIA) / 0603 (1608)      | Kemet                 | C0603C103K5RECAUTO  |
| C143, C144                                            | 2   | Capacitor   | 18 pF / 50 V / 2% / C0G (EIA) / NP0 / 0402 (1005) | MuRata                | GCM1555C1H180GA16   |
| C145                                                  | 1   | Capacitor   | 56 pF / 25 V / 2% / C0G (EIA) / NP0 / 0603 (1608) | MuRata                | CC0603GRNPO9BN560   |
| C146, C147                                            | 2   | Capacitor   | 15 pF / 25 V / 5% / C0G (EIA) / NP0 / 0402 (1005) |                       | 0402N150J250CT      |
| C148                                                  | 1   | Capacitor   | 47 uF / 10 V / 10% / X5R (EIA) / 1206 (3216)      | MuRata                | GRM31CR61A476KE15   |
| C150                                                  | 1   | Capacitor   | 22 uF / 25 V / 20% / X7S (EIA) / 1206 (3216)      | MuRata                | GRM31CC71E226ME15L  |
| C172, C173                                            | 2   | Capacitor   | 2 pF / 50 V / 500 fF / X8G (Murata) / 0603 (1608) | MuRata                | GCM1885G1H2R0DA16   |
| Cc1, Cc2, Cc3, Cc4                                    | 4   | Capacitor   | 1.5 nF / 25 V / 10% / X7R (EIA) / 0603 (1608)     | MuRata                | GCJ188R71E152KA01D  |
| CT1                                                   | 1   | Transformer | 1:100 / 50 A / DIP / Current Sense Transformers   | FANGCHENG ELECTRON    | FC-SCT1090-100T-50A |
| D1, D13, D14, D15                                     | 4   | Diode       | Schottky diode / PowerDI123                       | Diodes Incorporated   | DFLS1100-7          |
| D2, D3, D4, D20                                       | 4   | Diode       | Schottky diode / SOD-323F (SC-90)                 | Nexperia              | BAT46WJ,115         |
| D5, D6, D7, D8, D9, D10, D11, D12, D16, D17, D18, D19 | 12  | Diode       | Schottky diode / SC-79                            | Infineon Technologies | BAS3005A-02V        |
| D21                                                   | 1   | Diode       | TVS Diode / SOT-23-6                              | STMicroelectronics    | USBLC6-4SC6         |
| D22                                                   | 1   | Diode       | Standard Diode / SOD-123                          | Diodes Incorporated   | 1N4148W-7-F         |
| F1                                                    | 1   | Resistor    | 5A / 300V / THT / Radial                          | Littelfuse            | 36915000000         |
| J1                                                    | 1   | Connector   | TERM BLOCK HDR / 2POS / 5.08 mm                   | Würth Elektronik      | 691313510002        |
| J1a                                                   | 1   | Connector   | TERM BLOCK / PLUG / 2POS / 5.08 mm                | Würth Elektronik      | 691351500002        |
| JP1                                                   | 1   | Connector   | Header / 2.54 mm / 3-pin / vertical               | Amphenol ICC (FCI)    | 68001-203HLF        |

# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter



## 8 Bill of materials

| Reference                                                                                                                                                                                                       | Qty | Type                  | Value/rating                                                                             | Manufacturer              | Part number           |
|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----|-----------------------|------------------------------------------------------------------------------------------|---------------------------|-----------------------|
| P1, P2                                                                                                                                                                                                          | 2   | Connector             | 1x4P PH 4P Tin / -<br>25°C~+85°C / 2 A / 2mm<br>Brass Right-Angle Push-Pull              | SHOU HAN                  | 2.0-4P WZ-D           |
| P3                                                                                                                                                                                                              | 1   | Connector             | 1x4P / Vertical / 2.54 mm /<br>shrouded / white                                          | JST Sales<br>America Inc. | B4B-XH-A              |
| X1, X2, X3, X4,<br>X5, X6, X7, X8,<br>X9, X10, X11,<br>X12, X13, X14,<br>X15, X16, X17,<br>X18, X19, X20,<br>X21, X22, X23,<br>X24, X25, X26,<br>X27, X28, X29,<br>X30, X31, X32,<br>X33, X34, X35,<br>X36, X37 | 37  | Connector             | H62 Brass / 5x2x0.6 mm<br>Metal Products / SMT /<br>Copper Sheet                         | STEIPU                    | STHW4-DU-<br>HN050206 |
| IC1, IC2                                                                                                                                                                                                        | 2   | Integrated<br>Circuit | Half-Bridge Gate Driver IC<br>Non-Inverting / 8-VSON<br>(4x4)                            | Texas<br>Instruments      | UCC27211AD            |
| IC3                                                                                                                                                                                                             | 1   | Integrated<br>Circuit | 4.2-V to 80-V, 2-A,<br>synchronous buck with 40-<br>μA IQ / HSOIC-8                      | Texas<br>Instruments      | PLMR38020FDDAR        |
| IC4                                                                                                                                                                                                             | 1   | Integrated<br>Circuit | 3-V to 17-V Input, 2-A,<br>Synchronous Buck<br>Converters / SOT-563                      | Texas<br>Instruments      | TPS562242DRLR         |
| IC5, IC8, IC14,<br>IC15                                                                                                                                                                                         | 4   | Integrated<br>Circuit | CMOS Amplifier / 2 Circuit /<br>Rail-to-Rail / 8-SOIC                                    | Texas<br>Instruments      | OPA2350UA             |
| IC6                                                                                                                                                                                                             | 1   | Integrated<br>Circuit | Buffer / Non-Inverting / 2<br>Element / 4 Bit per Element<br>/ 3-State Output / 20-TSSOP | Texas<br>Instruments      | SN74AHCT244PWR        |

# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter



## 8 Bill of materials

| Reference  | Qty | Type               | Value/rating                                                                             | Manufacturer                 | Part number        |
|------------|-----|--------------------|------------------------------------------------------------------------------------------|------------------------------|--------------------|
| IC7        | 1   | Integrated Circuit | -5 A~5 A SOP-16-W Current Sensors ROHS                                                   | CrossChip Microsystems .Inc. | CC6921SO-5A        |
| IC9, IC10  | 2   | Integrated Circuit | Dual comparator / SOIC-8                                                                 | Texas Instruments            | LM2903D            |
| IC11, IC12 | 2   | Integrated Circuit | Buffer / Non-Inverting / 1 Element / 1 Bit per Element / 3-State Output / SOT-23-5       | Texas Instruments            | SN74AHCT1G125D BVR |
| IC13       | 1   | Integrated Circuit | 3-V to 16-V input voltage / 4-A FCCM mode / synchronous buck converter / SOT-563 package | Texas Instruments            | TPS564247DRLR      |
| K1         | 1   | Electro Mechanic   | General Purpose Relay / DPST-NO (2 Form A) / 5VDC Coil / Through Hole                    | Omron                        | G6B-2214P-US DC5   |
| L1         | 1   | Inductor           | 320 nH / Standard / SMD                                                                  | Pulse Electronics            | PG2290.321HLT      |
| L2         | 1   | Inductor           | 68 uH / Standard / SMD                                                                   | Coilcraft                    | MSS1210-683MED     |
| L3         | 1   | Inductor           | 3.3 uH / Standard / SMD                                                                  | TDK Corporation              | SPM5030T-3R3M      |

# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter



## 8 Bill of materials

| Reference                   | Qty | Type               | Value/rating                                                    | Manufacturer                  | Part number       |
|-----------------------------|-----|--------------------|-----------------------------------------------------------------|-------------------------------|-------------------|
| L4, L5, L6, L7, L8, L9, L12 | 7   | Inductor           | 220R / Ferrite Bead / 0603 (1608)                               | Würth Elektronik              | 742863122         |
| L10, L11                    | 2   | Inductor           | 1kR / Ferrite Bead / 0603 (1608)                                | MuRata                        | BLM18KG102SN1D    |
| L13                         | 1   | Inductor           | 1.5 µH Shielded Drum Core / 3.6 A / 25.63mOhm Max / Nonstandard | TDK Corporation               | SPM4030T-1R5M-HZ  |
| LD1, LD2, LD3, LD4          | 4   | Diode              | CHIP LED / GREEN / 573NM / 45MCD / 0603                         | Würth Elektronik              | 150060GS75000     |
| LD5, LD6                    | 2   | Diode              | CHIP LED / RED / 623NM / 180MCD / 0603                          | OSRAM Opto Semiconductors     | LR Q976.01-P2R2-1 |
| Lf1, Lf2                    | 2   | Inductor           | 4 mH / Custom / THT                                             | Shenzhen Yamaxi Technology Co | TBD               |
| Q                           | 1   | Integrated Circuit | VREF SHUNT ADJ / 0.5% / SOT23                                   | Diodes Incorporated           | AZ431LANTR-G1     |
| Q1, Q2, Q3, Q4              | 4   | Transistor FET     | N-Channel Enhancement / 279A / 80V / PG-TSON-8-3                | Infineon Technologies         | ISC014N08NM6      |

# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter



## 8 Bill of materials

| Reference                                                                                                                                | Qty | Type           | Value/rating                                                    | Manufacturer               | Part number     |
|------------------------------------------------------------------------------------------------------------------------------------------|-----|----------------|-----------------------------------------------------------------|----------------------------|-----------------|
| Q5, Q6                                                                                                                                   | 2   | Transistor FET | N-Channel Enhancement / 88A / 80V / PG-TSON-8-3                 | Infineon Technologies      | ISC056N08NM6    |
| Q7, Q8                                                                                                                                   | 2   | Transistor FET | N-Channel Enhancement bidirectional / 600 V / GaN G5 / HDSOP-16 | Infineon Technologies      | IGLT65R055B2    |
| Q9                                                                                                                                       | 1   | Transistor FET | N-Channel Enhancement / 500 mW / 1.4 A / 30 V / PG-SOT23-3-5    | Infineon Technologies      | BSS316N H6327   |
| R1                                                                                                                                       | 1   | Resistor       | 500 uR / 1% / 3 / 2512 (6432)                                   | Yageo                      | PA2512FKF7T0U5E |
| R2, R3                                                                                                                                   | 2   | Resistor       | 5.1R / 5% / 0.33 / 1206 (3216)                                  | KOA Speer Electronics Inc. | SG73P2BTDD5R1J  |
| R4, R8, R12, R16, R125, R127, Roff1, Roff2, Roff3, Roff4                                                                                 | 10  | Resistor       | 2R / 0.1% / 0.063 / 0603 (1608)                                 | TE Connectivity            | CPF0603B2R0E1   |
| R5, R9, R13, R17, R124, R126                                                                                                             | 6   | Resistor       | 5.1R / 1% / 0.1 / 0603 (1608)                                   | Vishay                     | CRCW06035R10FK  |
| R6, R11, R14, R19, R26, R27, R31, R32, R48, R54, R56, R58, R59, R65, R70, R72, R73, R80, R106, R108, R114, R129, R131, R132, R157, R158, | 49  | Resistor       | 10k / 1% / 0.125 / 0603 (1608)                                  | Stackpole Electronics      | RNCP0603FTD10K0 |

# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter



## 8 Bill of materials

| Reference                                                                                                                                                                                                             | Qty | Type     | Value/rating                  | Manufacturer               | Part number    |
|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----|----------|-------------------------------|----------------------------|----------------|
| R159, R166,<br>R167, R172,<br>R173, R174,<br>R175, R176,<br>R177, R178,<br>R179, R180,<br>R181, R182,<br>R183, R184,<br>R186, R191,<br>R193, R195,<br>R197, R221,<br>R222                                             |     |          |                               |                            |                |
| R7, R10, R15,<br>R18, R20, R21,<br>R23, R24, R45,<br>R107, R116,<br>R121, R134,<br>R151, R152,<br>R153, R154,<br>R155, R156,<br>R160, R161,<br>R162, R163,<br>R164, R165,<br>R168, R169,<br>R170, R171,<br>R217, R218 | 31  | Resistor | 100R / 1% / 0.1 / 0603 (1608) | ROHM<br>Semiconduct<br>ors | MCR03EZPFX1000 |
| R22, R25                                                                                                                                                                                                              | 2   | Resistor | DO NOT POPULATE               |                            |                |
| R28                                                                                                                                                                                                                   | 1   | Resistor | DO NOT POPULATE               |                            |                |
| R29, R133, R147                                                                                                                                                                                                       | 3   | Resistor | 100k / 1% / 0.1 / 0603 (1608) | Panasonic                  | ERJ-3EKF1003V  |
| R30, R33, R35                                                                                                                                                                                                         | 3   | Resistor | 110k / 1% / 0.1 / 0603 (1608) | Vishay                     | CRCW0603110KFK |

# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter



## 8 Bill of materials

| Reference                                                                                                                                                                                                              | Qty | Type     | Value/rating                    | Manufacturer               | Part number          |
|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----|----------|---------------------------------|----------------------------|----------------------|
| R34                                                                                                                                                                                                                    | 1   | Resistor | 105k / 1% / 0.1 / 0603 (1608)   | Vishay                     | CRCW0603105KFK       |
| R36, R79, R86                                                                                                                                                                                                          | 3   | Resistor | 20k / 1% / 0.1 / 0603 (1608)    | Vishay                     | CRCW060320K0FK       |
| R37, R88, R96                                                                                                                                                                                                          | 3   | Resistor | 22k / 1% / 0.1 / 0603 (1608)    | Vishay                     | CRCW060322K0FK       |
| R38, R39, R40, R41, R42, R43, R46, R47, R49, R50, R51, R52, R53, R60, R61, R62, R74, R75, R76, R77, R81, R82, R83, R84, R189, R198, R199, R200, R201, R202, R204, R205, R207, R208, R210, R211, R212, R214, R215, R216 | 40  | Resistor | 1MEG / 1% / 0.25 / 1206 (3216)  | Vishay                     | CRCW12061M00FK       |
| R44, R55, R203, R213                                                                                                                                                                                                   | 4   | Resistor | 25k / 0.1% / 0.15 / 0603 (1608) | Vishay                     | PNM0603E2502BST<br>1 |
| R57, R63, R64, R66, R67, R68, R69, R71, R99, R128, R130, R187, R188, R190, R192, R194, R196, R206, R209                                                                                                                | 19  | Resistor | 0R / 0603 (1608)                | KOA Speer Electronics Inc. | RK73Z1JTDD           |

# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter



## 8 Bill of materials

| Reference                 | Qty | Type     | Value/rating                       | Manufacturer                     | Part number    |
|---------------------------|-----|----------|------------------------------------|----------------------------------|----------------|
| R136, R137,<br>R144, R145 | 4   | Resistor | 0R / 0402 (1005)                   | KOA Speer<br>Electronics<br>Inc. | RK73Z1ETTP     |
| R98                       | 0   | Resistor | DO NOT POPULATE                    |                                  |                |
| R87, R110, R135           | 3   | Resistor | 1k / 1% / 0.1 / 0603 (1608)        | Panasonic                        | ERJ3EKF1001V   |
| R219, R220                | 2   | Resistor | DO NOT POPULATE                    |                                  |                |
| R89                       | 1   | Resistor | 2.05k / 1% / 0.1 / 0603<br>(1608)  | Vishay                           | CRCW06032K05FK |
| R90, R93                  | 2   | Resistor | 510k / 1% / 0.125 / 0805<br>(2012) | Vishay                           | CRCW0805510KFK |
| R91, R97                  | 2   | Resistor | 39k / 1% / 0.1 / 0603 (1608)       | Vishay                           | CRCW060339K0FK |
| R92, R95                  | 2   | Resistor | 200R / 1% / 0.1 / 0603<br>(1608)   | Vishay                           | CRCW0603200RFK |

# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter



## 8 Bill of materials

| Reference                          | Qty | Type     | Value/rating                   | Manufacturer               | Part number            |
|------------------------------------|-----|----------|--------------------------------|----------------------------|------------------------|
| R94                                | 1   | Resistor | 6.2k / 1% / 0.1 / 0603 (1608)  | Vishay                     | CRCW06036K20FK         |
| R138, R143,<br>R146                | 3   | Resistor | 4.7k / 1% / 0.25 / 0603 (1608) | Vishay                     | CRCW06034K70FKE<br>AHP |
| R139, R140,<br>R141, R142,<br>R146 | 5   | Resistor | 2k / 1% / 0.1 / 0603 (1608)    | Vishay                     | CRCW06032K00FKE<br>A   |
| R103, R109,<br>R113, R120          | 4   | Resistor | 200k / 1% / 0.1 / 0603 (1608)  | Yageo                      | RC0603FR-07200KL       |
| R104                               | 1   | Resistor | 12k / 1% / 0.1 / 0603 (1608)   | Stackpole Electronics      | RMCF0603FT12K0         |
| R105, R111,<br>R112, R115,<br>R117 | 5   | Resistor | 2k / 1% / 0.1 / 0603 (1608)    | KOA Speer Electronics Inc. | RK73H1JTTD2001F        |
| R118, R119                         | 2   | Resistor | 20R / 1% / 0.25 / 1206 (3216)  | Vishay                     | CRCW120620R0FK         |
| R122, R123                         | 2   | Resistor | 1R / 1% / 0.1 / 0603 (1608)    | Panasonic                  | ERJ-3RQF1R0V           |

# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter



## 8 Bill of materials

| Reference              | Qty | Type     | Value/rating                    | Manufacturer                           | Part number          |
|------------------------|-----|----------|---------------------------------|----------------------------------------|----------------------|
| R148                   | 1   | Resistor | 135k / 0.1% / 0.1 / 0603 (1608) | Yageo                                  | RT0603BRD07135KL     |
| R149                   | 1   | Resistor | 59k / 1% / 0.1 / 0603 (1608)    | Vishay                                 | CRCW060359K0FK       |
| R100, R101, R102, R150 | 4   | Resistor | 30k / 1% / 0.1 / 0603 (1608)    | Vishay                                 | CRCW060330K0FK       |
| R185                   | 1   | Resistor | 510R / 1% / 0.1 / 0603 (1608)   | Yageo                                  | RC0603FR-07510RL     |
| Rin1, Rin2, Rin3, Rin4 | 4   | Resistor | 51k / 1% / 0.125 / 0805 (2012)  | Vishay                                 | CRCW080551K0FK       |
| Ron1, Ron2, Ron3, Ron4 | 4   | Resistor | 10R / 1% / 0.1 / 0603 (1608)    | ROHM Semiconductors                    | MCR03EZPFX10R0       |
| Rss1, Rss2, Rss3, Rss4 | 4   | Resistor | 680R / 0.1% / 0.1 / 0603 (1608) | Yageo                                  | RE0603BRE07680RL     |
| Rt1, Rt2, Rt3          | 3   | Resistor | NTC/ 100k / 0603 (1608)         | Shenzhen Sunlord Electronics Co., Ltd. | SDNT1608X104F3950FTF |

# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter



## 8 Bill of materials

| Reference                                                                                                                                                                                                                                                                                                                                                                                              | Qty | Type                | Value/rating                                                           | Manufacturer                           | Part number   |
|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----|---------------------|------------------------------------------------------------------------|----------------------------------------|---------------|
| Rzd1, Rzd3                                                                                                                                                                                                                                                                                                                                                                                             | 2   | Resistor            | 470R / 1% / 0.5 / 0805 (2012)                                          | Panasonic                              | ERJ-P06F4700V |
| Rzd2                                                                                                                                                                                                                                                                                                                                                                                                   | 1   | Resistor            | 300R / 1% / 0.5 / 0805 (2012)                                          | Panasonic                              | ERJ-P06F3000V |
| S1                                                                                                                                                                                                                                                                                                                                                                                                     | 1   | Electro<br>Mechanic | 2Bit SPST Black Flat toggle /<br>slotted / SMD-4P /<br>4.1x5.4mm / DIP | Dongguan<br>KINGTEK                    | DSHP02TSGET   |
| T1                                                                                                                                                                                                                                                                                                                                                                                                     | 1   | Transformer         | Buck with isolated windings<br>(SJTU MAG-1238)                         | Shenzhen<br>Yamaxi<br>Technology<br>Co | TBD           |
| TP1, TP2, TP3,<br>TP4, TP5, TP6,<br>TP7, TP11, TP12,<br>TP13, TP14,<br>TP15, TP16,<br>TP17, TP18,<br>TP19, TP20,<br>TP21, TP22,<br>TP23, TP24,<br>TP25, TP26,<br>TP27, TP28,<br>TP29, TP30,<br>TP31, TP32,<br>TP33, TP34,<br>TP35, TP36,<br>TP37, TP38,<br>TP39, TP40,<br>TP41, TP42,<br>TP43, TP44,<br>TP45, TP46,<br>TP47, TP48,<br>TP49, TP50,<br>TP51, TP52,<br>TP53, TP74,<br>TP75, TP76,<br>TP77 | 54  | Connector           | PC TEST POINT MINIATURE /<br>WHITE                                     | Keystone<br>Electronics                | 5002          |

# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter



## 8 Bill of materials

| Reference | Qty | Type               | Value/rating                                 | Manufacturer                  | Part number                  |
|-----------|-----|--------------------|----------------------------------------------|-------------------------------|------------------------------|
| TR1       | 1   | Transformer        | Resonant step-up transformer / 1 : 5         | Shenzhen Yamaxi Technology Co | TBD                          |
| U1, U2    | 2   | Integrated Circuit | DGTL ISO / 5.7KV / 2CH / GT DVR / DSO14      | Infineon Technologies         | 2EDR7259X                    |
| U3, U4    | 2   | Integrated Circuit | GATE DRVR / HIGH-SIDE / SOT23-6              | Infineon Technologies         | 1EDN8550B                    |
| U5        | 1   | Microcontroller    | ARM Cortex-M33 / 3.6V - 1.71V / PG-LQFP-80-3 | Infineon Technologies         | PSC3M5FDS2AFQ1               |
| U6, U7    | 2   | Diode              | TVS Diode / 6.1V / ST0201                    | STMicroelectronics            | ESDALC6V1-1U2                |
| U8        | 1   | Diode              | TVS Diode / 6.1V / SOT-23-3                  | STMicroelectronics            | ESDA6V1L                     |
| Y1        | 1   | Clock              | CRYSTAL 16.0000MHZ / 8PF / SMD               | Nihon Dempa Kogyo             | NX3225SA-16.000MHZ-STD-CSR-1 |
| Y2        | 1   | Clock              | CRYSTAL 32.7680KHZ / 12.5PF / SMD            | CTS Electronic Component      | TFA322PH327KR                |

# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter



## 8 Bill of materials

| Reference      | Qty | Type      | Value/rating                                                               | Manufacturer         | Part number     |
|----------------|-----|-----------|----------------------------------------------------------------------------|----------------------|-----------------|
| ZD1, ZD2, ZD3  | 3   | Diode     | Zener Diode / 7.5V / 500mW / SOD-123                                       | Diodes Incorporated  | MMSZ5236B-7-F   |
| M1, M2, M3, M4 | 4   | Fastner   | Nut / M2 x 0.5 / patch round                                               | Sinhoo               | SMTSO2005CTJ    |
| HSK1           | 1   | Heatsink  | Custom<br>REF_500W_CYCLO_BDSGAN_HSK1                                       | PT Heatsink          | H007242         |
| HSK2           | 1   | Heatsink  | Custom<br>REF_500W_CYCLO_BDSGAN_HSK2                                       | PT Heatsink          | H007243         |
|                | 1   | Insulator | 30mm Width 50m Long<br>Single Sided Strong Self-Adhesive Mylar Tape Yellow | Uxcell               | a17072400ux0845 |
|                | 1   | Insulator | Tflex HD720 18x18in cut pieces                                             | Laird                | A17536-02       |
|                | 4   | Fastner   | Screw / M2 x 8 / pan head                                                  | APM Hexseal          | RM2X8MM 2701    |
|                | 4   | Fastner   | HEX STANDOFF / #4-40 / SS / 1/2"                                           | Keystone Electronics | 2088            |

## CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter



### 8 Bill of materials

| Reference | Qty | Type    | Value/rating                            | Manufacturer         | Part number |
|-----------|-----|---------|-----------------------------------------|----------------------|-------------|
|           | 4   | Fastner | HEX NUT / 1/4" / STEEL / #4-40          | Keystone Electronics | 9600        |
| PCB       | 1   | PCB     | V1.4 / FR4 / 6 layers of 2oz Cu / Green |                      |             |



## 8 Bill of materials




## 9 Transformer and inductor specifications

### 9 Transformer and inductor specifications


#### 9.1 Step-up transformer (TR1)

The step-up transformer is a custom-made part designed to provide isolation with a 1:5 step-up ratio from the DC primary side to the grid tied AC side. It is designed to integrate a defined leakage inductance required to create the resonant tank. The core material is PC96 or equivalent ferrite with PQ4035 geometry modified by grinding to reduce the overall height from 35 mm to between 30 mm and 32 mm.

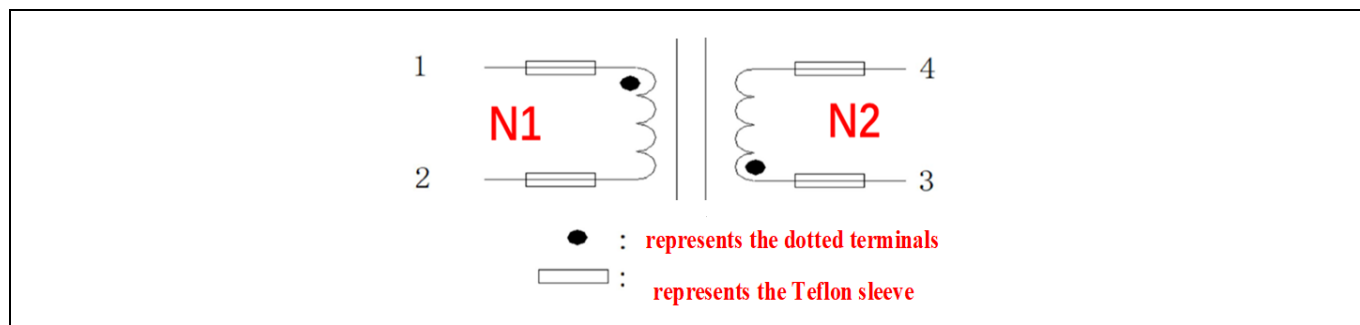


**Figure 102** Transformer format

A magnetic insert made from the same PC96 material as the cores is placed between the windings N1 and N2.

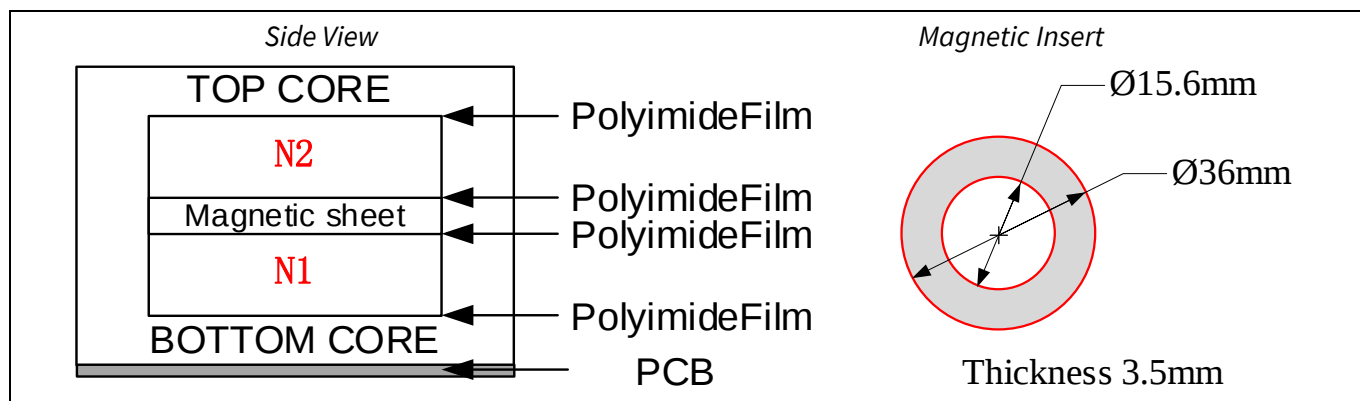

**Figure 103** Transformer structure

The transformer is attached to a base made from FR4 PCB material according to the dimensions shown in the following diagram:

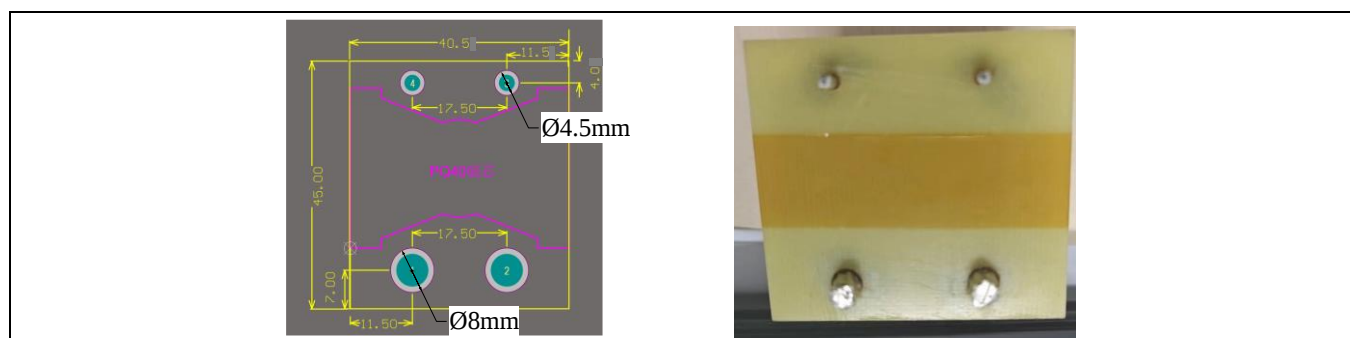

**Figure 104** Base and hole dimensions and picture showing protruding stripped wire terminations

# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter

## 9 Transformer and inductor specifications

Winding details and test parameters are as follows:


**Table 12 Transformer winding specifications**

| Winding | Start pin | Finish pin | Turns | Wire type                                                         | Winding notes                                        |
|---------|-----------|------------|-------|-------------------------------------------------------------------|------------------------------------------------------|
| N1      | 1         | 2          | 3     | Film-wrapped around Litz wire, 0.06 mm, 1100 strands x 2 parallel | Wound densely according to <a href="#">Figure 65</a> |
| N2      | 3         | 4          | 15    | Film-wrapped around Litz wire, 0.06 mm x 450 strands              | Wound densely according to <a href="#">Figure 65</a> |

**Table 13 Transformer test parameters**

| Parameter           | Unit             | Measurement point                                | Value                 | Test Condition                                         |
|---------------------|------------------|--------------------------------------------------|-----------------------|--------------------------------------------------------|
| Inductance          | $\mu\text{H}$    | Pin 3 to pin 4                                   | $\geq 500$            | 100 kHz, $1V_{\text{RMS}}$                             |
| Leakage Inductance  | $\mu\text{H}$    | Pin 3 to pin 4                                   | 59 to 61 <sup>1</sup> | Pins 1 and 2 are shorted<br>100 kHz, $1V_{\text{RMS}}$ |
| Dielectric strength | $V_{\text{RMS}}$ | Pin 1 to pin 3<br>Pin 1 to core<br>Pin 3 to core | 1500                  | 5 mA, 60 s                                             |

Leakage inductance is a critical parameter in this design and therefore, each core must be adjusted to provide a value within the specification above, which has a tolerance of less than 2 percent. The leakage inductance is reduced by grinding down the cores a little at a time and measuring the leakage inductance until the target specification is met. The core total core height should not be reduced below 30 mm. If the target leakage inductance is not achieved, the outer diameter of the magnetic sheet may also be reduced, which also serves to reduce leakage inductance. The finished transformer is shown in the following figure.

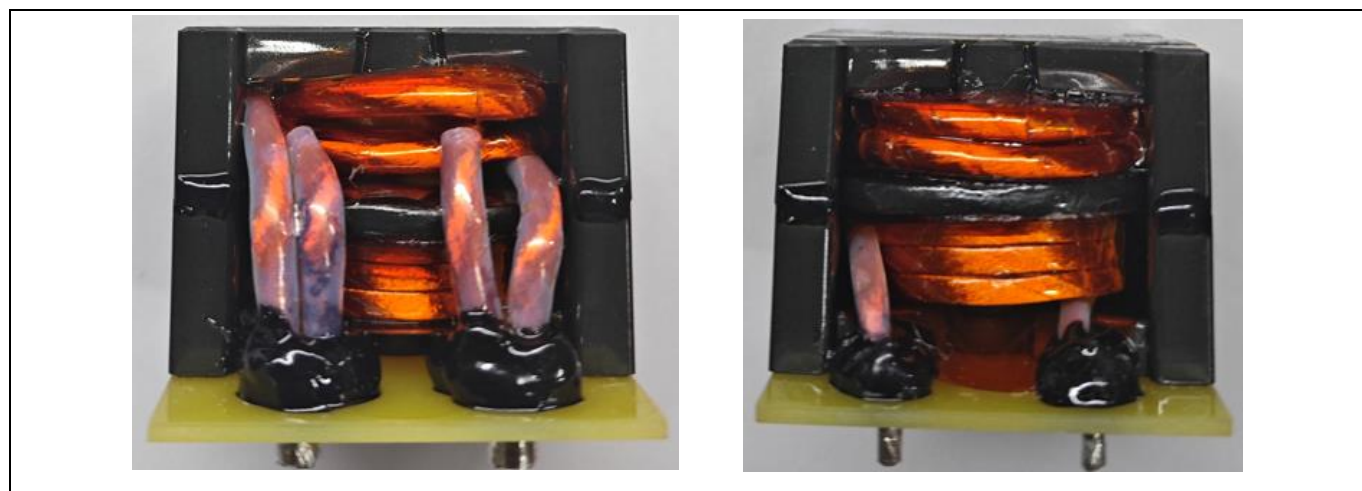


**Figure 105 Integrated transformer viewed from both sides**

<sup>1</sup> Values outside of this range may require some fine tuning of firmware parameters to achieve optimal efficiency.


## 9 Transformer and inductor specifications

### 9.2 Filter inductors (Lf1 and Lf2)

The filter inductors are common mode chokes custom-made as described in the following diagrams.

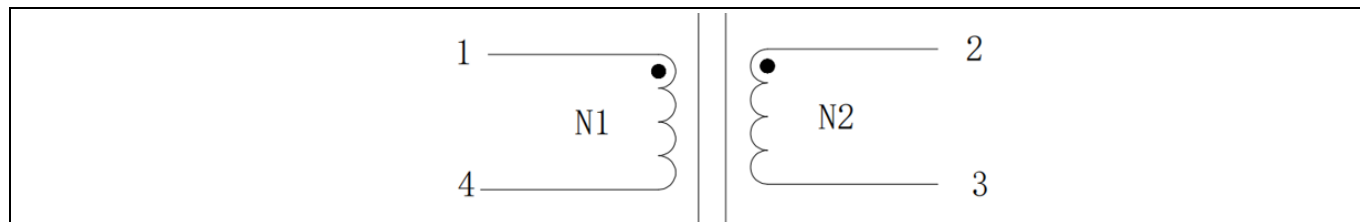


**Figure 106** Common mode filter format

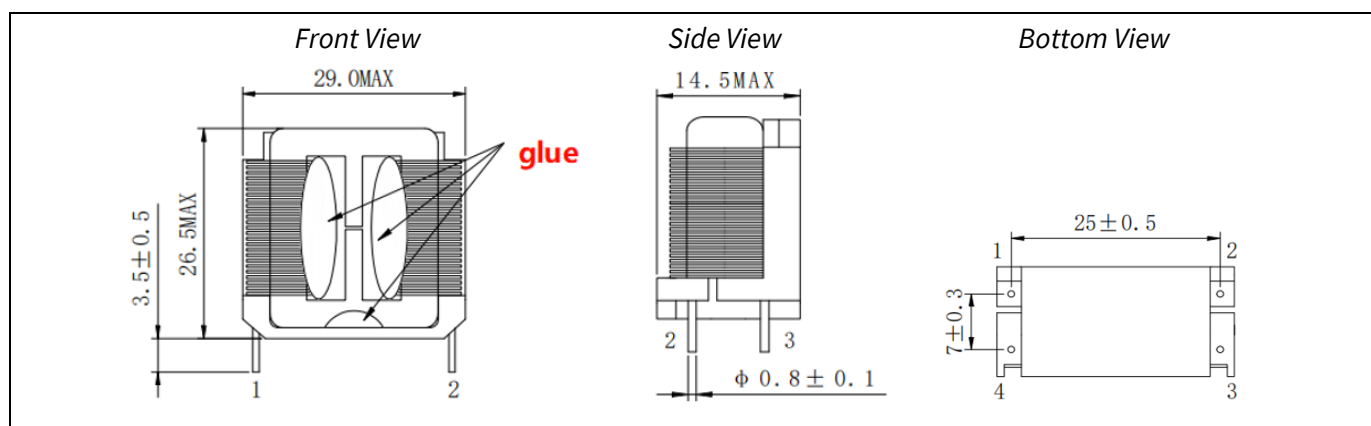

**Figure 107** Filter inductor illustration and dimensions

The cores are ETV2320 shape made from M10K high permeability magnetic steel material:

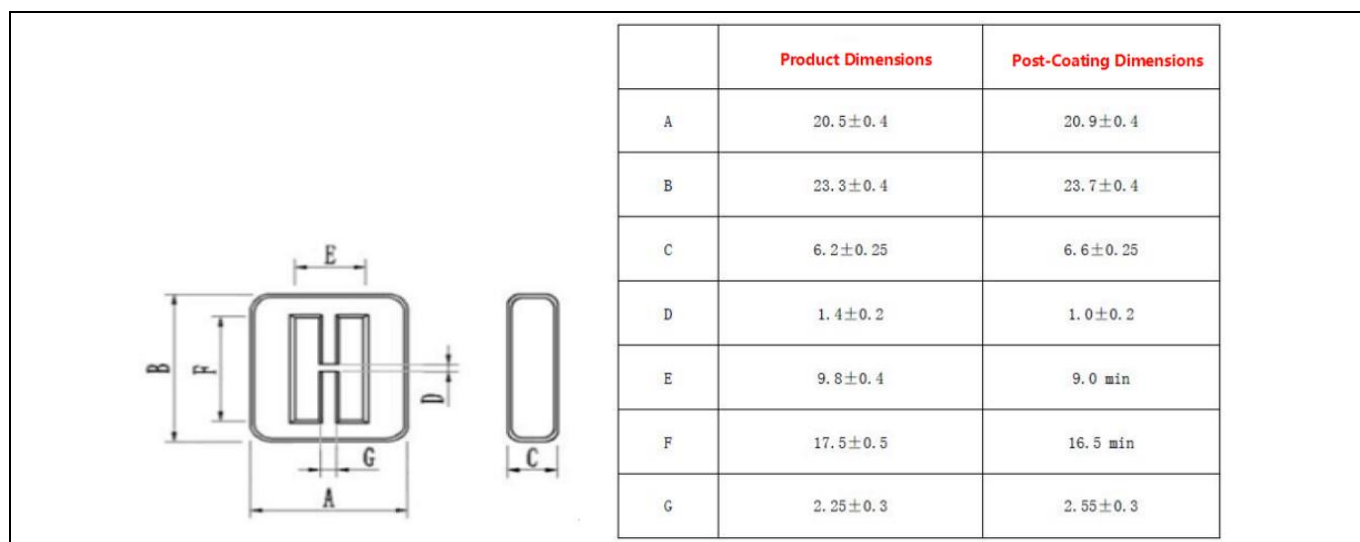


**Figure 108** Filter inductor ETV2320 cores

The cores are glued together using H907 epoxy (UL number E304477).

The bobbin is made from plastic material T375HF rated to 150°C (UL number E39481).

## 9 Transformer and inductor specifications

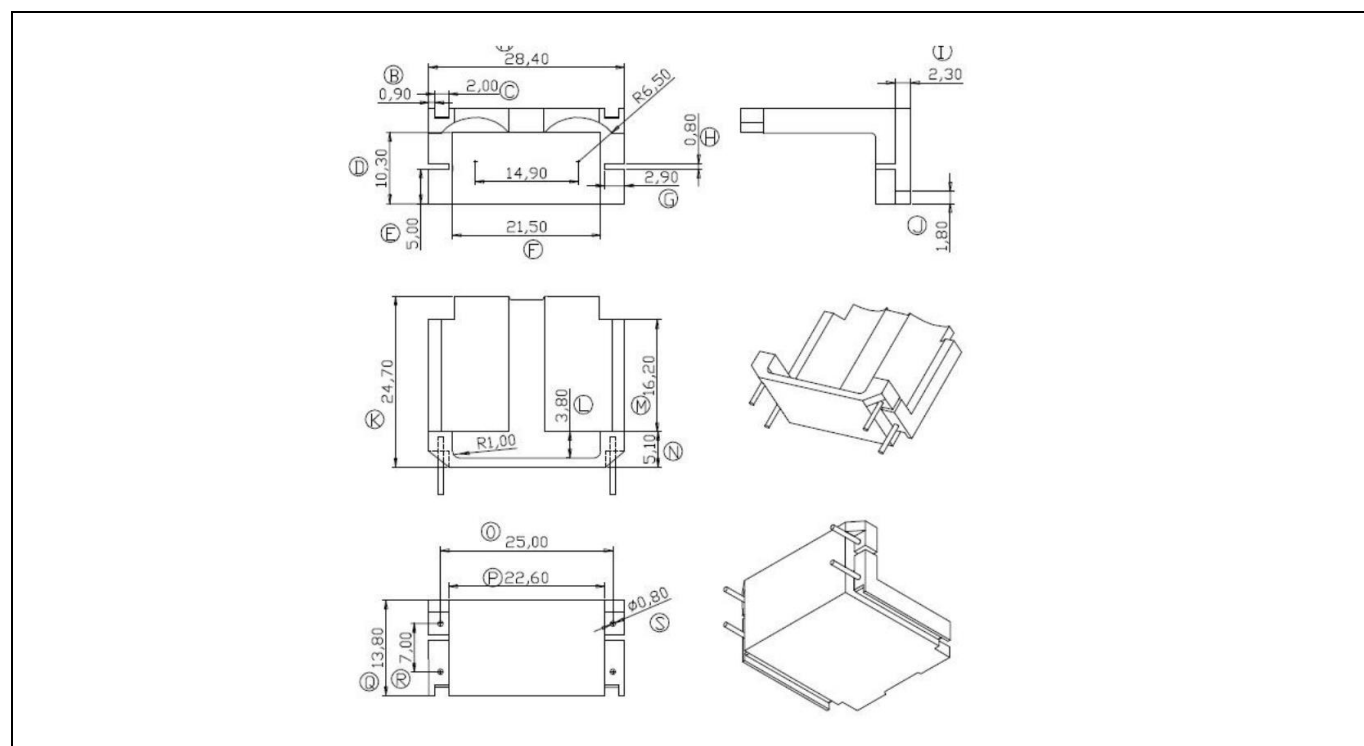

**Figure 109** Bobbin details and dimensions

**Table 14** Filter inductor winding specifications

| Winding | Start pin | Finish pin | Turns | Wire type                        | Winding notes |
|---------|-----------|------------|-------|----------------------------------|---------------|
| N1      | 1         | 4          | 31    | SFT - UEWH $\Phi 0.4 \times 1.8$ | Tightly wound |
| N2      | 2         | 3          | 31    | SFT - UEWH $\Phi 0.4 \times 1.8$ | Tightly wound |

Flat wire is used with insulation rated to 180°C (UL number E318511).


**Table 15** Transformer test parameters

| Parameter             | Unit             | Measurement point              | Value      | Test condition                                                                      |
|-----------------------|------------------|--------------------------------|------------|-------------------------------------------------------------------------------------|
| Inductance            | mH               | Pins 1 to 4 and 2 to 3         | $\geq 4$   | 100 kHz, 1 V <sub>RMS</sub>                                                         |
| Leakage Inductance    | $\mu$ H          | Pins 1 to 4<br>Pins 2 to 3     | 85 +/- 20% | Pins 2 and 3 are shorted<br>Pins 1 and 4 are shorted<br>100 kHz, 1 V <sub>RMS</sub> |
| DC Resistance         | m $\Omega$       | Pins 1 to 4 and 2 to 3         | 25 +/- 12% | 25°C                                                                                |
| Dielectric strength   | V <sub>RMS</sub> | Pin 1 to pin 2                 | 1000       | 5 mA, 60 s                                                                          |
| Dielectric strength   | V <sub>RMS</sub> | Pin 1 to core<br>Pin 2 to core | 1000       | 5 mA, 60 s                                                                          |
| Insulation Resistance | M $\Omega$       | Pin 1 to core<br>Pin 2 to core | > 100      | 500 V <sub>DC</sub> , 60 s                                                          |


## 9 Transformer and inductor specifications

### 9.3 Auxiliary power inductor (T1)

The auxiliary power supply uses a multi-winding inductor custom-made according to the details given in the following figure.

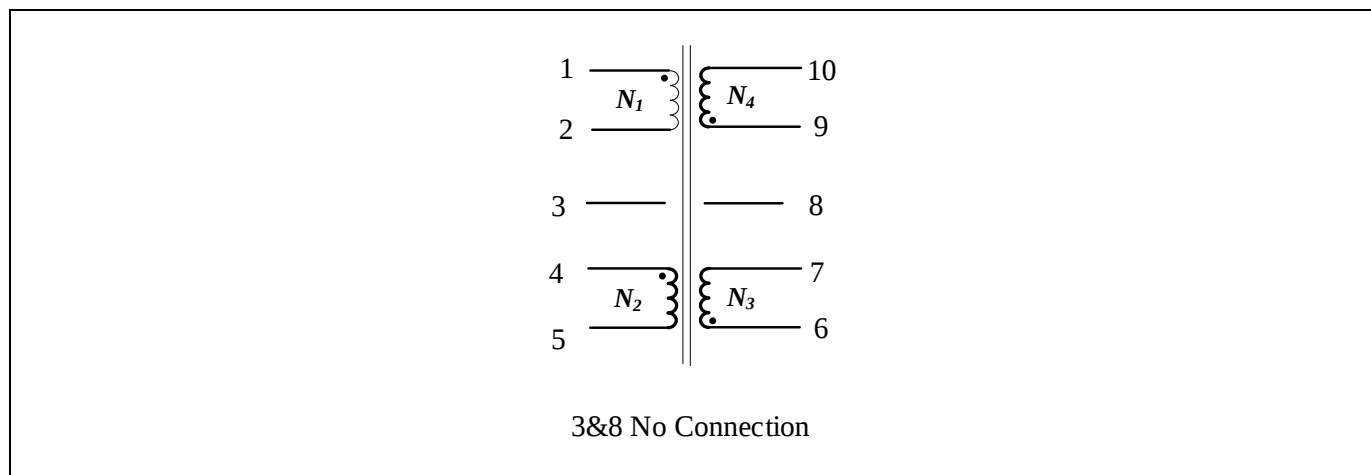


**Figure 110** Auxiliary power inductor format

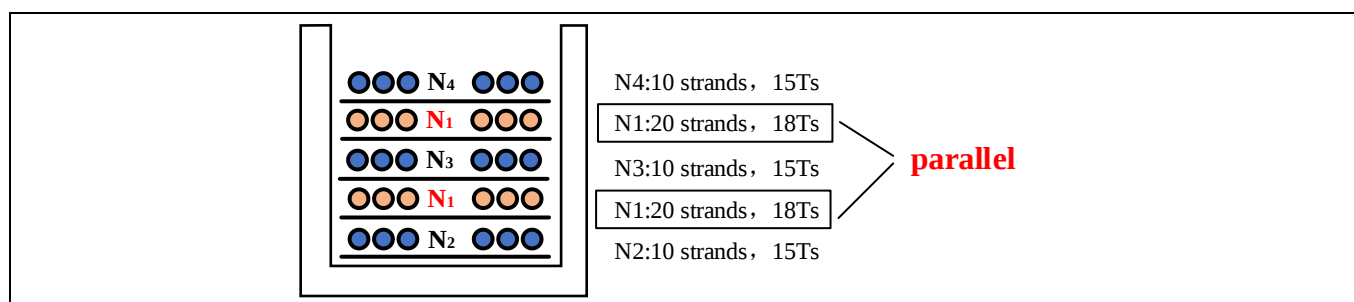

**Figure 111** Auxiliary power inductor winding stack-up


The cores are standard EE25 size made from PC95 material with the center post ground to create an air gap to provide the correct  $A_L$  value.

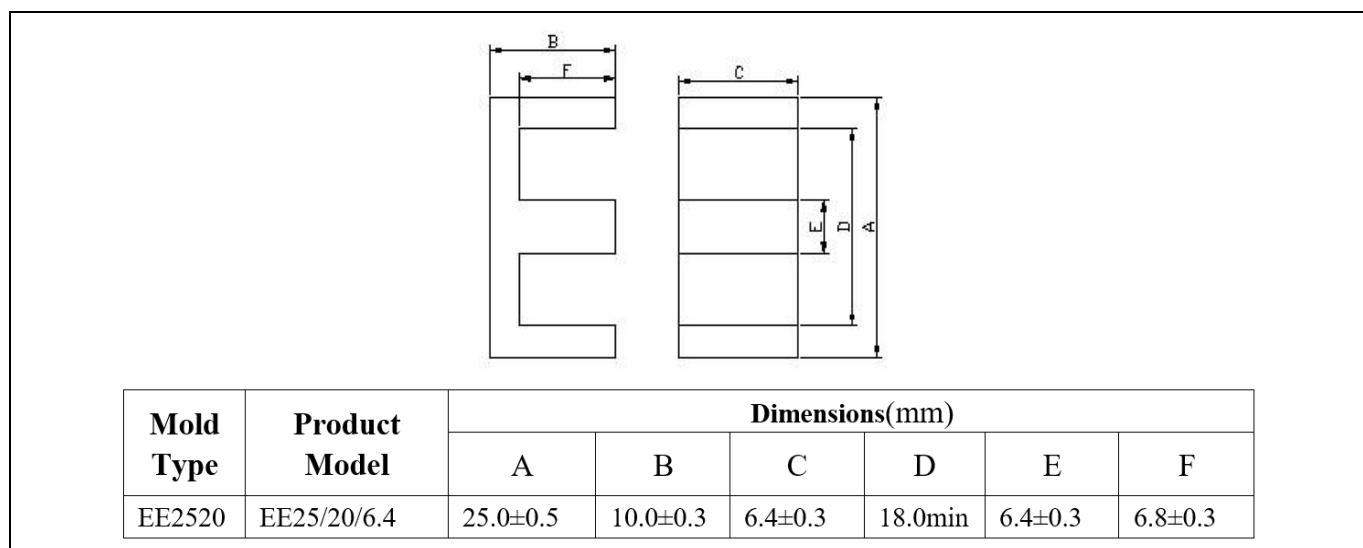

**Figure 112** Filter inductor cores

## 9 Transformer and inductor specifications

The bobbin is a horizontal single section type as shown in Figure 113.

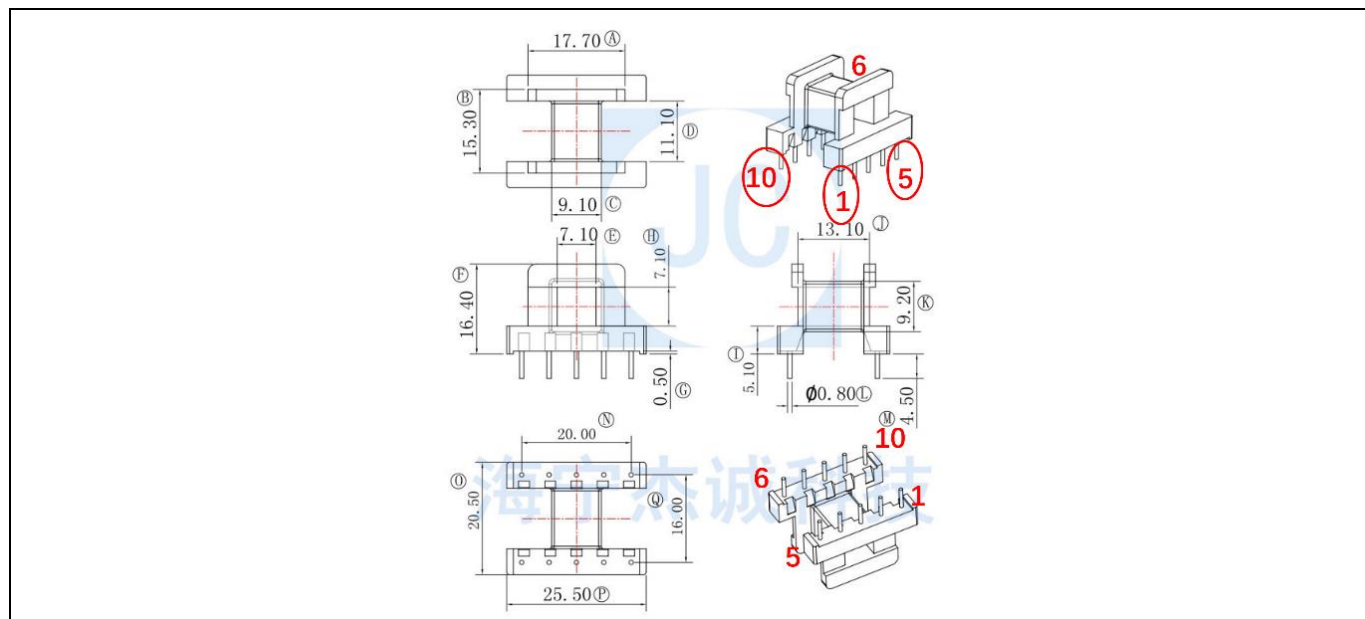

**Figure 113** Bobbin details and dimensions

**Table 16** Auxiliary power inductor winding specifications


| Winding                         | Start pin | Finish pin | Turns | Wire type                    | Winding notes |
|---------------------------------|-----------|------------|-------|------------------------------|---------------|
| N1                              | 1         | 2          | 18    | Ø0.1 mm Litz, 2 x 20 strands |               |
| Three layers of insulating tape |           |            |       |                              |               |
| N2                              | 4         | 5          | 15    | Ø0.1 mm Litz, 10 strands     |               |
| Three layers of insulating tape |           |            |       |                              |               |
| N3                              | 6         | 7          | 15    | Ø0.1 mm Litz, 10 strands     |               |
| Three layers of insulating tape |           |            |       |                              |               |
| N4                              | 9         | 10         | 15    | Ø0.1 mm Litz, 10 strands     |               |

**Table 17** Auxiliary power inductor test parameters


| Parameter             | Unit             | Measurement point                                                | Value      | Test condition              |
|-----------------------|------------------|------------------------------------------------------------------|------------|-----------------------------|
| Inductance            | µH               | Pins 1 to 2                                                      | 100 +/-15% | 100 kHz, 1 V <sub>RMS</sub> |
| DC Resistance         | mΩ               | Pins 1 to 2                                                      | < 100 mΩ   | 25°C                        |
| Dielectric strength   | V <sub>RMS</sub> | Pin 1 to pin 4<br>Pin 1 to pin 6<br>Pin 1 to pin 9               | 1500       | 50 Hz, 3 mA, 60 s           |
| Insulation Resistance | MΩ               | Pin 1 to core<br>Pin 4 to core<br>Pin 6 to core<br>Pin 9 to core | > 100      | 500 V <sub>DC</sub> , 60 s  |

### 10 PCB layout design


The main PCB is fabricated on 6-layer FR4 material using 2 oz. copper on all layers with all components mounted on the top side.

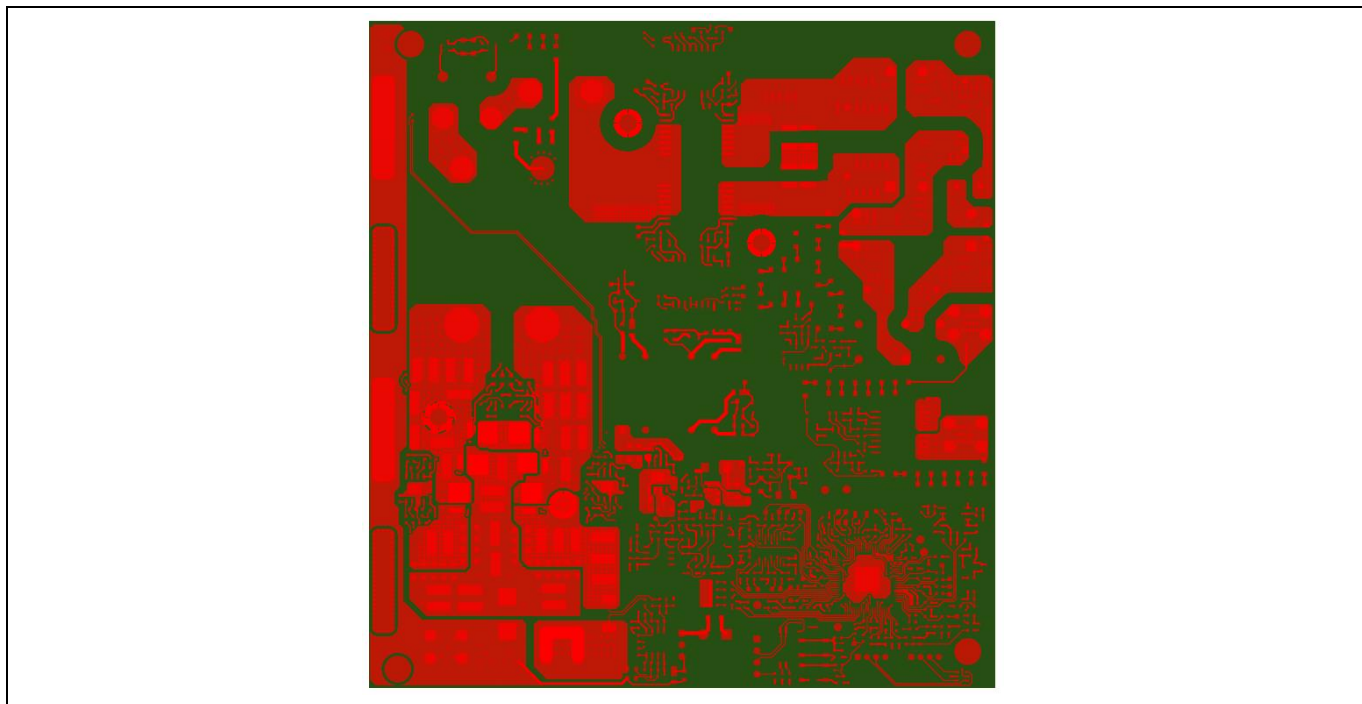


**Figure 114** Top layer copper

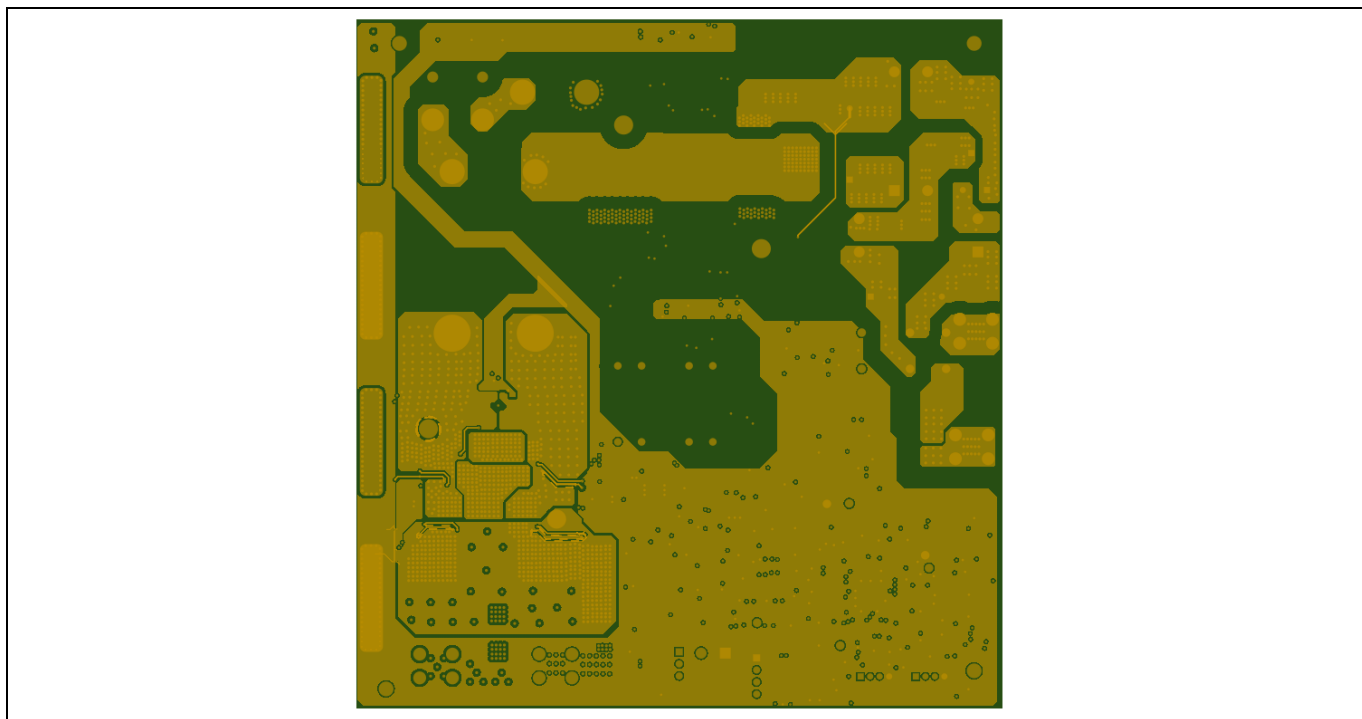


**Figure 115** First inner layer copper

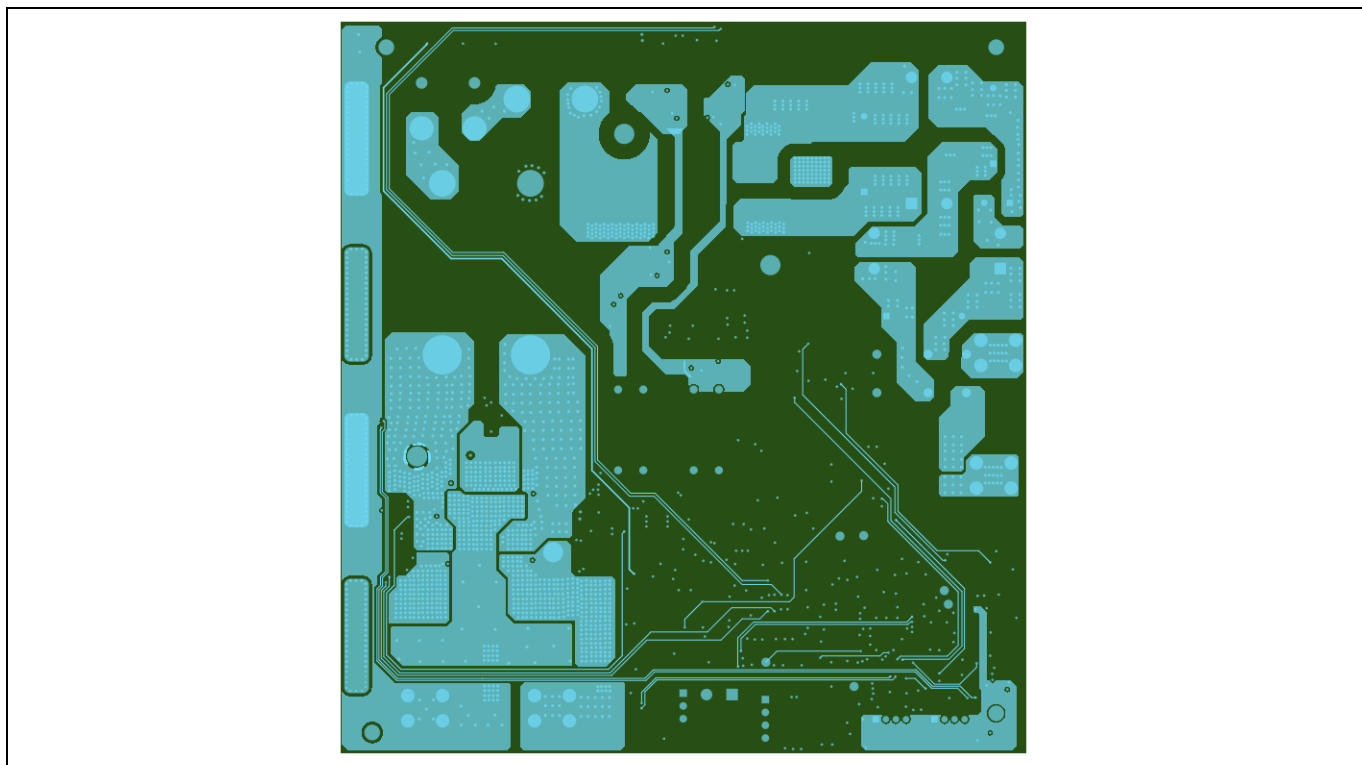


**Figure 116** Second inner layer copper

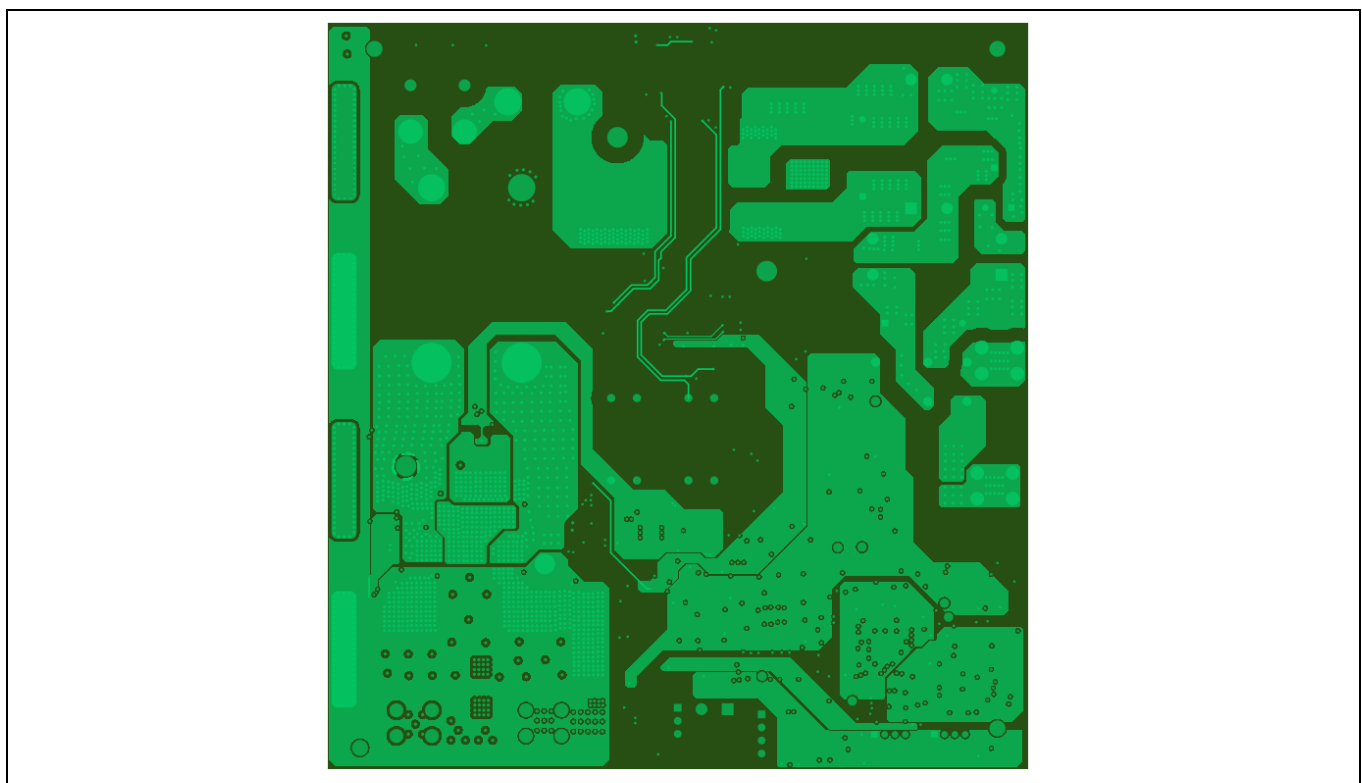

**Figure 117** Third inner layer copper

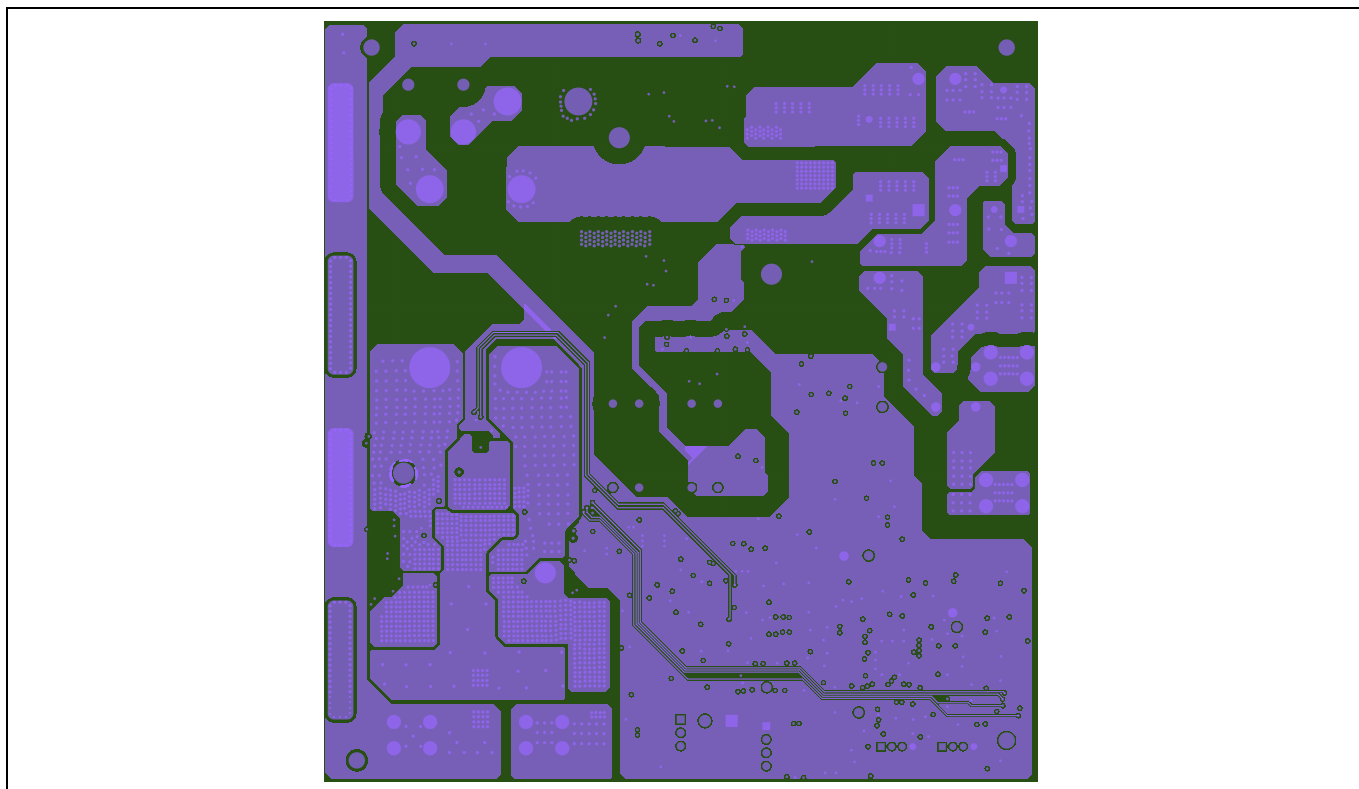

**Figure 118** Fourth inner layer copper

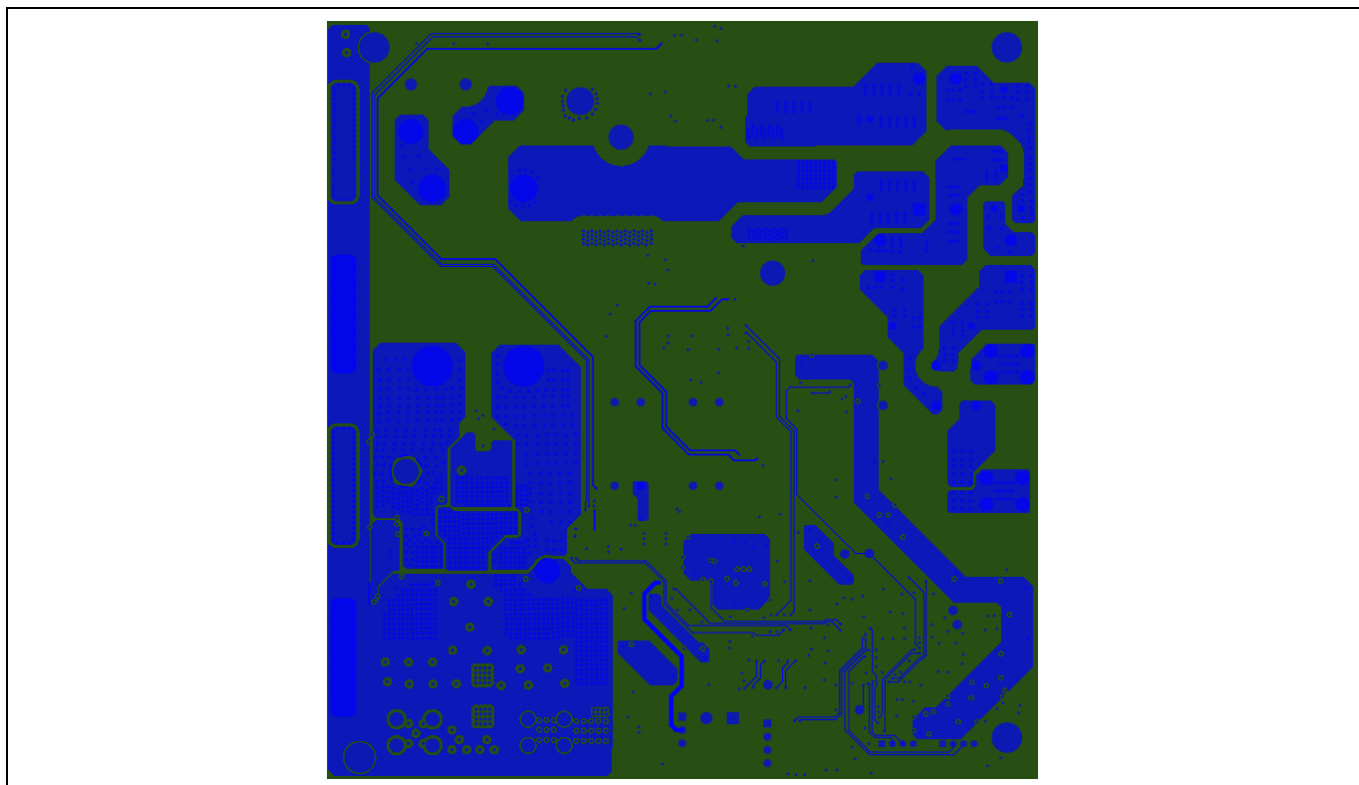

**Figure 119** Bottom layer copper

## 10 PCB layout design

The layer composition is as follows:


**Table 18 Layer organization**

| Layer       | Power planes                                                                                                                                                                     | Signal traces                                                         | Comment                                                              |
|-------------|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----------------------------------------------------------------------|----------------------------------------------------------------------|
| L1 (top)    | DC+ input terminal<br>DC- input current shunt<br>Electrolytic capacitor connections<br>Primary switches<br>Main transformer<br>Secondary switches<br>Output filter and terminals | MCU connections<br>Sensing amplifiers and other low control circuitry | The majority of the signal connections are located on this layer     |
| L2 (inner)  | DC- power plane<br>Primary ground plane<br>Primary switches<br>Main transformer<br>Output filter and terminals                                                                   | VAC- sensing                                                          | No other signal traces on this layer                                 |
| L3 (inner)  | DC+ input terminal<br>DC- input current shunt<br>Primary switches<br>Main transformer<br>Output filter and terminals                                                             |                                                                       | Some parallel signal sensing traces some miscellaneous signal traces |
| L4 (inner)  | Auxiliary power and voltage reference planes<br>Primary switches<br>Main transformer<br>Output filter and terminals                                                              |                                                                       | Some parallel signal sensing traces some miscellaneous signal traces |
| L5 (inner)  | DC+ input terminal<br>DC- input current shunt<br>Primary switches<br>Main transformer<br>Output filter and terminals<br>Large primary ground plane                               |                                                                       | Some parallel signal sensing traces some miscellaneous signal traces |
| L6 (bottom) | DC- power plane<br>Primary ground plane<br>Primary switches<br>Main transformer<br>Output filter and terminals                                                                   |                                                                       | Some parallel signal sensing traces some miscellaneous signal traces |


In general, the board has been designed to provide the maximum sized possible power planes duplicated on different layers to minimize conduction losses. Sensitive signal sensing traces and other PWM signals are carried along parallel traces to minimize inductance and surrounded by ground plane as much as possible.

### 10.1 Electrolytic capacitor board

The DC input electrolytic capacitors are mounted on a separate daughter card, which is inserted into slotted pads on the main board to provide a secure mechanical and electrical connection. This mounting method has been implemented because the capacitors are physically large with short snap-in type terminals.

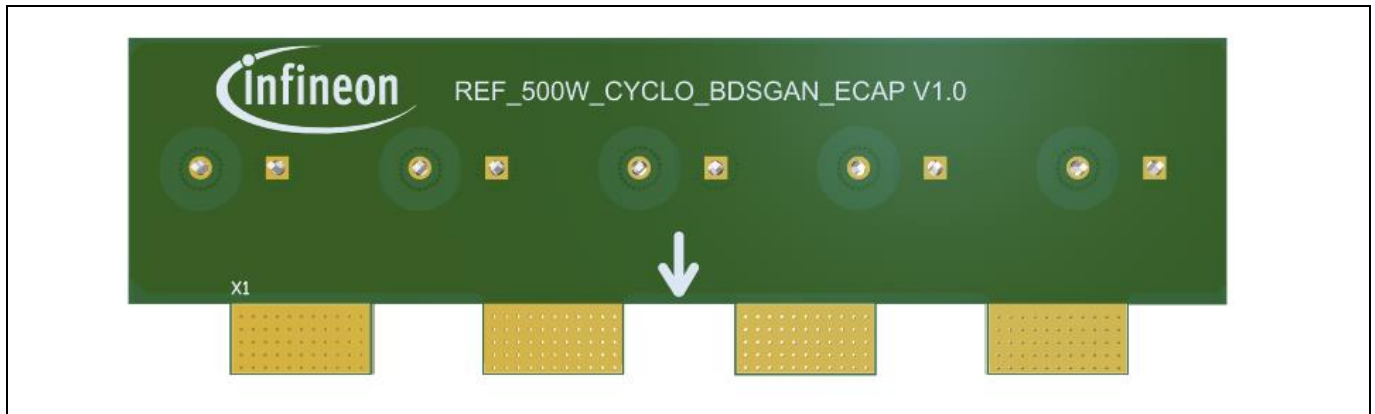

**Figure 120** Electrolytic capacitor board front

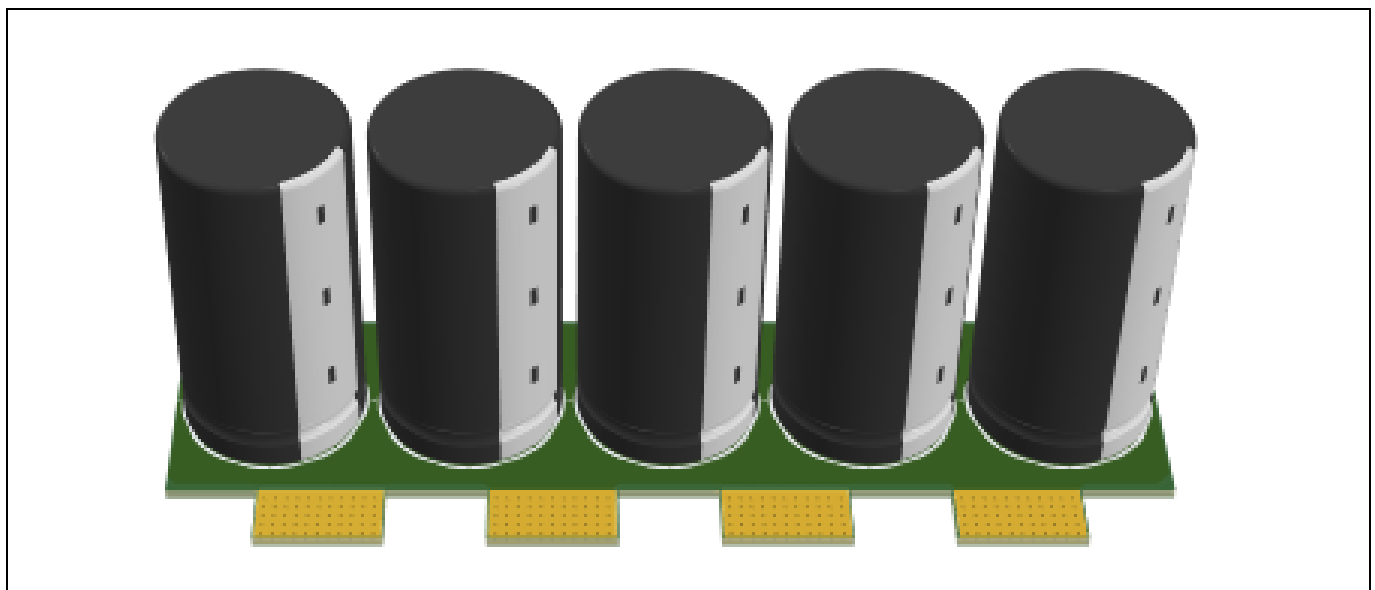

**Figure 121** Electrolytic capacitor board back

## 11 Test results

### 11 Test results

#### 11.1 Power and efficiency measurements


All measurements have been averaged over 64 samples to remove fluctuations due to ripple to provide stable and repeatable results.

##### 11.1.1 Off-grid operation

The following measurements were made for off-grid operation at 240 V<sub>RMS</sub> 60 Hz:

**Table 19** Test measurements – off grid operation

| DC Input voltage | DC input current | Input power | AC Output RMS voltage | AC Output RMS current | Power Factor | Output power | Efficiency | iTHD |
|------------------|------------------|-------------|-----------------------|-----------------------|--------------|--------------|------------|------|
| 36.021           | 3.5996           | 105.74      | 239.16                | 0.40606               | 0.999        | 97.1         | 91.83%     | 2.6% |
| 35.968           | 7.121            | 205.82      | 238.73                | 0.8329                | 0.999        | 198.85       | 96.61%     | 2.8% |
| 35.914           | 10.624           | 304.95      | 238.23                | 1.2471                | 0.999        | 296.82       | 97.33%     | 2.3% |
| 35.864           | 14.087           | 403.7       | 237.75                | 1.6561                | 0.999        | 393.47       | 97.47%     | 1.8% |
| 35.812           | 17.43            | 500.3       | 237.26                | 2.0539                | 1            | 487.07       | 97.36%     | 1.4% |

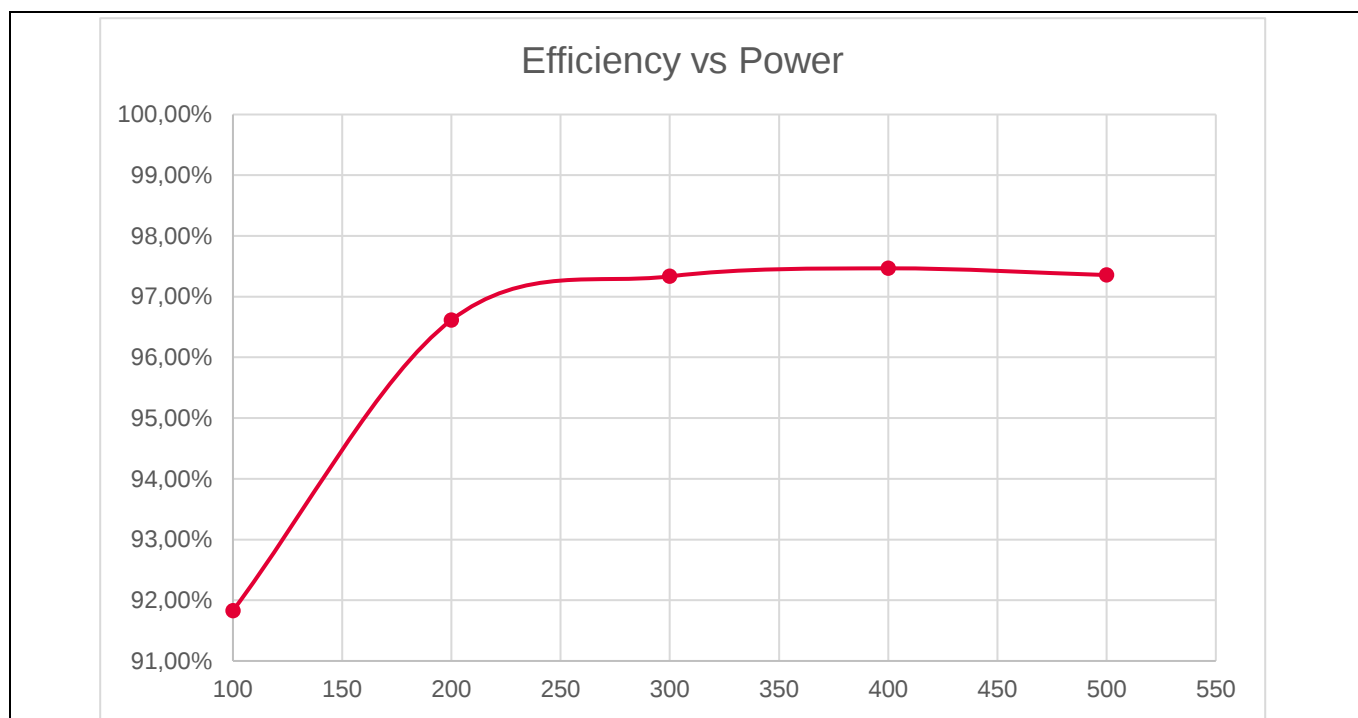


**Figure 122** Off-grid operation efficiency curve


## 11 Test results

### 11.1.1.1 Voltage and current harmonics

The following measurements of harmonic content of the voltage and current outputs from the fundamental to the 40<sup>th</sup> harmonic indicating low THD with the majority of harmonic content in the odd harmonics:

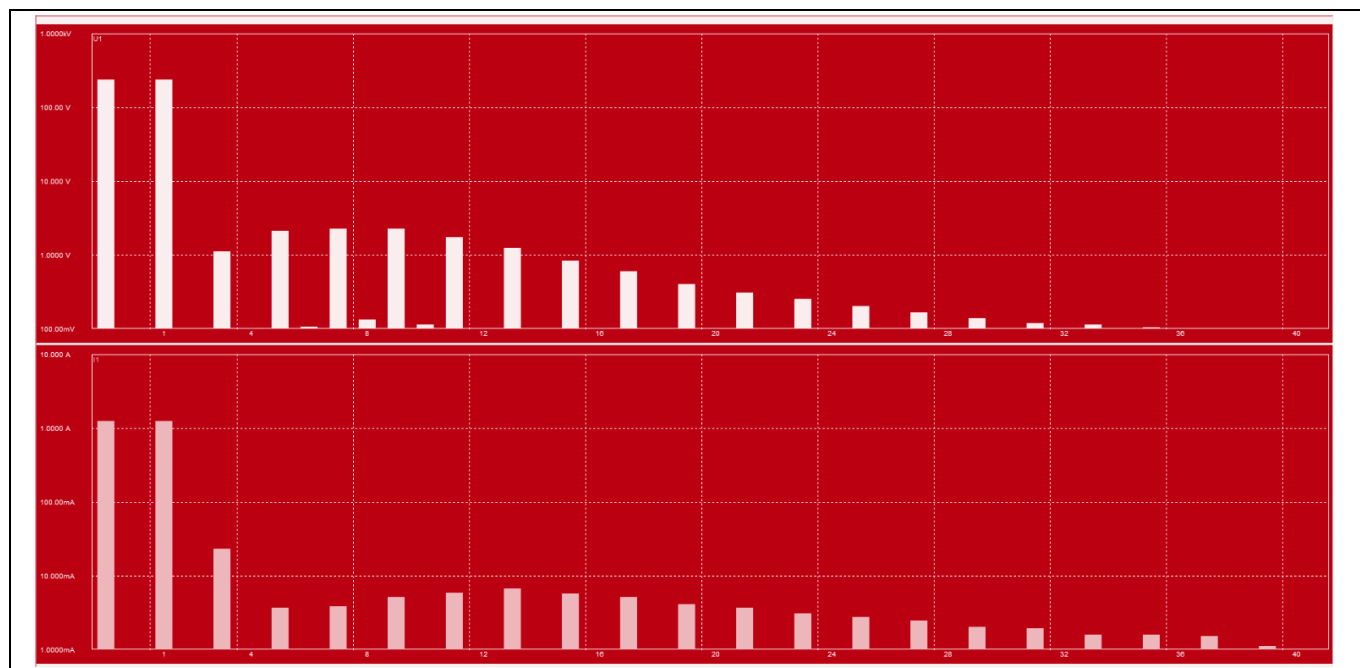

**Figure 123** Voltage (top) and current (bottom) harmonic content at 300 W output

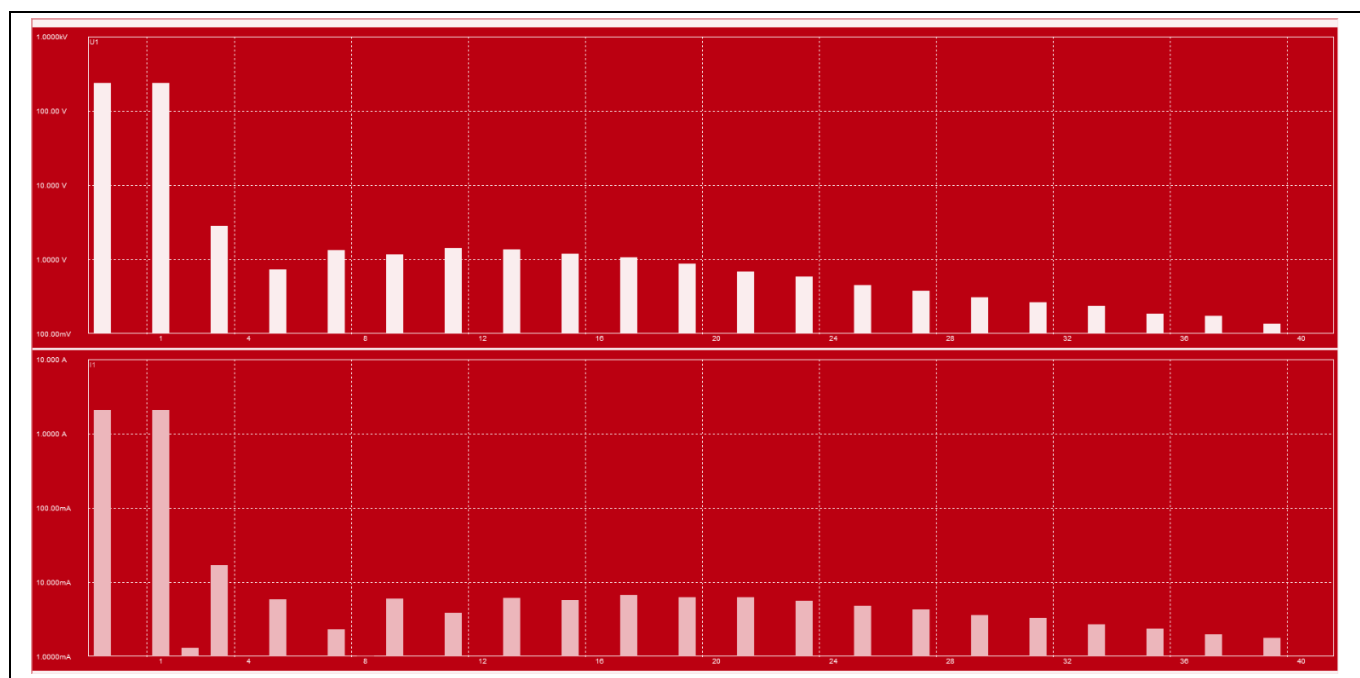

**Figure 124** Voltage (top) and current (bottom) harmonic content at 500 W output


## 11 Test results

### 11.1.2 On-grid operation with burst mode enabled

The following measurements were made for on-grid operation at 240 V<sub>RMS</sub> 60 Hz with burst mode enabled.

**Table 20 Test measurements – on-grid operation (burst mode enabled)**

| DC Input voltage | DC input current | Input power | AC Output RMS voltage | AC Output RMS current | Power Factor | Output power | Efficiency |
|------------------|------------------|-------------|-----------------------|-----------------------|--------------|--------------|------------|
| 36.042           | 4.244            | 63.300      | 240.160               | 0.498                 | 0.475        | 57.400       | 90.68%     |
| 36.015           | 5.901            | 124.150     | 240.160               | 0.693                 | 0.689        | 118.400      | 95.37%     |
| 35.983           | 8.826            | 180.700     | 240.280               | 1.014                 | 0.705        | 175.000      | 96.85%     |
| 35.946           | 8.549            | 247.570     | 240.380               | 1.001                 | 0.997        | 239.730      | 96.83%     |
| 35.912           | 10.676           | 308.190     | 240.470               | 1.250                 | 0.998        | 299.710      | 97.25%     |
| 35.881           | 12.830           | 369.300     | 240.570               | 1.498                 | 0.998        | 359.680      | 97.40%     |
| 35.847           | 14.950           | 429.800     | 240.650               | 1.743                 | 0.998        | 418.500      | 97.37%     |
| 35.816           | 17.046           | 488.700     | 240.730               | 1.979                 | 0.998        | 475.480      | 97.29%     |

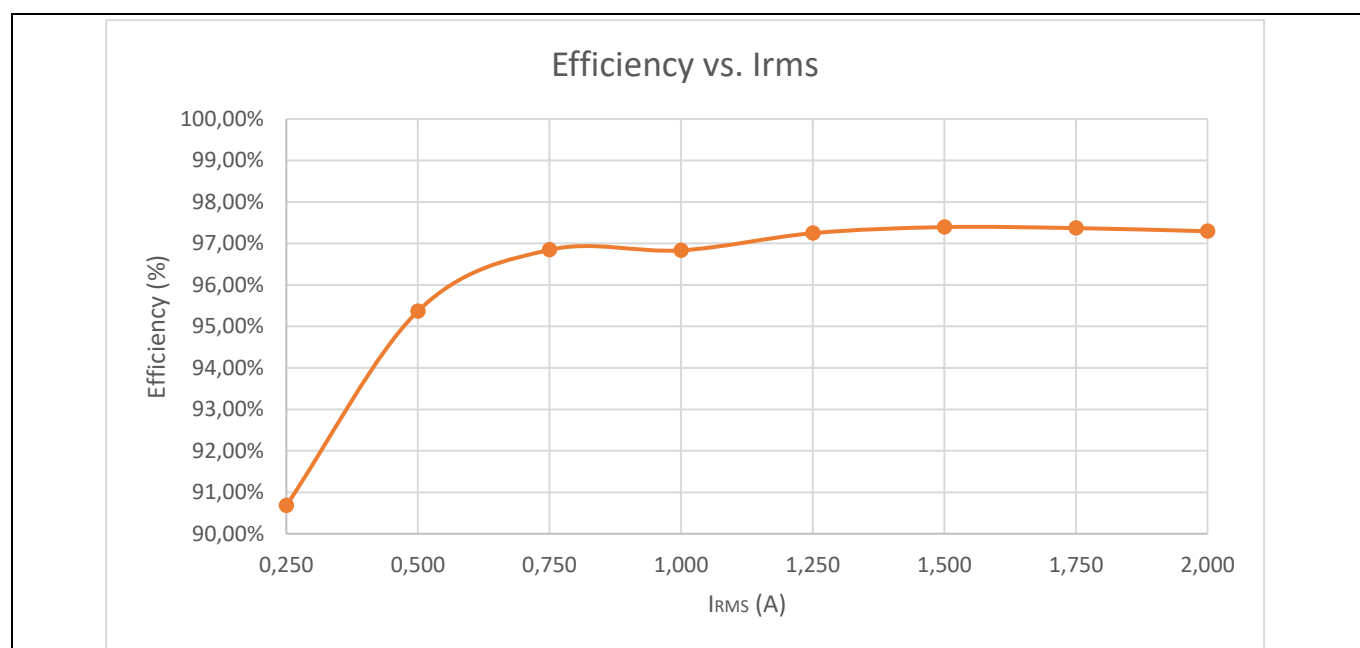

**Figure 125 On-grid operation with burst mode enabled efficiency curve**

The **peak efficiency is 97.4 percent**, measured at 1.5 A<sub>RMS</sub> output current corresponding to approximately 360 W, which is 72 percent of the maximum rated load.

The results shown here are for a fully optimized board including fine tuning of firmware parameters. Results may vary depending on component tolerances.


## 11 Test results

### 11.1.2.1 CEC weighted efficiency measurements and calculation

The following measurements were made for on-grid operation at 240 V<sub>RMS</sub> 60 Hz with burst mode enabled. Measurements are made for specific load levels defined for the CEC weighted efficiency formula. CEC measurements – on-grid operation (burst mode enabled) CEC.

**Table 21 CEC weighted efficiency measurements and calculation**

| Load | DC input voltage | DC input current | Input power | AC output RMS voltage | AC output RMS current | Power factor | Output power | Efficiency |
|------|------------------|------------------|-------------|-----------------------|-----------------------|--------------|--------------|------------|
| 5%   | 36.060           | 2.860            | 31.200      | 240.370               | 0.336                 | 0.303        | 24.420       | 78.269%    |
| 10%  | 36.048           | 4.030            | 55.050      | 240.180               | 0.472                 | 0.428        | 48.830       | 88.701%    |
| 20%  | 36.023           | 6.086            | 103.520     | 240.340               | 0.710                 | 0.570        | 97.500       | 94.185%    |
| 30%  | 36.000           | 7.263            | 146.800     | 240.200               | 0.850                 | 0.694        | 141.600      | 96.458%    |
| 50%  | 35.942           | 8.893            | 257.620     | 240.350               | 1.041                 | 0.997        | 249.720      | 96.933%    |
| 75%  | 35.871           | 13.379           | 384.800     | 240.590               | 1.561                 | 0.998        | 374.710      | 97.378%    |
| 100% | 35.806           | 17.748           | 508.300     | 240.760               | 2.057                 | 0.998        | 494.340      | 97.254%    |

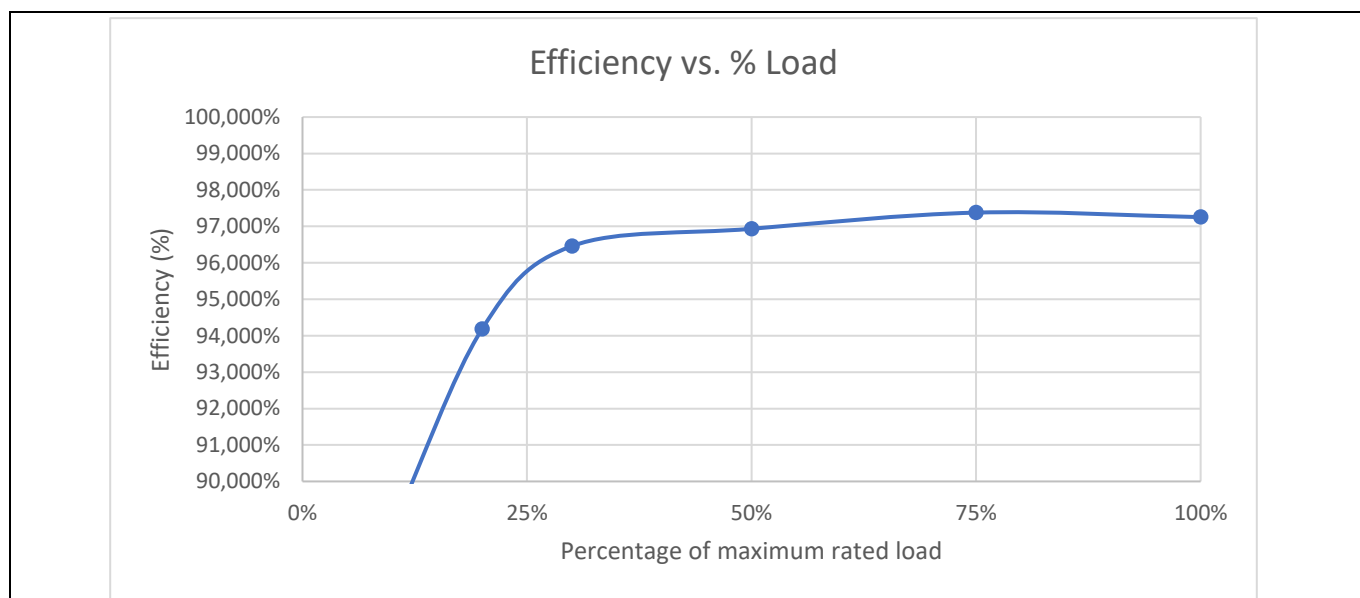

**Figure 126 On grid operation with burst mode enabled efficiency curve**

CEC weighted efficiency is calculated as follows:

$$EFF_{CECW} = (0.04 \times Eff@10\%) + (0.05 \times Eff@20\%) + (0.12 \times Eff@30\%) + (0.21 \times Eff@50\%) + (0.53 \times Eff@75\%) + (0.05 \times Eff@100\%)$$

$$EFF_{CECW} = 96.7\%$$

#### Equation 47

## 11 Test results

European weighted efficiency is calculated as follows:

$$EFF_{EU} = (0.03 \times Eff@5\%) + (0.06 \times Eff@10\%) + (0.13 \times Eff@20\%) + (0.1 \times Eff@30\%) + (0.48 \times Eff@50\%) + (0.2 \times Eff@100\%)$$

$$EFF_{EU} = 95.5\%$$

Equation 48

### 11.1.3 MPPT efficiency

The MPPT function of the REF\_500W\_CYCLO\_BDSGAN board is tested by connecting the DC inputs to a Chroma 62150H-1000S PV array simulator and the GUI to setting Grid ON mode and clicking the **MPPT ON/OFF** button to enable it instead of setting a defined output current. The AC grid simulator voltage is set to 240 V<sub>RMS</sub> and switched on before pressing the **START/STOP** button to begin operation.

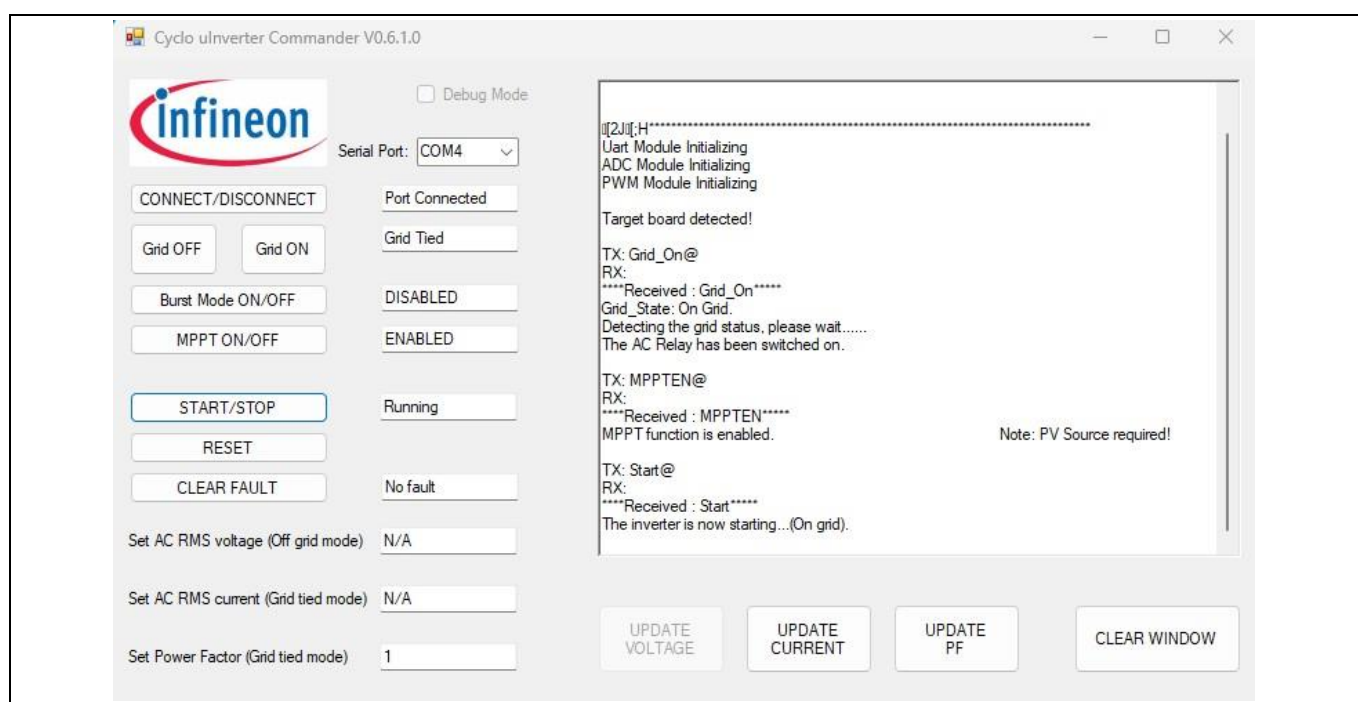


Figure 127 Setting MPPT mode for grid tied operation

Tests were performed at three different power levels at various input voltages:

Table 22 MPPT efficiency measurements at different input voltages and loads

| DC input voltage | 25% rated load | 50% rated load | 75% rated load |
|------------------|----------------|----------------|----------------|
| 30               | 99.32%         | 99.52%         | 99.69%         |
| 35               | 98.57%         | 99.88%         | 99.89%         |
| 40               | 97.46%         | 99.93%         | 99.90%         |
| 45               | 96.76%         | 99.89%         | 99.91%         |
| 50               | 96.05%         | 99.99%         | 99.99%         |

# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter

## 11 Test results

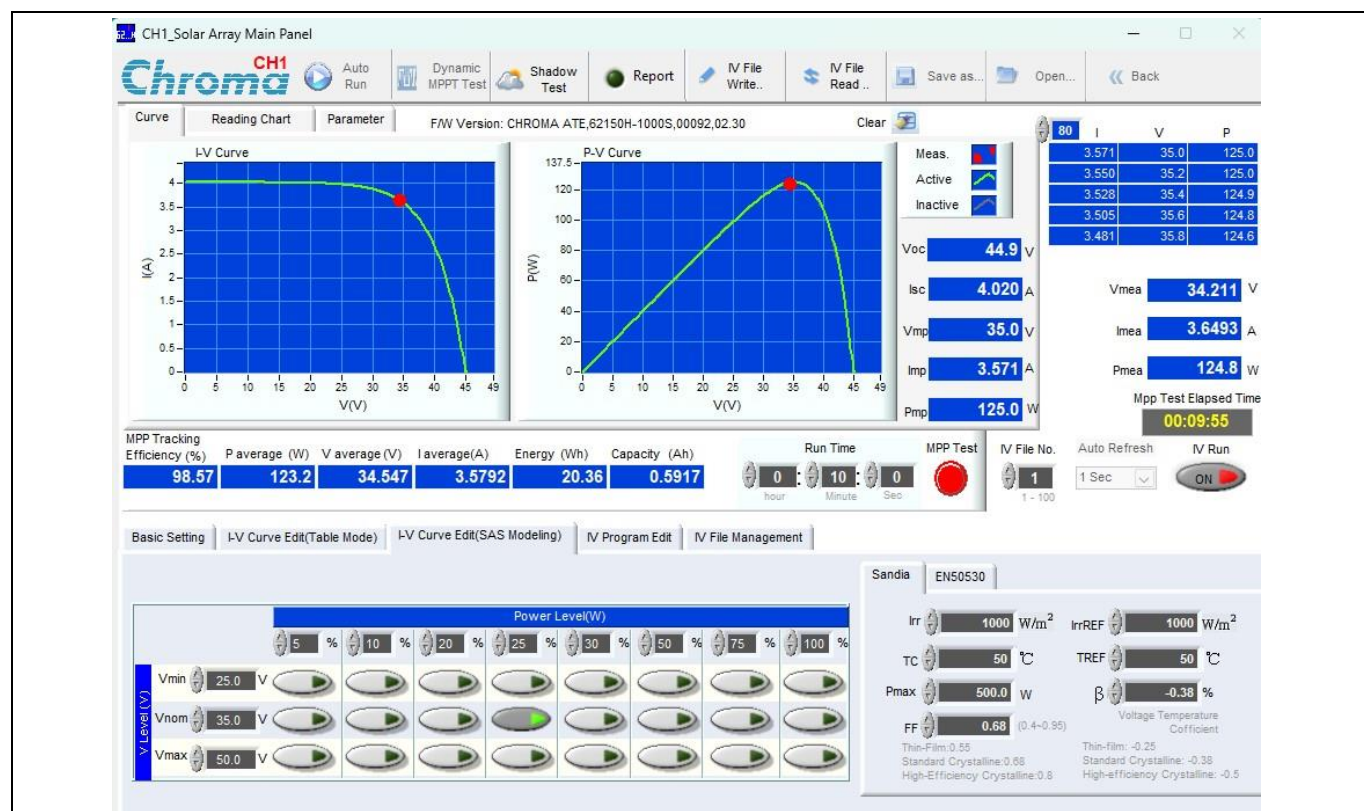


Figure 128 Operating point 35V input, 25% load

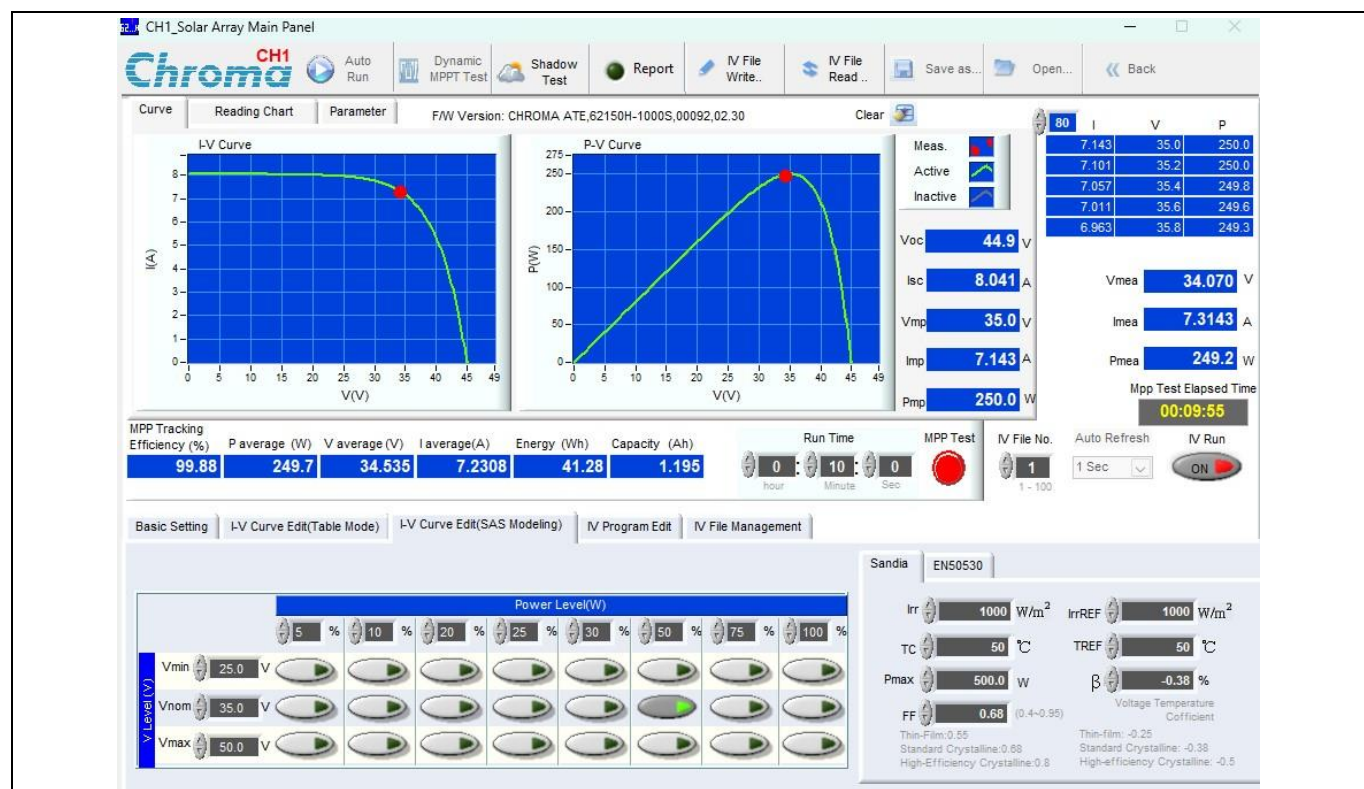


Figure 129 Operating point 35V input, 50% load

# CoolGaN™ bidirectional switch 650 V G5 cycloconverter-based solar microinverter

## 11 Test results

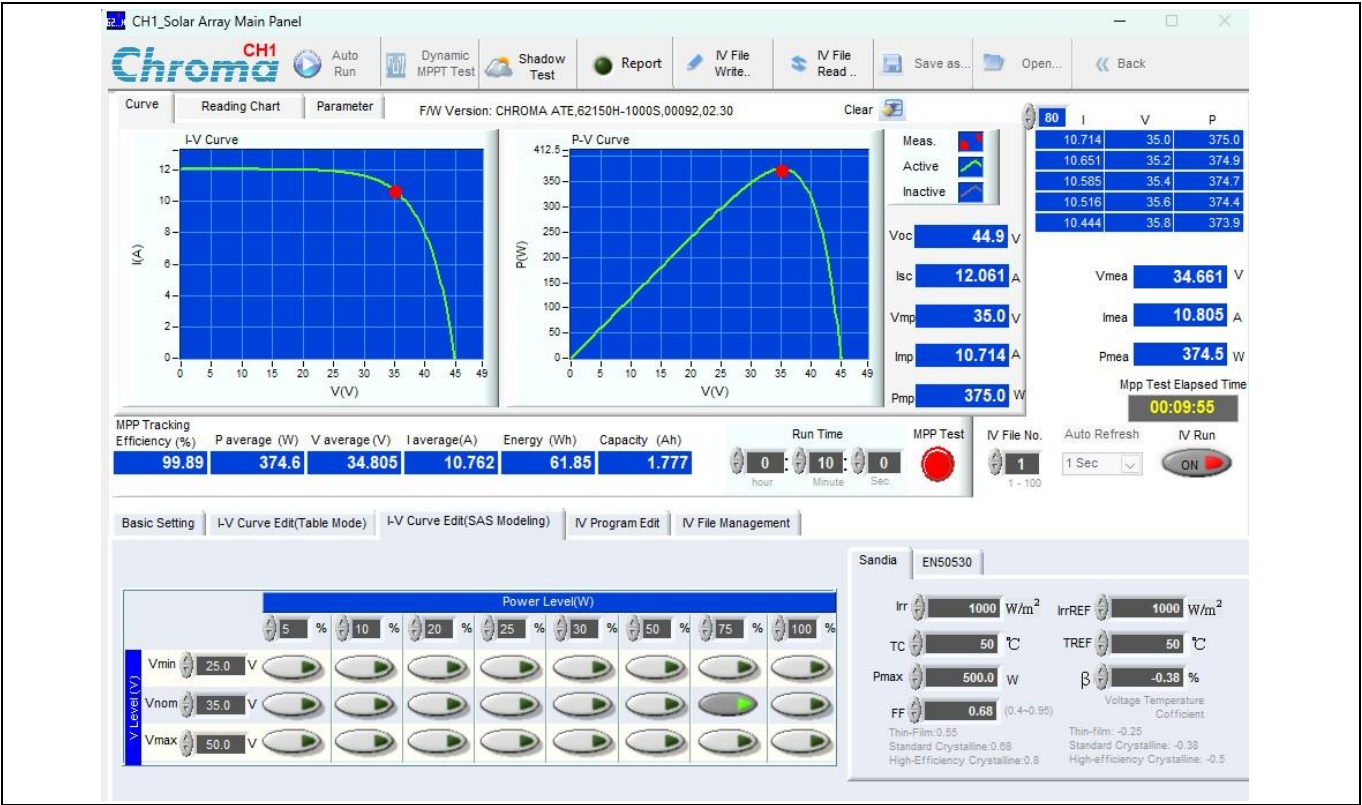


Figure 130 Operating point 35V input, 75% load

## 11.2 Thermal measurements

The following thermal image was captured after 30 minutes of operation at maximum load with no forced air cooling:



Figure 131 REF\_500W\_CYCLO\_BDSGAN thermal image


## 11 Test results

It can be seen that the maximum temperature on the board is around 62 degrees Celsius, measured at the main transformer and that the bidirectional GaN switches reach a similar temperature.


### 11.3 Operating waveforms

Measurements are taken at 35 V input and 240 V<sub>RMS</sub> output.

#### 11.3.1 Off-grid operation

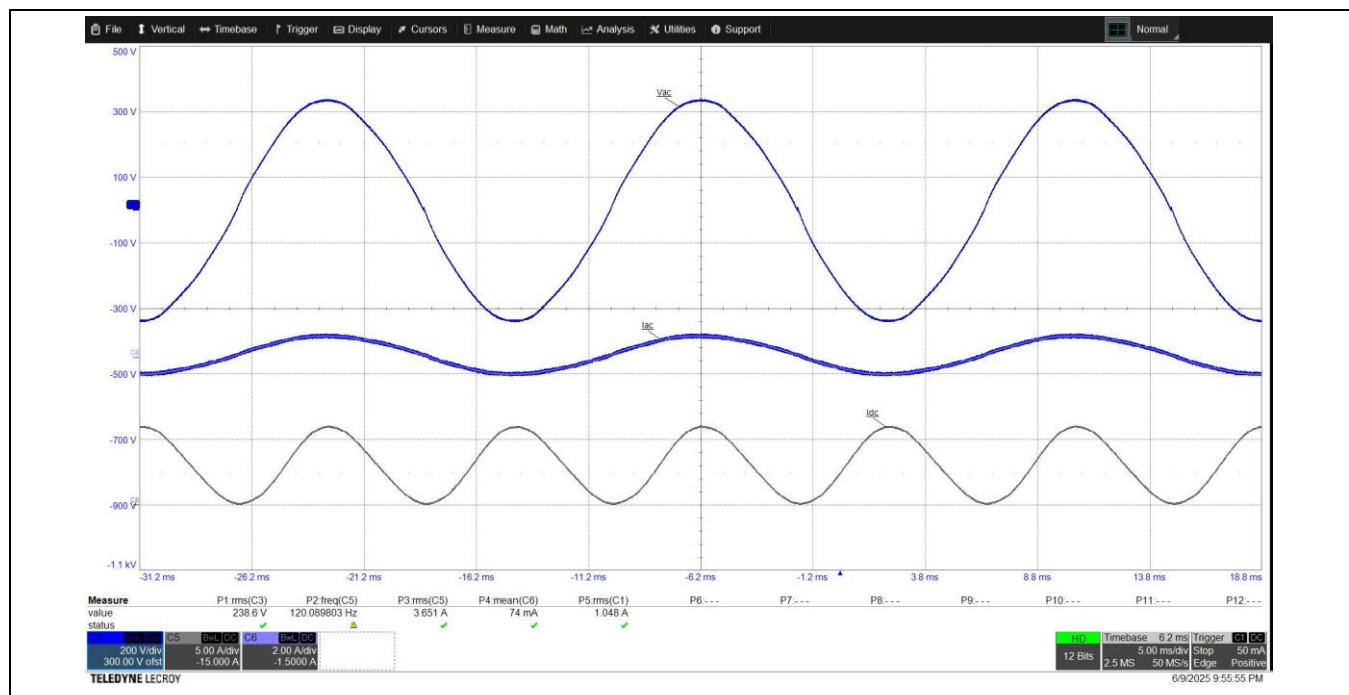

**Figure 132** Load 100 W - output voltage (blue), output current (purple), DC input current (gray)

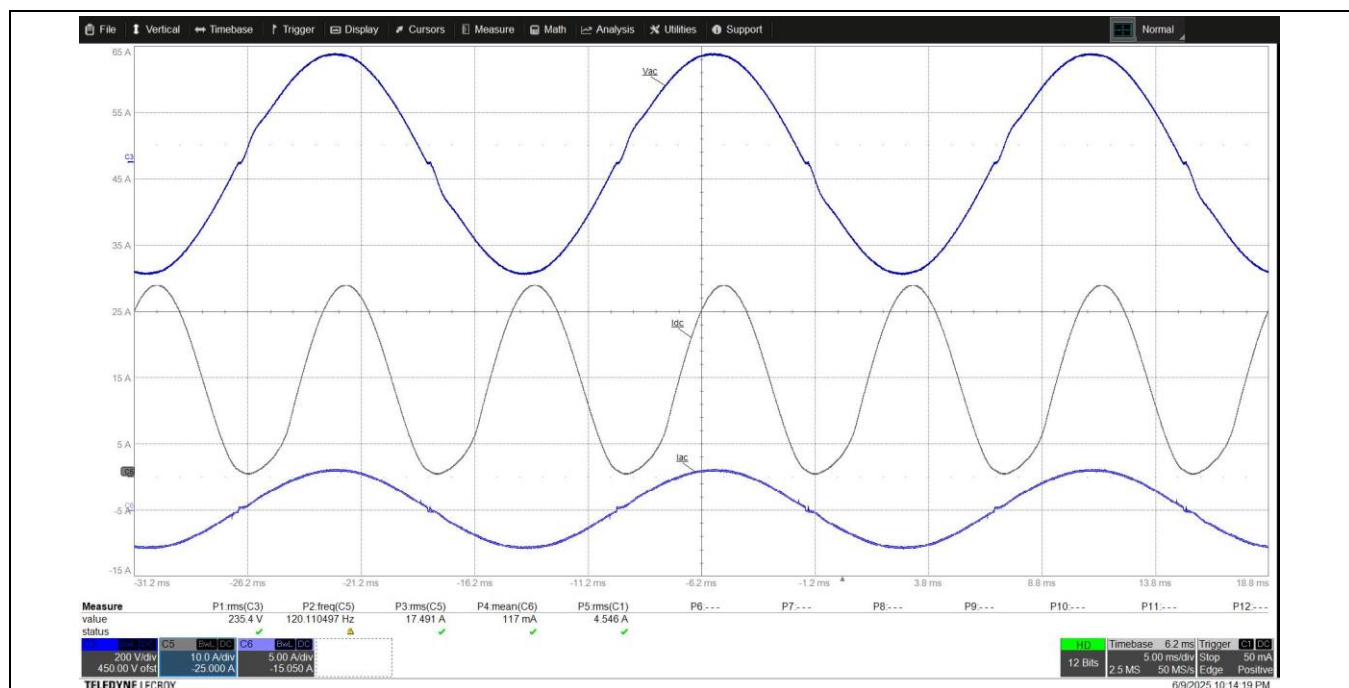


**Figure 133** Load 500 W - output voltage (blue), output current (purple), DC input current (gray)

## 11 Test results


### 11.3.2 On-grid operation

Measurements are taken at 240 V<sub>RMS</sub> output.

#### 11.3.2.1 Input 35 VDC

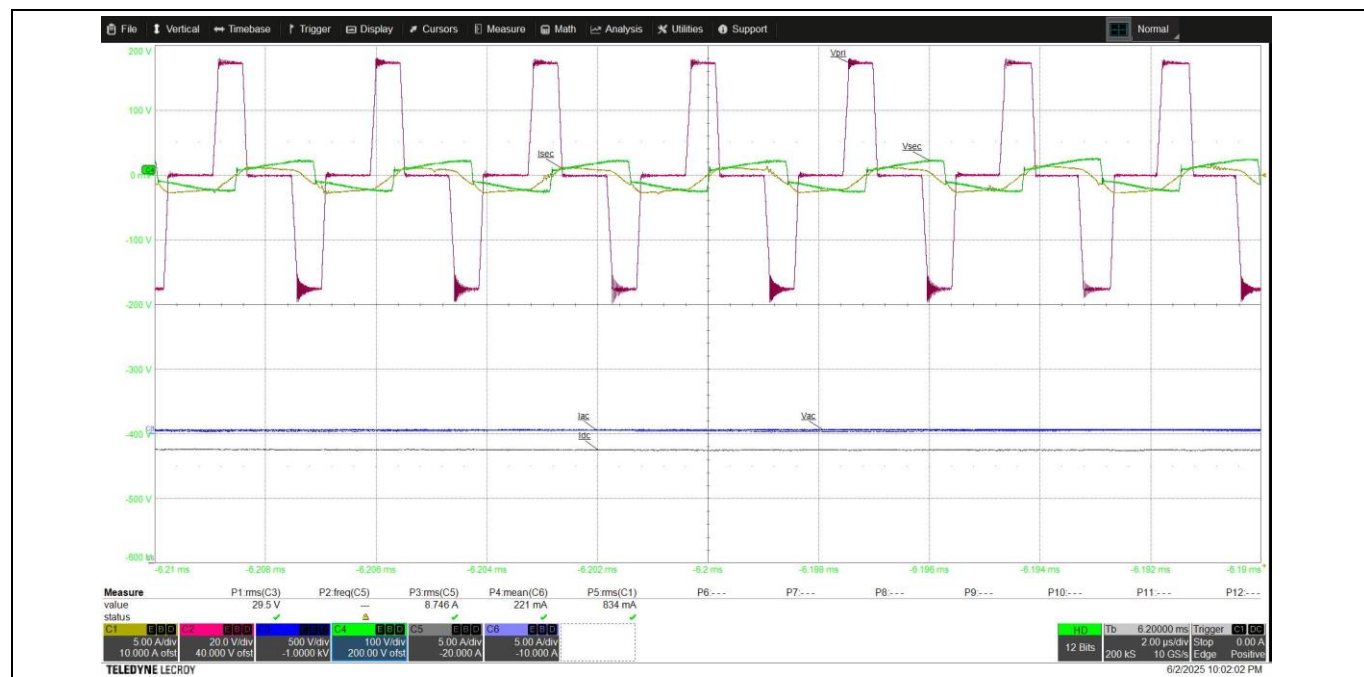


**Figure 134** Output 1.0 A<sub>RMS</sub> - primary voltage (red), secondary voltage (green), resonant current (yellow)

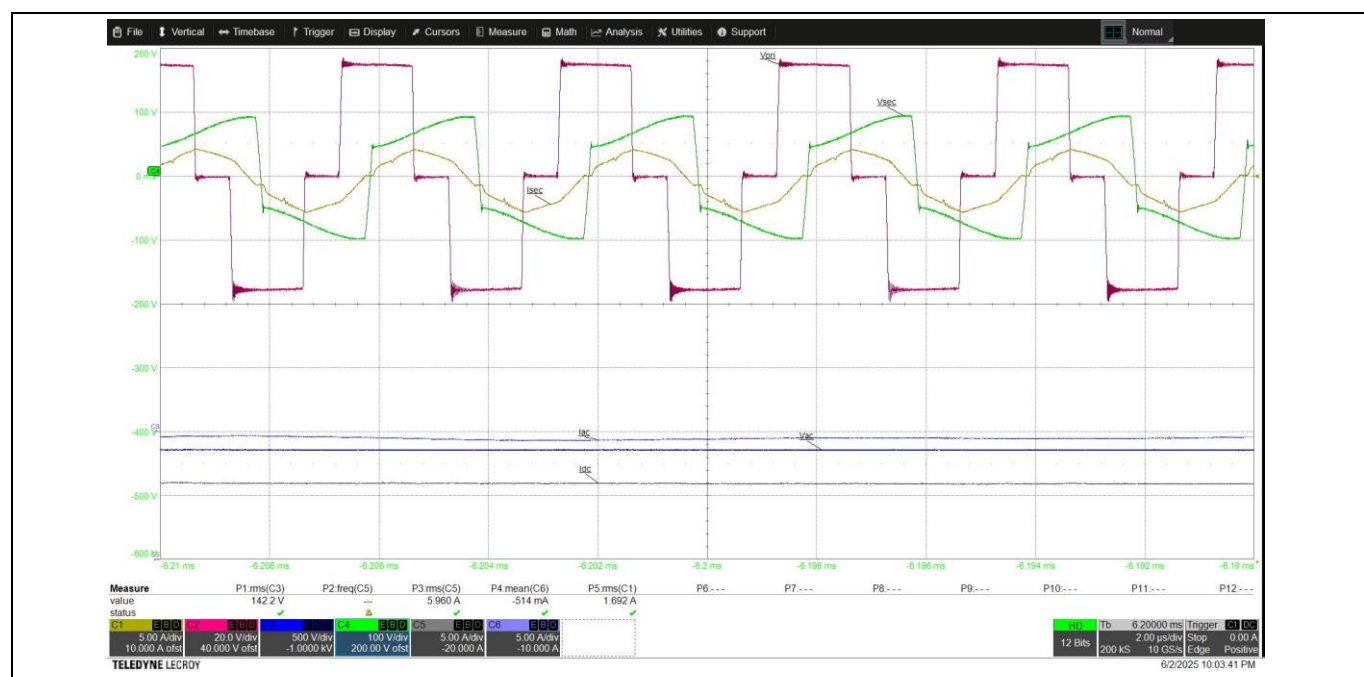


**Figure 135** Output 1.0 A<sub>RMS</sub> - primary voltage (red), secondary voltage (green), resonant current (yellow)

## 11 Test results

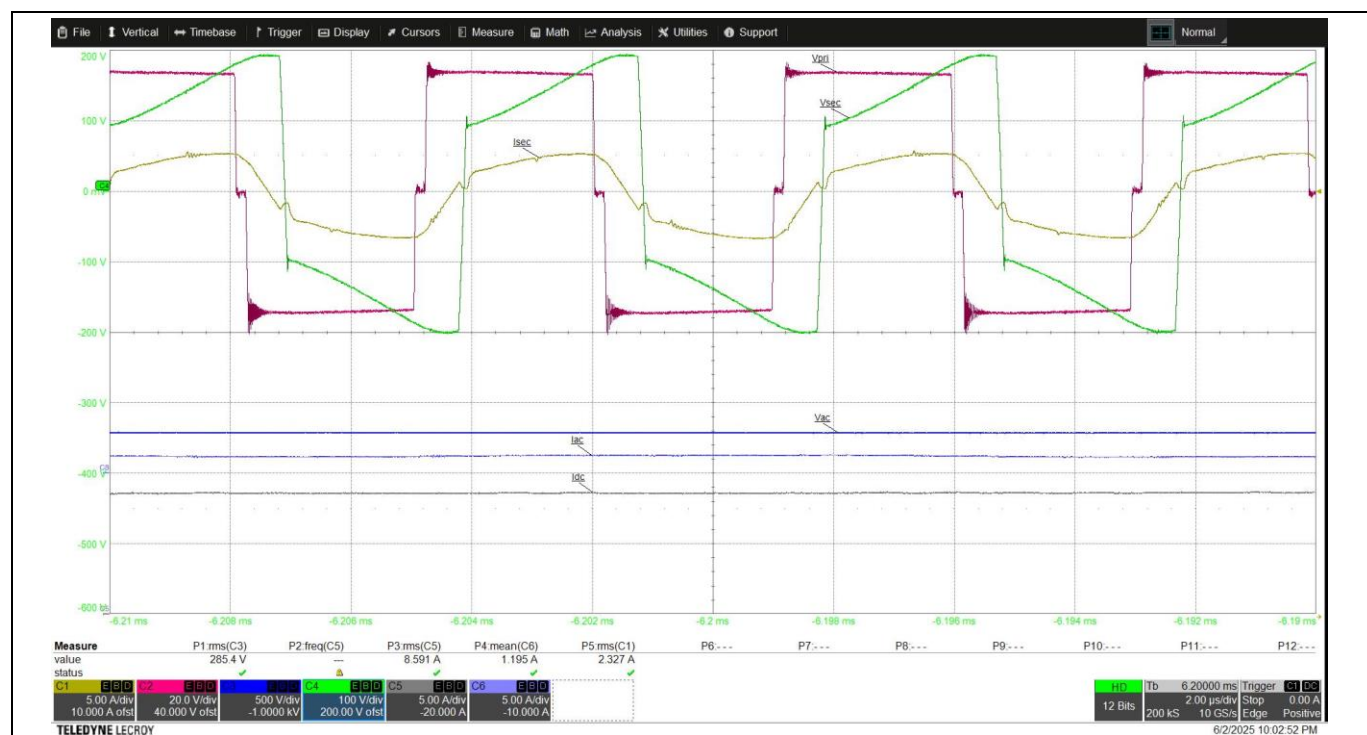


**Figure 136** Output 1.0 A<sub>RMS</sub> - primary voltage (red), secondary voltage (green), resonant current (yellow)

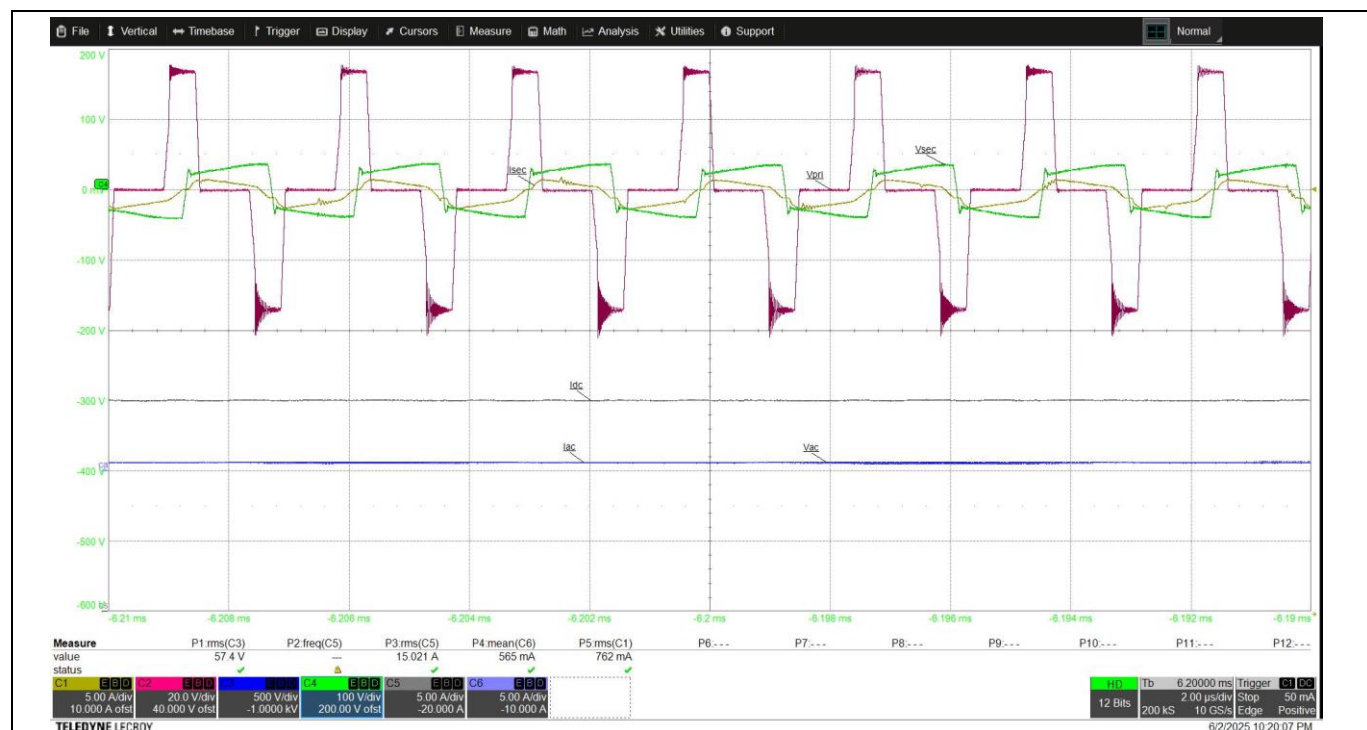


**Figure 137** Output 2.0 A<sub>RMS</sub> - primary voltage (red), secondary voltage (green), resonant current (yellow)

## 11 Test results

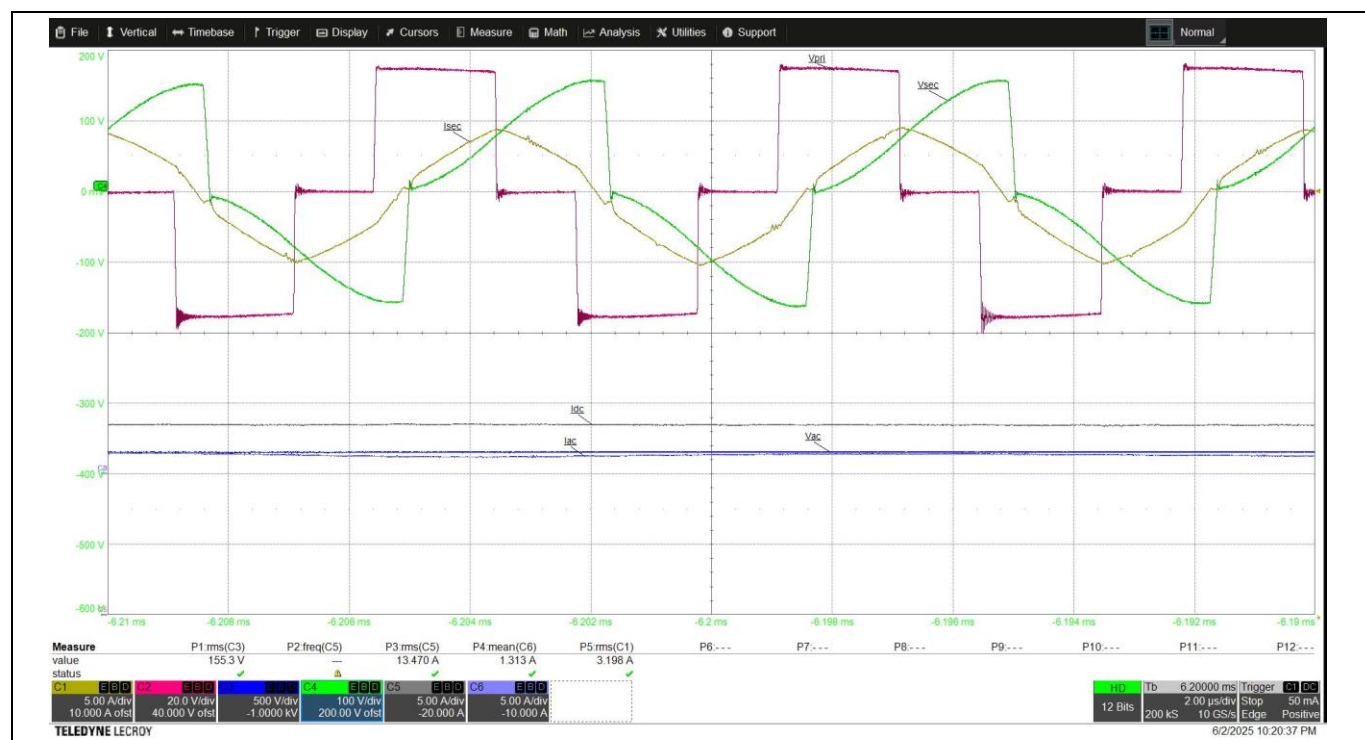


**Figure 138** Output 2.0 A<sub>RMS</sub> - primary voltage (red), secondary voltage (green), resonant current (yellow)

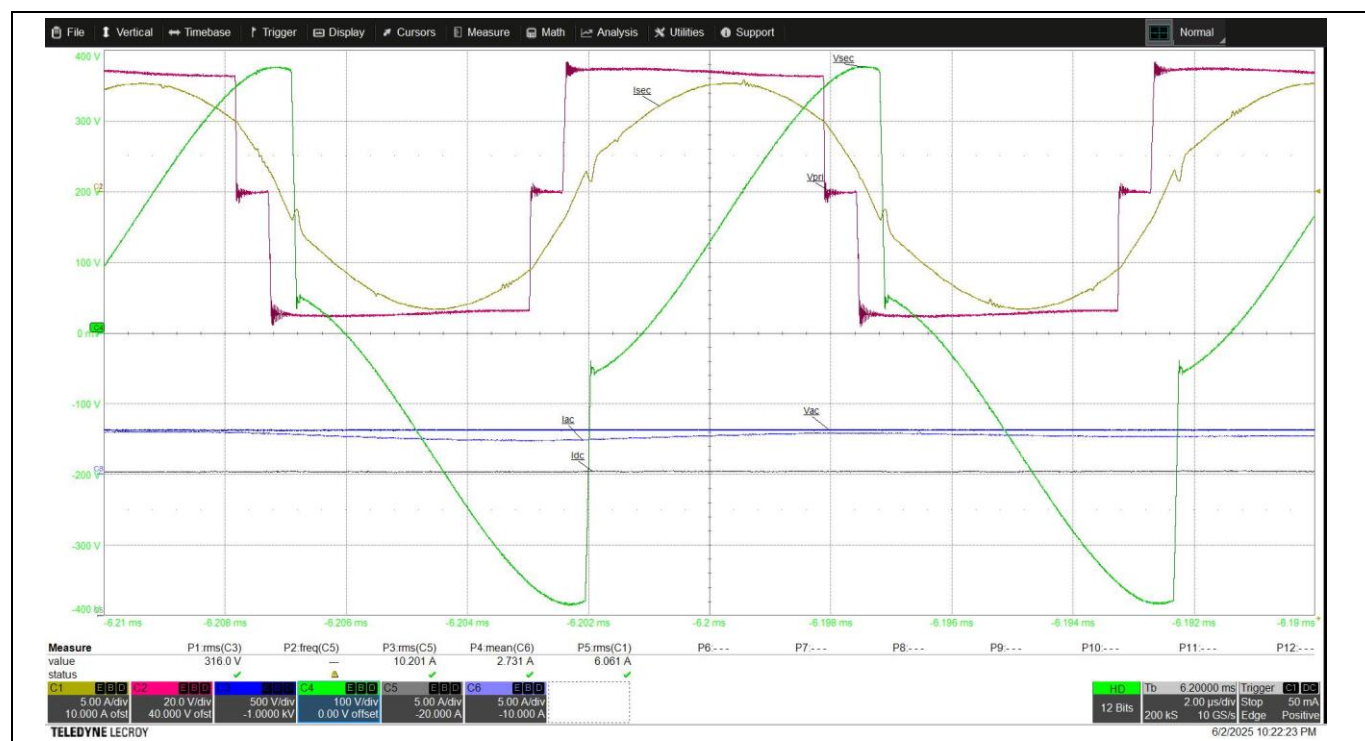


**Figure 139** Output 2.0 A<sub>RMS</sub> - primary voltage (red), secondary voltage (green), resonant current (yellow)

## 11 Test results

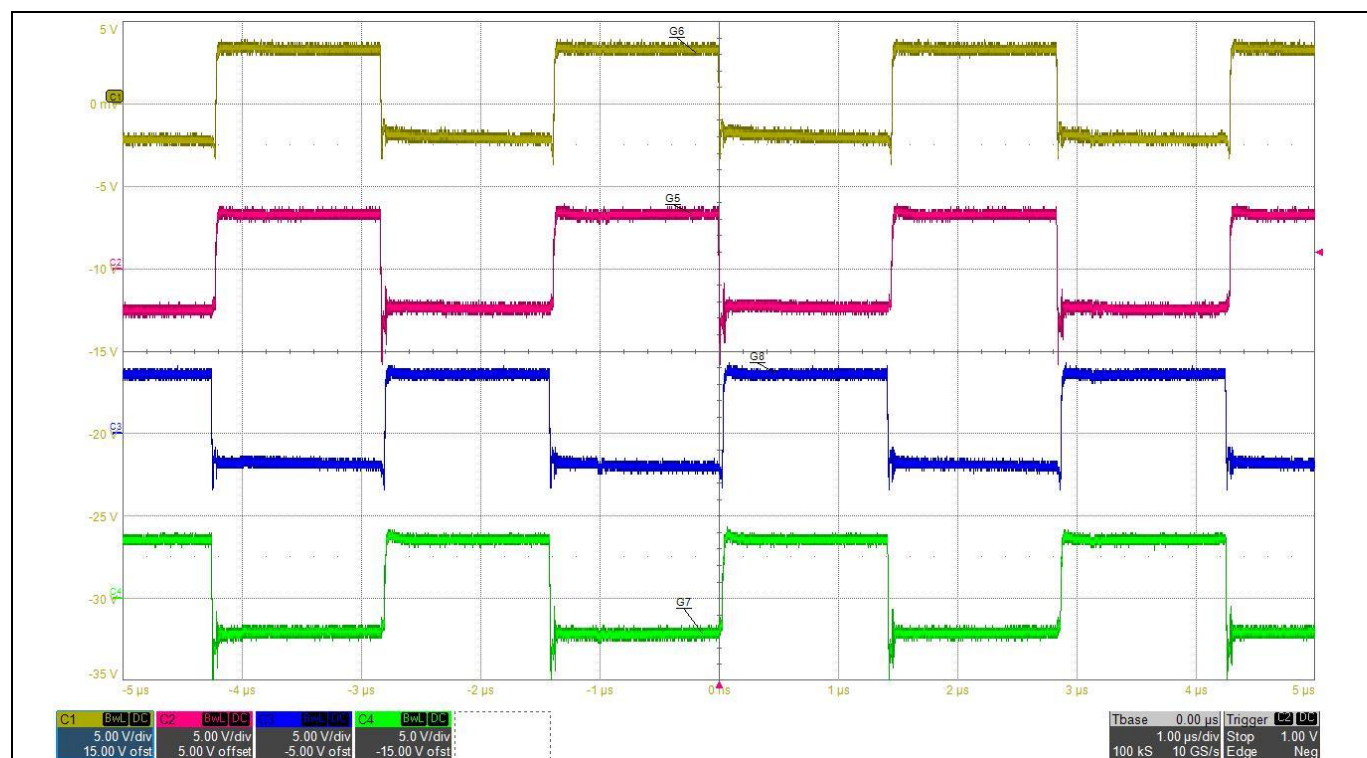


**Figure 140** Bi-directional GaN  $V_{GS}$  gate drive voltages – Q7-G6 (yellow), Q7-G5 (red), Q8-G8 (blue), Q8-G7 (green)

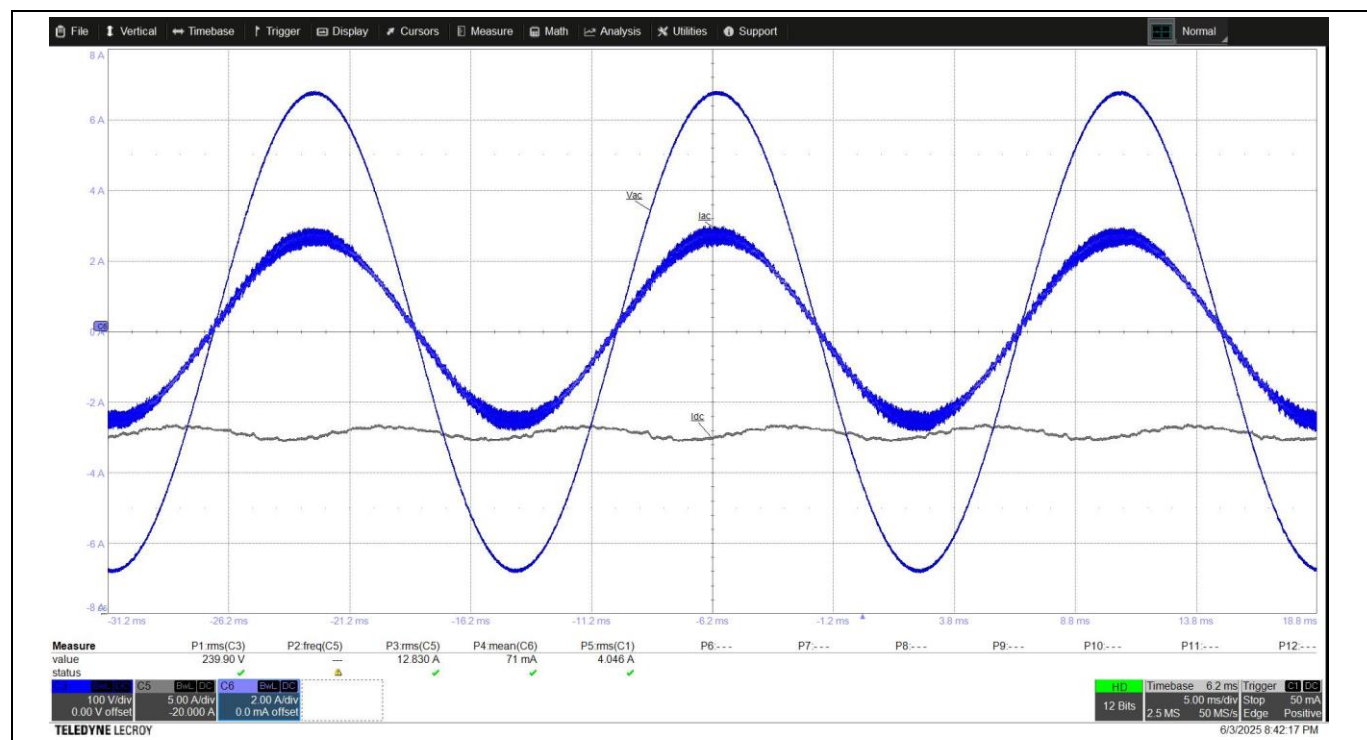


**Figure 141** Load 450 W, PF 1.0 - output voltage (blue), output current (purple), DC input current (gray)

## 11 Test results

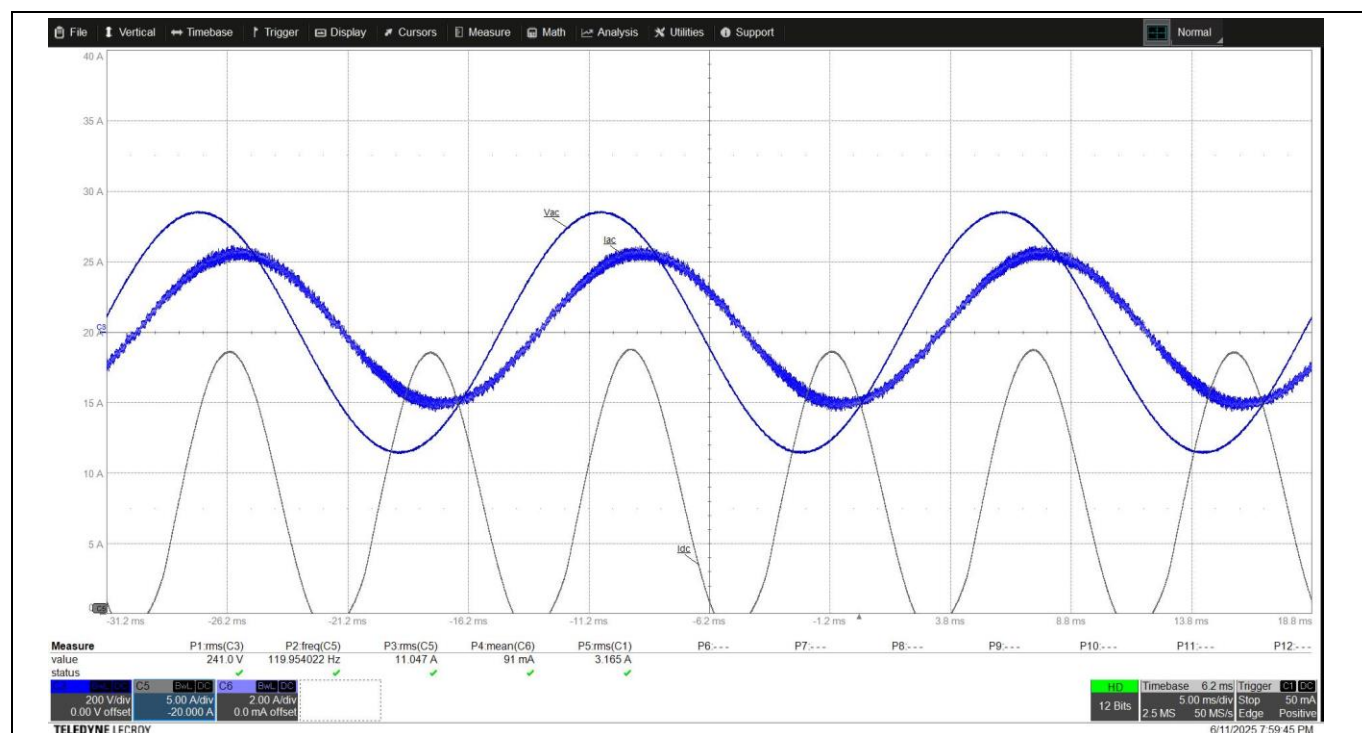


**Figure 142** Load 1.5 A<sub>RMS</sub>, PF 0.8 (lagging) - output voltage (blue), output current (purple), DC input current (gray)

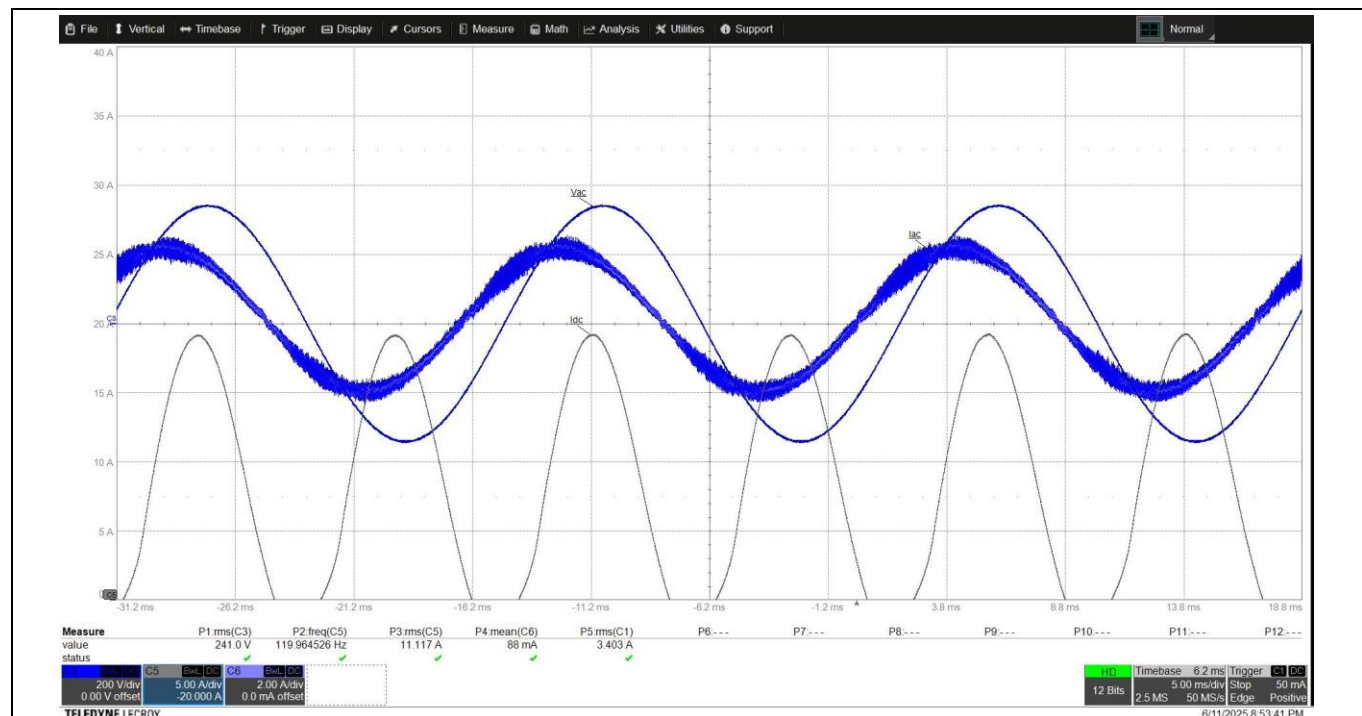


**Figure 143** Load 1.5 A<sub>RMS</sub>, PF -0.8 (leading) - output voltage (blue), output current (purple), DC input current (gray)

## 11 Test results

### 11.3.2.2 Input 50 VDC

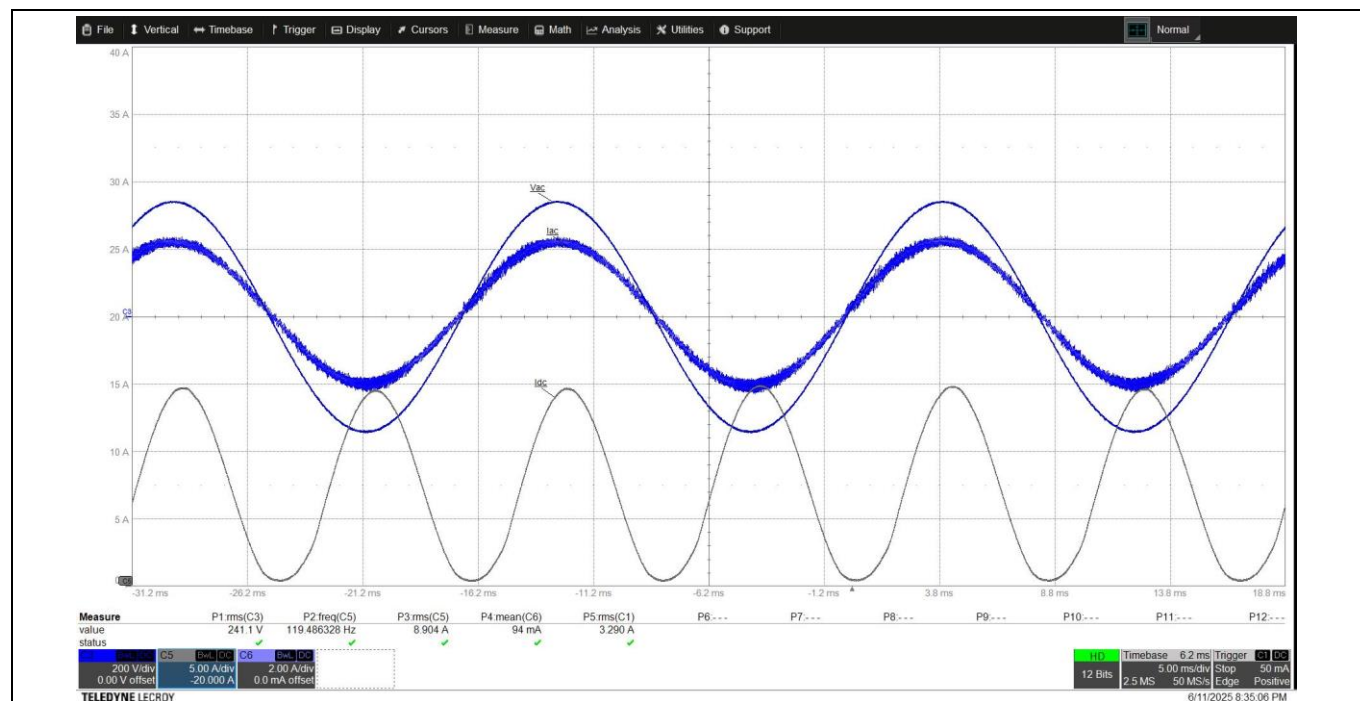


**Figure 144** Load 1.5 A<sub>RMS</sub>, PF 1.0 - output voltage (blue), output current (purple), DC input current (gray)

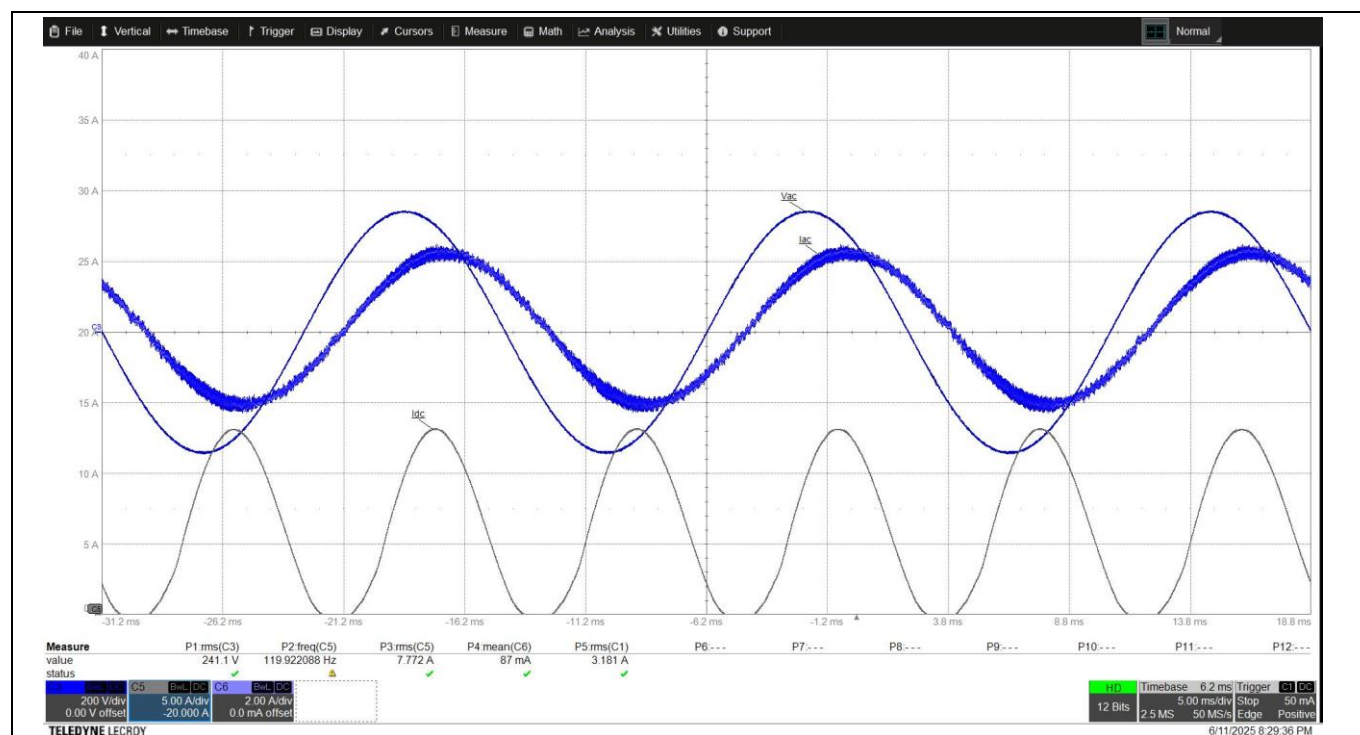

**Figure 145** Load 1.5 A<sub>RMS</sub>, PF 0.8 (lagging) - output voltage (blue), output current (purple), DC input current (gray)

## 11 Test results

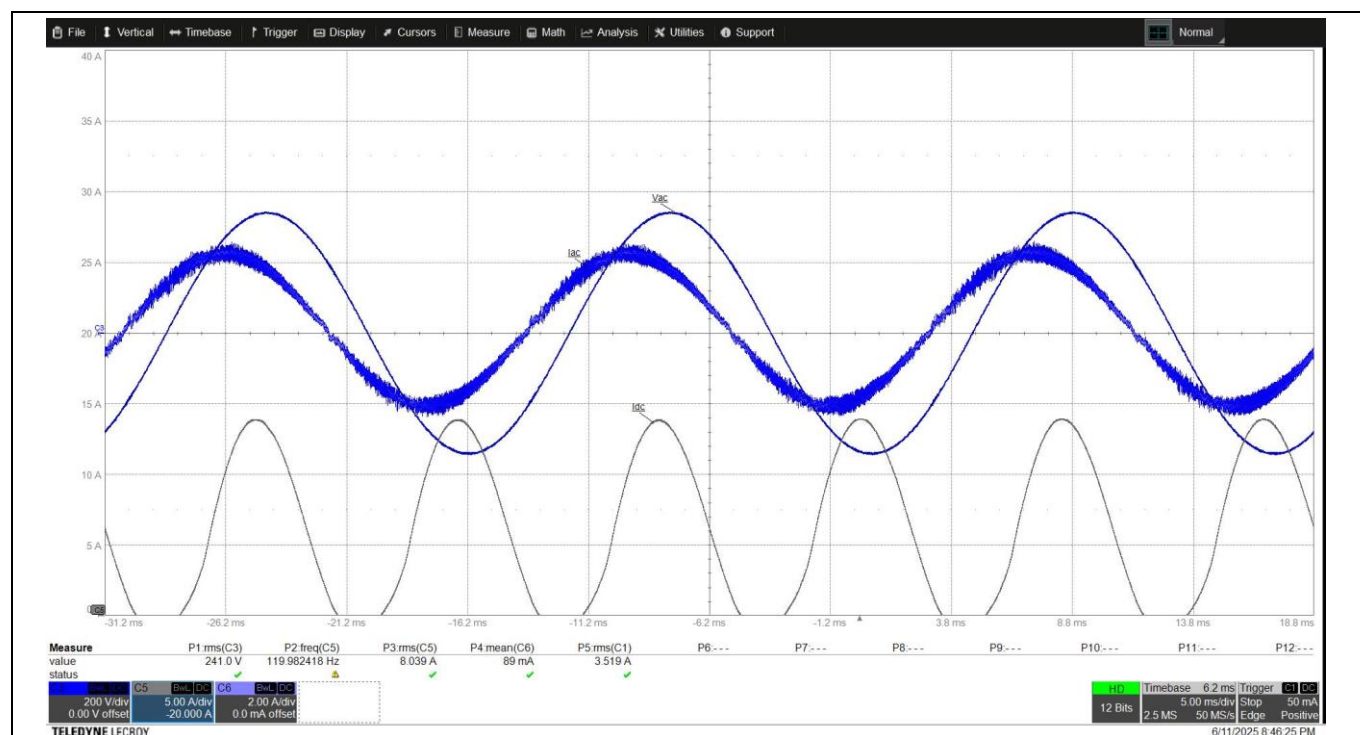


**Figure 146** Load 1.5 A<sub>RMS</sub>, PF -0.8 (leading) - output voltage (blue), output current (purple), DC input current (gray)


## 11 Test results

### 11.3.3 On-grid operation in burst mode

When burst mode is enabled through the GUI, the operating waveforms at light load can be seen as follows:

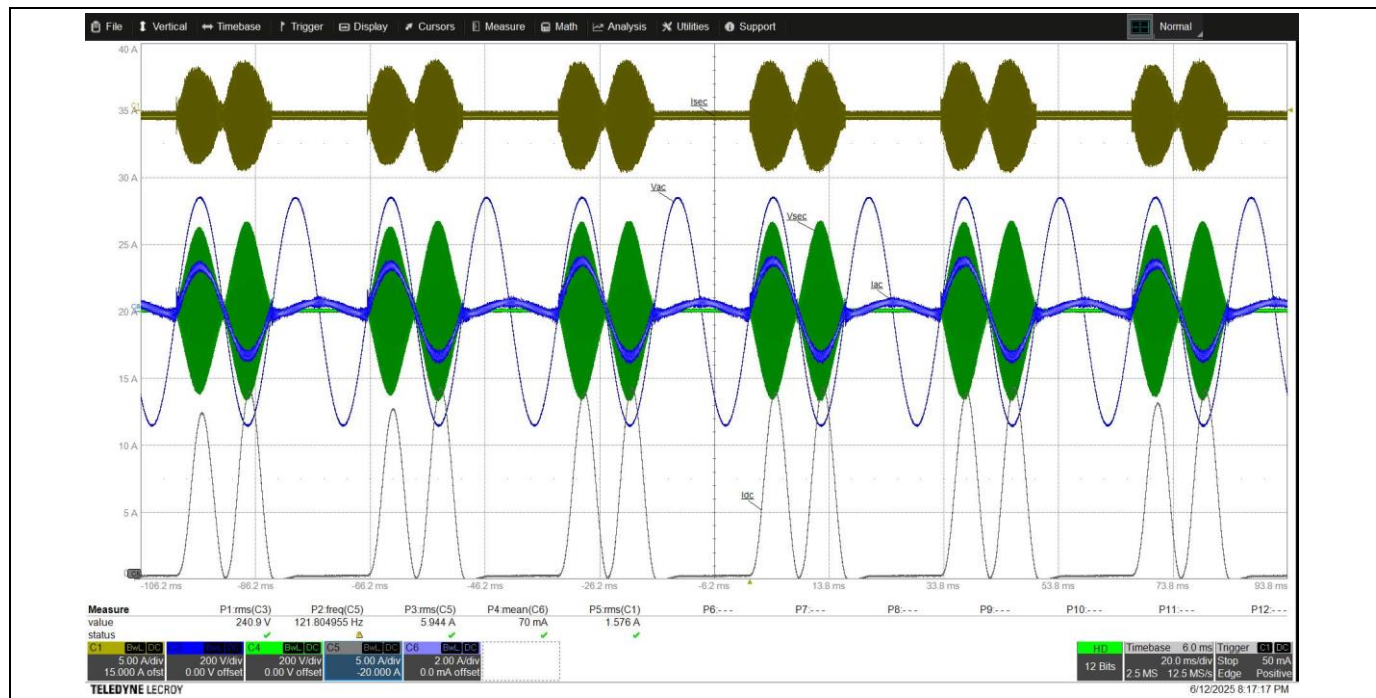

**Figure 147** Load 0.5 A<sub>RMS</sub>, PF 1.0 - grid voltage (blue), output current (purple), DC input current (gray), secondary voltage (green), secondary current (brown)

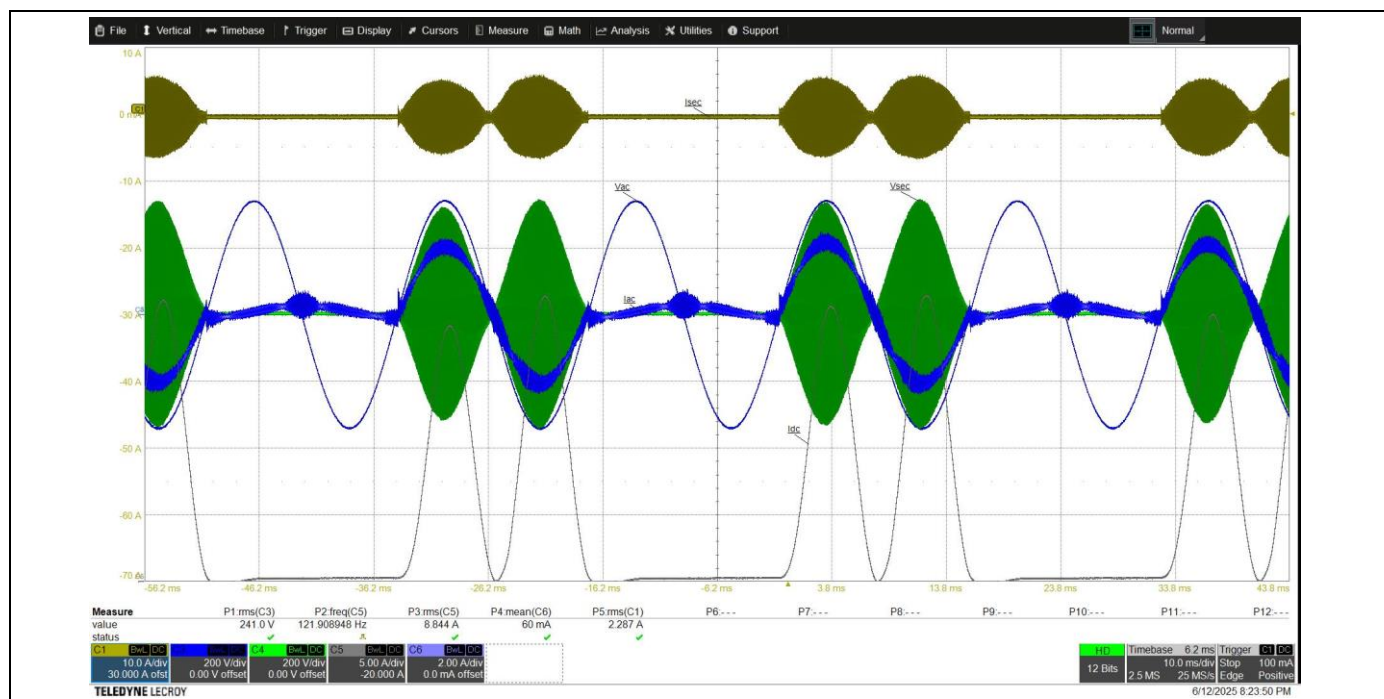

**Figure 148** Load 0.75 A<sub>RMS</sub>, PF 1.0 - grid voltage (blue), output current (purple), DC input current (gray), secondary voltage (green), secondary current (brown)

## 12 Conclusion

### 12 Conclusion

The REF\_500W\_CYCLO\_BDSGAN reference design meets the design objectives. Control of the cyclo-microinverter board is realized through the dedicated GUI tool, which has been used to demonstrate the different operating modes. The test results demonstrate a peak efficiency greater than 97 percent and a CEC-weighted efficiency of 96.7 percent. The AC current THD is well below the 5 percent maximum limit for operation from 50 to 100 percent of full rated load. The component temperature reaches no more than 65 degrees Celsius at maximum load in an ambient temperature of approximately 20 degrees after more than 30 minutes of operation where thermal equilibrium has been reached.

Excellent performance has been achieved by maintaining ZVS over a wide operating range, which is made possible in part due to the benefits of HV GaN with its low and voltage stable  $C_{OSS}$  combined with low conduction losses. This is further aided by the OptiMOS™ 6 power MOSFETs used in the primary side based on Infineon's thin wafer technology enabling >24% lower  $R_{DS(on)}$  and ~40% improved  $FOM_{Qg \times R_{DS(on)}}$  and  $FOM_{Qgd \times R_{DS(on)}}$  compared against the previous generation.

Burst mode operation has also been demonstrated at low output conditions, which can be enabled to maintain high efficiency during periods of reduced sunlight.

The control implementation based on the PSOC™ Control C3 MCU with Infineon's firmware solution has demonstrated stable, accurate and reliable operation over a wide range of line, load and power factor conditions with protection against fault conditions successfully implemented. MPPT efficiency is measured at higher than 99 percent for loads above 50% over a wide input voltage range.

The output current and power factor can be changed while the unit is operating in grid tied mode using the Infineon PC based GUI tool without causing any fault or damage to the system. It is also possible to change the DC input voltage and AC line voltage during operation without causing any disruption.

The protection schemes implemented enable the unit to shut down safely if a fault condition or unexpected disconnect occurs.

In conclusion, the REF\_500W\_CYCLO\_BDSGAN offers a reliability, high-efficiency solution based on a cycloinverter topology, with performance comparable to state-of-the-art microinverters currently in the market.

### 13 Related resources

## 13 Related resources

- [CoolGaN™ GaN bidirectional switches webpage](#)
- [CoolGaN™ GaN developer community](#)
- [OptiMOS™ 6 power MOSFET 80 V webpage](#)
- [MOSFET \(Si/SiC\) developer community](#)
- [PSOC™ Control C3 Main Line MCUs webpage](#)
- [PSOC™ Control C3 developer community](#)

## References

---

## References

- [1] Infineon Technologies AG: *Considerations and guidelines for using high-voltage CoolGaN™ switches in power systems*, [Available online](#)
- [2] Infineon Technologies AG: *CoolGaN™ Bidirectional switch 650 V G5: Fundamentals and design considerations*, [Available online](#)
- [3] Imperix: *Proportional resonant controller (TN110)*; [Available online](#)
- [4] Imperix: *SOGI PLL (TN104)*; [Available online](#)
- [5] Infineon Technologies: *PSOC™ Control C3 - PSC3P5xD, PSC3M5xD datasheet*; [Available online](#)
- [6] Infineon Technologies: *CoolGaN™ BDS 650 V G5 datasheet*; [Available online](#)
- [7] Infineon Technologies: *ISC014N08NM6 datasheet*; [Available online](#)
- [8] Infineon Technologies: *EiceDRIVER™ 1EDNx550 datasheet*; [Available online](#)
- [9] Infineon Technologies: *EiceDRIVER™ 2EDL803X datasheet*; [Available online](#)
- [10] Infineon Technologies: *EiceDRIVER™ 2EDR8259H, 2EDRx259X, 2EDRx258X datsheet*; [Available online](#)

## Revision history

### Revision history

| Document revision | Date       | Description of changes          |
|-------------------|------------|---------------------------------|
| V 1.0             | 2025-08-19 | Initial release                 |
| V 1.1             | 2025-09-18 | Correction to figures 10 and 13 |

#### Trademarks

All referenced product or service names and trademarks are the property of their respective owners.

**Edition 2025-09-18**

**Published by**

**Infineon Technologies AG**

**81726 Munich, Germany**

**© 2025 Infineon Technologies AG.  
All Rights Reserved.**

**Do you have a question about this document?**

**Email:** [erratum@infineon.com](mailto:erratum@infineon.com)

**Document reference**

**AN211819**

#### Important notice

The information contained in this application note is given as a hint for the implementation of the product only and shall in no event be regarded as a description or warranty of a certain functionality, condition or quality of the product. Before implementation of the product, the recipient of this application note must verify any function and other technical information given herein in the real application. Infineon Technologies hereby disclaims any and all warranties and liabilities of any kind (including without limitation warranties of non-infringement of intellectual property rights of any third party) with respect to any and all information given in this application note.

The data contained in this document is exclusively intended for technically trained staff. It is the responsibility of customer's technical departments to evaluate the suitability of the product for the intended application and the completeness of the product information given in this document with respect to such application.

#### Warnings

Due to technical requirements products may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies office.

Except as otherwise explicitly approved by Infineon Technologies in a written document signed by authorized representatives of Infineon Technologies, Infineon Technologies' products may not be used in any applications where a failure of the product or any consequences of the use thereof can reasonably be expected to result in personal injury.