

AN-2085 LMZ23605/03, LMZ22005/03 Evaluation Board

1 Introduction

The LMZ23605/03, LMZ22005/03 evaluation boards are designed to be an easy-to-use platform to evaluate the full capabilities of this family of SIMPLE SWITCHER® power modules. The PCB construction has excellent thermal performance and includes extra locations for optional components that may not be required in the end application.

The LMZ23605/03 can accept an input voltage rail between 6V and 36V and the LMZ22005/03 can accept an input voltage rail between 6V and 20V. The devices can deliver an adjustable and highly accurate output voltage as low as 0.8V and as high as 6V. The control architecture is constant frequency PWM with emulated current mode sensing. The control loop operates well with low ESR output capacitors such as ceramics or specialty polymer. The precision enable input allows for programmable UVLO on the input supply or flexibility in sequencing. The external soft-start capacitor facilitates controlled output rise time at startup. The module family is a reliable and robust solution with cycle-by-cycle valley current limit to protect for over current or short-circuit faults. Additionally there is thermal shutdown protection, and they will start up into a pre-biased output. The free-running switching frequency is 812 kHz (typ) and a 650 kHz to 950 kHz synchronization range is supported.

2 Board Specifications

- V_{IN} = 6V to 36V (LMZ22005/03 limited to 20V)
- Enable UVLO = 5.7V
- V_{OUT} = 3.3V
- I_{OUT} = 0 to 5A (LMZ23603 and LMZ22003 limited to 3A)
- θ_{JA} = 12°C / W, θ_{JC} = 1.9°C/W
- PCB designed on four layers; Inner are 2 oz; Outer are 3 oz.
- Measures 3.5 in. x 3.5 in. (8.9 cm x 8.9 cm) and is 62mil (.062") thick of FR4 laminate material
- Max ambient temp of 70°C at full 5A load (12 Vin)

For additional circuit considerations refer to the Applications Section of the LMZ23605/03 or LMZ22005/03 data sheets. For negative output voltage connections follow the method shown in AN-2027.


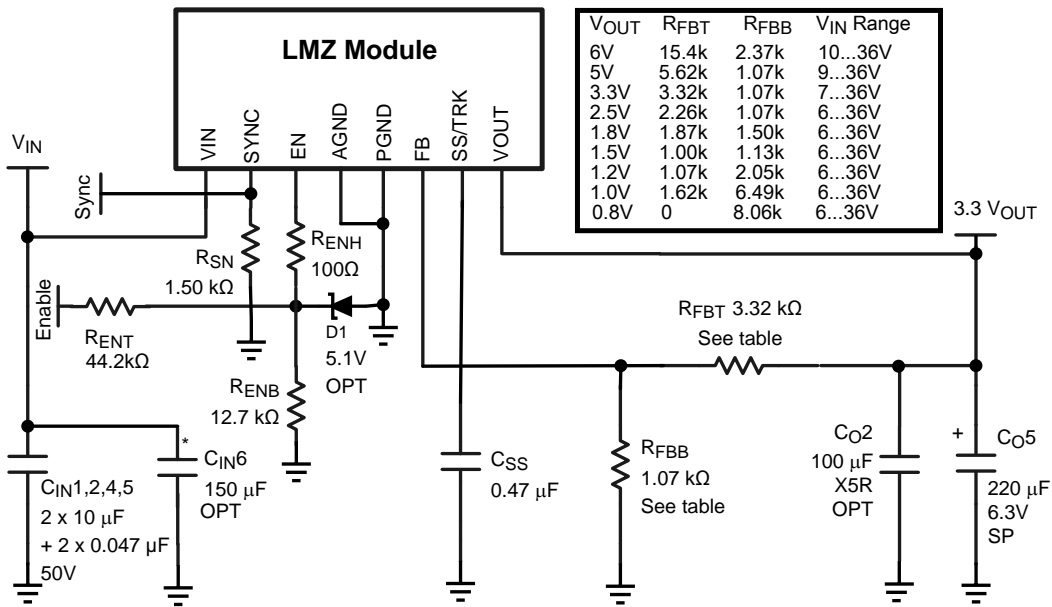



Figure 1. Evaluation Board Simplified Schematic

3 Performance Characteristics

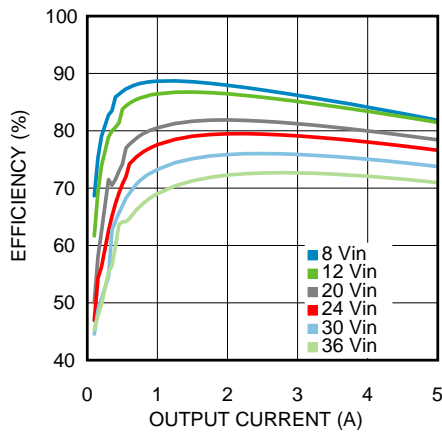
LMZ23605 3.3Vout Efficiency @ 25°C Ambient



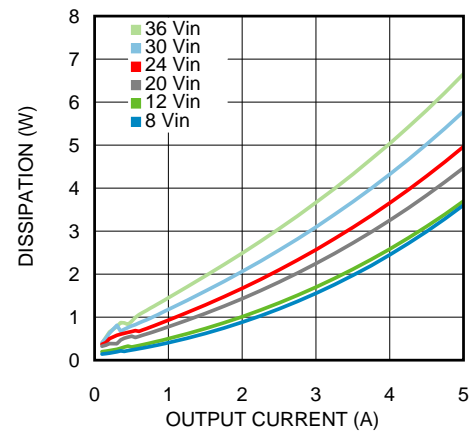
LMZ23605 3.3Vout Dissipation @ 25°C Ambient




LMZ23605 3.3Vout Efficiency @ 85°C

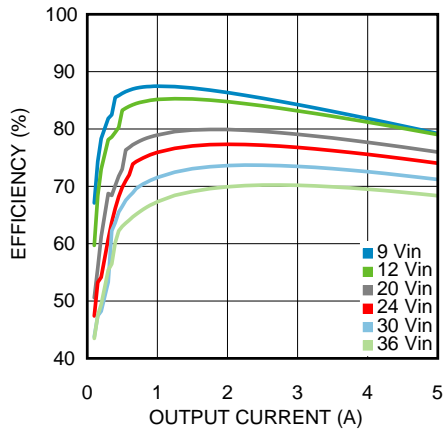


LMZ23605 3.3Vout Dissipation @ 85°C

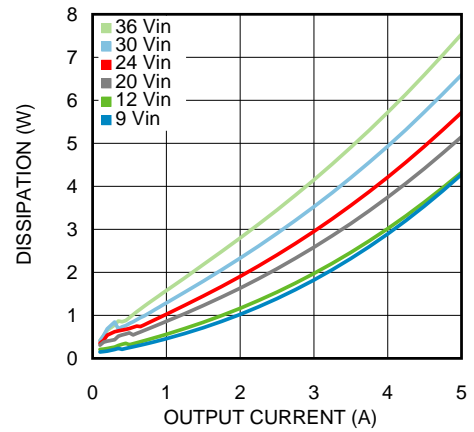

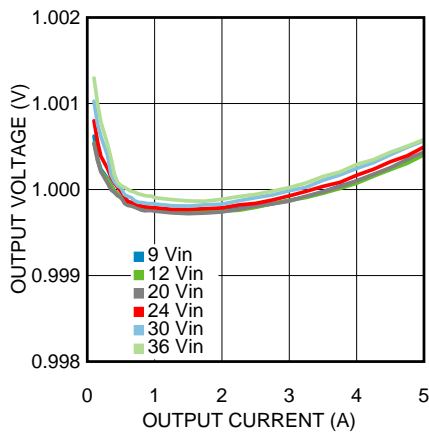
LMZ23605 Load and Line Regulation @ 25°C Ambient




LMZ23605 Current Limit $V_{OUT} = 3.3V$




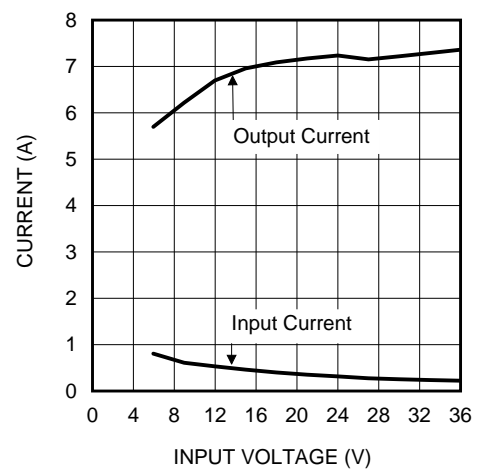


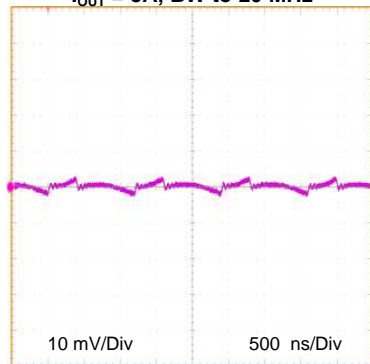Output Ripple $V_{OUT} = 3.3V$
 $I_{OUT} = 5A$, BW to 20 MHz



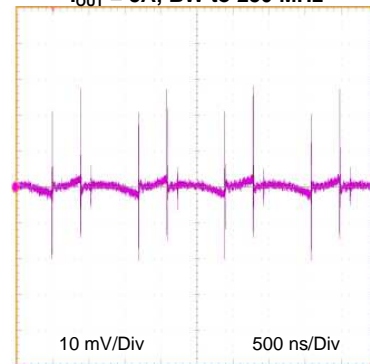Output Ripple $V_{OUT} = 3.3V$
 $I_{OUT} = 5A$, BW to 250 MHz



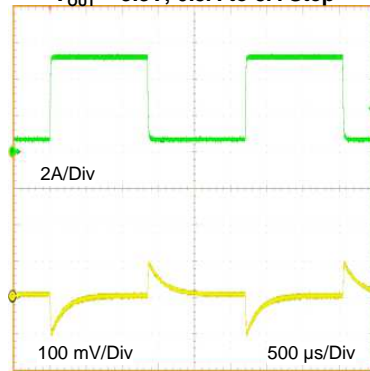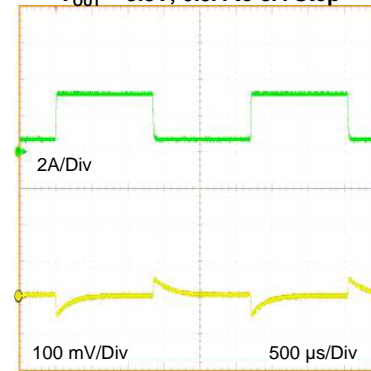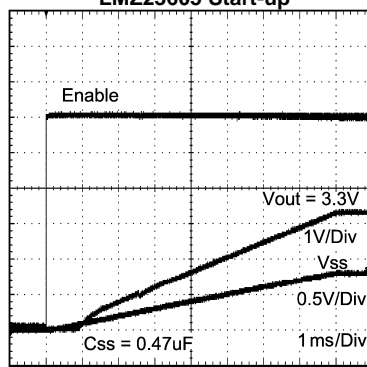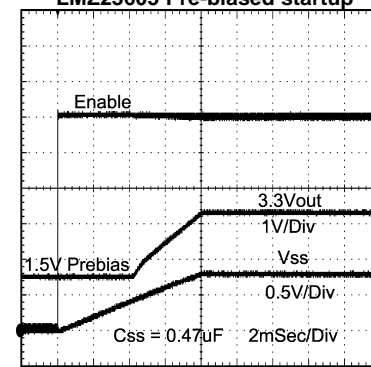**LMZ23605 Load Step Response $V_{IN} = 12V$
 $V_{OUT} = 3.3V$, 0.5A to 5A Step**

**LMZ23603 Load Step Response $V_{IN} = 12V$
 $V_{OUT} = 3.3V$, 0.5A to 3A Step**

LMZ23605 Start-up

LMZ23605 Pre-biased startup


4 Notes

Solder turrets are located on the edge of the PCB assembly for evaluation hookup to bench test equipment. The Enable input turret is designed for direct connection to the V_{IN} turret. There is a resistive divider implemented on the board that establishes the 5.5V precision UVLO level of the board. A common user change to this divider is to raise the value of R_{ENT} to increase the operating UVLO to that of the target application. Refer to the respective data sheet for calculation. Note that if in the end application the module pin 3 enable voltage does not exceed 5.5V at maximum V_{in} , then enable clamp zener D1 can be omitted.

Each implementation of the evaluation board is preset to 3.3V output; with current rating and maximum input voltage rating dictated by the model of module installed. A common user change is to adjust the output voltage for different requirements. A table of suggested resistor pairs are listed in [Figure 1](#) for quick reference.

Locations are provide for testing the operation as a coincident turn-on tracking supply (slave). To implement this feature, remove C_{SS} and install R_{tkl} and R_{tkb} . Calculations are suggested in the respective data sheets.

A turret is also provided for applying a clock to synchronize the module switching frequency anywhere between 650 kHz and 950 kHz. Note that a sustained “logic one” on this input corresponds to “zero hertz” and will cause the module to stop switching.

J1 and J2 are for input and output noise measurement. To implement this feature, populate the 1µF blocking capacitors and the 49.9 ohm source resistors. Install Amphenol coax connectors type 112404 (Digikey #ACX1051). The added R-C network forms a 2X scope probe when used in conjunction with an input termination of 50 ohms at the oscilloscope, providing 5 times more sensitivity than a conventional 10x probe.

J3 is for connection to a frequency response analyzer such as A/P Instruments (Ridley) or Venable Industries products. Refer to the FRA operating manual for this connection. Note: Do not place any type of shorting jumper to these three posts as that will cause a malfunction.

Inductor current can be monitored by connecting a loop of wire between module pin 7 (Vout) and the Co array. First cut the top side conducting etch between the two vias adjacent to pin 7, then install a 5" loop of 22 ga insulated wire in the two vias. Monitor the inductor sense loop with an AC/DC oscilloscope current probe.

The Vin input plane has solder mask openings where an input LC network can be placed to accommodate improved differential mode and conducted EMI performance.

Additional component mounting pads are available to experiment with alternative Cin and Cout combinations. See [Figure 7](#) for corresponding schematic locations.

5 PCB View and layout diagrams

Gerber and CAD files can be downloaded from the LMZ23605 /03, LMZ22005/03 respective product folders.

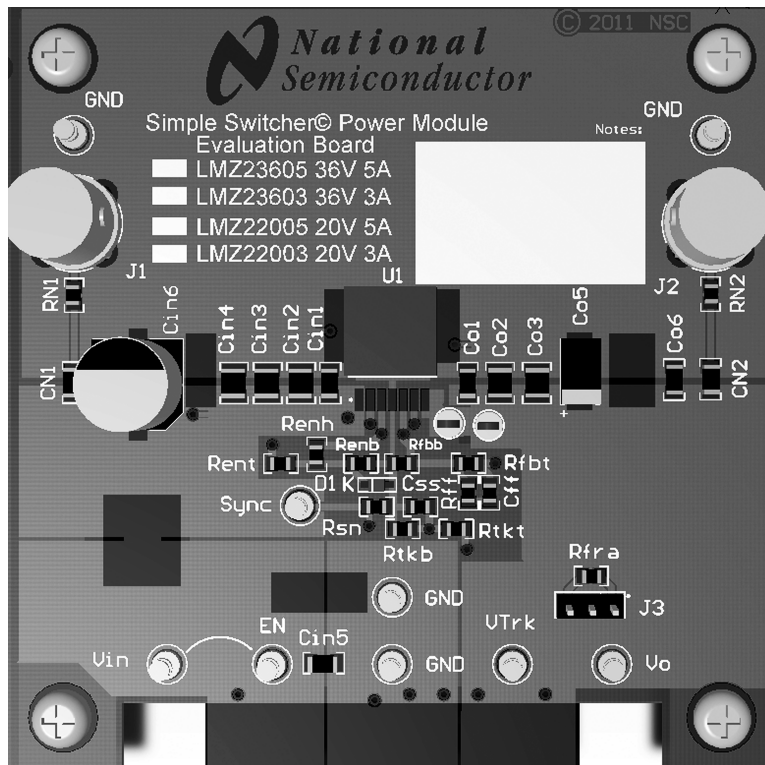


Figure 2. Top View of Assembly

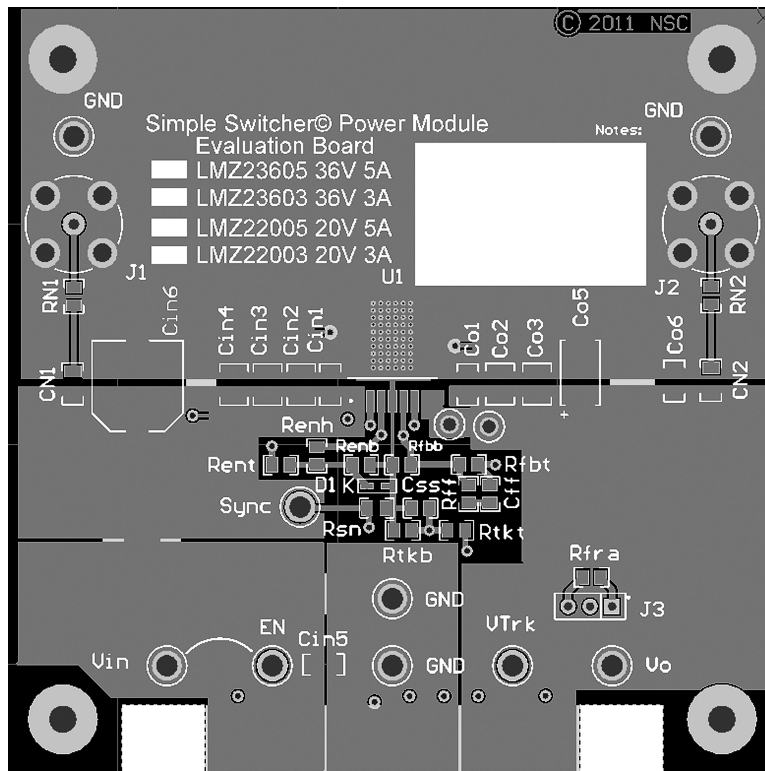


Figure 3. Top Layer



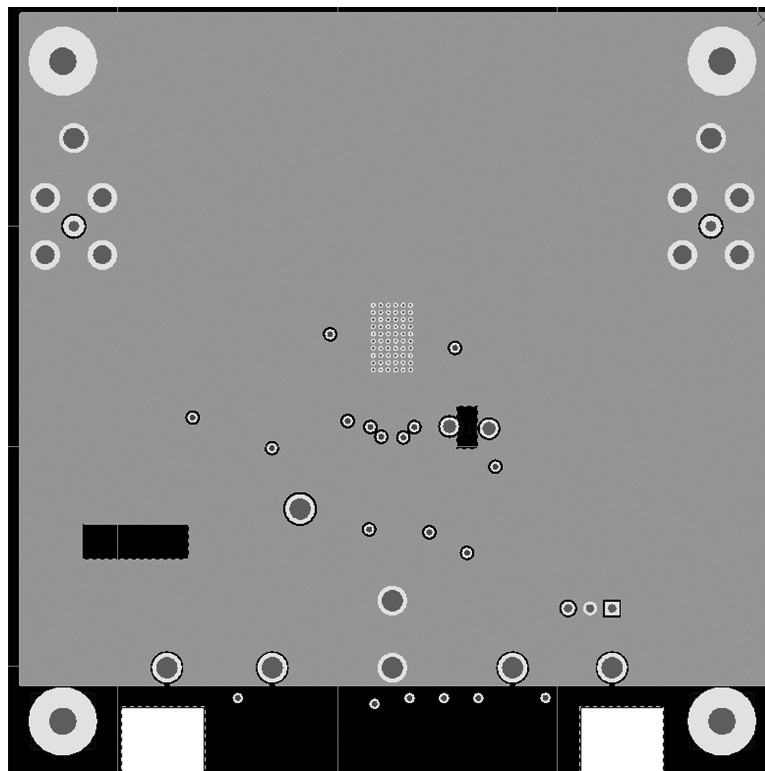



Figure 4. Internal Layer I (Ground)
Heat Sinking Layer

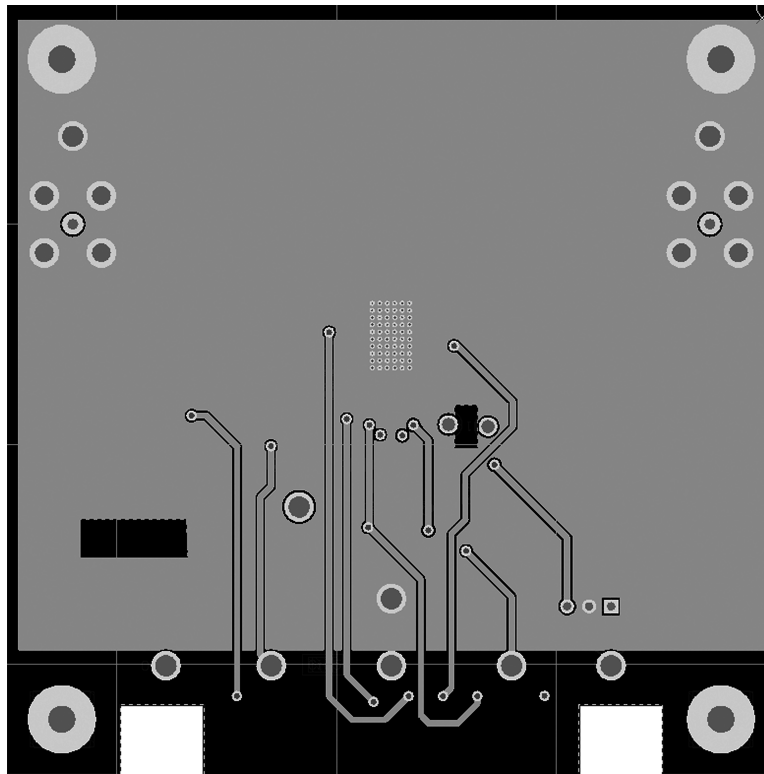

**Figure 5. Internal Layer II (Ground and Routing)
Heat Sinking Layer**

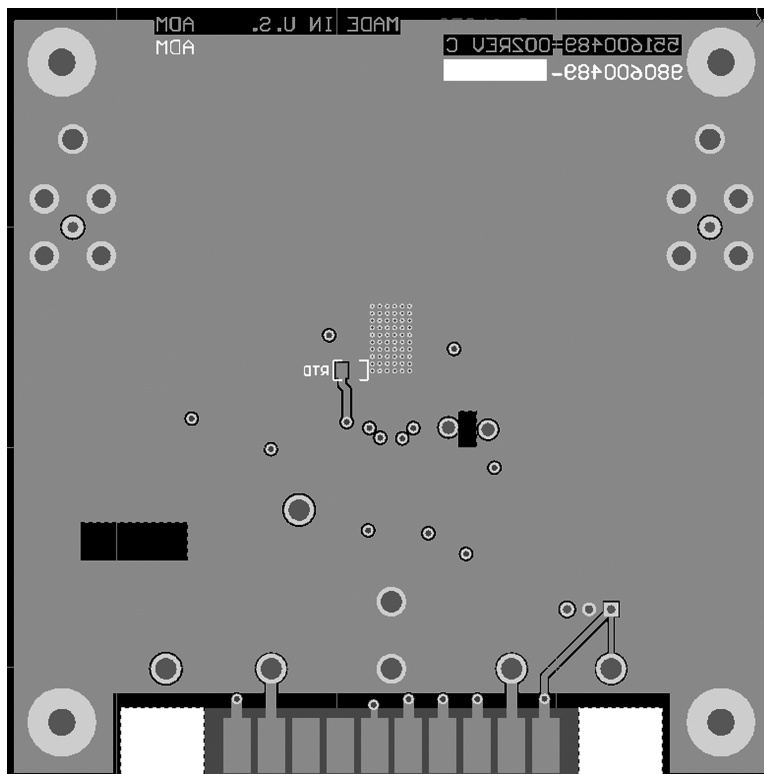

**Figure 6. Bottom Layer (Ground)
Heat Sinking Layer**

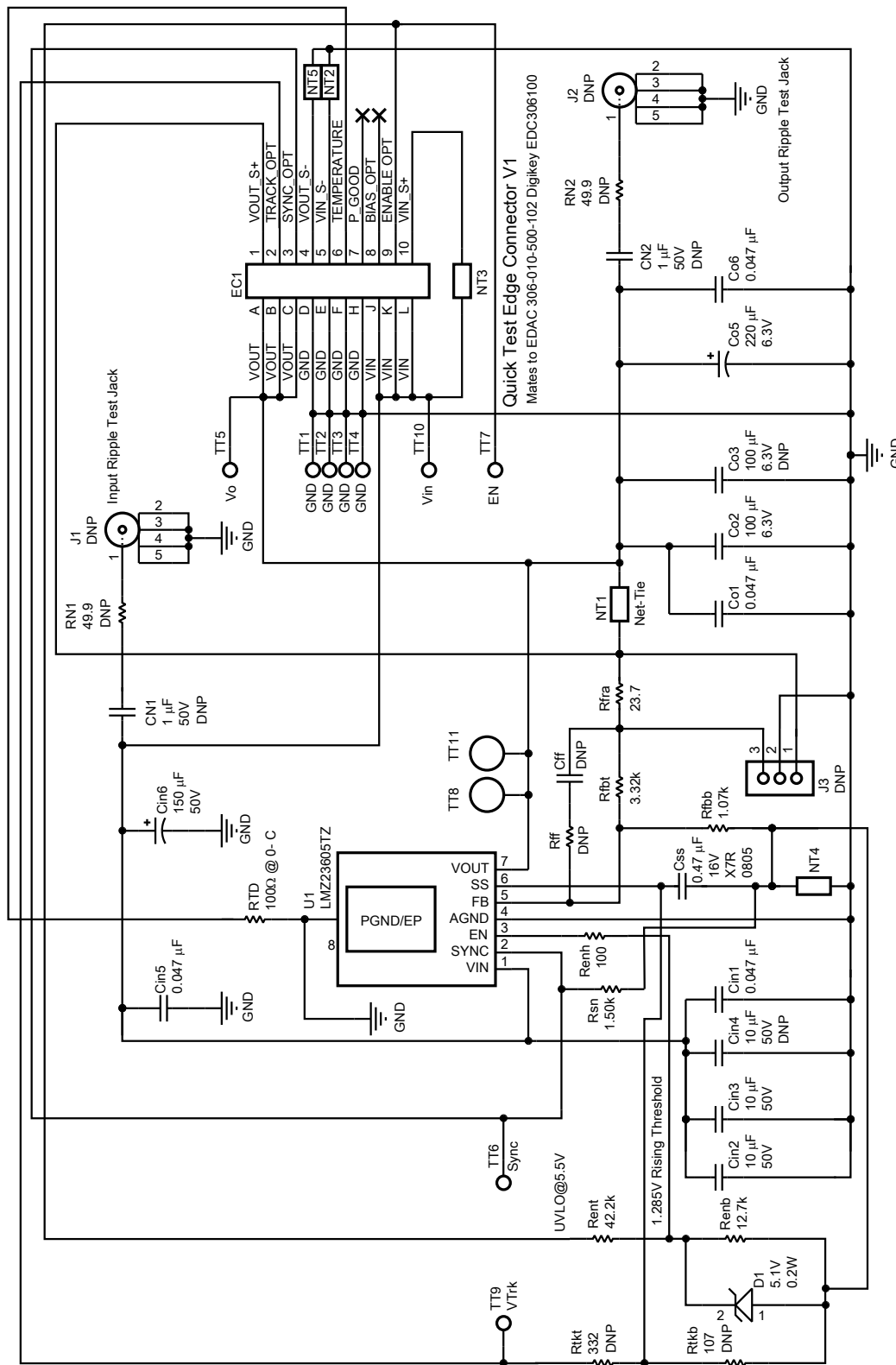

A DNP = Component not populated

Figure 7. LMZ2360x / LMZ2200x PCB CAD Package Schematic

Table 1. Bill of Materials⁽¹⁾⁽²⁾

Designator	Description	Case Size	Manufacturer	Manufacturer P/N	Quantity
U1	SIMPLE SWITCHER®	TO-PMOD-7	Texas Instruments	LMZ23605TZ or LMZ23603TZ or LMZ22005TZ or LMZ22003TZ	1
C _{IN1} C _{IN5} C _{O1} C _{O6}	0.047 µF, X7R, 50V	1206	Yageo America	CC1206KRX7R9BB473	4
C _{IN2} C _{IN3}	10 µF, X5R, 50V	1210	Taiyo Yuden	UMK325BJ106MM-T	2
C _{IN6} OPT	150 µF, Aluminum Electrolytic, 50V	G	Panasonic	EEE-FK1H151P	1
C _{O2} OPT	100 µF, X5R, 6.3V	1210	TDK	C3225X5R0J107M	1
C _{O5}	220 µF, Specialty Polymer, 6.3V		Panasonic	EEF-UE0J221LR	1
C _{FF}	DNP				
C _{SS}	0.47µF, X7R, 16V	0805	AVX	0805YC474KAT2A	1
D1	5.1V 200mW	SOD-323	Diodes Inc.	MMSZ5231BS-7-F	1
R _{ENB}	12.7 kΩ	0805	Panasonic	ERJ-6ENF1272V	1
R _{ENT}	42.2 kΩ	0805	Panasonic	ERJ-6ENF4222V	1
R _{ENH}	100 Ω	0805	Vishay-Dale	CRCW0805100RFKEA	1
R _{FBT}	3.32 kΩ	0805	Vishay-Dale	CRCW08053K32FKEA	1
R _{FBB}	1.07 kΩ	0805	Vishay-Dale	CRCW08051K07FKEA	1
R _{FRA}	23.7 Ω	0805	Vishay-Dale	CRCW080523R7FKEA	1
R _{FF}	DNP				
R _{SN}	1.50 kΩ	0805	Vishay-Dale	CRCW08051K50FKEA	1

⁽¹⁾ V_{IN} = 6V to 36V, V_{OUT} = 3.3V, I_{OUT (MAX)} = 5A (3A)

⁽²⁾ Note: The same BOM applies to all implementations

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com